

Fundamentals of Electronics (4311102) - Summer 2024 Solution

Milav Dabgar

June 21, 2024

Question Question 1 [14 marks]

Answer any seven out of ten.

Question 1(1): Define resistor and give its unit.

Solution

A **resistor** is an electronic component that opposes the flow of electric current. Its unit is **Ohm** (Ω).

Table 1. Resistor Properties

| Property | Description |
|----------|---------------------|
| Symbol | _____ |
| Unit | Ohm (Ω) |
| Function | Limits current flow |

Mnemonic

“Resistors Oppose Current (ROC)”

Question 1(2): Give two examples of active and passive components each.

Solution

Table 2. Electronic Components Classification

| Active Components | Passive Components |
|-------------------|--------------------|
| 1. Transistors | 1. Resistors |
| 2. Diodes | 2. Capacitors |


Mnemonic

“TARD - Transistors And Resistors Differ”

Question 1(3): Draw symbols of any two semiconductor devices.

Solution

Figure 1. Semiconductor Device Symbols

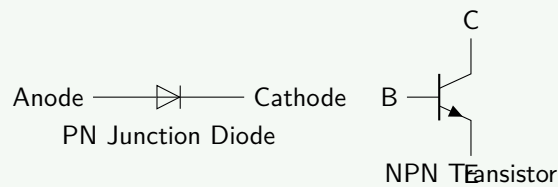**Mnemonic**

“Diodes Direct, Transistors Transfer”

Question 1(4): Differentiate between intrinsic and extrinsic semiconductor.

Solution**Table 3.** Intrinsic vs Extrinsic Semiconductors

| Intrinsic | Extrinsic |
|---------------------------------------|---|
| Pure semiconductor without impurities | Semiconductor with added impurities |
| Equal number of holes and electrons | Unequal holes and electrons |
| Examples: Pure Silicon, Germanium | Examples: Silicon doped with Phosphorus |


Mnemonic

“Pure In, Doped Ex”

Question 1(5): LED stands for _____.

Solution

LED stands for **Light Emitting Diode**.

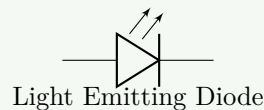Figure 2. LED Symbol**Mnemonic**

“Light Emitters Dazzle”

Question 1(6): State any two applications of Photo-diode.

Solution**Table 4.** Photo-diode Applications

| Application | How it works |
|-----------------------|---|
| Light sensors | Converts light to electrical current |
| Optical communication | Detects optical signals in fiber optics |


Mnemonic

“Light Sensing Communication (LSC)”

Question 1(7): List the types of transistor and draw their symbols.

Solution**Types of Transistors:**

1. NPN Transistor
2. PNP Transistor

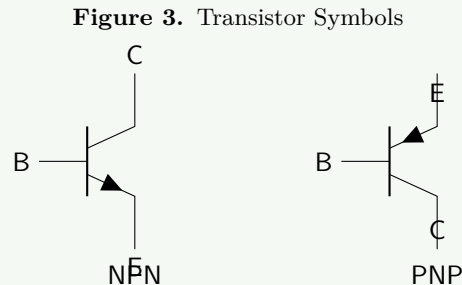**Mnemonic**

“Not Pointing iN, Pointing outP”

Question 1(8): Give the value of forward voltage drop of Germanium and Silicon diode.

Solution

Table 5. Forward Voltage Drop Values

| Diode Type | Forward Voltage Drop |
|------------|----------------------|
| Germanium | 0.3V |
| Silicon | 0.7V |

Mnemonic


“Germanium’s Three, Silicon’s Seven (0.3V, 0.7V)”

Question 1(9): The _____ diode can be used as a light detector.

Solution

The **Photodiode** can be used as a light detector.

Figure 4. Photodiode Symbol

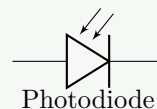**Mnemonic**

“Photo Detects Light (PDL)”

Question 1(10): Define Q-factor of a coil.

Solution

Q-factor (Quality factor) of a coil is the ratio of its inductive reactance to its resistance, indicating how efficiently it stores energy.

Table 6. Q-Factor

| Parameter | Description |
|-----------|----------------------------------|
| Formula | $Q = \frac{X_L}{R}$ |
| Higher Q | Better quality, less energy loss |
| Lower Q | Poor quality, more energy loss |

Mnemonic

“Quality equals Reactance over Resistance (QRR)”

Question Question 2(a) [3 marks]

Question 2(a): Explain colour coding method of resistor.

Solution

Resistor color coding uses colored bands to indicate resistance value and tolerance.

Table 7. Resistor Color Code

| Color | Digit | Multiplier |
|--------|-------|------------|
| Black | 0 | 10^0 |
| Brown | 1 | 10^1 |
| Red | 2 | 10^2 |
| Orange | 3 | 10^3 |
| Yellow | 4 | 10^4 |
| Green | 5 | 10^5 |
| Blue | 6 | 10^6 |
| Violet | 7 | 10^7 |
| Grey | 8 | 10^8 |
| White | 9 | 10^9 |

For a 4-band resistor:

- First band: First digit
- Second band: Second digit
- Third band: Multiplier
- Fourth band: Tolerance

Mnemonic

“Bad Boys Race Our Young Girls But Violet Generally Wins (Black, Brown, Red, Orange, Yellow, Green, Blue, Violet, Grey, White)”

Question 2(a) OR: Explain Light Dependent Resistor with its characteristics.

Solution


LDR is a resistor whose resistance decreases when light intensity increases.

Characteristics:

Table 8. LDR Properties

| Parameter | Behavior |
|------------------|-------------------------------|
| Dark condition | High resistance ($M\Omega$) |
| Bright condition | Low resistance ($k\Omega$) |
| Response time | Few milliseconds |

Figure 5. LDR Characteristics

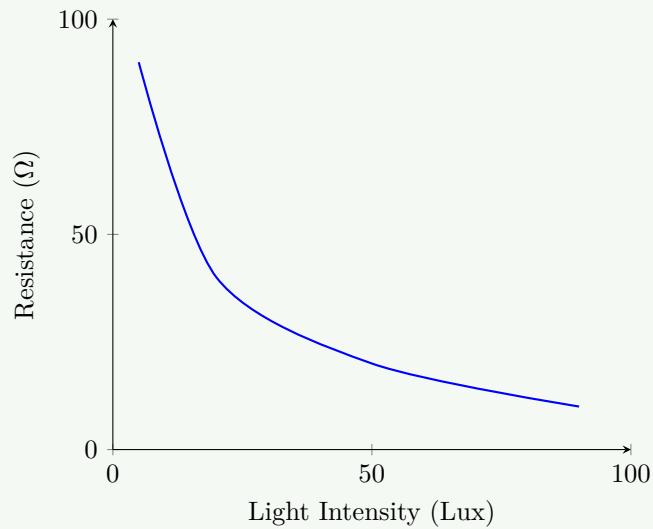**Mnemonic**

“Light Up, Resistance Down (LURD)”

Question Question 2(b) [3 marks]

Question 2(b): Explain classification of capacitors in detail.

Solution

Capacitors are classified based on dielectric material and construction.

Figure 6. Classification of Capacitors

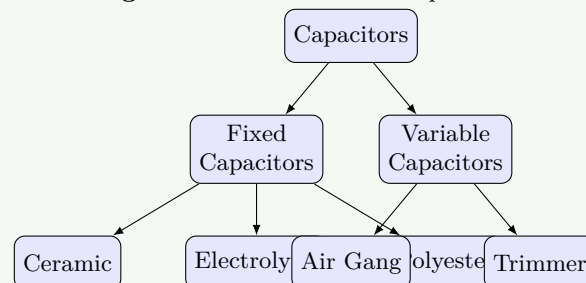


Table 9. Capacitor Classifications

| Type | Dielectric | Applications |
|--------------|----------------|----------------------|
| Ceramic | Ceramic | High frequency |
| Electrolytic | Aluminum oxide | Power supplies |
| Polyester | Plastic film | General purpose |
| Tantalum | Tantalum oxide | Small, high capacity |

Mnemonic

“CEPT (Ceramic, Electrolytic, Polyester, Tantalum)”

Question 2(b) OR: Explain classification of inductor in detail.

Solution

Inductors are classified based on core material and construction.

Figure 7. Classification of Inductors

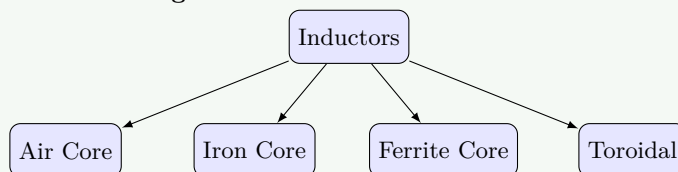


Table 10. Inductor Classifications

| Type | Core | Characteristics |
|--------------|-------------|-------------------------------|
| Air core | Air | Low inductance, low losses |
| Iron core | Iron | High inductance, high losses |
| Ferrite core | Ferrite | Medium inductance, low losses |
| Toroidal | Ring shaped | High efficiency, low EMI |

Mnemonic

“Air Iron Ferrite Toroid (AIFT)”

Question Question 2(c) [4 marks]

Question 2(c): State and explain Faraday’s laws of Electromagnetic Induction.

Solution

Faraday’s laws explain how electromagnetic induction works.


Faraday’s First Law: When a magnetic field linked with a conductor changes, an EMF is induced in the conductor.

Faraday’s Second Law: The magnitude of induced EMF is proportional to the rate of change of magnetic flux.

Table 11. Faraday’s Laws Summary

| Law | Statement | Formula |
|------------|--------------------------------------|---------------------------|
| First Law | Change in magnetic field induces EMF | - |
| Second Law | EMF \propto rate of change of flux | $E = -N \frac{d\Phi}{dt}$ |

Figure 8. Faraday's Law

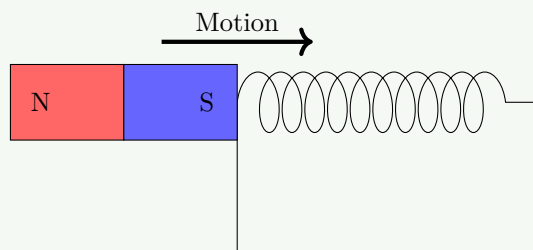**Mnemonic**

“Change Magnetic Field, Create Electric Current (CMFCEC)”

Question 2(c) OR: Enlist specifications of capacitors and explain two in detail.

Solution**Specifications of Capacitors:**

1. Capacitance value
2. Voltage rating
3. Tolerance
4. Leakage current
5. Temperature coefficient

Detailed Explanation:

1. **Capacitance Value:** The amount of charge a capacitor can store per volt, measured in Farads (F).
2. **Voltage Rating:** The maximum voltage that can be applied without damaging the capacitor.

Table 12. Capacitor Specifications

| Specification | Description | Typical Values |
|----------------|-------------------------|----------------|
| Capacitance | Charge storage capacity | pF to mF |
| Voltage Rating | Maximum safe voltage | 16V, 25V, 50V |

Mnemonic

“Capacitors Very Tolerant of Low Temperatures (CVTLT)”

Question Question 2(d) [4 marks]

Question 2(d): Write colour band of $47\Omega \pm 5\%$ resistance.

Solution

For $47\Omega \pm 5\%$ resistor, the color bands are:

Table 13. Color Bands for $47\Omega \pm 5\%$

| Band | Color | Represents |
|----------|--------|---------------|
| 1st band | Yellow | 4 |
| 2nd band | Violet | 7 |
| 3rd band | Black | $\times 10^0$ |
| 4th band | Gold | $\pm 5\%$ |

Figure 9. Resistor Color Code: $47 \pm 5\%$ 

Yellow (4) Black (7) $(\times 10^1)$ Gold ($\pm 5\%$)

Mnemonic

“Yellow Violets Bring Gold”

Question 2(d) OR: Calculate value of resistor and tolerance for a given colour code: Brown, Black, yellow.

Solution**Table 14.** Interpretation of Brown, Black, Yellow

| Band | Color | Value | Meaning |
|------|--------|--------|--------------|
| 1st | Brown | 1 | First digit |
| 2nd | Black | 0 | Second digit |
| 3rd | Yellow | 10^4 | Multiplier |

Calculation:

- 1st digit: 1
- 2nd digit: 0
- Multiplier: 10^4

$$\text{Value} = 10 \times 10^4 = 100,000\Omega = 100k\Omega$$

No 4th band means $\pm 20\%$ tolerance.

Figure 10. Resistor: $100k\Omega$ 

Brown (1) Black (0) $(\times 10^4)$ Band ($\pm 20\%$)

Mnemonic

“Big Black Yield (Brown-Black-Yellow)”

Question Question 3(a) [3 marks]


Question 3(a): Define doping. Give the name of semiconductor materials fabricated by doping with an example of each.

Solution

Doping is the process of adding impurities to a pure semiconductor to modify its electrical properties.

Table 15. Doped Semiconductors

| Type | Dopant Added | Example | Majority Carriers |
|--------|-----------------------------------|----------------------|-------------------|
| P-type | Trivalent (Boron, Gallium) | Silicon + Boron | Holes |
| N-type | Pentavalent (Phosphorus, Arsenic) | Silicon + Phosphorus | Electrons |

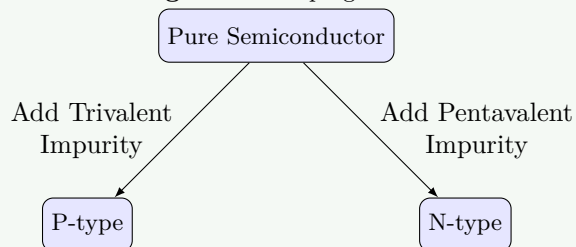Figure 11. Doping Process**Mnemonic**

“Positive has Plus Holes, Negative has Numerous Electrons (PHNE)”

Question 3(a) OR: Define Ripple factor, Peak Inverse Voltage (PIV), Rectification efficiency.

Solution**Table 16.** Rectifier Terms

| Term | Definition | Formula |
|--------------------------|---|---|
| Ripple Factor | Measure of AC component in DC output | $r = \frac{V_{rms(AC)}}{V_{dc}}$ |
| Peak Inverse Voltage | Max reverse voltage diode can withstand | - |
| Rectification Efficiency | Ratio of DC output to AC input power | $\eta = \frac{P_{dc}}{P_{ac}} \times 100\%$ |

Mnemonic

“Ripples Peak Efficiently (RPE)”

Question Question 3(b) [3 marks]


Question 3(b): Explain working of Crystal diode.

Solution

A **Crystal Diode** is a point-contact diode used for detecting RF signals.

Construction: It consists of a semiconductor crystal (Germanium/Silicon) and a thin tungsten wire (cat's whisker) pressing against it.

Function: It rectifies high-frequency radio signals (demodulation).

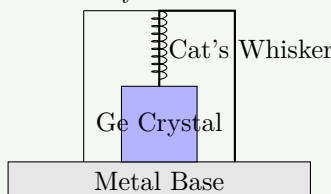Figure 12. Crystal Diode Construction**Mnemonic**


“Crystal Detects Radio Frequencies (CDRF)”

Question 3(b) OR: Explain working of photodiode.**Solution**

Photodiode converts light energy into electrical current when operated in reverse bias.

Working:



1. Light strikes the PN junction.
2. Photons generate electron-hole pairs.
3. Reverse bias field sweeps carriers across junction, creating a current.

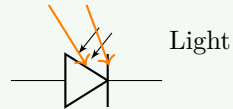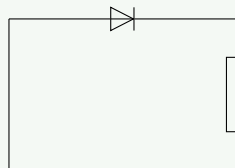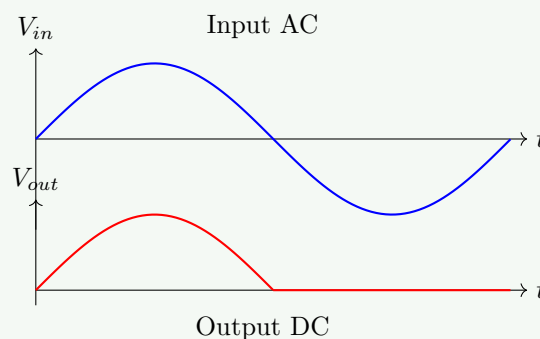Figure 13. Photodiode Operation**Mnemonic**

"Light In, Current Out (LICO)"

Question Question 3(c) [4 marks]**Question 3(c): Explain half-wave rectifier with circuit diagram and waveforms.****Solution**

Half-wave rectifier converts AC to pulsating DC by conducting only during positive half cycles.

Figure 14. Half-Wave Rectifier Circuit**Figure 15.** Half-Wave Waveforms**Mnemonic**

"Half Wave Passes Half (HWPH)"

Question 3(c) OR: Explain full-wave rectifier with circuit diagram and waveforms.

Solution

Full-wave rectifier (Bridge Type) converts both halves of AC input to DC.

Figure 16. Bridge Rectifier Circuit

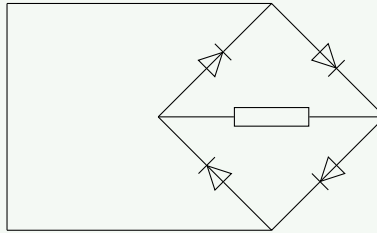
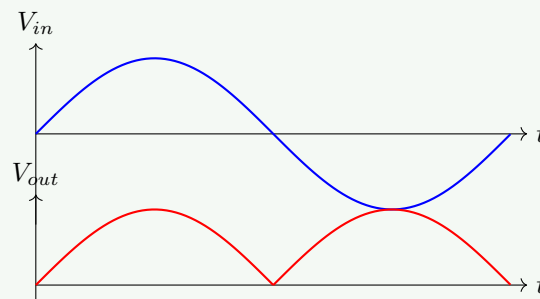


Figure 17. Full-Wave Waveforms

**Mnemonic**

“Full Wave Makes Full Use (FWMFU)”

Question Question 3(d) [4 marks]

Question 3(d): Draw and explain VI characteristics of PN junction diode.

Solution

Figure 18. VI Characteristics of PN Diode

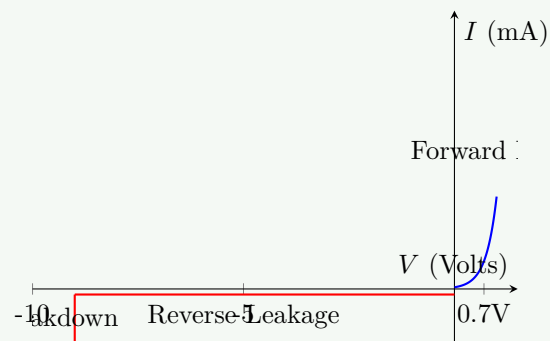


Table: Characteristics

| Region | Behavior |
|--------------|--|
| Forward Bias | Current rises exponentially after 0.7V (V_k) |
| Reverse Bias | Negligible leakage current |
| Breakdown | Sharp current increase at high reverse voltage |

Mnemonic

“Forward Flows, Reverse Restricts”

Question 3(d) OR: Write difference between P-type and N-type semiconductor.

Solution**Table 17.** P-type vs N-type

| Property | P-type | N-type |
|-------------------|-------------------|--------------------------|
| Dopant | Trivalent (Boron) | Pentavalent (Phosphorus) |
| Majority Carriers | Holes | Electrons |
| Minority Carriers | Electrons | Holes |

Mnemonic

“Positive has Plus Holes, Negative has Numerous Electrons”


Question Question 4(a) [3 marks]

Question 4(a): Explain the principle of operation of LED.

Solution

LED works on the principle of **Electroluminescence**.

Operation: When forward biased, electrons from N-region recombine with holes in P-region at the junction. This recombination releases energy in the form of photons (light).

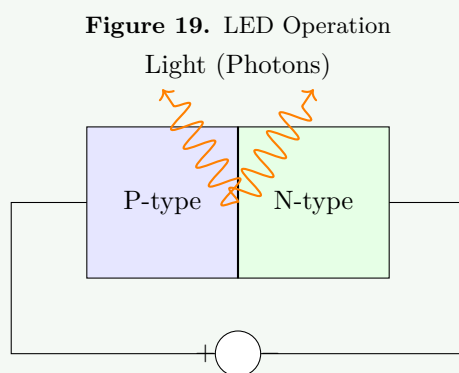**Mnemonic**

“Forward Current Emits Light (FCEL)”

Question 4(a) OR: State applications of LED.

Solution**Table 18.** LED Applications

| Application | Advantage |
|------------------------------|------------------------|
| Display indicators | Low power |
| Digital displays (7-segment) | Varied colors |
| Lighting (Bulbs) | Energy efficient |
| Remote controls | Infrared communication |
| Traffic signals | High visibility |


Question Question 4(b) [4 marks]

Question 4(b): Explain Zener diode as voltage regulator.

Solution

A **Zener Diode** maintains a constant output voltage across the load when operated in the reverse breakdown region.

Figure 20. Zener Voltage Regulator

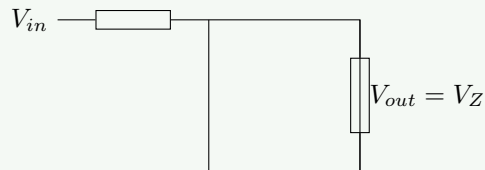

Working:

- The series resistor R_S absorbs voltage fluctuations.
- The Zener diode conducts variable current to keep voltage across it constant (V_Z).

Mnemonic

“Zeners Break to Regulate”

Question 4(b) OR: Give limitations of zener voltage regulator.

Solution

Table 19. Limitations

| Limitation | Effect |
|-------------------|-------------------------------------|
| Power Dissipation | Limited by Zener wattage rating |
| Current Capacity | Suitable only for low load currents |
| Efficiency | Poor due to power loss in R_S |

Question Question 4(c) [7 marks]

Question 4(c): Discuss the necessity of filter circuit in rectifier. List various types of filter circuits used in rectifier and explain any one with neat diagram.


Solution

Necessity: Rectifier output is pulsating DC (contains AC ripples). Filter circuits remove these ripples to provide a steady DC voltage required by electronic circuits.

Types of Filters:

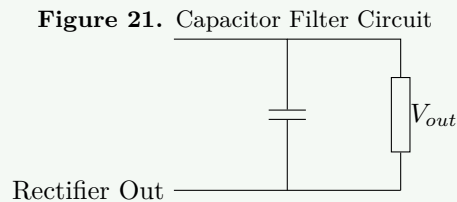
1. Capacitor Filter (Shunt)
2. Inductor Filter (Series)
3. LC Filter (L-Section)
4. π -Filter (C-L-C)

Capacitor Filter Explanation: A capacitor is connected in parallel with the load.



Operation:

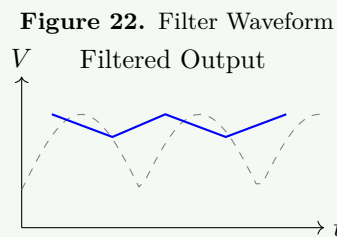- During voltage peak, capacitor charges to V_{peak} .
- During voltage drop, capacitor discharges through load, maintaining voltage.
- Result: Reduced ripple, smoother DC.



Mnemonic

“Capacitors Hold Voltage During Drops”

Question Question 5(a) [3 marks]

Question 5(a): Define e-waste. List common e-waste items.

Solution

E-waste (Electronic Waste) refers to discarded electrical or electronic devices that are near the end of their useful life.

Table 20. Common E-waste

| Category | Examples |
|-----------------|--------------------------------|
| Computing | Laptops, PCs, Tablets |
| Communication | Mobile phones, Landlines |
| Home Appliances | TVs, Fridges, Washing Machines |
| Components | Batteries, PCBs, Cables |

Mnemonic

“Computers, Communication, Components (CCC)”

Question 5(b): State and explain various strategies of e-waste management.

Solution

Table 21. Management Strategies

| Strategy | Description |
|----------|--------------------------------------|
| Reduce | Buy less, maintain devices longer |
| Reuse | Repair, donate, or sell old devices |
| Recycle | Extract valuable metals (Au, Ag, Cu) |
| Disposal | Safe disposal of hazardous materials |

Mnemonic

“3 R’s: Reduce, Reuse, Recycle”


Question Question 5(c) [4 marks]

Question 5(c): Explain transistor as switch.

Solution

A transistor acts as a switch by operating in **Cutoff** (OFF) and **Saturation** (ON) regions.

Figure 23. Transistor Switch Circuit

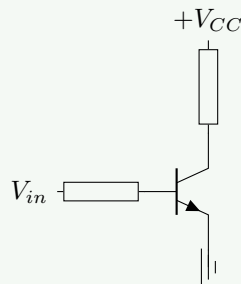**States:**

- **OFF (Open Switch):** $V_{in} = 0V$. Base current $I_B = 0$, so Collector current $I_C = 0$. $V_{CE} = V_{CC}$.
- **ON (Closed Switch):** $V_{in} = High$. I_B flows, transistor saturates. $V_{CE} \approx 0V$.

Mnemonic

“No Base No Current”

Question Question 5(d) [4 marks]

Question 5(d): Derive relation between α and β for CE configuration of transistor.

Solution**Definitions:**

- $\alpha = \frac{I_C}{I_E}$ (Common Base Gain)
- $\beta = \frac{I_C}{I_B}$ (Common Emitter Gain)

Derivation: We know that emitter current is the sum of base and collector currents:

$$I_E = I_C + I_B \quad (1)$$

Divide equation (1) by I_C :

$$\frac{I_E}{I_C} = \frac{I_C}{I_C} + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\frac{1}{\alpha} = \frac{\beta + 1}{\beta}$$

Inverting both sides:

$$\alpha = \frac{\beta}{1 + \beta}$$

Rearranging for β :

$$\beta = \frac{\alpha}{1 - \alpha}$$

Mnemonic

“Beta equals Alpha over One minus Alpha”