

Electronic Circuits & Applications (4321103) - Summer 2024 Solution

Milav Dabgar


June 18, 2024

Question 1 [a marks]

3 Explain amplifier parameters A_i , R_i and R_o for CE configuration.

Solution

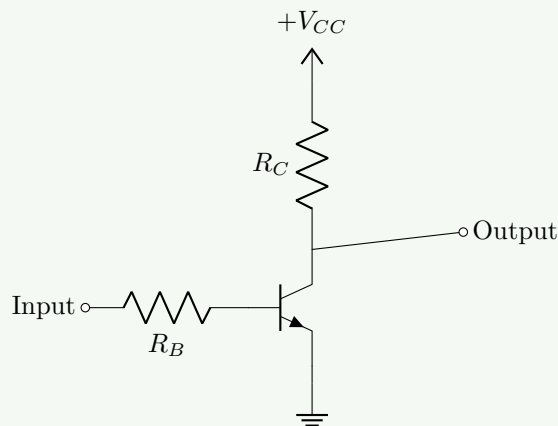In **Common Emitter (CE)** configuration, the key parameters are:



- **Current Gain (A_i):** Ratio of output current to input current (I_c/I_b). Typically 50-200 in CE configuration.
- **Input Resistance (R_i):** Opposition to input current at base terminal. Ranges from 1-2 k Ω in CE.
- **Output Resistance (R_o):** Opposition at collector terminal. Typically 50 k Ω in CE.


Mnemonic

CIR parameters - Current gain, Input resistance, and output Resistance determine amplifier performance

Question 1 [b marks]

4 Write short-note on heat sink.

Solution

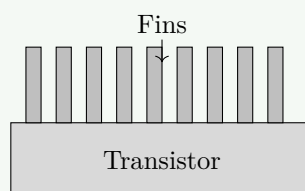

- **Purpose:** Dissipates excess heat from electronic components (like power transistors) to prevent thermal damage.
- **Types:**
 - **Passive:** Aluminum or copper fins that rely on natural convection.
 - **Active:** Uses fans or liquid cooling for forced convection.
- **Thermal Resistance:** Lower thermal resistance (θ , measured in $^{\circ}\text{C}/\text{W}$) indicates better heat dissipation capability.
- **Materials:** Copper (best conductivity) or Aluminum (lightweight, cost-effective).


Mnemonic

HARD sinks - **H**eat **A**way using **R**adiation and **D**issipation through metal sinks

Question 1 [c marks]

7 Describe Thermal Runaway and Thermal Stability. How can overcome thermal run away in transistor?

Solution

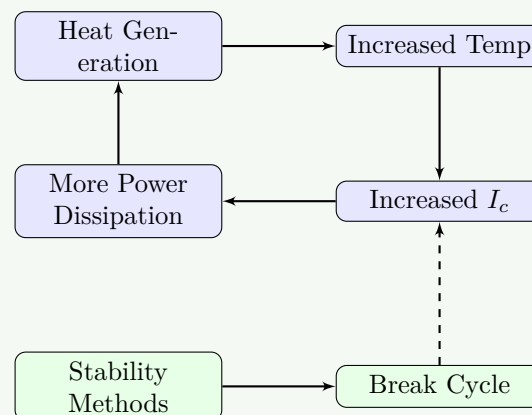

Thermal Runaway:

- **Definition:** A self-accelerating destructive process where the transistor heats up, causing more current to flow, which generates even more heat.
- **chain Reaction:** Increase in temperature \rightarrow Increases leakage current (I_{CO}) \rightarrow Increases collector current ($I_C = \beta I_B + (1 + \beta)I_{CO}$) \rightarrow Increases Power Dissipation ($P_D = V_{CE}I_C$) \rightarrow Further Temperature Rise.
- **Result:** If unchecked, it leads to the physical destruction of the transistor.

Thermal Stability:

- **Definition:** The ability of a circuit to maintain a stable operating point (Q -point) despite variations in temperature.
- **Measure:** Quantified by the **Stability Factor (S)**. Lower values of S indicate better thermal stability.

Overcoming Thermal Runaway:

1. **Heat Sinks:** Increasing surface area to dissipate heat into the air.
2. **Emitter Resistor:** Using an unbypassed emitter resistor (R_E) provides negative feedback. If I_C rises, voltage drop across R_E increases, reducing V_{BE} , which reduces I_B and thus opposes the rise in I_C .
3. **Biasing Methods:** Using circuits like **Voltage Divider Bias** which offer better stability than fixed bias.
4. **Compensation:** Using temperature-sensitive components (thermistors, diodes) in the bias circuit to counteract parameter changes.

Mnemonic

SHEER protection - **S**inks for **H**eat, **E**mitter resistors, **E**xternal cooling, and **R**obust biasing prevent thermal runaway

Question 1 [c marks]

7 Write down types of biasing methods. Explain the voltage divider biasing method in details.

Solution

Types of Biasing Methods:

| Method | Stability | Complexity |
|--------------------|-----------|------------|
| Fixed Bias | Poor | Simple |
| Collector Feedback | Medium | Medium |
| Emitter Bias | Good | Medium |
| Voltage Divider | Excellent | Complex |

Voltage Divider Biasing:

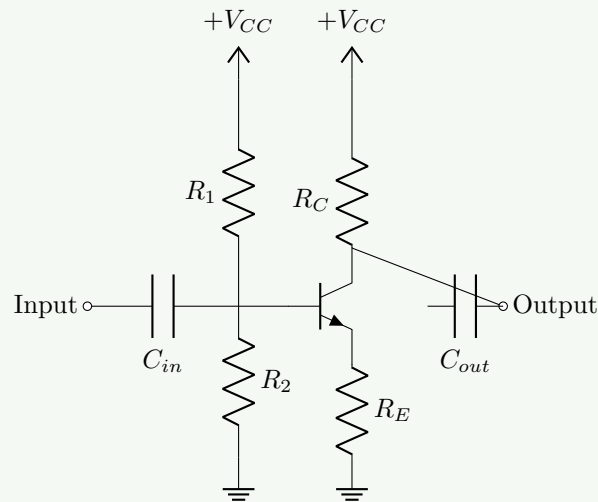


Figure 1. Voltage Divider Bias Circuit

- **Circuit Structure:** Uses two resistors R_1 and R_2 connected in series across the supply V_{CC} to provide a fixed potential at the base.
- **Operating Principle:** The voltage across R_2 (base voltage V_B) forward biases the emitter junction.
- **Base Voltage:** $V_B = V_{CC} \times \frac{R_2}{R_1 + R_2}$
- **Stability:** This is the most widely used method because the operating point is almost independent of the transistor's β .
 - If I_C increases due to temperature, I_E increases ($I_E \approx I_C$).
 - Voltage drop across R_E ($V_E = I_E R_E$) increases.
 - Since V_B is constant, $V_{BE} = V_B - V_E$ decreases.
 - Decreased V_{BE} reduces I_B , which in turn reduces I_C , stabilizing the circuit.
- **Advantage:** High stability factor ($S \approx 1$).


Mnemonic

DIVE for stability - Divider Is Very Effective for temperature and β variations

Question 2 [a marks]

3 Explain Stability Factor with features.

Solution

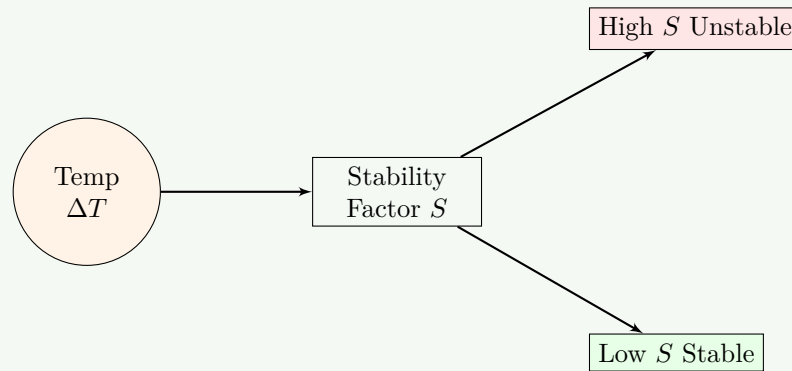

- **Definition:** Stability factor (S) indicates the degree of change in collector current (I_C) with respect to the reverse saturation current (I_{CO}), keeping β and V_{BE} constant.
- **Formula:** $S = \frac{dI_C}{dI_{CO}}$
- **Ideal Value:** Ideally $S = 1$. The lower the value of S , the better the thermal stability.
- **Significance:** It quantifies how sensitive the Q-point is to temperature variations. A circuit with $S = 10$ is less stable than one with $S = 2$.


Mnemonic

LESS is better - Lower values Ensure Stable System for temperature changes

Question 2 [b marks]

4 Describe direct coupling technique of cascading.

Solution

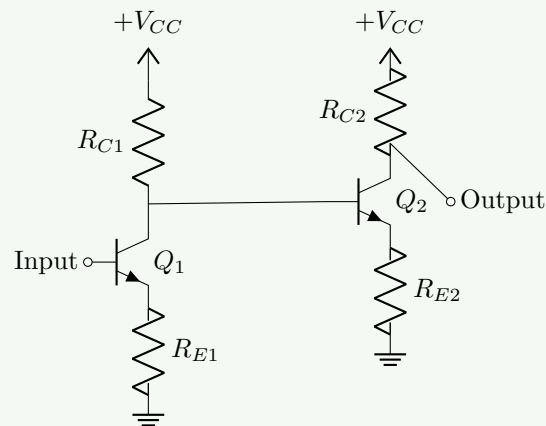


- **Definition:** In direct coupling, the output of the first stage is directly connected to the input of the next stage without any coupling capacitor or transformer.
- **Working:** The DC collector voltage of the first stage provides the DC base bias for the second stage.
- **Advantages:**
 - Can amplify extremely low frequencies (including DC).
 - Simple circuit, fewer components (no capacitors/transformers).
 - Easy to fabricate in Integrated Circuits (ICs).
- **Disadvantages:**
 - Thermal drift (shift in Q-point) is amplified stage by stage.
 - Requires careful design to match DC levels.

Mnemonic

DIAL for DC - **D**irect **I**nterconnection **A**mplifies **L**ow frequencies without capacitors

Question 2 [c marks]

7 Explain frequency response of two stages RC coupled amplifier.

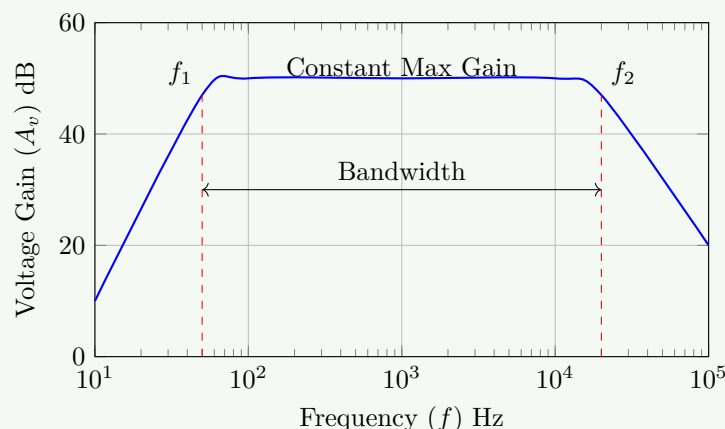Solution**Frequency Response Analysis:**

- Low Frequency Region ($f < f_1$):**
 - The reactance of coupling capacitors ($C_C = 1/2\pi fC$) is high.
 - A significant voltage drop occurs across C_C , reducing the signal reaching the next stage.
 - The emitter bypass capacitor (C_E) also has high reactance, reducing the gain due to negative feedback.
- Mid Frequency Region ($f_1 < f < f_2$):**
 - Capacitors act as short circuits.
 - Gain remains constant and maximum.
- High Frequency Region ($f > f_2$):**
 - Reactance of internal transistor capacitances (inter-electrode capacitance) becomes low.
 - These shunt the signal to ground, reducing the gain.
 - Wiring capacitance also contributes to gain reduction.
- Bandwidth:** The range of frequencies between the lower cut-off (f_1) and upper cut-off (f_2) where gain is at least 70.7% (-3dB) of the maximum is the bandwidth.

Mnemonic

LMH frequency regions - **L**ow has rising gain, **M**iddle has flat gain, **H**igh has falling gain

Question 2 [a marks]

3 Briefly explain bandwidth and gain-bandwidth product of an amplifier.

Solution**Bandwidth (BW):**

- It is the range of frequencies over which the amplifier provides satisfactory gain (usually defined as gain being $\geq 70.7\%$ of maximum).

- Formula: $BW = f_2 - f_1$, where f_2 is upper cut-off and f_1 is lower cut-off frequency.

Gain-Bandwidth Product (GBW):

- For a given amplifier, the product of voltage gain (A_v) and bandwidth (BW) is a constant.
- $GBW = A_v \times BW = \text{Constant}$.
- **Significance:** If we increase gain (e.g., by cascading), the bandwidth decreases, and vice versa. It represents the figure of merit for an amplifier.

Mnemonic

BIG value - **B**andwidth and gain **I**nverse relationship is a **G**iven constant

Question 2 [b marks]

4 Explain effects of emitter bypass capacitor and coupling capacitor on frequency response of an amplifier.

Solution

| Capacitor | Low Freq | Mid Freq | High Freq |
|--------------------------|--|---|--------------------------|
| Emitter Bypass (C_E) | High reactance, reduces gain (feedback active) | Short circuit, max gain (feedback bypassed) | Short circuit, no effect |
| Coupling (C_C) | High reactance, blocks/attenuates signal | Short circuit, allows full signal | Short circuit, no effect |

- **Coupling Capacitor (C_C):**
 - Blocks DC to prevent bias interaction between stages.
 - At low frequencies, its high reactance (X_C) causes signal loss, defining the lower cut-off frequency f_1 .
- **Emitter Bypass Capacitor (C_E):**
 - Connected in parallel with R_E to bypass AC signals to ground.
 - Prevents degeneration (negative feedback) at signal frequencies, thus increasing voltage gain.
 - At low frequencies, if X_C is high, feedback occurs, reducing gain.

Mnemonic

CABLE effect - **C**apacitors **A**ct as **B**arriers at **L**ow frequencies, improving at higher frequencies


Question 2 [c marks]

7 Compare transformer coupled amplifier and RC coupled amplifier.


Solution

| Parameter | Transformer Coupled | RC Coupled |
|--------------------|--|--|
| Coupling Device | Transformer | Capacitor & Resistor |
| Impedance Matching | Excellent (adjustable via turns ratio) | Poor |
| Frequency Response | Poor (limited due to transformer inductance) | Excellent (wide and flat over audio range) |
| Efficiency | High (no power loss in collector resistor) | Low (power wasted in collector resistor) |
| Size & Weight | Bulky and Heavy | Compact and Light |
| Cost | Expensive | Inexpensive |
| Application | Power Amplifiers (Impedance matching) | Voltage Amplifiers (Audio/Pre-amps) |

Transformer Coupled

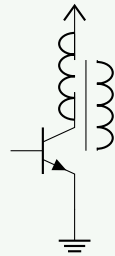

RC Coupled

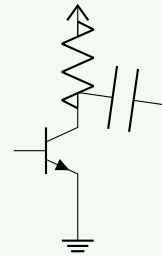


Mnemonic

TREE factors - **T**Ransformers provide **E**fficiency and **E**xcellent impedance matching, RC provides **C**ost savings

Question 3 [a marks]

3 Describe the transistorized tuned amplifier.

Solution

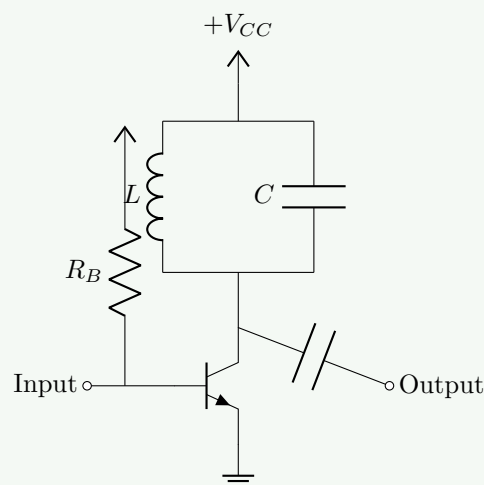

- **Definition:** An amplifier that uses a parallel LC circuit (tank circuit) as the collector load to amplify a specific narrow band of frequencies.
- **Resonance:** The LC circuit resonates at frequency $f_r = \frac{1}{2\pi\sqrt{LC}}$.
- **Gain:** At resonance, the impedance of the tank circuit is maximum (resistive), resulting in maximum voltage

gain.

- **Applications:** Used in the Radio Frequency (RF) and Intermediate Frequency (IF) stages of receivers.


Mnemonic

TRIP to resonance - **T**uned **R**esonant circuits **I**mprove **P**erformance at specific frequencies

Question 3 [b marks]

4 Explain in brief Direct coupled amplifier.

Solution

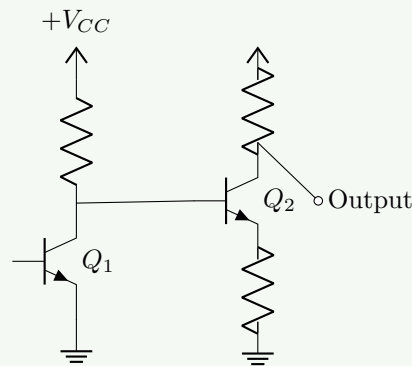

- **Definition:** A multi-stage amplifier where the output of one stage is connected directly to the input of the next stage without any reactive components.
- **Characteristics:**
 - **Low Frequency Response:** Excellent, can amplify down to DC (0 Hz).
 - **Simplicity:** Requires fewer components (no bulky capacitors).
 - **Issues:** Suffers from **DC drift** (thermal instability shifting the operating point).
- **Application:** Linear ICs, Operational Amplifiers, low-frequency instrumentation.

Mnemonic

COLD advantages - **C**ompact design, **O**utstanding low-frequency response, **L**ess components, **D**irect connection

Question 3 [c marks]

7 Describe the importance of h parameters in two port network. Draw h-parameters circuit for CE amplifier.

Solution

Transistor h-parameter Model (CE Configuration):

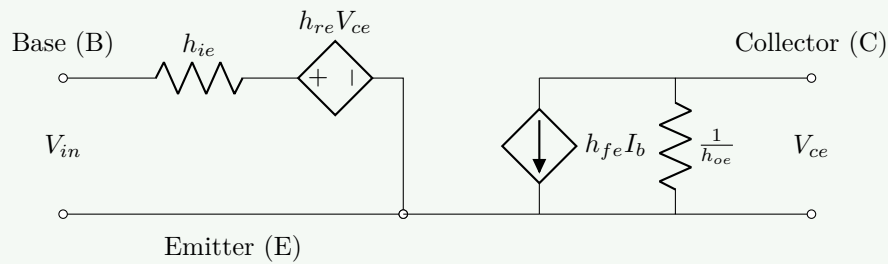


Figure 2. h-parameter Equivalent Circuit for CE

Importance of h-parameters:

- **Hybrid Nature:** They use a mix of units (Ω , Siemens, dimensionless), hence "hybrid".
- **Ease of Measurement:** They are defined based on open-circuit and short-circuit conditions which are easy to implement practically.
- **Accuracy:** They provide accurate results for small-signal analysis at low frequencies.
- **Standardization:** Manufacturers specify transistor characteristics using these parameters (h_{fe} , h_{ie} , etc.).

CE Parameters:

- h_{ie} (h_{11}): Input Impedance.
- h_{re} (h_{12}): Reverse Voltage Ratio.
- h_{fe} (h_{21}): Forward Current Gain.
- h_{oe} (h_{22}): Output Admittance.

Mnemonic

FINE parameters - **F**our **I**nterconnected **N**etwork **E**lements define transistor completely

Question 3 [a marks]

3 Compare transformer coupled amplifier and direct coupled amplifier.

Solution

| Parameter | Transformer Coupled | Direct Coupled |
|--------------------|---------------------|------------------------|
| DC Isolation | Complete | None |
| Freq Response | Poor (limited band) | Excellent (down to DC) |
| Size/Weight | Bulky/Heavy | Compact/Light |
| Impedance Matching | Excellent | Poor |
| Cost | High | Low |
| Drift | No drift problem | Severe drift problem |


Mnemonic

TIP for selection - **T**ransformer for **I**mpedance matching and **P**ower transfer, **D**irect for low frequencies

Question 3 [b marks]

4 Draw and Explain circuit diagram of common emitter amplifier.

Solution

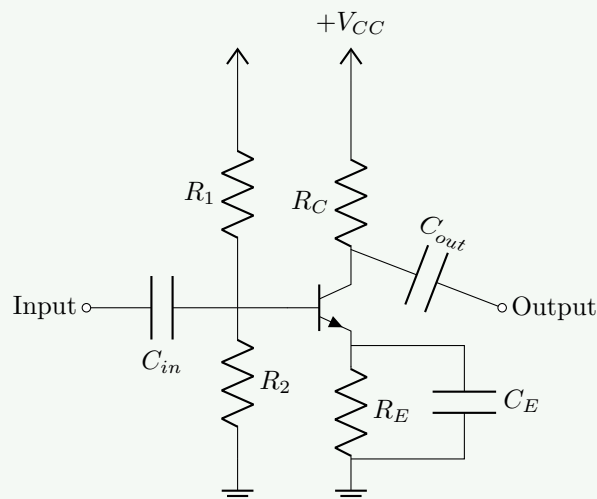

- **Circuit:** Uses Voltage Divider Bias (R_1, R_2) for stability. Capacitors C_{in} and C_{out} block DC. C_E bypasses R_E to prevent AC gain application.
- **Operation:** Small AC input at base varies base current, which is amplified by β at the collector.
- **Phase Shift:** Output is **180° out of phase** with input.
- **Characteristics:** Moderate input/output impedance, high voltage and current gain.

Mnemonic


GAIN characteristics - **G**ood **A**mplification with **I**nverted output and **N**otable efficiency

Question 3 [c marks]

7 Draw Transistor Two Port Network and describe h-parameters for it. Write down advantages of hybrid parameters.

Solution

Two-Port Network:

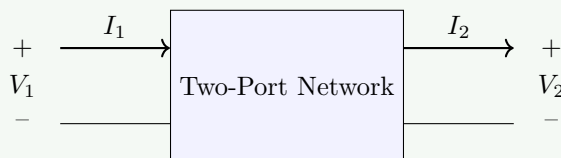

h-Parameter Equations:

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

Advantages:

- **Realizable:** Parameters correspond to easy-to-measure physical quantities (impedance, gain, etc.).
- **Low Frequency Suitability:** Highly accurate for analyzing audio frequency circuits.
- **Universal:** Apply to any active device (BJT, FET) treated as a black box.
- **Dimensional Variety:** Since they mix ohms, siemens, and dimensionless ratios, they flexibly describe complex interactions.


Mnemonic

SMART parameters - **S**imple **M**easurement, **A**ccurate modeling, **R**eliable, **T**emperature-stable

Question 4 [a marks]

3 Explain Darlington pair and its applications.

Solution

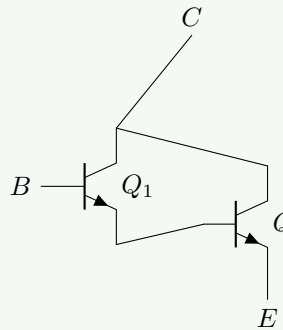

- **Definition:** Two transistors connected such that the emitter current of the first becomes the base current of the second, often packaged as a single device.
- **Current Gain:** The total current gain is the product of individual gains ($\beta_{total} \approx \beta_1 \times \beta_2$). Extremely high.
- **Input Impedance:** Very high.
- **Applications:** High current drivers (relays, motors), input stages of high-impedance amplifiers.

Mnemonic


HIGH gain - **H**ugely **I**ncreased **G**ain from **H**arnessing two transistors

Question 4 [b marks]

4 Describe the diode clamper circuit with necessary diagram.

Solution

Positive Clamper:

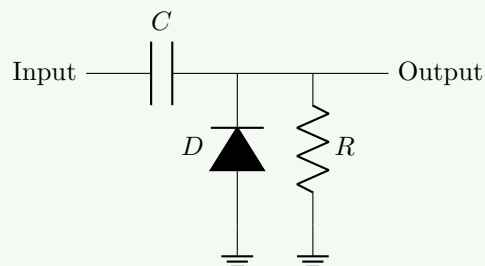

- **Function:** Adds a DC shift to the input signal without changing its shape (DC Restorer).
- **Positive Clamper:** Shifts the signal UP so negative peaks sit on zero (or reference) level.
- **Operation:**
 - During the negative half-cycle, Diode conducts, charging Capacitor to V_p (polarity: + on right).
 - During the positive half-cycle, Diode is reverse biased.
 - Output voltage $V_o = V_{in} + V_C = V_{in} + V_p$.

Mnemonic


CAPS effect - **C**apacitor **A**nd diode **P**air **S**hifts signal by exact DC level

Question 4 [c marks]

7 Explain the construction, working and applications of OLED.

Solution

OLED Construction:

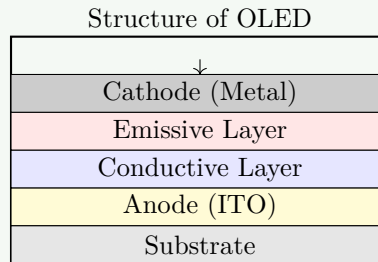

- **Construction:** Consists of organic semiconductor layers sandwiched between two electrodes (Anode and Cathode) deposited on a substrate.
- **Layers:**
 - **Emissive Layer:** Organic molecules that emit light.
 - **Conductive Layer:** Transports holes from anode.
- **Working:**
 - When voltage is applied, current flows from cathode to anode.
 - Cathode gives electrons to emissive layer; Anode removes electrons (adds holes) to conductive layer.
 - Electrons and holes recombine in the emissive layer, releasing energy as photons (Light).
- **Applications:** Premium smartphones, TVs, flexible displays, digital signage.


Mnemonic

OLED benefits - **O**rganic materials, **L**ightweight design, **E**fficient operation, **D**irect emission

Question 4 [a marks]

3 Explain Short note on LDR.

Solution

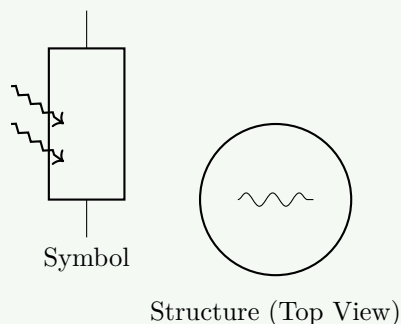

- **Full Form:** Light Dependent Resistor.
- **Principle:** Photoconductivity. Resistance decreases when light intensity increases.
- **Material:** Made of Cadmium Sulfide (CdS).
- **Operation:** In dark, resistance is very high ($M\Omega$). In light, electron-hole pairs are generated, resistance drops (to few $100\ \Omega$).
- **Use:** Automatic street lights, camera exposure meters.

Mnemonic


DARK increases resistance - **D**ecreasing light **A**nd **R**ising darkness **K**eeP resistance high

Question 4 [b marks]

4 Describe the diode clipper circuit with necessary diagram.

Solution

Positive Clipper (Series):

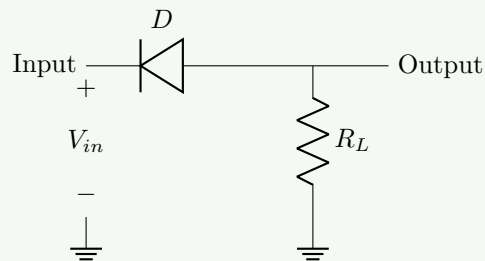

- **Definition:** A circuit that removes (clips) a portion of the input signal waveform.
- **Positive Clipper:** Removes the positive half cycle.
- **Working:**
 - During positive half cycle, Diode is reverse biased (Open). No current flows to load. Output = 0.
 - During negative half cycle, Diode is forward biased (Short). Current flows. Output = Input (approx).
- **Applications:** Waveform shaping, protection against voltage spikes.

Mnemonic


CLIP waves - **C**ircuit **L**imits **I**nput **P**eaks by using diode conduction

Question 4 [c marks]

7 Explain Half Wave and Full wave Voltage Doubler.


Solution

Half-Wave Voltage Doubler:

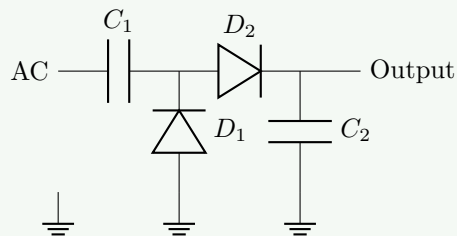

- **Operation:**
 - Negative Cycle: D_1 conducts, C_1 charges to V_m (peak).
 - Positive Cycle: D_2 conducts. Input voltage (V_m) + C_1 voltage (V_m) charges C_2 to $2V_m$.
- **Output:** DC voltage $\approx 2V_m$.

Full-Wave Voltage Doubler:

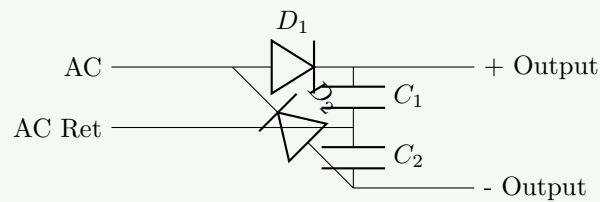

- **Operation:** Charges one capacitor during the positive cycle and the other during the negative cycle. The output is the sum across both.
- **Advantage:** Higher ripple frequency (easier to filter).


Mnemonic

CHASE 2V - Capacitors **H**old **A**lternating **S**upply **E**nergy to produce 2× Voltage

Question 5 [a marks]

3 Draw circuit diagram for +5v Power Supply using its IC and explain in brief.

Solution

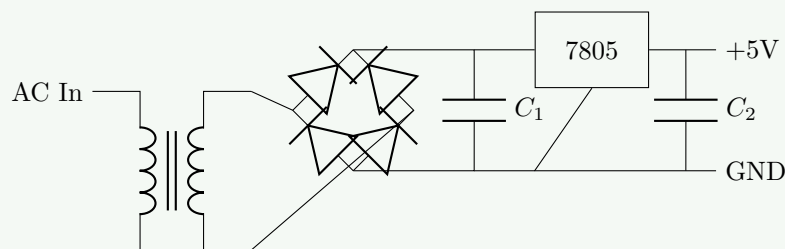

- **Components:**
 - **Transformer:** Steps down AC mains (230V to 9V).
 - **Rectifier:** Converts AC to pulsating DC.
 - **Filter (C_1):** Smooths pulsations to produce unregulated DC.
 - **IC 7805:** Voltage regulator that provides constant +5V output.
 - **Capacitor (C_2):** Removes high-frequency noise/transients.
- **Working:** The AC is rectified, filtered, and then regulated by the 7805 IC which dissipates excess voltage as heat to maintain 5V.



Mnemonic

FIRM voltage - **F**iltered **I**nput, **R**egulated by 7805 **M**akes stable voltage

Question 5 [b marks]

4 Discuss load regulation and line regulation in reference to power supply.

Solution

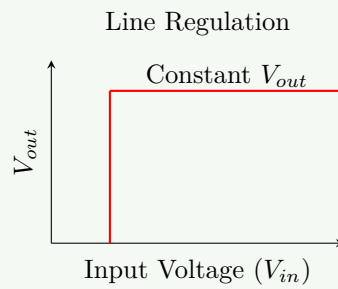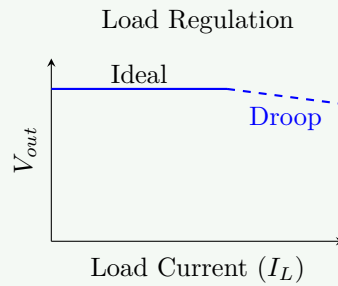

- **Load Regulation:**
 - **Definition:** The ability of a power supply to maintain constant output voltage despite changes in load current.
 - **Formula:** $\%LR = \frac{V_{NoLoad} - V_{FullLoad}}{V_{FullLoad}} \times 100$
 - **Ideal:** 0% (Perfectly stiff voltage source).
- **Line Regulation:**
 - **Definition:** The ability to maintain constant output voltage despite changes in AC input (mains) voltage.
 - **Formula:** $\%SR = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100$
 - **Significance:** Ensures voltage stability during brownouts or surges.


Mnemonic

LIVER health - **L**ine regulation for **V**ariations in Input, load regulation for **E**xternal **R**esistance changes

Question 5 [c marks]

7 Explain adjustable voltage regulator using LM317 with circuit diagram.

Solution

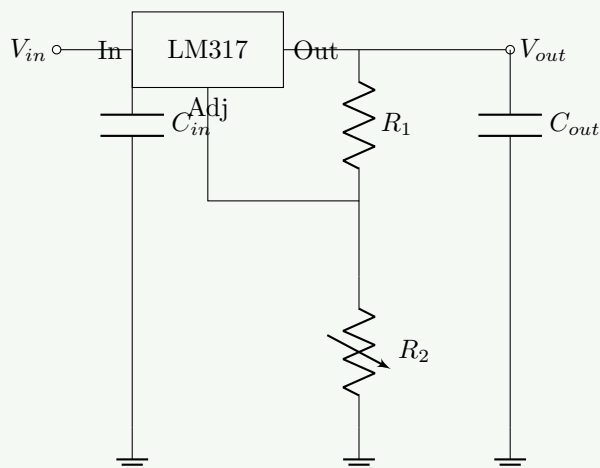

- **Description:** LM317 is a popular adjustable positive voltage regulator capable of supplying more than 1.5A over a 1.25V to 37V output range.
- **Working:**
 - It develops a nominal 1.25V reference voltage (V_{ref}) between the Output and Adjustment terminal.
 - This reference voltage is impressed across resistor R_1 , causing a constant current I_1 to flow.
 - This current also flows through R_2 (ignoring small I_{Adj}).
- **formula:** $V_{out} = 1.25V \left(1 + \frac{R_2}{R_1}\right) + I_{Adj}R_2$
- **Applications:** Variable bench power supplies, battery chargers.


Mnemonic

VAIR control - **V**ariable **A**ddjustable **I**ntegrated **R**egulator controls voltage precisely

Question 5 [a marks]

3 Explain working of solar battery charger circuits.

Solution

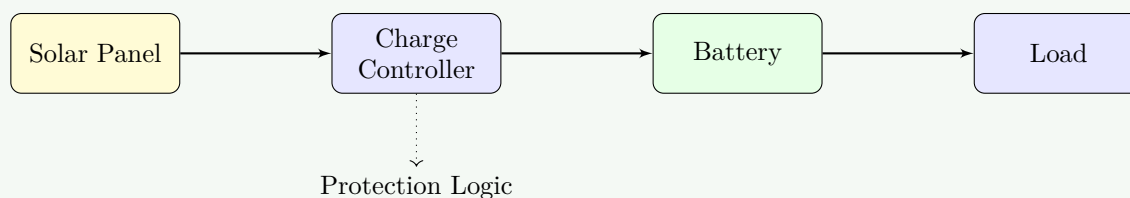


- **Function:** Converts solar energy into electrical energy to charge a rechargeable battery.
- **Charge Controller:**
 - Regulates voltage and current from solar panels.
 - Prevents **Overcharging** (which damages battery) and **Reverse Current** (battery discharging into panel at night).
- **Operation:** Panel generates DC → Controller adjusts levels → Battery stores energy → Load uses it.

Mnemonic

SCBL system - **S**olar panel **C**onverts sunlight, **B**attery stores, **L**oad consumes


Question 5 [b marks]

4 Explain working of UPS.

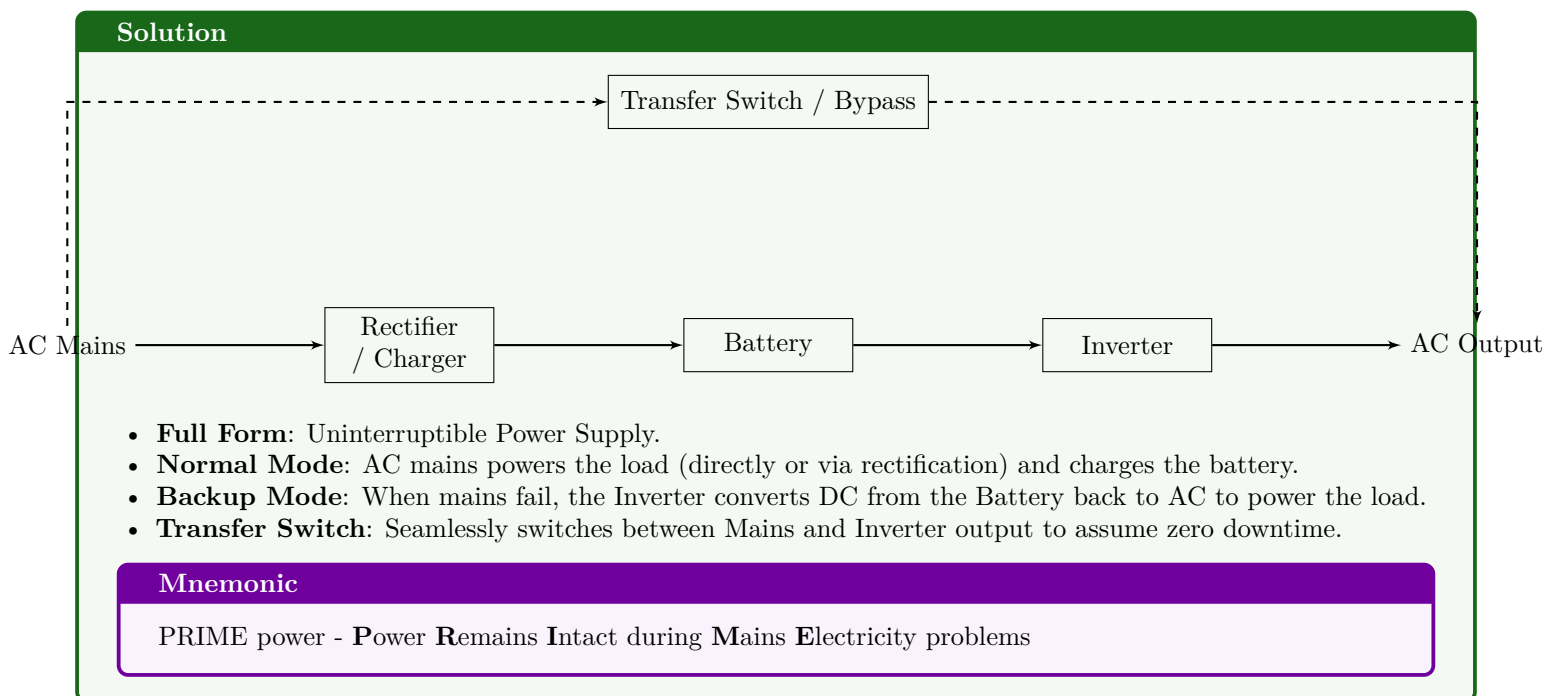

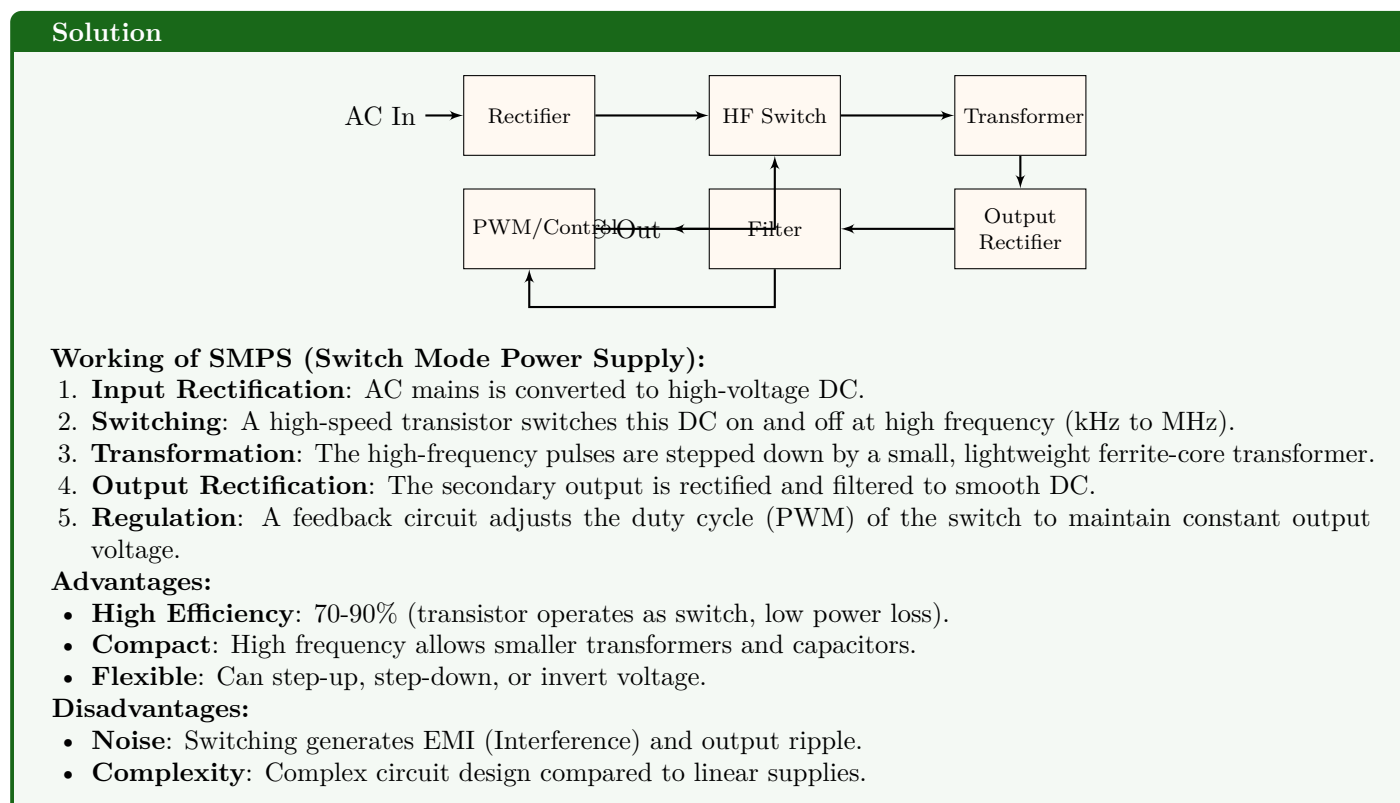Question 5 [c marks]

7 Draw and explain SMPS block diagram with its advantages and disadvantages.



Mnemonic

FISH factors - **F**requency switching, **I**solation, **S**mall size, **H**igh efficiency are SMPS benefits