

VLSI Technology (4361102) - Summer 2025 Solution

Milav Dabgar

May 12 , 2025

Question 1(a) [3 marks]

State importance of scaling

Solution

Scaling is crucial for advancing semiconductor technology and improving device performance.

Table 1. Scaling Benefits

Scaling Benefits	Description
Device Size	Reduces transistor dimensions for higher density
Speed	Faster switching due to shorter channel length
Power	Lower power consumption per operation
Cost	More chips per wafer, reducing cost per function

- **Technology advancement:** Enables Moore's Law continuation
- **Performance boost:** Higher frequency operation possible
- **Market competitiveness:** Smaller, faster, cheaper products

Mnemonic

"Small Devices Speed Progress Cheaply"

Question 1(b) [4 marks]

Compare Planar MOSFET and FinFET

Solution

FinFET technology addresses limitations of planar MOSFET at smaller nodes.

Table 2. Planar MOSFET vs FinFET

Parameter	Planar MOSFET	FinFET
Structure	2D flat channel	3D fin-shaped channel
Gate Control	Single gate	Tri-gate/multi-gate
Short Channel Effects	High at small nodes	Significantly reduced
Leakage Current	Higher subthreshold leakage	Much lower leakage

- **Scalability:** FinFET enables sub-22nm technology nodes
- **Power efficiency:** FinFET offers better power-performance ratio
- **Manufacturing:** FinFET requires more complex fabrication

Mnemonic

“Fins Control Current Better Than Flat”

Question 1(c) [7 marks]

Draw and Explain VDS-ID AND VGS-ID characteristics of N channel MOSFET

Solution

N-channel MOSFET characteristics show device behavior in different operating regions.

Diagram:

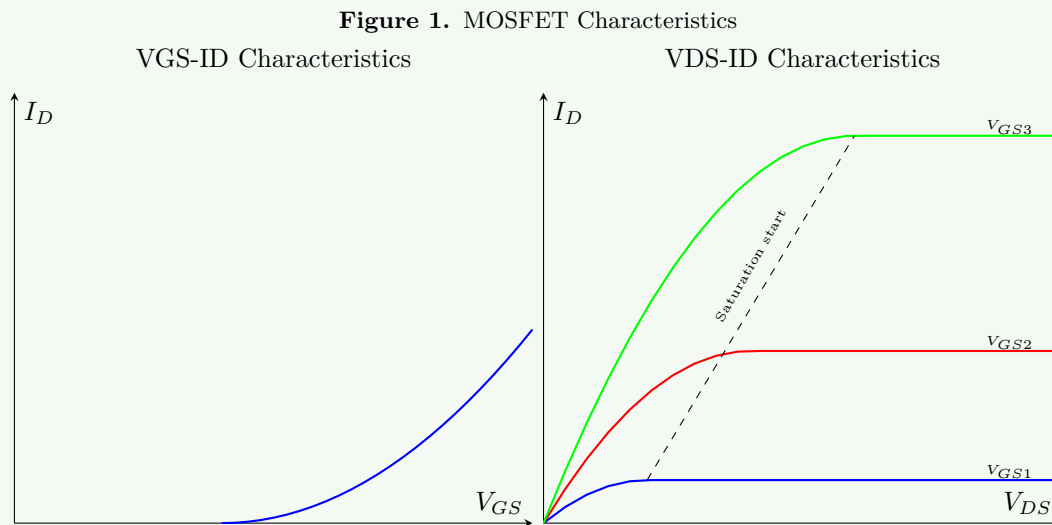


Table 3. MOSFET Operating Regions

Region	Condition	Current Equation
Cutoff	$V_{GS} < V_T$	$I_D = 0$
Linear	$V_{DS} < (V_{GS} - V_T)$	$I_D \propto V_{DS}$
Saturation	$V_{DS} \geq (V_{GS} - V_T)$	$I_D \propto (V_{GS} - V_T)^2$

- **Cutoff:** No current flows, acts as open switch.
- **Linear/Triode:** Current increases linearly with V_{DS} , acts as resistor.
- **Saturation:** Current is constant, independent of V_{DS} , acts as current source.

Mnemonic


“Threshold Gates Linear Saturation”

OR

(c) Explain different condition of MOS under external bias [7 marks]

Answer: External bias creates different charge distributions affecting MOS capacitor behavior.

Diagram:

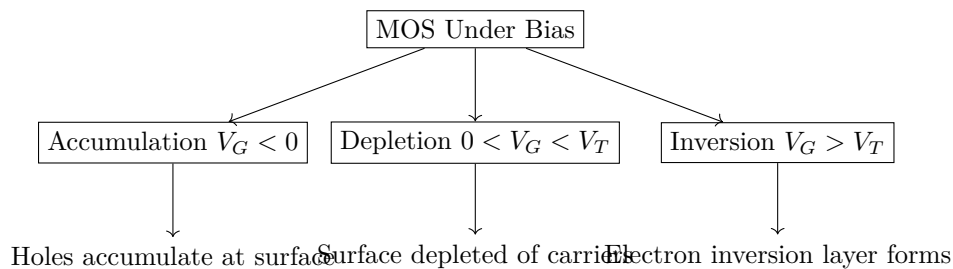**Figure 2.** MOS Bias Modes

Bias Condition	Surface State	Capacitance
Accumulation	Majority carriers at surface	High (C_{ox})
Depletion	No mobile carriers	Medium
Inversion	Minority carriers form channel	High (C_{ox})

- **Flat band voltage:** No charge separation exists
- **Energy band bending:** Determines carrier distribution
- **Surface potential:** Controls inversion layer formation

Mnemonic

[Mnemonic] "Accumulate, Deplete, then Invert"


Question 2(a) [3 marks]

Draw voltage transfer characteristic of ideal inverter

Solution

Ideal inverter provides sharp transition between logic levels with infinite gain.

Diagram:

 Figure 3. Ideal Inverter VTC

- **Sharp transition:** Infinite slope at switching point
- **Noise margins:** $NMH = V_{OH} - V_{IH}$, $NML = V_{IL} - V_{OL}$
- **Perfect logic levels:** $V_{OH} = V_{DD}$, $V_{OL} = 0V$

Mnemonic

“Sharp Switch, Perfect Levels”

Question 2(b) [4 marks]

Explain noise immunity and noise margin

Solution

Noise immunity measures circuit's ability to reject unwanted signal variations.

Table 4. Noise Margin Parameters

Parameter	Definition	Formula
NMH	High-level noise margin	$V_{OH} - V_{IH}$
NML	Low-level noise margin	$V_{IL} - V_{OL}$
Noise Immunity	Ability to reject noise	$Min(NMH, NML)$

- **Logic threshold levels:** V_{IH} (input high), V_{IL} (input low)
- **Output levels:** V_{OH} (output high), V_{OL} (output low)
- **Better immunity:** Larger noise margins provide better protection
- **Design goal:** Maximize noise margins for robust operation

Mnemonic

“Margins Protect Against Noise”

Question 2(c) [7 marks]

Describe inverter circuit with saturated and linear depletion load nMOS inverter

Solution

Depletion load nMOS inverters use depletion transistor as active load resistor.

Diagram:

Figure 4. Depletion Load Inverter

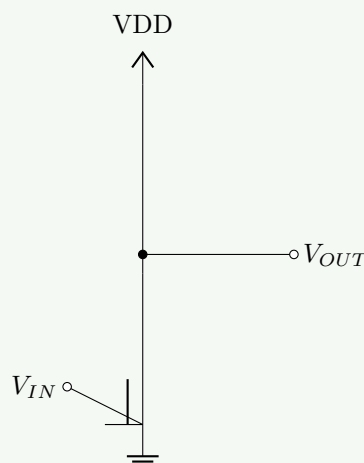


Table 5. Load Types

Load Type	Gate Connection	Operation
Saturated Load	$V_G = V_D$	Always in saturation
Linear Load	$V_G = V_{DD}$	Can operate in linear region

- **Depletion device:** Conducts with $V_{GS} = 0$, acts as current source
- **Load line analysis:** Determines operating point intersection
- **Power consumption:** Always conducting, higher static power
- **Switching speed:** Faster pull-down than pull-up

Mnemonic

“Depletion Loads Drive Outputs”

OR


Question 2(a) [3 marks]

Draw and explain enhancement load inverter

Solution

Enhancement load inverter uses enhancement MOSFET as load with special biasing.

Diagram:

 Figure 5. Enhancement Load Inverter

- **Bootstrap connection:** Gate connected to drain for load
- **Limited output high:** $V_{OUT(max)} = V_{DD} - V_T$
- **Threshold loss:** Enhancement load causes voltage drop

Mnemonic

“Enhancement Loses Threshold”

Question 2(b) [4 marks]

List the advantages of CMOS inverter

Solution

CMOS technology offers superior performance compared to NMOS inverters.

Table 6. CMOS Advantages

Advantage	Benefit
Zero static power	No current path in steady state
Rail-to-rail output	Full V_{DD} and 0V output levels
High noise immunity	Large noise margins
Symmetric switching	Equal rise and fall times

- **Power efficiency:** Only dynamic power during switching
- **Scalability:** Works well at all technology nodes
- **Fan-out capability:** Can drive multiple inputs
- **Temperature stability:** Performance less sensitive to temperature

Mnemonic

“CMOS Saves Power Perfectly”


Question 2(c) [7 marks]

Draw and Explain operating mode of region for CMOS Inverter

Solution

CMOS inverter operation involves five distinct regions based on input voltage.

Diagram:

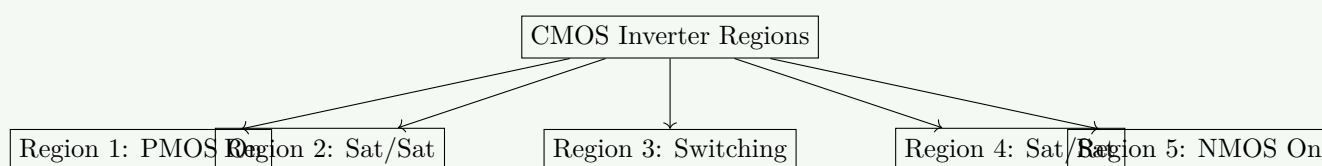Figure 6. CMOS Operation Regions**Table 7.** CMOS Operating Regions

Region	NMOS State	PMOS State	Output
1	OFF	Linear	$V_{OH} \approx V_{DD}$
2	Saturation	Saturation	Transition
3	Saturation	Saturation	$V_{DD}/2$
4	Saturation	Saturation	Transition
5	Linear	OFF	$V_{OL} \approx 0V$

- **Switching threshold:** VTC crosses $V_{DD}/2$ at region 3
- **Current flow:** Only during transition regions 2,3,4
- **Noise margins:** Regions 1 and 5 provide immunity
- **Gain:** Maximum in region 3 (switching point)


Question 3(a) [3 marks]

Draw two input NOR gate using CMOS

Solution

CMOS NOR gate implements De Morgan's law using complementary networks.

Diagram:

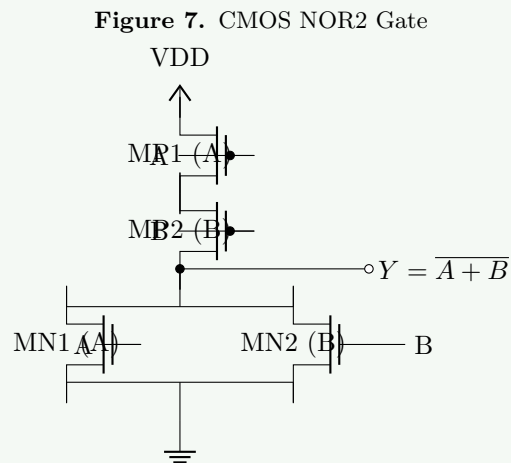

- **Pull-up network:** Series PMOS transistors (A AND B both low for high output)
- **Pull-down network:** Parallel NMOS transistors (A OR B high for low output)
- **Logic function:** $Y = (A + B)' = A' \cdot B'$

Mnemonic

“Series PMOS, Parallel NMOS”

Question 3(b) [4 marks]


Implement Boolean function $Z = [(A+B)C+DE]'$ using CMOS

Solution

Complex CMOS logic uses AOI (AND-OR-Invert) structure for efficient implementation.

Diagram:

Figure 8. CMOS Implementation of $Z = [(A + B)C + DE]'$

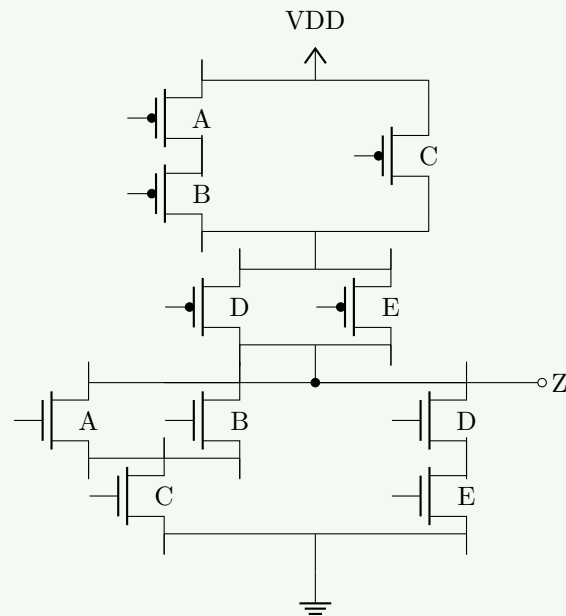

- **AOI structure:** Efficient single-stage implementation
- **Dual networks:** Complementary pull-up and pull-down
- **Logic optimization:** Fewer transistors than separate gates

Mnemonic

“AOI Inverts Complex Logic Efficiently”

Question 3(c) [7 marks]

Draw and explain CMOS NAND2 gate with the parasitic device capacitances

Solution

Parasitic capacitances in CMOS gates affect switching speed and power consumption.

Diagram:

Figure 9. CMOS NAND2 with Parasitics

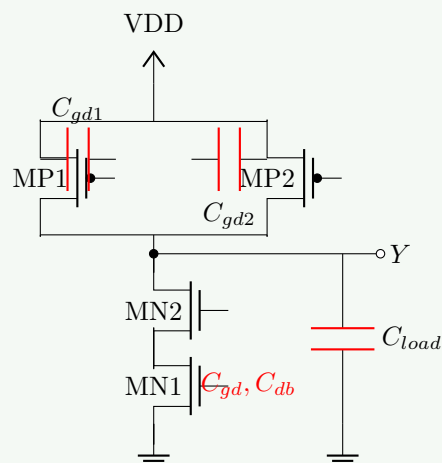


Table 8. Parasitic Capacitances

Capacitance	Location	Effect
C _{gs}	Gate-Source	Input capacitance
C _{gd}	Gate-Drain	Miller effect
C _{db}	Drain-Bulk	Output loading
C _{sb}	Source-Bulk	Source loading

- **Switching delay:** Parasitic capacitances slow transitions
- **Power consumption:** Charging/discharging parasitic caps
- **Miller effect:** C_{gd} creates feedback, slows switching
- **Layout optimization:** Minimize parasitic capacitances

Mnemonic

“Parasitics Slow Gates Down”

OR


Question 3(a) [3 marks]

Draw and explain NOR based Clocked SR latch using CMOS

Solution

Clocked SR latch uses NOR gates with clock enable for synchronous operation.

Diagram:

 

- **Clock control:** S and R effective only when CLK = 1
- **Transparent mode:** Output follows input when clock active
- **Hold mode:** Output maintains state when clock inactive
- **Basic building block:** Foundation for flip-flops

Mnemonic

“Clock Controls Transparent Latching”

Question 3(b) [4 marks]

Implement Boolean function $Z = [AB + C(D + E)]'$ using CMOS

Solution

This function implements inverted sum-of-products using AOI logic structure.

Logic Analysis: $Z = [AB + C(D + E)]' = [AB + CD + CE]'$

Diagram:

Figure 11. CMOS Implementation of $Z = [AB + C(D + E)]'$

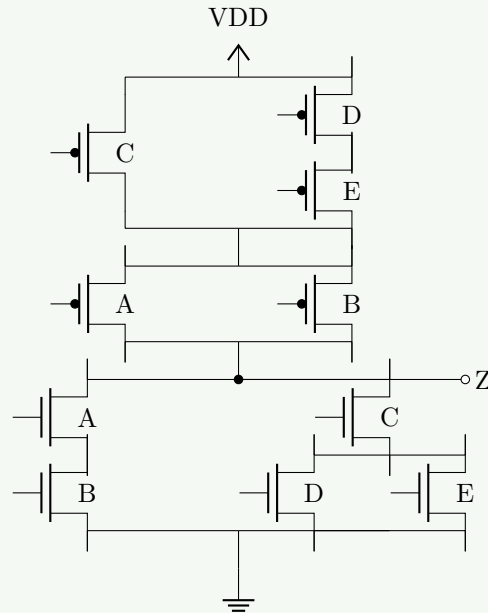


Table 9. Boolean Terms

Term	Inputs	Function
Term 1	A, B	AB
Term 2	C, D	CD
Term 3	C, E	CE
Output	All terms	$(AB + CD + CE)'$

- **AOI implementation:** Single stage, efficient design
- **Transistor count:** Fewer than separate gate implementation
- **Performance:** Fast switching, low power

Mnemonic

“Three AND Terms Feed One NOR”

Question 3(c) [7 marks]

Differentiate AOI and OAI Logic with example

Solution

AOI and OAI are complementary logic families for efficient CMOS implementation.

Table 10. AOI vs OAI

Parameter	AOI (AND-OR-Invert)	OAI (OR-AND-Invert)
Structure	AND gates \rightarrow OR \rightarrow Invert	OR gates \rightarrow AND \rightarrow Invert
Function	$(AB + CD + \dots)'$	$((A + B)(C + D)\dots)'$
PMOS Network	Series-parallel	Parallel-series
NMOS Network	Parallel-series	Series-parallel

AOI Example: $Y = (AB + CD)'$

- PMOS: Series A-B in parallel with Series C-D
- NMOS: Parallel A,B in series with Parallel C,D

OAI Example: $Y = ((A + B)(C + D))'$

- PMOS: Parallel A,B in series with Parallel C,D
- NMOS: Series A-B in parallel with Series C-D
- **Design choice:** Select based on Boolean function form
- **Optimization:** Minimizes transistor count and delay
- **Duality:** AOI and OAI are De Morgan duals

Mnemonic

“AOI ANDs then ORs, OAI ORs then ANDs”

Question 4(a) [3 marks]

Define: 1) Regularity 2) Modularity 3) Locality

Solution

Design hierarchy principles essential for managing VLSI complexity and ensuring successful implementation.

Table 11. Design Principles

Principle	Definition	Benefit
Regularity	Repeated use of similar structures	Easier layout, testing
Modularity	Breaking design into smaller blocks	Independent design, reuse
Locality	Interconnections mostly local	Reduced routing complexity

- **Design efficiency:** Principles reduce design time and effort
- **Verification:** Modular approach simplifies testing
- **Scalability:** Enables larger, more complex designs

Mnemonic

“Regular Modules Stay Local”


Question 4(b) [4 marks]

Implement SR latch (NAND gate) using CMOS inverter

Solution

SR latch using NAND gates provides set-reset functionality with active-low inputs.

Diagram:

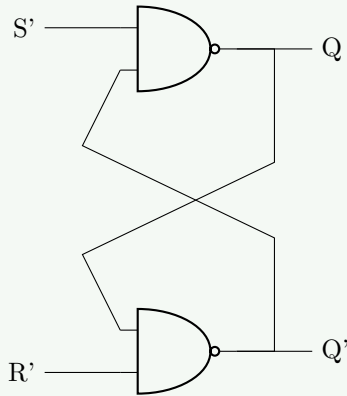Figure 12. NAND SR Latch**Table 12.** SR Latch Truth Table

S'	R'	Q	Q'	State
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q	Q'	Hold
0	0	1	1	Invalid

- **Cross-coupled structure:** Provides memory function
- **Active-low inputs:** $S' = 0$ sets, $R' = 0$ resets
- **Forbidden state:** Both inputs low simultaneously

Mnemonic

“Cross-Coupled NANDS Remember State”

Question 4(c) [7 marks]

Explain VLSI design flow

Solution

VLSI design flow follows systematic steps from specification to fabrication.

Diagram:

Figure 13. VLSI Design Flow

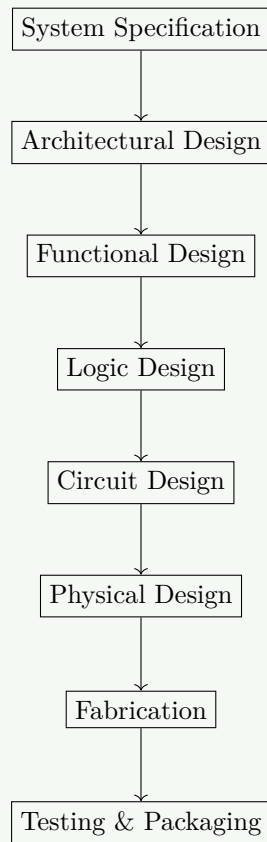


Table 13. Design Steps

Level	Activities	Output
System	Requirements analysis	Specifications
Architecture	Block-level design	System architecture
Logic	Boolean optimization	Gate netlist
Circuit	Transistor sizing	Circuit netlist
Physical	Layout, routing	GDSII file

- **Design verification:** Each level requires validation
- **Iteration:** Feedback loops for optimization
- **CAD tools:** Automation essential for complex designs
- **Time-to-market:** Efficient flow reduces design cycle

Mnemonic

“System Architects Love Circuit Physical Fabrication”

OR


Question 4(a) [3 marks]

Draw and explain Y-chart

Solution

Y-chart represents three design domains and their abstraction levels in VLSI design.

Diagram:

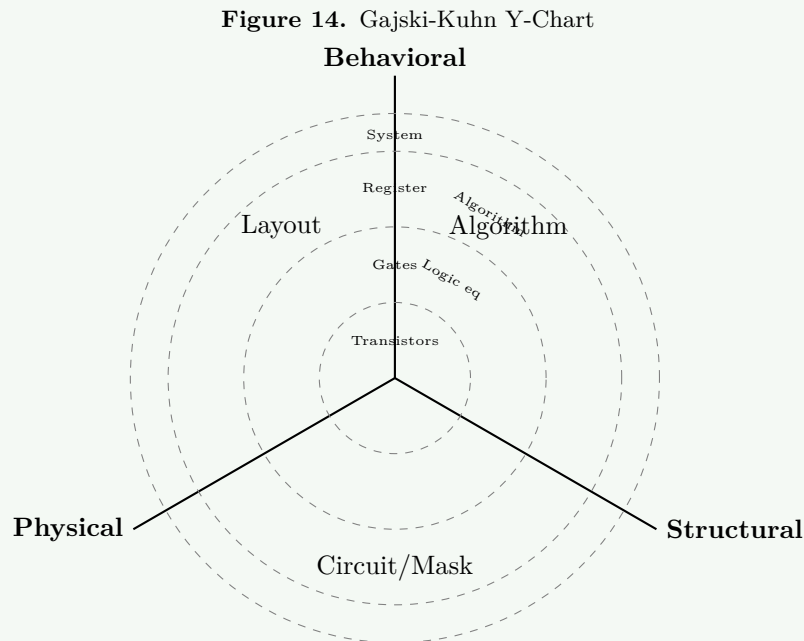

- **Three domains:** Behavioral (function), Structural (components), Physical (geometry)
- **Abstraction levels:** System → Algorithm → Gate → Circuit → Layout
- **Design methodology:** Move between domains at same abstraction level

Mnemonic

“Behavior, Structure, Physics at All Levels”

Question 4(b) [4 marks]

Implement clocked JK latch (NOR gate) using CMOS inverter

Solution

JK latch eliminates forbidden state of SR latch with toggle capability.

Diagram:

Figure 15. Clocked JK Latch

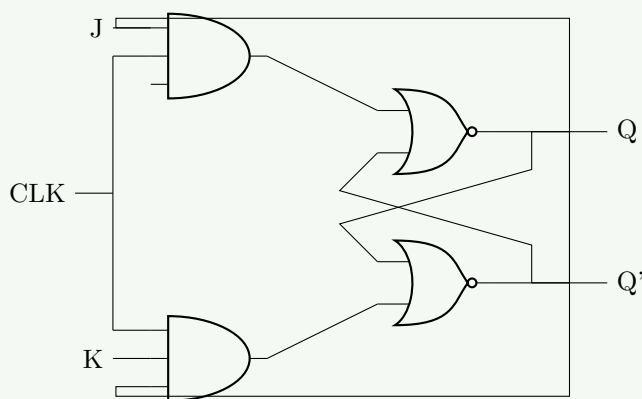


Table 14. JK Latch Truth Table

J	K	Q(next)	Operation
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set
1	1	Q'	Toggle

- **Toggle mode:** J=K=1 flips output state
- **Clock enable:** Active only when CLK=1
- **Feedback:** Uses current output to enable inputs

Mnemonic

“JK Toggles, No Forbidden State”

Question 4(c) [Explain the terms Lithography, Etching, Deposition, Oxidation, Ion implantation, Diffusion marks]

7

Solution

Semiconductor fabrication processes essential for creating integrated circuits.

Table 15. Fabrication Processes

Process	Purpose	Method
Lithography	Pattern transfer	UV exposure through masks
Etching	Material removal	Wet/dry chemical processes
Deposition	Layer addition	CVD, PVD, sputtering
Oxidation	Insulator growth	Thermal/plasma oxidation
Ion Implantation	Doping introduction	High-energy ion bombardment
Diffusion	Dopant distribution	High-temperature spreading

- **Pattern definition:** Lithography creates device features
- **Selective removal:** Etching removes unwanted material
- **Layer building:** Deposition adds required materials
- **Doping control:** Implantation and diffusion create junctions
- **Quality control:** Each step affects final device performance

Mnemonic

“Light Etches Deposited Oxides, Ions Diffuse”

Question 5(a) [3 marks]

Implement 2 input XNOR gate using Verilog

Solution

XNOR gate produces high output when inputs are equal.

Listing 1. Verilog Code for XNOR Gate

```

1 module xnor_gate(
2     input a, b,
3     output y
4 );
5     assign y = ~(a ^ b);
6 endmodule

```

- **Logic function:** $Y = (A \oplus B)' = A'B' + AB$
- **High Output:** When both inputs are 0 or both are 1
- **Applications:** Equality comparison, parity checking

Mnemonic

“XNOR Equals Equal Inputs”

Question 5(b) [4 marks]

Implement Encoder (8:3) using CASE statement in Verilog

Solution

Priority encoder converts 8-bit input to 3-bit binary output using case statement for behavioral modeling.

Listing 2. 8:3 Priority Encoder using CASE

```

1 module encoder_8to3(
2     input [7:0] in,
3     output reg [2:0] out
4 );
5     always @(*) begin
6         case(in)
7             8'b00000001: out = 3'b000;
8             8'b00000010: out = 3'b001;
9             8'b00000100: out = 3'b010;
10            8'b00001000: out = 3'b011;
11            8'b00010000: out = 3'b100;
12            8'b00100000: out = 3'b101;
13            8'b01000000: out = 3'b110;
14            8'b10000000: out = 3'b111;
15            default: out = 3'b000;
16        endcase
17    end
18 endmodule

```

- **Behavioral Modeling:** Case statement describes function conceptually

- **Combinational Logic:** always @(*) block used
- **Default case:** Handles undefined states (e.g., all zeros)

Mnemonic

“One Hot Input, Binary Output”

Question 5(c) [7 marks]

Explain CASE statement in Verilog with suitable examples

Solution

CASE statement provides multi-way branching based on expression value, typically used in combinational logic (decoders, muxes) and state machines.

Syntax:

```

1 case (expression)
2     value1: statement1;
3     value2: statement2;
4     default: default_statement;
5 endcase

```

Example 1: 4:1 Multiplexer

```

1 module mux_4to1(
2     input [1:0] sel,
3     input [3:0] in,
4     output reg out
5 );
6     always @(*) begin
7         case(sel)
8             2'b00: out = in[0];
9             2'b01: out = in[1];
10            2'b10: out = in[2];
11            2'b11: out = in[3];
12        endcase
13    end
14 endmodule

```

Benefits:

- **Readability:** Clearer than multiple if-else statements
- **Synthesis:** Efficiently maps to multiplexers or ROMs
- **Parallel Evaluation:** Hardware checks all conditions simultaneously

Table 16. CASE Statement Variants

Variant	Syntax	Usage
case	case(expr)	Exact bit matching (0, 1, x, z)
casex	casex(expr)	Treats 'x' and 'z' as don't care
casez	casez(expr)	Treats 'z' as don't care

Mnemonic

“CASE Chooses Actions Systematically Everywhere”