

# Basic Electronics Solutions

DI01000051 – Winter 2024

Semester 1 Study Material

*Detailed Solutions and Explanations*

## Question 1(a) [3 marks]

Define Active and Passive Components with example.

### Solution

Table 1: Active vs Passive Components

| Component Type            | Definition   | Power                     | Examples                      |
|---------------------------|--|---------------------------|-------------------------------|
| <b>Active Components</b>  | Components that can amplify signals and control current flow | Can provide power gain    | Transistor, Diode, IC         |
| <b>Passive Components</b> | Components that cannot amplify signals                       | Cannot provide power gain | Resistor, Capacitor, Inductor |

- **Active components:** Control and amplify electrical signals using external power
- **Passive components:** Store or dissipate energy without amplification

### Mnemonic

“Active Amplifies, Passive Preserves”

## Question 1(b) [4 marks]

Explain construction and working of LDR.

### Solution

#### Construction:

- **Serpentine track** of cadmium sulfide on ceramic substrate
- **Metal electrodes** at both ends for connections
- **Protective coating** prevents moisture damage

#### Working Principle:

Light ↓

CdS Track      Resistance decreases  
{ }  
LDR

Terminal   Terminal

- **Light intensity ↑:** Resistance ↓ (conducts more)
- **Darkness:** Resistance ↑ (conducts less)
- **Applications:** Street lights, automatic cameras

### Mnemonic

“Light Low Resistance”

### Question 1(c) [7 marks]

Define Capacitance and explain Aluminum Electrolytic wet type capacitor.

#### Solution

**Capacitance Definition:** Ability to store electrical charge.  $C = Q/V$  (Farads)

**Aluminum Electrolytic Capacitor:**

Positive Terminal

|         |            |
|---------|------------|
| Al Foil | Anode      |
| Oxide   | Dielectric |
| Electro | Cathode    |
| Al Foil | Negative   |

Negative Terminal

**Construction:**

- **Anode:** Aluminum foil with oxide layer
- **Dielectric:** Thin aluminum oxide film
- **Cathode:** Liquid electrolyte with aluminum foil
- **Polarity:** Must be connected correctly

**Features:**

- **High capacitance** values (1 $\mu$ F to 10,000 $\mu$ F)
- **Polarized** - has positive and negative terminals
- **Applications:** Power supply filtering, coupling

#### Mnemonic

“Aluminum Always Amplifies”

### Question 1(c OR) [7 marks]

Explain the color band coding method of Resistor. Write color band of  $32\ \Omega \pm 10\%$  resistance.

#### Solution

Color Code Table:

| Color  | Digit | Multiplier | Tolerance    |
|--------|-------|------------|--------------|
| Black  | 0     | 1          | -            |
| Brown  | 1     | 10         | $\pm 1\%$    |
| Red    | 2     | 100        | $\pm 2\%$    |
| Orange | 3     | 1K         | -            |
| Yellow | 4     | 10K        | -            |
| Green  | 5     | 100K       | $\pm 0.5\%$  |
| Blue   | 6     | 1M         | $\pm 0.25\%$ |
| Violet | 7     | 10M        | $\pm 0.1\%$  |
| Gray   | 8     | 100M       | $\pm 0.05\%$ |
| White  | 9     | 1G         | -            |
| Silver | -     | 0.01       | $\pm 10\%$   |
| Gold   | -     | 0.1        | $\pm 5\%$    |

For  $32\ \Omega \pm 10\%$  :

|        |     |      |        |
|--------|-----|------|--------|
| Orange | Red | Gold | Silver |
| 3      | 2   | 0.1  | 10\%   |
| ↓      | ↓   | ↓    | ↓      |
| 1st    | 2nd | Mult | Tol    |

Calculation:  $3 \times 2 \times 0.1 = 3.2 \times 10 = 32$

#### Mnemonic

“Big Boys Race Our Young Girls But Violet Generally Wins”

### Question 2(a) [3 marks]

Define following terms: 1) Rectifier 2) Ripple factor 3) Filter

#### Solution

| Term          | Definition                                      |
|---------------|---|
| Rectifier     | Circuit that converts AC to pulsating DC        |
| Ripple Factor | Ratio of AC component to DC component in output |
| Filter        | Circuit that smooths pulsating DC to pure DC    |

- Rectifier: Uses diodes to allow current in one direction
- Ripple factor: Lower value means better filtering
- Filter: Uses capacitors/inductors to reduce ripples

#### Mnemonic

“Rectify Ripples, Filter Fixes”

### Question 2(b) [4 marks]

Draw and explain positive clipper circuit with waveform.

#### Solution

Circuit Diagram:

|                     |        |
|---------------------|--------|
| Input               | Output |
| D1 ↓ (Diode)        |        |
| +V (Clipping Level) |        |

Working:

- When  $V_{in} > +V$ : Diode conducts, output = +V
- When  $V_{in} < +V$ : Diode off, output follows input
- Result: Clips positive peaks above +V level

Waveform:

|       |        |
|-------|--------|
| Input | Output |
| V     |        |

Applications: Signal limiting, protection circuits

Mnemonic


“Positive Peaks Prevented”

### Question 2(c) [7 marks]

Explain working of full wave rectifier with two diodes.

**Solution**

**Circuit Diagram:**

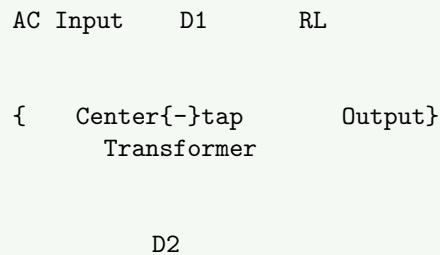

**Working:**

- Positive half-cycle: D1 conducts, D2 off
- Negative half-cycle: D2 conducts, D1 off
- Both diodes work alternately
- Output frequency =  $2 \times \text{input frequency}$

**Key Parameters:**

| Parameter            | Value  |
|----------------------|--------|
| Peak Inverse Voltage | $2V_m$ |
| Efficiency           | 81.2%  |
| Ripple Factor        | 0.48   |
| Form Factor          | 1.11   |

**Advantages:**

- Better efficiency than half-wave
- Lower ripple content
- Higher transformer utilization

Mnemonic

“Two Diodes, Two Halves”

### Question 2(a OR) [3 marks]

Define rectifier and write its applications.

**Solution**

**Definition:** Electronic circuit that converts alternating current (AC) into direct current (DC) using diodes.

**Applications:**

| Application      | Use                                |
|------------------|------------------------------------|
| Power Supplies   | DC voltage for electronic circuits |
| Battery Chargers | Converting AC mains to DC          |
| DC Motors        | Providing DC for motor drives      |

### Electronic Devices Laptops, phones, LED drivers

- Primary function: AC to DC conversion
- Essential component: In all electronic devices

#### Mnemonic

“Rectify AC, Deliver DC”

### Question 2(b OR) [4 marks]

Explain working of Pi ( ) type capacitor filter.

#### Solution

Circuit Diagram:

Input    C1    L    C2    Output  
  ||    UUU    ||

Ground

Working:

- C1: Filters initial ripples from rectifier
- Inductor L: Opposes current changes, smooths further
- C2: Final filtering for smooth DC output
- Combined effect: Excellent ripple reduction

Characteristics:

| Parameter     | Value                       |
|---------------|-----------------------------|
| Ripple Factor | Very low ( $< 0.01$ )       |
| Regulation    | Good                        |
| Cost          | Higher due to inductor      |
| Applications  | High-quality power supplies |

Advantages:

- Excellent filtering performance
- Low ripple content
- Good voltage regulation

#### Mnemonic

“Pi Provides Perfect”

### Question 2(c OR) [7 marks]

Compare half wave and full wave bridge rectifier.

#### Solution

Comparison Table:

| Parameter       | Half Wave | Full Wave Bridge     |
|-----------------|-----------|----------------------|
| Diodes Required | 1         | 4                    |
| Transformer     | Simple    | No center-tap needed |
| Efficiency      | 40.6%     | 81.2%                |
| Ripple Factor   | 1.21      | 0.48                 |

|                         |       |          |
|-------------------------|-------|----------|
| PIV                     | $V_m$ | $V_m$    |
| Output Frequency        | $f$   | $2f$     |
| Transformer Utilization | 28.7% | 81.2%    |
| Cost                    | Low   | Moderate |

#### Circuit Diagrams:

##### Half Wave:

AC    D1    Output  
RL

##### Full Wave Bridge:

AC    D1    Output  
RL  
  
AC    D2

#### Key Differences:

- Full wave: Better efficiency and lower ripple
- Half wave: Simpler but poor performance
- Bridge: No center-tap transformer required

#### Mnemonic

“Half Wastes, Full Works”

### Question 3(a) [3 marks]

Draw the symbols of following: 1) Zener diode 2) LED 3) Varactor diode

#### Solution

##### Electronic Symbols:

Zener Diode:                  LED:                  Varactor Diode:  
  
Z

##### Symbol Details:

| Component      | Symbol Feature                                 |
|----------------|--|
| Zener Diode    | Normal diode with Z-shaped cathode             |
| LED            | Diode with arrows showing light emission       |
| Varactor Diode | Diode with parallel lines (variable capacitor) |

- Zener: Z indicates zener characteristics
- LED: Arrows show light output direction
- Varactor: Lines represent variable capacitance

### Mnemonic

“Zener Zigs, LED Lights, Varactor Varies”

### Question 3(b) [4 marks]

Explain construction and working of LED.

#### Solution

##### Construction:

Light Output ↑

Wire Bond

P{-N Junction }

Cathode Anode

LED Chip

##### Materials:

- P-type: Boron-doped semiconductor
- N-type: Phosphorus-doped semiconductor
- Common materials: GaAs, GaP, GaN

##### Working Principle:

- Forward bias: Electrons recombine with holes
- Energy release: In form of photons (light)
- Color: Depends on semiconductor material and bandgap
- Efficiency: High light output with low power

##### Applications:

- Indicators: Status lights, displays
- Lighting: LED bulbs, strips
- Electronics: Seven-segment displays

### Mnemonic


“Light Emitting, Energy Efficient”

### Question 3(c) [7 marks]

Explain working characteristics of Zener diode.

#### Solution

##### V-I Characteristics:

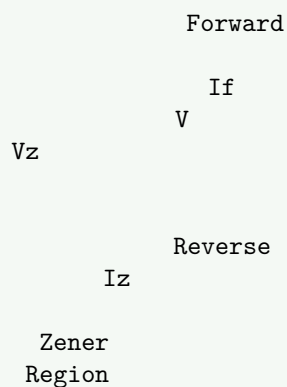

##### Key Regions:

| Region       | Characteristics               |
|--------------|-------------------------------|
| Forward Bias | Normal diode operation (0.7V) |
| Reverse Bias | Small leakage current         |
| Zener Region | Constant voltage ( $V_z$ )    |
| Breakdown    | Sharp voltage breakdown       |

Important Parameters:

- Zener Voltage ( $V_z$ ): Breakdown voltage
- Zener Current ( $I_z$ ): Current in breakdown region
- Maximum Power:  $V_z \times I_{z(max)}$
- Temperature coefficient: Voltage variation with temperature

Applications:

- Voltage regulation: Maintains constant output
- Reference voltage: Precise voltage source
- Overvoltage protection: Protects circuits

Advantages:

- Sharp breakdown: Well-defined voltage
- Low dynamic resistance: Good regulation
- Wide range: Available in many voltages

**Mnemonic**

“Zener Zones Zero variation”

### Question 3(a OR) [3 marks]

Enlist the applications of varactor diode.

**Solution**

Applications Table:

| Application                    | Function                       |
|--------------------------------|--------------------------------|
| Voltage Controlled Oscillators | Frequency tuning with voltage  |
| Automatic Frequency Control    | Maintains oscillator frequency |
| Electronic Tuning              | Radio/TV channel selection     |
| Phase Locked Loops             | Frequency synchronization      |
| Frequency Multipliers          | Harmonic generation            |
| Parametric Amplifiers          | Low-noise amplification        |

Key Features:

- Voltage variable: Capacitance changes with reverse voltage
- No mechanical parts: Electronic tuning only
- Fast response: Quick frequency changes

**Mnemonic**

“Voltage Varies Capacitance”

### Question 3(b OR) [4 marks]

Explain working of photo diode.

**Solution**

Construction & Symbol:

Light ↓ ↓ ↓



Cathode    Anode

- **Light absorption:** Creates electron-hole pairs
- **Reverse bias:** Widens depletion region
- **Photocurrent:** Proportional to light intensity
- **Fast response:** Quick detection capability

| Parameter     | Description                   |
|---------------|-------------------------------|
| Dark Current  | Current without light         |
| Photocurrent  | Current proportional to light |
| Responsivity  | Current per unit light power  |
| Response Time | Speed of detection            |

- **Light sensors:** Automatic lighting systems
- **Optical communication:** Fiber optic receivers
- **Safety systems:** Smoke detectors
- **Solar panels:** Light to electrical energy

**“Photo Produces Proportional current”**

**Explain Zener diode as a voltage regulator.**

Ground

- Zener operates in breakdown region
- Output voltage remains constant at  $V_z$
- Series resistor  $R_s$  limits current
- Load changes don't affect output voltage

| Parameter         | Formula                      |
|-------------------|------------------------------|
| Series Resistance | $R_s = (V_{in} - V_z) / I_z$ |
| Load Current      | $I_L = V_z / R_L$            |
| Zener Current     | $I_z = I_s - I_L$            |
| Power Dissipation | $P_z = V_z \times I_z$       |

#### Regulation Characteristics:

- Line regulation: Output change with input variation
- Load regulation: Output change with load variation
- Efficiency: Generally low due to Zener power loss

#### Advantages:

- Simple circuit: Few components required
- Good regulation: Stable output voltage
- Fast response: Quick voltage correction

#### Limitations:

- Poor efficiency: Power wasted in Zener
- Limited current: Cannot supply high currents
- Temperature sensitivity: Voltage varies with temperature

#### Applications:

- Reference voltage: Precise voltage source
- Simple regulators: Low current applications
- Protection circuits: Overvoltage protection

#### Mnemonic

“Zener Zones provide Zero variation”

### Question 4(a) [3 marks]

Draw the symbol and construction of PNP and NPN transistor with proper notation.

#### Solution

##### Transistor Symbols:

NPN Transistor:

Collector (C)

Base

Emitter  
(E)

PNP Transistor:

Collector (C)

Base

Emitter  
(E)

##### Construction Diagrams:

NPN Structure:

Collector  
N{-}type

P{-}type     Base

N{-}type  
Emitter

PNP Structure:

Collector  
P{-}type

N{-}type     Base     }

P{-}type  
Emitter

##### Terminal Identification:

- Emitter: Heavily doped, arrow shows current direction
- Base: Thin, lightly doped middle region
- Collector: Moderately doped, collects charge carriers

##### Current Direction:

- NPN: Arrow points outward (emitter to base)
- PNP: Arrow points inward (base to emitter)

### Mnemonic

“NPN: Not Pointing iN, PNP: Pointing iN Please”

### Question 4(b) [4 marks]

Draw and Explain characteristics of CE amplifier.

#### Solution

##### CE Amplifier Circuit:

V<sub>cc</sub>

R<sub>c</sub>

V<sub>out</sub>

C Collector

B Base V<sub>in</sub>

E Emitter

R<sub>e</sub>

Ground

##### Input Characteristics (I<sub>B</sub> vs V<sub>BE</sub>):

I<sub>B</sub>  
(mA)

V<sub>BE</sub> (V)  
0 0.7

##### Output Characteristics (I<sub>C</sub> vs V<sub>CE</sub>):

I<sub>C</sub> I<sub>B</sub> = 40μA  
(mA)

I<sub>B</sub> = 30μA

I<sub>B</sub> = 20μA

I<sub>B</sub> = 10μA

V<sub>CE</sub> (V)  
0 5 10

##### Key Features:

| Parameter        | CE Configuration                        |
|------------------|---|
| Current Gain     | = I <sub>C</sub> /I <sub>B</sub> (high) |
| Voltage Gain     | High                                    |
| Power Gain       | Very high                               |
| Input Impedance  | Medium                                  |
| Output Impedance | High                                    |
| Phase Shift      | 180°                                    |

**Regions of Operation:**

- Cut-off: Both junctions reverse biased
- Active: BE forward, BC reverse biased
- Saturation: Both junctions forward biased

**Mnemonic**

“Common Emitter, Current Enlarged”

**Question 4(c) [7 marks]**

Derive relation between current gains  $\alpha$ ,  $\beta$  and  $\gamma$ .

**Solution****Current Gain Definitions:**

| Gain    | Configuration    | Formula     |
|---------|------------------|-------------|
| (Alpha) | Common Base      | $= I_C/I_E$ |
| (Beta)  | Common Emitter   | $= I_C/I_B$ |
| (Gamma) | Common Collector | $= I_E/I_B$ |

**Derivation:**

Step 1: Basic Current Relation  $I_E = I_B + I_C$  ... (Kirchhoff's Current Law)

Step 2: Express  $I_C$  in terms of  $I_E$   $I_C = \alpha I_E$  ... (1)

Step 3: Substitute in current equation  $I_E = I_B + \alpha I_E$   $I_E - \alpha I_E = I_B$   $I_E(1 - \alpha) = I_B$   $I_E = I_B/(1 - \alpha)$  ... (2)

Step 4: Find  $\beta = I_C/I_B$  From (1):  $I_C = \alpha I_E$  From (2):  $I_E = I_B/(1 - \alpha)$  Therefore:  $I_C = \alpha I_B/(1 - \alpha)$

Step 5: Final relation for  $\beta = I_C/I_B = \alpha/(1 - \alpha)$  ... (3)

Step 6: Express  $\gamma$  in terms of  $\beta$  From equation (3):  $(1 - \alpha) = \alpha/\beta$   $1 - \alpha = \alpha/\beta$

$1 = \alpha/\beta + \alpha = \alpha(1/\beta + 1)$  Therefore:

$1 = \alpha(1/\beta + 1)$  ... (4)

Step 7: Find  $\gamma = I_E/I_B$  From (2):  $\gamma = 1/(1 - \alpha)$  Substituting  $\alpha$  from (4):

$\gamma = 1/(1 - \alpha/(1 + \beta))$

$\gamma = (1 + \beta)/(1 + \beta - \alpha)$

$\gamma = 1 + \beta$

... (5)

**Final Relations:**

| Relation                     | Formula                            |
|------------------------------|------------------------------------|
| $\alpha$ in terms of $\beta$ | $\alpha = \beta/(1 + \beta)$       |
| $\beta$ in terms of $\alpha$ | $\beta = \alpha/(1 - \alpha)$      |
| $\gamma$ in terms of $\beta$ | $\gamma = 1 + \beta$               |
| Verification                 | $\alpha + \beta \times \gamma = 1$ |

**Typical Values:**

- $\alpha \approx 0.98$  to  $0.995$
- $\beta \approx 50$  to  $200$

- $\gamma \approx 51$  to  $201$

**Mnemonic**

“Alpha Beta Gamma, Always Better Gains”

**Question 4(a OR) [3 marks]**

Define Active, Saturation and Cut-off region for transistor amplifier.

## Solution

### Operating Regions:

| Region     | Base-Emitter   | Base-Collector | Characteristics      |
|------------|----------------|----------------|----------------------|
| Active     | Forward Biased | Reverse Biased | Amplification region |
| Saturation | Forward Biased | Forward Biased | Switch ON state      |
| Cut-off    | Reverse Biased | Reverse Biased | Switch OFF state     |

### Detailed Description:

#### Active Region:

- Normal amplification mode
- $I_C = \beta I_B$  relationship holds
- Linear operation for small signals

#### Saturation Region:

- Both junctions forward biased
- Maximum collector current flows
- $V_{CE} \approx 0.2V$  (very low)
- Used in switching applications

#### Cut-off Region:

- No base current ( $I_B = 0$ )
- No collector current ( $I_C = 0$ )
- Transistor acts like open switch

## Mnemonic

“Active Amplifies, Saturated Switches, Cut-off Cuts”

## Question 4(b OR) [4 marks]

Explain working of Transistor as an amplifier.

## Solution

### Amplifier Circuit:

Vcc

Rc

Vout (amplified)

C NPN Transistor

Vin B

E

Re

Ground

### Working Principle:

- Small input signal applied to base-emitter
- Input resistance is low (few  $k\Omega$ )
- Small base current controls large collector current
- Output taken from collector-emitter
- Current amplification:  $I_C = \beta I_B$

### Amplification Process:

| Parameter    | Input               | Output            |
|--------------|---------------------|-------------------|
| Signal Level | Small               | Large             |
| Current      | $\mu\text{A}$ range | $\text{mA}$ range |
| Voltage      | $\text{mV}$ range   | $\text{V}$ range  |
| Power        | $\mu\text{W}$ range | $\text{mW}$ range |

**Key Features:**

- Current gain: (50-200 typical)
- Voltage gain: Depends on load resistance
- Power gain: Product of current and voltage gains
- Phase inversion:  $180^\circ$  in CE configuration

**Applications:**

- Audio amplifiers: Music systems
- RF amplifiers: Radio transmitters
- Op-amp stages: Integrated circuits

**Mnemonic**

“Tiny signal Triggers Tremendous output”

**Question 4(c OR) [7 marks]**

Compare CB, CC, and CE amplifier configuration.

**Solution**

**Comprehensive Comparison:**

| Parameter          | Common Base (CB)                | Common Emitter (CE)            | Common Collector (CC)             |
|--------------------|---------------------------------|--------------------------------|-----------------------------------|
| Input Terminal     | Emitter                         | Base                           | Base                              |
| Output Terminal    | Collector                       | Collector                      | Emitter                           |
| Common Terminal    | Base                            | Emitter                        | Collector                         |
| Current Gain       | $< 1$                           | $\gg 1$                        | $= (1 + \beta)$                   |
| Voltage Gain       | High                            | High                           | $< 1$ ( $\approx 1$ )             |
| Power Gain         | Medium                          | Very High                      | Medium                            |
| Input Resistance   | Very Low ( $20-50\Omega$ )      | Medium ( $1-5\text{k}\Omega$ ) | Very High ( $100\text{k}\Omega$ ) |
| Output Resistance  | Very High ( $1\text{M}\Omega$ ) | High ( $50\text{k}\Omega$ )    | Low ( $25\Omega$ )                |
| Phase Shift        | $0^\circ$                       | $180^\circ$                    | $0^\circ$                         |
| Frequency Response | Excellent                       | Good                           | Good                              |
| Applications       | RF Amplifiers                   | Audio Amplifiers               | Buffer, Impedance Matching        |

### Circuit Diagrams:

#### Common Base:

|          |          |        |
|----------|----------|--------|
| Vcc      | Vcc      | Vcc    |
| Rc       | Rc       | Re     |
| Vout     | Vout     | Vin    |
| C        | C        | C      |
| B Ground | Vin B    | B      |
| Vin E    | E Ground | E Vout |

### Key Characteristics:

#### Common Base (CB):

- High frequency performance
- No current gain but high voltage gain
- Input-output isolation excellent
- Used in: RF amplifiers, high-frequency circuits

#### Common Emitter (CE):

- Most popular configuration
- High current and voltage gain
- Good compromise of all parameters
- Used in: Audio amplifiers, general amplification

#### Common Collector (CC):

- Unity voltage gain (voltage follower)
- High current gain
- Impedance transformation (high to low)
- Used in: Buffer amplifiers, impedance matching

#### Selection Criteria:

| Application           | Best Configuration | Reason                           |
|-----------------------|--------------------|----------------------------------|
| High Frequency        | CB                 | Excellent frequency response     |
| General Amplification | CE                 | High power gain                  |
| Buffer/Isolation      | CC                 | High input, low output impedance |
| Power Amplifiers      | CE                 | Maximum power gain               |

### Mnemonic

“CB for Communication, CE for Common use, CC for Coupling”

### Question 5(a) [3 marks]

Draw the pin diagram of IC 555.

### Solution

#### IC 555 Pin Diagram:

|        |         |   |                 |
|--------|---------|---|-----------------|
| IC 555 |         |   |                 |
| 1      | Ground  | 8 | Vcc             |
| 2      | Trigger | 7 | Discharge       |
| 3      | Output  | 6 | Threshold       |
| 4      | Reset   | 5 | Control Voltage |

DIP{-8 Package}

#### Pin Functions:

| Pin | Name      | Function                   |
|-----|-----------|----------------------------|
| 1   | Ground    | 0V reference               |
| 2   | Trigger   | Start timing cycle         |
| 3   | Output    | Timer output               |
| 4   | Reset     | Master reset (active low)  |
| 5   | Control   | Voltage reference control  |
| 6   | Threshold | Stop timing cycle          |
| 7   | Discharge | Timing capacitor discharge |
| 8   | Vcc       | Power supply (+5V to +18V) |

**Key Points:**

- Dual-in-line 8-pin package
- Power supply: 5V to 18V DC
- Output current: Up to 200mA
- Reset pin: Normally connected to Vcc

**Mnemonic**

“Great Timer, Great Pins”

**Question 5(b) [4 marks]**

List out Features of 555 Timer IC.

**Solution**

**Key Features:**

| Feature           | Specification                 |
|-------------------|-------------------------------|
| Supply Voltage    | 5V to 18V                     |
| Output Current    | 200mA source/sink             |
| Temperature Range | 0 <sup>o</sup> to 70          |
| Timing Range      | µs to hours                   |
| Accuracy          | ±1% <i>typical</i>            |
| Modes             | Monostable, Astable, Bistable |

**Technical Features:**

- CMOS/TTL compatible output levels
- High current output capability
- Wide supply voltage range
- Temperature stable operation

**Functional Features:**

- Three operating modes available
- External timing components
- Reset capability for control
- Low power consumption design

**Advantages:**

- Versatile timer for multiple applications
- Easy to use with minimal external components
- Reliable operation in various conditions

**Mnemonic**

“Fantastic Features, Flexible Functions”

**Question 5(c) [7 marks]**

Explain Mono stable multivibrator using 555 timer IC.



## Solution

### Monostable Circuit:

Vcc

8 (Vcc)

R 7 (Discharge)

6 (Threshold)

2 4 (Reset)

5 (Control)

3

1 (Ground)

C

Ground

### Working Principle:

#### Stable State:

- Output LOW (approximately 0V)
- Capacitor discharged through pin 7
- Threshold voltage below  $V_{cc}/3$

#### Triggered State:

- Negative pulse applied to trigger (pin 2)
- Output goes HIGH immediately
- Discharge transistor turns OFF
- Capacitor starts charging through R

#### Timing Period:

- Duration:  $T = 1.1 \times R \times C$
- Output remains HIGH for calculated time
- Automatic return to stable state

#### Return to Stable:

- Capacitor voltage reaches  $2V_{cc}/3$
- Threshold triggered (pin 6)
- Output returns to LOW
- Discharge begins again

#### Key Characteristics:

| Parameter       | Description          |
|-----------------|----------------------|
| Pulse Width     | $T = 1.1 RC$         |
| Trigger Level   | $V_{cc}/3$           |
| Threshold Level | $2V_{cc}/3$          |
| Output High     | $\sim V_{cc} - 1.5V$ |
| Output Low      | $\sim 0.1V$          |

#### Applications:

- Pulse generation: Fixed width pulses
- Time delays: Switch-on delays
- Missing pulse detection: Watchdog timers
- Debouncing circuits: Switch contact cleaning

Design Example: For  $T = 1ms$ : If  $C = 0.1\mu F$ , then  $R = 9.1k\Omega$

## Mnemonic

“Mono means One pulse Only”

### Question 5(a OR) [3 marks]

List out applications of IC 555.

#### Solution

##### Timer Applications:

| Category         | Applications                            |
|------------------|---|
| Timing Circuits  | Delay timers, Pulse generators          |
| Oscillators      | Clock generators, Frequency dividers    |
| Control Circuits | PWM controllers, Motor speed control    |
| Detection        | Missing pulse detectors, Burglar alarms |
| Communication    | Tone generators, Frequency shift keying |
| Automotive       | Turn signal flashers, Windshield wipers |

##### Mode-wise Applications:

###### Monostable Mode:

- Time delays in circuits
- Pulse width generation
- Debouncing switches

###### Astable Mode:

- LED flashers and blinkers
- Clock signals generation
- Tone generation for buzzers

###### Bistable Mode:

- Flip-flop circuits
- Memory elements
- Latch circuits

###### Common Projects:

- Electronic dice using LEDs
- Traffic light controllers
- Digital clocks and timers

#### Mnemonic


“Timer for Tremendous Tasks”


### Question 5(b OR) [4 marks]

Draw and explain the internal block diagram of IC 555.

#### Solution

##### Internal Block Diagram:

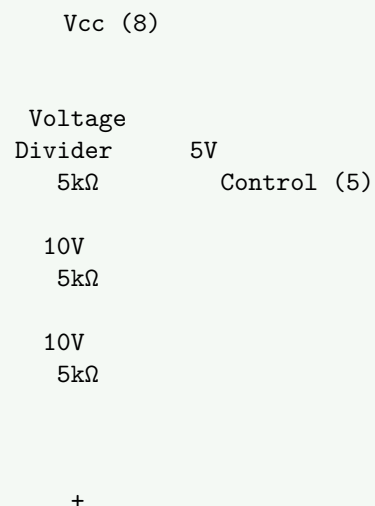

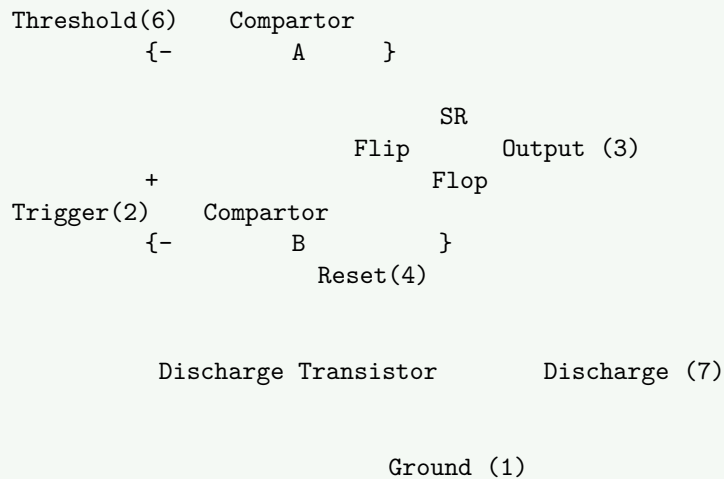

## Block Functions:

| Block                | Function                                      |
|----------------------|---|
| Voltage Divider      | Creates $V_{cc}/3$ and $2V_{cc}/3$ references |
| Comparator A         | Compares threshold with $2V_{cc}/3$           |
| Comparator B         | Compares trigger with $V_{cc}/3$              |
| SR Flip-Flop         | Controls output state                         |
| Discharge Transistor | Discharges timing capacitor                   |
| Output Buffer        | Provides high current output                  |

**Working:**

- Comparators set and reset flip-flop
- Output buffer amplifies flip-flop output
- Discharge transistor controlled by flip-flop
- Reference voltages set trigger levels

### Mnemonic

## “Internal Intelligence, Integrated Implementation”

**Question 5(c OR) [7 marks]**

**Explain astable multivibrator using 555 timer IC.**

## Solution

### Astable Circuit:

```

Vcc
    8 (Vcc)
    4 (Reset)
R1    7 (Discharge)
    6 (Threshold)
R2
    5 (Control)
2
    3 (Output)
    1 (Ground)
C
Ground

```

### Working Principle:

#### Charging Phase:

- Capacitor charges through  $R1 + R2$
- Output HIGH during charging
- Charging time:  $T1 = 0.693(R1 + R2)C$
- Voltage rises from  $V_{cc}/3$  to  $2V_{cc}/3$

#### Discharging Phase:

- Capacitor discharges through  $R2$  only
- Output LOW during discharging
- Discharging time:  $T2 = 0.693 \times R2 \times C$
- Voltage falls from  $2V_{cc}/3$  to  $V_{cc}/3$

#### Frequency Calculations:

| Parameter    | Formula                                 |
|--------------|---|
| Time HIGH    | $T1 = 0.693(R1 + R2)C$                  |
| Time LOW     | $T2 = 0.693 \times R2 \times C$         |
| Total Period | $T = T1 + T2 = 0.693(R1 + 2R2)C$        |
| Frequency    | $f = 1.44/[(R1 + 2R2)C]$                |
| Duty Cycle   | $D = (R1 + R2)/(R1 + 2R2) \times 100\%$ |

#### Waveforms:

Vout

T1    T2  
Time  
Period T

Design Example: For  $f = 1\text{kHz}$ ,  $D = 60\%$ :

- Choose  $C = 0.1\mu\text{F}$
- Calculate  $R1 = 7.2\text{k}\Omega$ ,  $R2 = 3.6\text{k}\Omega$

#### Key Features:

- Continuous oscillation without external trigger
- Frequency adjustable by R and C values
- Duty cycle always  $> 50\%$  in basic circuit
- Stable operation over wide temperature range

#### Applications:

- LED flashers and blinkers
- Clock generators for digital circuits
- Tone generators for alarms
- PWM signal generation

#### Modifications for 50% Duty Cycle:

- Add diode in parallel with  $R2$
- Separate paths for charge and discharge
- Equal charge/discharge times possible

#### Mnemonic

“Astable Always Alternates Automatically”