

# Elements of Electrical & Electronics Engineering (1313202) - Winter 2023

## Solution

Milav Dabgar

January 17, 2024

### Question 1(a) [3 marks]

Explain difference between Active and passive network.

#### Solution

Active Network	Passive Network
Contains at least one energy source	Contains no energy source
Can deliver power to other elements	Cannot deliver power to other elements
Examples: Transistors, Op-amps, Batteries	Examples: Resistors, Capacitors, Inductors

#### Mnemonic

“Active Adds Power, Passive Pulls Power”


### Question 1(b) [4 marks]

State and explain Kirchhoff's voltage law (KVL).

#### Solution

**Kirchhoff's Voltage Law (KVL):** The algebraic sum of all voltages around any closed path (loop) in a circuit is zero.

**Mathematical Form:**  $\sum V = 0$  or  $V_1 + V_2 + V_3 + V_4 = 0$

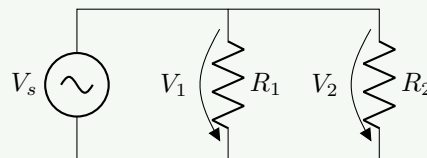

**Figure 1.** Closed Loop for KVL

- **Circuit Application:** When moving around a loop, voltage rises (batteries) are positive and voltage drops (components) are negative.
- **Physical Meaning:** Total energy in a closed loop is conserved.

#### Mnemonic

“Voltage Loop Sum Zero”

## Question 1(c) [7 marks]

Define the following terms: (1) Charge (2) Current (3) Potential (4) E.M.F. (5) Inductance (6) Capacitance (7) Frequency.

### Solution

Term	Definition
<b>Charge</b>	The basic electrical quantity measured in coulombs (C); flow of electrons creates electricity.
<b>Current</b>	The rate of flow of electric charge, measured in amperes (A); $I = dQ/dt$ .
<b>Potential</b>	Electric potential energy per unit charge, measured in volts (V).
<b>E.M.F.</b>	Electromotive force, energy supplied by source per unit charge, measured in volts (V).
<b>Inductance</b>	Property of a conductor to oppose change in current, measured in henry (H).
<b>Capacitance</b>	Ability of a component to store electric charge, measured in farad (F).
<b>Frequency</b>	Number of cycles per second of an alternating quantity, measured in hertz (Hz).

### Mnemonic

“Careful Currents Pass Easily Into Circuit Frequently”

## Question 1(c) OR [7 marks]

State Ohm’s law. Write its application and limitation.

### Solution

**Ohm’s Law:** The current flowing through a conductor is directly proportional to the potential difference across it and inversely proportional to its resistance.

**Mathematical Form:**  $I = V/R$

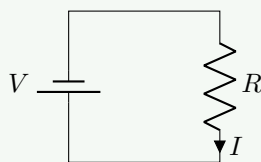


Figure 2. Ohm’s Law Circuit

#### Applications of Ohm’s Law:

- Computing current, voltage, resistance in circuits.
- Design of electrical networks.
- Power calculations ( $P = VI = I^2R = V^2/R$ ).
- Voltage division and current division.

#### Limitations of Ohm’s Law:

- Not valid for non-linear elements (diodes, transistors).
- Not applicable at very high frequencies.
- Not valid for non-metallic conductors like semiconductors.
- Not applicable for vacuum tubes and gaseous devices.

### Mnemonic


“Voltage Drives, Resistance Restricts”

## Question 2(a) [3 marks]

Draw and explain energy band diagrams for insulator, conductor and Semiconductor.

### Solution

#### Energy Band Diagrams:

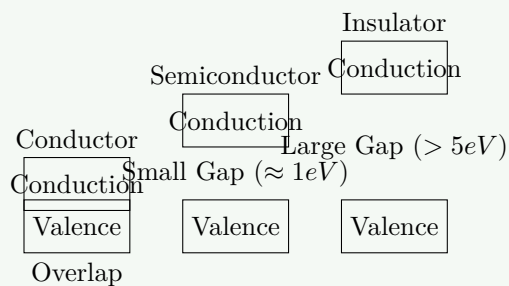

**Figure 3.** Energy Band Diagrams

- **Conductor:** Valence and conduction bands overlap, allowing easy electron flow.
- **Semiconductor:** Small energy gap ( $\approx 1 \text{ eV}$ ) between bands; electrons can jump with thermal energy.
- **Insulator:** Large energy gap ( $> 5 \text{ eV}$ ) prevents electron movement between bands.

### Mnemonic


“Conductors Connect, Semiconductors Sometimes, Insulators Impede”

## Question 2(b) [4 marks]

Write statement of Maximum power transfer theorem and reciprocity theorem.

### Solution

Theorem	Statement
<b>Maximum Power Transfer Theorem</b>	Maximum power is transferred from source to load when load resistance equals the source internal resistance ( $R_L = R_S$ ).
<b>Reciprocity Theorem</b>	In a linear passive network with a single source, if the source is moved from position A to B, the current at A due to source at B will equal the current at B when source was at A.

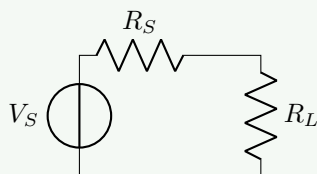

Max Power when  $R_L = R_S$

### Mnemonic


“Match Resistance to Maximize Power; Switch Source and Sink, Current Stays Same”

## Question 2(c) [7 marks]

Explain the formation and conduction of N-type materials.

### Solution

**N-type Semiconductor Formation:**

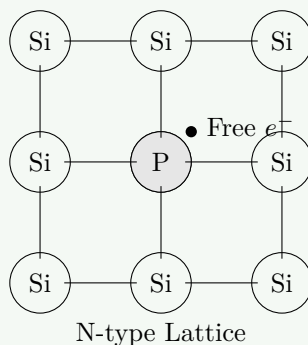

**Figure 4.** Pentavalent Doping (N-type)

- **Doping Process:** Silicon/Germanium (4 valence  $e^-$ ) doped with pentavalent elements (P, As, Sb).
- **Extra Electron:** Each dopant atom provides 1 extra electron after covalent bonding.
- **Conduction Mechanism:**
  - **Majority Carriers:** Free electrons (negative charge carriers).
  - **Minority Carriers:** Holes (very few).
- **Electrical Properties:** Increased conductivity and negative charge carriers.

### Mnemonic


“Pentavalent Provides Plus one Electron, Negative-type”

## Question 2(a) OR [3 marks]

Define valence band, conduction band and forbidden gap.

### Solution

Term	Definition
<b>Valence Band</b>	The highest energy band filled with electrons, where electrons are bound to atoms.
<b>Conduction Band</b>	The band above valence band where electrons move freely and contribute to electrical conduction.
<b>Forbidden Gap</b>	The energy range between valence and conduction bands where no electron states exist.

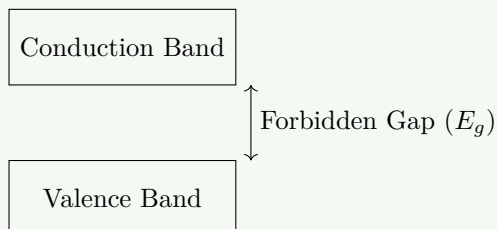

**Mnemonic**


“Valence Holds, Forbidden Blocks, Conduction Flows”

**Question 2(b) OR [4 marks]**

Define the terms active power, reactive power and power factor with power triangle.

**Solution****Power Terms in AC Circuits:**

Term	Definition
<b>Active Power (P)</b>	Actual power consumed, measured in watts (W); $P = VI \cos \theta$ .
<b>Reactive Power (Q)</b>	Power oscillating between source and load, measured in VAR; $Q = VI \sin \theta$ .
<b>Power Factor (PF)</b>	Ratio of active power to apparent power; $PF = \cos \theta$ .

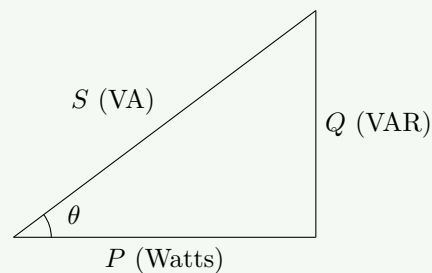**Power Triangle:**

**Figure 5.** Power Triangle

- **Apparent Power (S):** Vector sum of active and reactive power.
- **Power Factor:**  $\cos \theta = P/S$  (0 to 1).

**Mnemonic**


“Active Power Works, Reactive Power Waits”

**Question 2(c) OR [7 marks]**

Explain the structure of atom of trivalent, tetravalent and pentavalent elements.

**Solution****Atomic Structures:**

Element Type	Valence Electrons	Examples	Electronic Configuration
<b>Trivalent</b>	3	Boron, Aluminum, Gallium	3 electrons in outermost shell
<b>Tetravalent</b>	4	Carbon, Silicon, Germanium	4 electrons in outermost shell
<b>Pentavalent</b>	5	Nitrogen, Phosphorus, Arsenic	5 electrons in outermost shell

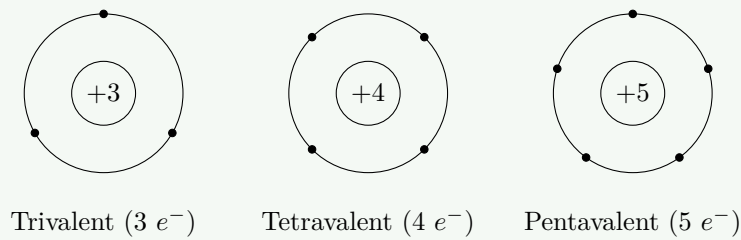

**Figure 6.** Valence Shell Electrons

- **Trivalent Elements:** Used as p-type dopants in semiconductors.
- **Tetravalent Elements:** Form semiconductor base materials.
- **Pentavalent Elements:** Used as n-type dopants in semiconductors.

#### Mnemonic


“Three Tries to Bond, Four Forms Full bonds, Five Frees an Electron”

### Question 3(a) [3 marks]

Draw the symbol of photodiode and state it's application.

#### Solution

**Photodiode Symbol:**

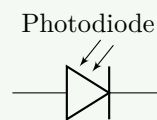

**Applications of Photodiode:**

- Light sensors and detectors.
- Optical communication systems.
- Camera exposure controls.
- Barcode scanners.
- Medical instruments.
- Solar cells.

#### Mnemonic

“Photons Produce Current”

### Question 3(b) [4 marks]

Write a Short note on LED.

#### Solution

**LED (Light Emitting Diode):**

Parameter	Description
<b>Structure</b>	p-n junction with special doping materials.
<b>Working</b>	Electrons recombine with holes, releasing energy as photons.
<b>Materials</b>	GaAs (red), GaP (green), GaN (blue), etc.
<b>Voltage</b>	Forward voltage typically 1.8V to 3.3V depending on color.

**Advantages:**

- High efficiency (low power consumption).
- Long life (50,000+ hours).
- Small size and durability.
- Various colors available.

**Applications:**


- Indicators and displays.
- Lighting systems.
- TV/monitor backlights.
- Traffic signals.

**Mnemonic**

“Light Emits when Diode conducts”

**Question 3(c) [7 marks]**

Draw and explain VI characteristic of PN junction diode.

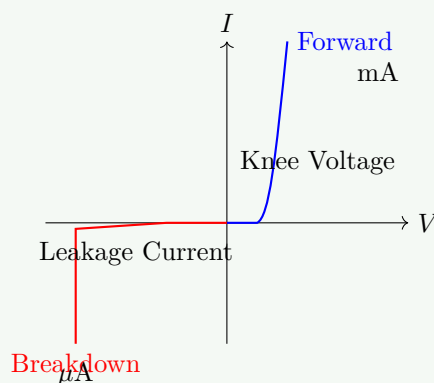**Solution****P-N Junction Diode V-I Characteristic:**

**Figure 7.** V-I Characteristics

**Forward Bias Region:**

- **Knee Voltage:** 0.3V (Ge), 0.7V (Si) where current starts flowing.
- **Current Equation:**  $I = I_s(e^{qV/kT} - 1)$ .
- **Conductivity:** High (low resistance).

**Reverse Bias Region:**

- **Leakage Current:** Very small reverse current (micro-amps).
- **Breakdown Region:** Sharp increase in current at breakdown voltage.
- **Conductivity:** Very low (high resistance).

**Key Points:**

- **Barrier Potential:** Decreases in forward bias, increases in reverse bias.
- **Diode Resistance:** Dynamic resistance changes with applied voltage.
- **Temperature Effect:** Voltage drop decreases with temperature increase.

**Mnemonic**

“Forward Flows Freely, Reverse Resists”

**Question 3(a) OR [3 marks]**

List the applications of PN junction diode.

**Solution****Applications of PN Junction Diode:**


Application Category	Examples
<b>Rectification</b>	Half-wave rectifier, Full-wave rectifier, Bridge rectifier.
<b>Signal Processing</b>	Signal demodulation, Clipping circuits, Clamping circuits.
<b>Protection</b>	Voltage spike protection, Reverse polarity protection.
<b>Logic Gates</b>	Diode logic circuits, Switching applications.
<b>Voltage Regulation</b>	Zener diodes for voltage references.
<b>Light Applications</b>	LEDs, Photodiodes, Solar cells.

**Mnemonic**

“Rectify, Process, Protect, Logic, Regulate, Light”

**Question 3(b) OR [4 marks]**

Explain the formation of depletion region in unbiased P-N junction.

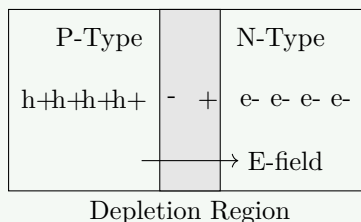**Solution****Depletion Region Formation:**

**Figure 8.** Depletion Region

**Process:**

- **Diffusion:** Electrons from n-side diffuse to p-side; holes from p-side diffuse to n-side.
- **Recombination:** Electrons and holes recombine at the junction.
- **Immobile Ions:** Exposed positive ions in n-region, negative ions in p-region.
- **Electric Field:** Forms between positive and negative ions, opposing further diffusion.
- **Equilibrium:** Diffusion current equals drift current; no net current flows.

**Properties of Depletion Region:**

- No free charge carriers.
- Acts as insulator.
- Width depends on doping levels.
- Contains built-in potential barrier.




**Mnemonic**

“Diffusion Depletes Carriers, Creating Electric barrier”

**Question 3(c) OR [7 marks]**

Explain construction, working and applications of PN junction diode.

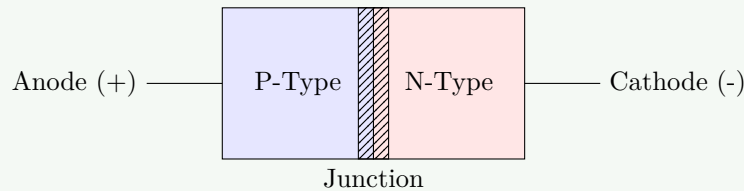**Solution****Construction of PN Junction Diode:**

**Figure 9.** PN Junction Construction

- **P-Type Region:** Silicon/Germanium doped with trivalent impurities (boron, aluminum).
- **N-Type Region:** Silicon/Germanium doped with pentavalent impurities (phosphorus, arsenic).
- **Junction:** Interface between p and n regions with depletion layer.
- **Terminals:** Anode (p-side) and Cathode (n-side).

**Working Principle:**

Bias Condition	Behavior
Forward Bias	Depletion region narrows, current flows when $V > 0.7V$ (Si).
Reverse Bias	Depletion region widens, only small leakage current flows.

**Applications:**

- Rectification in power supplies.
- Signal demodulation in radios.
- Voltage regulation (Zener).
- Signal clipping and clamping.
- Logic gates and switching.
- Light emission and detection.

**Mnemonic**

“Forward Flow, Reverse Restrict, Convert AC to DC”

**Question 4(a) [3 marks]**

Define: (1) Ripple frequency (2) Ripple factor (3) PIV of a diode.

**Solution**

Term	Definition
<b>Ripple Frequency</b>	The frequency of AC component present in rectified DC output; for half-wave $f = f_{in}$ , for full-wave $f = 2f_{in}$ .
<b>Ripple Factor (<math>\gamma</math>)</b>	Ratio of RMS value of AC component to DC component in rectifier output; $\gamma = V_{ac(rms)}/V_{dc}$ .
<b>PIV of Diode</b>	Peak Inverse Voltage - maximum reverse voltage a diode can withstand without breakdown.

**Mnemonic**

“Ripples Per second, Ripple Proportion, Reverse Peak Voltage”

**Question 4(b) [4 marks]**

Give comparison between full wave rectifier with two diodes and full wave bridge rectifier.

**Solution**

Parameter	Center-Tapped Full Wave	Bridge Rectifier
Diodes Used	2 diodes	4 diodes
Transformer	Center-tapped required	No center tap needed
PIV of Diode	$2V_m$	$V_m$
Output Voltage	$V_{dc} = 0.637V_m$	$V_{dc} = 0.637V_m$
Ripple Factor	0.48	0.48
Efficiency	81.2%	81.2%
TUF	0.693	0.812

**Mnemonic**


“Bridge Beats Tap with Lower PIV but Needs More Diodes”

**Question 4(c) [7 marks]**

Explain zener diode as voltage regulator.

**Solution**

**Zener Diode Voltage Regulator:**

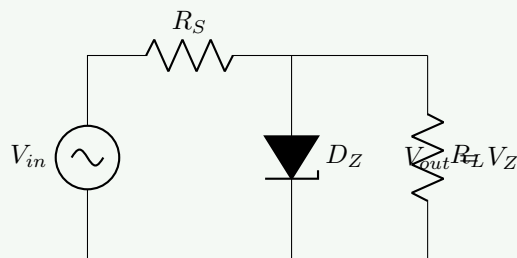

**Figure 10.** Zener Voltage Regulator

**Working Principle:**

- **Reverse Biased:** Zener operates in breakdown region.
- **Constant Voltage:** Maintains fixed voltage ( $V_Z$ ) across its terminals.
- **Current Regulation:** Series resistor ( $R_S$ ) limits current.
- **Load Changes:** When load current changes, Zener current changes to maintain constant output voltage.

**Design Equations:**

- $R_S = (V_{in} - V_Z)/(I_L + I_Z)$ .
- Power rating of Zener:  $P_Z = V_Z \times I_{Z(max)}$ .

**Mnemonic**

“Zener Stays at breakdown Voltage despite Current changes”


**Question 4(a) OR [3 marks]**

What is rectifier? Explain full wave rectifier with waveforms.


**Solution**

**Rectifier:** A circuit that converts AC voltage to pulsating DC voltage by allowing current flow in one direction only.

**Full Wave Rectifier (Center-Tapped):**

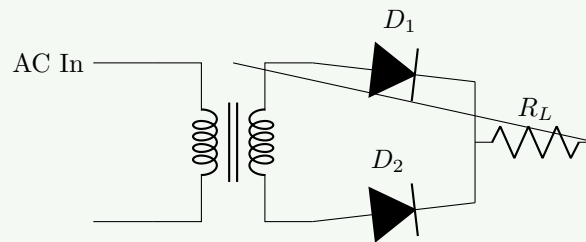

**Waveforms:**

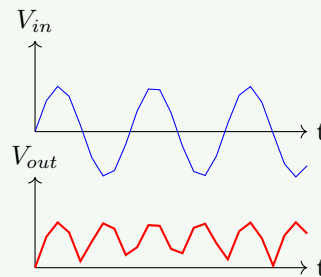

**Figure 11.** Full Wave Rectifier Waveforms

- **Operation:** Both half cycles of AC input are converted to same polarity.
- **Frequency:** Output ripple frequency is twice the input frequency.
- **Voltage:**  $V_{dc} = 0.637V_m$ .

**Mnemonic**

“Full Wave Forms Full Output”

**Question 4(b) OR [4 marks]**

Why filter is required in rectifier? State the different types of filter and explain any one type of filter.


**Solution**

**Need for Filters:** Rectifiers produce pulsating DC with large ripples; filters smooth this output to provide steady DC voltage.

**Types of Filters:**

- Capacitor (C) filter.

- Inductor (L) filter.
- LC filter.
- $\pi$  (Pi) filter.
- RC filter.

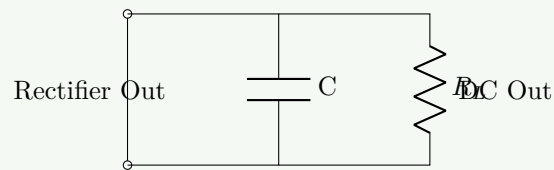**Capacitor Filter:****Figure 12.** Capacitor Filter**Working Principle:**

- Capacitor charges during voltage rise to peak.
- Discharges slowly through load during voltage fall.
- Reduces ripple by providing discharge path with time constant  $RC$ .

**Mnemonic**


“Capacitor Catches Charge and Releases Slowly”

**Question 4(c) OR [7 marks]**

Write the need of rectifier. Explain bridge rectifier with circuit diagram and draw its input and output waveforms.

**Solution****Need for Rectifiers:**

- Convert AC to DC for electronic devices.
- Power supplies and battery charging.
- Signal demodulation.

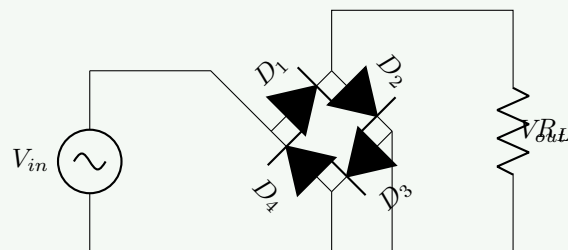**Bridge Rectifier Circuit:****Figure 13.** Bridge Rectifier**Working Principle:**

- **Positive Half Cycle:**  $D_1$  and  $D_3$  conduct.
- **Negative Half Cycle:**  $D_2$  and  $D_4$  conduct.
- **Result:** Unidirectional current through  $R_L$ .

**Waveforms:** Input is sine wave, Output is pulsating DC (full-wave rectified).

**Mnemonic**

“Bridge Brings Both halves to Direct Current”

### Question 5(a) [3 marks]

Explain causes of electronic waste.

#### Solution

Causes of Electronic Waste:	Cause	Description
	<b>Rapid Technology Change</b>	Frequent upgrades and obsolescence of electronics.
	<b>Short Lifecycle</b>	Devices designed with limited useful life.
	<b>Consumer Behavior</b>	Preference for new gadgets over repair.
	<b>Manufacturing Issues</b>	Poor quality leading to early failures.
	<b>Marketing Strategies</b>	Promoting new models through planned obsolescence.

#### Mnemonic

“Upgrade, Use, Throw, Repeat”

### Question 5(b) [4 marks]

Compare PNP and NPN transistors.

#### Solution

Parameter	PNP Transistor	NPN Transistor
Majority Carriers	Holes	Electrons
Current Flow	Emitter to Collector	Collector to Emitter
Biasing	Emitter +ve, Collector -ve	Collector +ve, Emitter -ve
Switching Speed	Slower	Faster
Usage	Less common	More common

#### Mnemonic

“PNP: Positive-Negative-Positive; NPN: Negative-Positive-Negative”

### Question 5(c) [7 marks]

Draw the symbol, explain the construction and working of MOSFET.

#### Solution

MOSFET (N-Channel Enhancement):

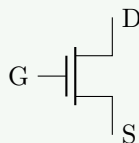


Figure 14. MOSFET Symbol

Construction:

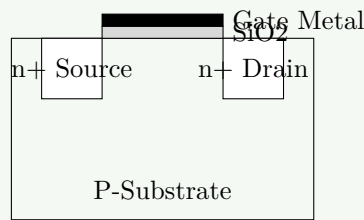


Figure 15. MOSFET Construction

**Working Principle (Enhancement Mode):**

- No channel exists initially.
- When positive voltage applied to Gate ( $V_{GS} > V_{Th}$ ), electrons are attracted to surface.
- An N-channel is formed connecting Source and Drain, allowing current flow.

**Mnemonic**

“Gate Voltage Controls Electron Channel”

**Question 5(a) OR [3 marks]**

Explain methods to handle electronic waste.

**Solution****Methods to Handle E-Waste:**

- **Reduce:** Designing long-lasting products.
- **Reuse:** Refurbishing used electronics.
- **Recycle:** Recovering materials.
- **Recover:** Extracting energy/metals.

**Mnemonic**

“Reduce, Reuse, Recycle, Recover Resources”

**Question 5(b) OR [4 marks]**

Derive the relationship between  $\alpha_{dc}$  and  $\beta_{dc}$ .

**Solution****Given:**

- $\alpha_{dc} = I_C / I_E$
- $\beta_{dc} = I_C / I_B$

**Derivation:** From KCL:  $I_E = I_C + I_B$  Divide by  $I_C$ :

$$\frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\frac{1}{\alpha} = \frac{\beta + 1}{\beta}$$

Similarly,

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

### Mnemonic


“Alpha approaches One as Beta approaches Infinity”

## Question 5(c) OR [7 marks]

Explain common collector configuration with its input and output characteristics.

### Solution

**Common Collector (Emitter Follower):**

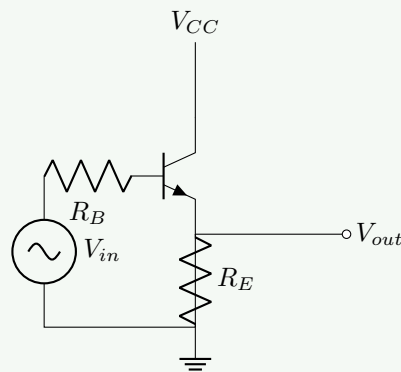

**Figure 16.** Common Collector Circuit

**Characteristics:**

- **Input:** Plot of  $I_B$  vs  $V_{BC}$ . High input impedance.
- **Output:** Plot of  $I_E$  vs  $V_{CE}$ . Low output impedance.
- **Voltage Gain:**  $\approx 1$ .
- **Current Gain:** High ( $\beta + 1$ ).

### Mnemonic

“Collector Common, Current amplifies, Voltage follows”