

# Subject Name Solutions

4331102 – Winter 2023

Semester 1 Study Material

*Detailed Solutions and Explanations*

## Question 1(a) [3 marks]

Give Definition of Accuracy, Reproducibility and Repeatability.

### Solution

Term	Definition
<b>Accuracy</b>	Closeness of measured value to the true or actual value of the quantity being measured
<b>Reproducibility</b>	Ability of an instrument to give identical measurements for the same input when measured under different conditions (different operators, locations, times)
<b>Repeatability</b>	Ability of an instrument to give identical measurements for the same input when measured repeatedly under the same conditions

### Mnemonic

“ARR - Accurate Results Repeatedly”

## Question 1(b) [4 marks]

Draw and Explain Wheatstone bridge.

### Solution

Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Supply+] --- R1
    A --- R3
    R1 --- B[Output+]
    R3 --- C[Output{-}]
    B --- R2
    C --- R4
    R2 --- D[Supply{-}]
    R4 --- D
{Highlighting}
{Shaded}
```

Feature	Description
<b>Configuration</b>	Four resistors connected in diamond pattern
<b>Balance Condition</b>	$R1/R2 = R3/R4$ (when output voltage is zero)
<b>Application</b>	Precise measurement of unknown resistance
<b>Operation</b>	Unknown resistor placed in one arm, remaining resistors adjusted until bridge is balanced

### Mnemonic

“WBMP - When Balanced, Measure Precisely”

### Question 1(c) [7 marks]

Explain Principle of Q meter. Also draw and explain Practical Q Meter.

#### Solution

##### Principle of Q Meter:

The Q-meter operates on the principle of series resonance, where Q factor is measured as the ratio of voltage across the capacitor to the applied voltage at resonance.

##### Diagram of Practical Q Meter:

##### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[RF Oscillator] --> B[Work Coil]
    B --> C[Series Circuit]
    C --> D[Unknown Inductor L]
    D --> E[Variable Capacitor C]
    E --> F[VTVM]
    F --> G[Q-Scale]
{Highlighting}
{Shaded}
```

Component	Function
RF Oscillator	Provides variable frequency signals
Work Coil	Inductively couples signal to test circuit
Resonant Circuit	Test inductor L in series with variable capacitor C
VTVM	Measures voltage across capacitor
Q-Scale	Calibrated to read Q value directly

- **Resonant Formula:**  $f = 1/(2\pi\sqrt{LC})$
- **Q Calculation:**  $Q = V_c/V_s$  (voltage across capacitor / source voltage)

### Mnemonic


“RIVQ - Resonance Indicates Valuable Quality”

### Question 1(c OR) [7 marks]

Draw and explain construction of Moving coil type instruments.

#### Solution

##### Diagram:

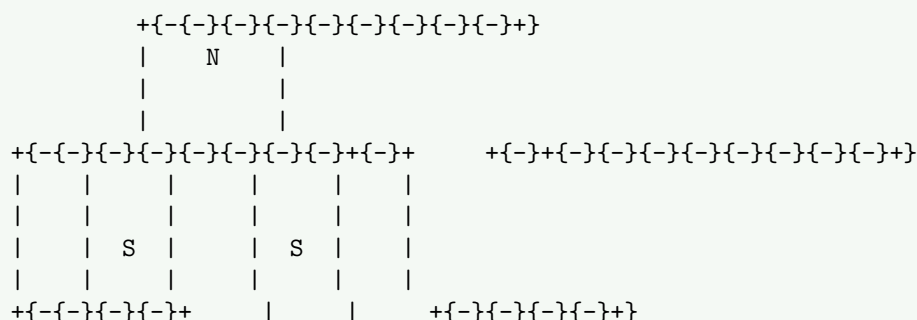

The diagram illustrates the internal components of a D'Arsonval movement. At the top, a vertical line represents the central spindle, with a horizontal line indicating the coil's position. Below this, the components are listed in a column: Permanent Magnet, Moving Coil, Springs, Pointer, and Core. To the right of these labels, a series of horizontal lines represent the assembly structure, showing how the components are stacked and connected. The bottom part of the diagram shows the final assembly, with the coil wound on a cylindrical core, and the pointer attached to the coil's spindle.

Component	Description
<b>Permanent Magnet</b>	Creates strong magnetic field
<b>Moving Coil</b>	Lightweight coil wound on aluminum frame
<b>Springs</b>	Provide controlling torque and electrical connections
<b>Pointer</b>	Attached to coil, moves over calibrated scale
<b>Core</b>	Soft iron cylindrical core to concentrate magnetic flux

- **Operating Principle:** Deflecting torque =  $BILN$  (B-field strength, I-current, l-length, N-turns)
- **Controlling Torque:** Provided by springs proportional to deflection angle

**Mnemonic**  
“MAPS-C: Magnet Acts, Pointer Shows Current”

**Mnemonic**  
“MAPS-C: Magnet Acts, Pointer Shows Current”

Question 2(a) [3 marks]

**List out different Types of errors. Explain any Two.**

### Solution

Types of Errors	
Gross Errors	
Systematic Errors	
Random Errors	
Environmental Errors	
Loading Errors	

**Explanation of Two Errors:**

- Systematic Errors:**
  - Consistent and predictable deviations from actual value
  - Caused by instrument calibration, design, or method
- Random Errors:**
  - Unpredictable variations in measurements
  - Caused by noise, environmental fluctuations, or observer limitations

Types of Errors	
Gross Errors	
Systematic Errors	
Random Errors	
Environmental Errors	
Loading Errors	
<b>Explanation of Two Errors:</b> <ol style="list-style-type: none"> <li><b>Systematic Errors:</b> <ul style="list-style-type: none"> <li>Consistent and predictable deviations from actual value</li> <li>Caused by instrument calibration, design, or method</li> </ul> </li> <li><b>Random Errors:</b> <ul style="list-style-type: none"> <li>Unpredictable variations in measurements</li> <li>Caused by noise, environmental fluctuations, or observer limitations</li> </ul> </li> </ol>	

- | Types of Errors      |  |
|----------------------|--|
| Gross Errors         |  |
| Systematic Errors    |  |
| Random Errors        |  |
| Environmental Errors |  |
| Loading Errors       |  |

**Explanation of Two Errors:**

  - Systematic Errors:**
    - Consistent and predictable deviations from actual value
    - Caused by instrument calibration, design, or method
  - Random Errors:**
    - Unpredictable variations in measurements
    - Caused by noise, environmental fluctuations, or observer limitations

**Mnemonic**

“GSREL - Good Systems Reduce Error Levels”

**Mnemonic**

“GSREL - Good Systems Reduce Error Levels”

Question 2(b) [4 marks]

**Draw and Explain Maxwell's bridge.**

## Solution

**Diagram:**

```
graph LR; A[Supply] --- A; style A fill:#add8e6; style A fill:#add8e6;
```

**Mermaid Diagram (Code)**

```
{Shaded}
{Highlighting}[]
graph LR
    A[Supply] --{-}{-} R1}
    A --{-}{-}{-} R3}
```

**Diagram:**

```
graph LR; A[Supply] --- A; style A fill:#add8e6; style A fill:#add8e6;
```

**Mermaid Diagram (Code)**

```
{Shaded}
{Highlighting}[]
graph LR
    A[Supply] --{-}{-} R1}
    A --{-}{-}{-} R3}
```

**Diagram:**

```
graph LR; A[Supply] --- A; style A fill:#add8e6; style A fill:#add8e6;
```

**Mermaid Diagram (Code)**

```
{Shaded}
{Highlighting}[]
graph LR
    A[Supply] --{-}{-} R1}
    A --{-}{-}{-} R3}
```

Component	Function
<b>R1, R2, R3, R4</b>	Precision resistors in bridge arms
<b>Unknown L</b>	Inductor with resistance to be measured
<b>Capacitor C</b>	Standard capacitor in opposite arm
<b>Detector</b>	Null detector (galvanometer)

- **Balance Equation:**  $L = CR_2R_3$
- **Resistance Equation:**  $R_L = R_2R_3/R_4$
- **Application:** Measures inductance with significant resistance

“MBLR - Maxwell Bridge Links Resistance”

Question 2(c) [7 marks]

**Draw and explain construction of moving iron type instruments.**

Diagram:

[illegible]

Component	Description
<b>Coil</b>	Fixed coil that carries measuring current
<b>Iron Vanes</b>	Two soft iron pieces (one fixed, one movable)
<b>Pointer</b>	Attached to movable vane
<b>Control Spring</b>	Provides restraining torque
<b>Damping Mechanism</b>	Air friction damping using light aluminum piston

- **Working Principle:** When current flows through coil, both iron pieces get magnetized with same polarity causing repulsion
- **Advantages:** Suitable for both AC and DC, robust construction
- **Disadvantages:** Non-uniform scale, higher power consumption than PMMC

#### Mnemonic

“IRAM - Iron Repulsion Activates Movement”

### Question 2(a OR) [3 marks]

Explain basic DC voltmeter.

#### Solution

Diagram:

```

+{ }{ }{ }{ }{ }{ }{ }{ }+   +{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }+   +{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }+
| PMMC |{ }{ }{ }| Series |{ }{ }{ }| Scale |}
| Meter | | Resistor | | Calibrated |
+{ }{ }{ }{ }{ }{ }{ }{ }+   +{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }+   +{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }{ }+

```

Component	Function
<b>PMMC Movement</b>	Basic current-sensitive movement
<b>Multiplier Resistor</b>	High-value series resistor
<b>Scale</b>	Calibrated to read voltage directly

- **Working Principle:** Voltmeter is PMMC meter with series resistor
- **Calculation:**  $R_s = (V/I_m) - R_m$  ( $R_s$ =series resistor,  $V$ =voltage,  $I_m$ =full scale current,  $R_m$ =meter resistance)

#### Mnemonic

“SVM - Series Voltage Measurement”

### Question 2(b OR) [4 marks]

Draw and Explain Schering bridge.

#### Solution

Diagram:

Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph LR
    A[AC Supply] -- C1["Unknown Capacitance"] --> B[Detector]
    A -- R3 --> C[Detector]
    B -- R1 --> D[Ground]
    C -- C4["Standard C"] --> D
    D -- R4["Variable R"] --> A
{Highlighting}
{Shaded}

```

Component	Function
<b>C1</b>	Unknown capacitor (with loss)
<b>R1</b>	Resistance representing loss in C1
<b>R3, R4</b>	Precision resistors
<b>C4</b>	Standard loss-free capacitor
<b>Detector</b>	Null indicator

- **Balance Equations:**  $C1 = C4(R3/R1)$
- **Dissipation Factor:**  $D = C1R1 = C4R4$
- **Application:** Measurement of capacitance and dielectric loss

#### Mnemonic

“SCDR - Schering Capacitance Determines Resistance”

### Question 2(c OR) [7 marks]

Write shortnote on Electronic Multimeter.

#### Solution

Diagram:

#### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Input] --> B[Attenuator/Range Selector]
    B --> C[Signal Converter]
    C --> D[Amplifier]
    D --> E[Rectifier/Detector]
    E --> F[Display]
{Highlighting}
{Shaded}
```

Feature	Description
<b>Functions</b>	Measures voltage (AC/DC), current (AC/DC), resistance, and other parameters
<b>Sensitivity</b>	Higher sensitivity than analog meters (10MΩ input impedance typical)
<b>Ranges</b>	Multiple selectable measurement ranges
<b>Accuracy</b>	0.1% to 3% depending on quality and parameter
<b>Display</b>	Digital readout or analog pointer

- **Types:** Analog electronic multimeter, Digital multimeter (DMM)
- **Advantages:** High input impedance, minimal loading effect, multiple functions
- **Key Circuit:** Input attenuator, signal converter, amplifier, rectifier, display driver

#### Mnemonic

“VCAR-D: Voltage, Current And Resistance - Displayed”

### Question 3(a) [3 marks]

Explain Various probes for CRO.

### Solution

Type of Probe	Description
<b>Passive Probe (1X)</b>	Direct connection probe with no attenuation
<b>Passive Probe (10X)</b>	Attenuates signal by factor of 10, reduces circuit loading
<b>Active Probe</b>	Contains active components for high impedance, low capacitance
<b>Current Probe</b>	Measures current by sensing magnetic field

- **Selection Criteria:** Bandwidth, loading effect, measurement range
- **Compensation:** 10X probes require compensation adjustment for accurate waveforms

### Mnemonic


“PAC-S: Probes Allow Circuit Sensing”

### Question 3(b) [4 marks]

Draw and explain construction of Clamp on Meter.

### Solution

Diagram:

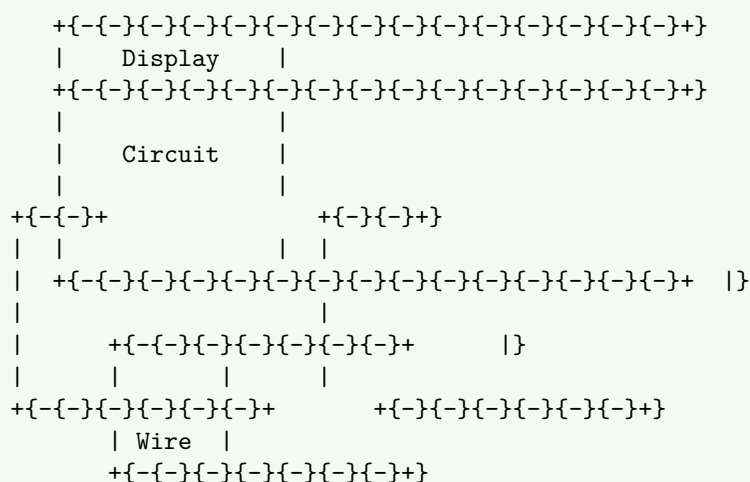

Component	Function
<b>Split Core CT</b>	Ferrite core that clamps around conductor
<b>Coil Winding</b>	Secondary winding that generates induced current
<b>Signal Circuitry</b>	Converts current to measurable signal
<b>Display Unit</b>	Digital/analog display calibrated in amps
<b>Trigger Mechanism</b>	Opens/closes core around conductor

- **Working Principle:** Based on current transformer, measures current without breaking circuit
- **Applications:** Measuring AC current in live conductors safely

### Mnemonic

“CAMP - Current Analyzed by Magnetic Principle”

### Question 3(c) [7 marks]

Write shortnote on successive approximation type DVM.



### Signal Conditioner

Amplifies and processes the millivolt signal

- **Working Principle:** Generates voltage proportional to hydrogen ion concentration
- **Output:** ~59 mV per pH unit at 25
- **Range:** 0-14 pH scale (acidic to alkaline)

### Mnemonic

“PHRV - PH Related to Voltage”

## Question 3(b OR) [4 marks]

Draw and explain construction of Electronic Watt Meter.

### Solution

Block Diagram:

#### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Current Input] --> B[Current Transformer]
    C[Voltage Input] --> D[Voltage Transformer]
    B --> E[Multiplier Circuit]
    D --> E
    E --> F[Integrator]
    F --> G[Digital Display]
{Highlighting}
{Shaded}
```

Component	Function
<b>Current Sensor</b>	Measures load current via CT or shunt
<b>Voltage Sensor</b>	Measures voltage via potential divider
<b>Multiplier</b>	Multiplies instantaneous voltage and current
<b>Integrator</b>	Averages power over time
<b>Display</b>	Digital readout in watts

- **Working Principle:**  $\text{Power} = V \times I \times \cos(\text{power factor})$
- **Advantages:** High accuracy, wide range, digital display
- **Types:** True RMS, average sensing

### Mnemonic

“VIMP - Voltage & Intensity Make Power”

## Question 3(c OR) [7 marks]

Write shortnote on Integrating type DVM.

### Solution

Block Diagram:

#### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
```

```
graph LR
    A[Input] --> B[Integrator]
    B --> C[Comparator]
    D[Clock] --> E[Counter & Control]
    C --> E
    E --> F[Digital Display]
```

{Highlighting}  
{Shaded}

Type	Working Principle
<b>Dual-Slope</b>	Integrates input for fixed time, then measures discharge time with reference
<b>Voltage-to-Frequency</b>	Converts voltage to frequency, counts pulses over fixed time
<b>Charge-Balance</b>	Balances input charge with reference charge

#### Key Features:

- **Noise Rejection:** Excellent rejection of power line noise (50/60Hz)
- **Accuracy:** High accuracy due to time averaging
- **Conversion Speed:** Slower than successive approximation type
- **Resolution:** Typically 4½ to 6½ digits

**Applications:** Precision measurements, noisy environments, bench instruments

#### Mnemonic

“TINA - Time Integration Nullifies Average”

### Question 4(a) [3 marks]

Write advantages and applications of Digital storage oscilloscope.

#### Solution

Advantages	Applications
<b>Pre-trigger Viewing</b>	Capturing transient events
<b>Signal Storage</b>	Analyzing intermittent faults
<b>Waveform Processing</b>	Complex signal analysis
<b>Higher Bandwidth</b>	High-speed digital circuit testing
<b>Multiple Channel Display</b>	Comparing multiple signals

- **Key Benefits:** Can capture one-time events, store waveforms for later analysis
- **Digital Features:** Automated measurements, FFT analysis, PC connectivity

#### Mnemonic

“SPADE - Storage, Processing, Analysis, Display, Events”

### Question 4(b) [4 marks]

Write shortnote on Electronic Energy Meter.

#### Solution

**Block Diagram:**

**Mermaid Diagram (Code)**

```
{Shaded}
{Highlighting}[]
graph LR
    A[Voltage Sensor] --> C[Multiplier]
```

```

B[Current Sensor] {-}{-}{ C}
C {-}{-}{ D[Integrator]}
D {-}{-}{ E[Pulse Generator]}
E {-}{-}{ F[Counter]}
F {-}{-}{ G[Display]}
{Highlighting}
{Shaded}

```

Component	Function
<b>Voltage &amp; Current Sensors</b>	Measure line voltage and load current
<b>Multiplier Circuit</b>	Calculates instantaneous power
<b>Integrator</b>	Converts power to energy over time
<b>Microcontroller</b>	Processes signals and controls display
<b>LCD Display</b>	Shows energy consumption in kWh

- **Working Principle:** Energy =  $\int P \cdot dt$  (integral of power over time)
- **Advantages:** No moving parts, high accuracy, tamper detection
- **Features:** Multiple tariff support, bi-directional measurement, remote reading

### Mnemonic

“VICES - Voltage & Current Energy Summation”

## Question 4(c) [7 marks]

Draw and explain Block diagram of Analog C.R.O. and working of each block in brief.

### Solution

Block Diagram:

#### Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph LR
    A[Vertical Input] {-}{-}{ B[Vertical Attenuator]}
    B {-}{-}{ C[Vertical Amplifier]}
    C {-}{-}{ D[Vertical Deflection Plates]}
    E[Trigger Circuit] {-}{-}{ F[Time Base Generator]}
    F {-}{-}{ G[Horizontal Amplifier]}
    G {-}{-}{ H[Horizontal Deflection Plates]}
    I[Cathode Ray Tube] {-}{-}{ J[Screen]}
    D {-}{-}{ I}
    H {-}{-}{ I}
    K[Power Supply] {-}{-}{ All}
{Highlighting}
{Shaded}

```

Block	Function
<b>Vertical System</b>	Controls amplitude display (signal attenuation, amplification)
<b>Horizontal System</b>	Controls time base (sweep generation)
<b>Trigger System</b>	Synchronizes horizontal sweep with input signal
<b>CRT</b>	Displays signal (electron gun, deflection plates, phosphor screen)
<b>Power Supply</b>	Provides required voltages to all circuits

- **Vertical System:** Processes input signal, controls Y-axis deflection
- **Horizontal System:** Controls X-axis deflection (time base)
- **Triggering:** Stabilizes waveform display by starting sweep at same point
- **CRT Display:** Converts electrical signals to visible trace

**Mnemonic**

“VTHCP - Vertical, Time, Horizontal, CRT, Power”

**Question 4(a OR) [3 marks]**

**Draw and explain PIEZO-ELECTRIC transducer.**

## Solution

Diagram:

Diagram:

```
Force  
↓  
+{-}{-}{-}{-}{-}{-}{-}{-}+}  
|           |  
| Quartz |{-}{-}{-} Output Voltage}  
| Crystal|  
|           |  
+{-}{-}{-}{-}{-}{-}{-}{-}+}
```

Property	Description
<b>Principle</b>	Generates electric charge when mechanically stressed
<b>Materials</b>	Quartz, Rochelle salt, PZT ceramics
<b>Operation</b>	Direct effect: force → <i>voltage</i> , <i>Inverse effect</i> : <i>voltage</i> → <i>displacement</i>
<b>Output</b>	High impedance voltage proportional to applied force

- **Applications:** Pressure sensors, accelerometers, ultrasonic devices
- **Advantages:** High sensitivity, fast response, wide frequency range
- **Limitations:** High output impedance, temperature sensitive

**Mnemonic**

“PFVD - Pressure Forms Voltage via Displacement”

Question 4(b OR) [4 marks]

**Draw and explain Measurement of Frequency by using CRO.**

**Solution**

### Method 1: Using Lissajous Patterns


```

Method 1: Using Lissajous Patterns

+{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}+}
|
|   o o o
|   o       o
|  o         o
|   o       o
|   o o o
|
+{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}{-{-}}+}

```


### Method 2: Using Time Base

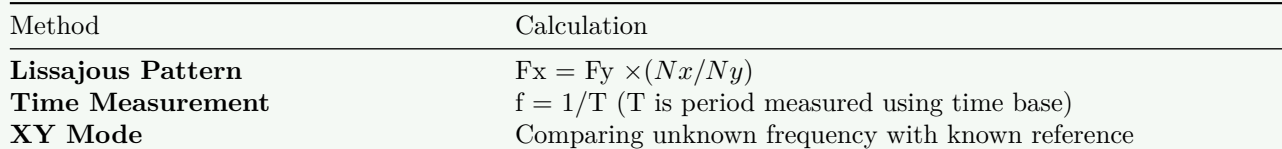

- Mnemonic**  
“LTX - Lissajous or Time for X-axis”

**Draw and explain Thermistor and Thermocouple.**

### Thermistor Diagram:

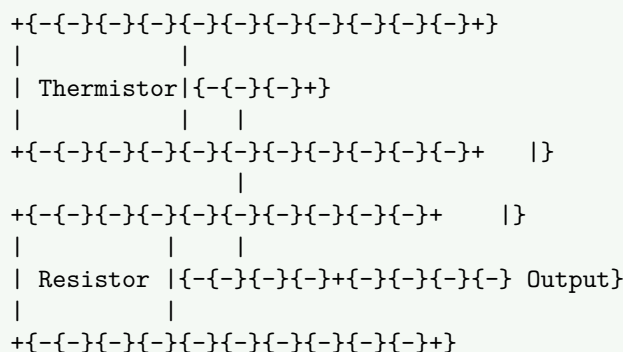
$$\frac{\text{Metal A} + \{-\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\} \{ \} + \{-\{-\}\{-\}\} \text{Output}}{\text{Metal B} + \{-\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\} + \text{Metal B}}$$

Transducer	Principle	Characteristics
<b>Thermistor</b>	Resistance changes with temperature	High sensitivity, non-linear, limited range
<b>Thermocouple</b>	Junction of dissimilar metals generates voltage	Wide range, linear, low sensitivity

**Thermistor Types:**

- **NTC:** Negative Temperature Coefficient (resistance decreases with temperature)
- **PTC:** Positive Temperature Coefficient (resistance increases with temperature)

**Thermocouple Types:**


- **Type K:** Chromel-Alumel ( $-200^{\circ}\text{C}$  to  $1350^{\circ}\text{C}$ )
- **Type J:** Iron-Constantan ( $-40^{\circ}\text{C}$  to  $750^{\circ}\text{C}$ )
- **Type T:** Copper-Constantan ( $-200^{\circ}\text{C}$  to  $350^{\circ}\text{C}$ )

**Mnemonic**

“TRT/TVJ - Temperature Resistance/Voltage Junction”

**Question 5(a) [3 marks]**

Draw and Explain Velocity transducer.

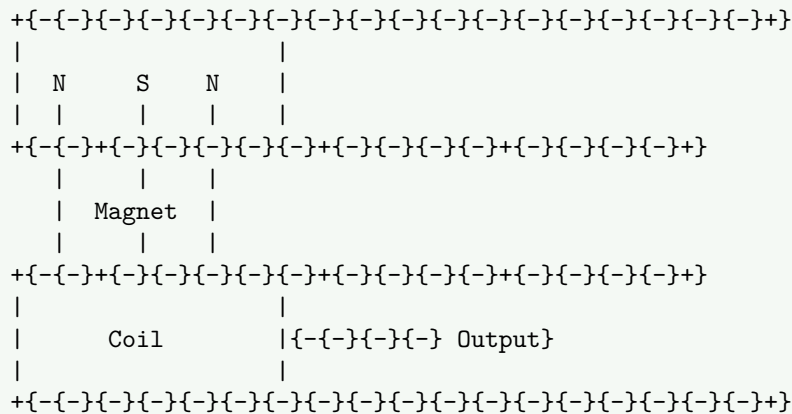**Solution****Diagram:**

Component	Function
<b>Permanent Magnet</b>	Creates magnetic field
<b>Moving Coil</b>	Generates voltage proportional to velocity
<b>Housing</b>	Supports structure and magnetic circuit
<b>Output Circuit</b>	Conditions signal for measurement

- **Working Principle:** Based on Faraday's law of electromagnetic induction
- **Output:** Voltage proportional to velocity ( $V = Blv$ )
- **Applications:** Vibration measurement, seismic monitoring, motion control

**Mnemonic**

“VMMF - Velocity Makes Magnetic Flux”

**Question 5(b) [4 marks]**

Give Classification of transducers and explain it.

## Solution

Classification	Types
<b>By Energy Conversion</b>	Active (self-generating) vs. Passive (requiring external power)
<b>By Measurement Method</b>	Primary vs. Secondary
<b>By Physical Principle</b>	Resistive, Capacitive, Inductive, Photoelectric, etc.
<b>By Application</b>	Temperature, Pressure, Flow, Level, etc.

### Explanation:

Type	Examples	Characteristics
<b>Active</b>	Thermocouple, Piezoelectric	Generate output without external power
<b>Passive</b>	RTD, Strain gauge	Require external excitation
<b>Resistive</b>	Thermistor, Potentiometer	Change resistance with input
<b>Capacitive</b>	Pressure sensors, Proximity	Change capacitance with input
<b>Inductive</b>	LVDT, Proximity	Change inductance with input

## Mnemonic

“APRCI - Active Passive Resistive Capacitive Inductive”

## Question 5(c) [7 marks]

Write shortnote on LVDT.

## Solution

### Diagram:

### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Primary Coil] --- B[Core]
    B --- C[Secondary Coil 1]
    C --- D[Secondary Coil 2]
    D --- E[AC Excitation]
    E --- A
    C --- F[Phase Sensitive Detector]
    F --- D
    F --- G[Output]
{Highlighting}
{Shaded}
```

Component	Function
<b>Primary Coil</b>	Excitation coil connected to AC source
<b>Secondary Coils</b>	Two identical coils connected in series opposition
<b>Ferromagnetic Core</b>	Movable core that varies mutual inductance
<b>Signal Conditioner</b>	Converts differential output to displacement measurement

**Working Principle:**

- At null position: Equal voltage induced in both secondaries, net output zero
- Core movement: Creates imbalance in secondary voltages
- Output voltage: Proportional to displacement, phase indicates direction

**Characteristics:**

- **Range:** Typically  $\pm 0.5mm$  to  $\pm 25cm$
- **Linearity:** Excellent within rated range
- **Resolution:** Virtually infinite (limited by readout circuit)
- **Advantages:** Frictionless, robust, reliable, high resolution

- Working Principle:**

  - At null position: Equal voltage induced in both secondaries, net output zero
  - Core movement: Creates imbalance in secondary voltages
  - Output voltage: Proportional to displacement, phase indicates direction

**Characteristics:**

  - **Range:** Typically  $\pm 0.5mm$  to  $\pm 25cm$
  - **Linearity:** Excellent within rated range
  - **Resolution:** Virtually infinite (limited by readout circuit)
  - **Advantages:** Frictionless, robust, reliable, high resolution

**Working Principle:**

- At null position: Equal voltage induced in both secondaries, net output zero
- Core movement: Creates imbalance in secondary voltages
- Output voltage: Proportional to displacement, phase indicates direction

**Characteristics:**

- **Range:** Typically  $\pm 0.5mm$  to  $\pm 25cm$
- **Linearity:** Excellent within rated range
- **Resolution:** Virtually infinite (limited by readout circuit)
- **Advantages:** Frictionless, robust, reliable, high resolution

- Working Principle:**

  - At null position: Equal voltage induced in both secondaries, net output zero
  - Core movement: Creates imbalance in secondary voltages
  - Output voltage: Proportional to displacement, phase indicates direction

**Characteristics:**

  - **Range:** Typically  $\pm 0.5mm$  to  $\pm 25cm$
  - **Linearity:** Excellent within rated range
  - **Resolution:** Virtually infinite (limited by readout circuit)
  - **Advantages:** Frictionless, robust, reliable, high resolution

**Mnemonic**  
“CPSO: Core Position Shifts Output”

**Mnemonic**  
“CPSO: Core Position Shifts Output”

**Question 5(a OR) [3 marks]**

Draw and Explain block diagram of simple frequency Counter.

**Question 5(a OR) [3 marks]**

Draw and Explain block diagram of simple frequency Counter.

Solution

Block Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Input] --> B[Input Conditioning]
    B --> C[Gate Control]
    C --> D[Time Base]
    D --> E[Counter]
    E --> F[Display]
{Highlighting}
{Shaded}
```

Block	Function
<b>Input Conditioning</b>	Amplifies, shapes input signal into pulses
<b>Gate Control</b>	Controls counting period based on time base
<b>Time Base</b>	Provides accurate reference time interval
<b>Counter</b>	Counts input pulses during gate period
<b>Display</b>	Shows count result (frequency)

- Working Principle:** Counts pulses over precise time interval (typically 1 second)
- Frequency Calculation:**  $f = \text{counts} / \text{time interval}$
- Resolution:** Determined by time base accuracy and gate time

Solution

Block Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Input] --> B[Input Conditioning]
    B --> C[Gate Control]
    C --> D[Time Base]
    D --> E[Counter]
    E --> F[Display]
{Highlighting}
{Shaded}
```

Block	Function
<b>Input Conditioning</b>	Amplifies, shapes input signal into pulses
<b>Gate Control</b>	Controls counting period based on time base
<b>Time Base</b>	Provides accurate reference time interval
<b>Counter</b>	Counts input pulses during gate period
<b>Display</b>	Shows count result (frequency)

- Working Principle:** Counts pulses over precise time interval (typically 1 second)
- Frequency Calculation:**  $f = \text{counts} / \text{time interval}$
- Resolution:** Determined by time base accuracy and gate time

Solution

Block Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Input] --> B[Input Conditioning]
    B --> C[Gate Control]
    C --> D[Time Base]
    D --> E[Counter]
    E --> F[Display]
{Highlighting}
{Shaded}
```

Block	Function
<b>Input Conditioning</b>	Amplifies, shapes input signal into pulses
<b>Gate Control</b>	Controls counting period based on time base
<b>Time Base</b>	Provides accurate reference time interval
<b>Counter</b>	Counts input pulses during gate period
<b>Display</b>	Shows count result (frequency)

- Working Principle:** Counts pulses over precise time interval (typically 1 second)
- Frequency Calculation:**  $f = \text{counts} / \text{time interval}$
- Resolution:** Determined by time base accuracy and gate time

Solution

Block Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Input] --> B[Input Conditioning]
    B --> C[Gate Control]
    C --> D[Time Base]
    D --> E[Counter]
    E --> F[Display]
{Highlighting}
{Shaded}
```

Block	Function
<b>Input Conditioning</b>	Amplifies, shapes input signal into pulses
<b>Gate Control</b>	Controls counting period based on time base
<b>Time Base</b>	Provides accurate reference time interval
<b>Counter</b>	Counts input pulses during gate period
<b>Display</b>	Shows count result (frequency)

- Working Principle:** Counts pulses over precise time interval (typically 1 second)
- Frequency Calculation:**  $f = \text{counts} / \text{time interval}$
- Resolution:** Determined by time base accuracy and gate time

- Solution

Block Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Input] --> B[Input Conditioning]
    B --> C[Gate Control]
    C --> D[Time Base]
    D --> E[Counter]
    E --> F[Display]
{Highlighting}
{Shaded}
```

Block	Function
Input Conditioning	Amplifies, shapes input signal into pulses
Gate Control	Controls counting period based on time base
Time Base	Provides accurate reference time interval
Counter	Counts input pulses during gate period
Display	Shows count result (frequency)

- Working Principle:** Counts pulses over precise time interval (typically 1 second)
  - Frequency Calculation:**  $f = \text{counts} / \text{time interval}$
  - Resolution:** Determined by time base accuracy and gate time

**Mnemonic**

“IGTCD - Input Gated Time Counts Display”

**Mnemonic**

“IGTCD - Input Gated Time Counts Display”

**Question 5(b OR) [4 marks]**

**Draw and Explain Capacitive Transducer.**

**Question 5(b OR) [4 marks]**

**Draw and Explain Capacitive Transducer.**

**Solution**

**Diagram:**

+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+

|      Fixed      |

**Solution**

**Diagram:**

+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+

|      Fixed      |

**Solution**

**Diagram:**

+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+

|      Fixed      |

[illegible]

**Mnemonic**

“CGAD - Capacitance Gap Area Dielectric”

**Mnemonic**

“CGAD - Capacitance Gap Area Dielectric”

Question 5(c OR) [7 marks]

**Draw and Explain block diagram of Function generator.**

### Solution

**Block Diagram:**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; B --> D[Amplifier & Attenuator]; D --> E[Output Buffer]; E --> F[Sweep Circuit]; F --> G[AM/FM Modulator]; G --> E;
```

**Mermaid Diagram (Code)**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; B --> D[Amplifier & Attenuator]; D --> E[Output Buffer]; E --> F[Sweep Circuit]; F --> G[AM/FM Modulator]; G --> E;
```

**Block Diagram:**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; B --> D[Amplifier & Attenuator]; D --> E[Output Buffer]; E --> F[Sweep Circuit]; F --> G[AM/FM Modulator]; G --> E;
```

**Mermaid Diagram (Code)**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; B --> D[Amplifier & Attenuator]; D --> E[Output Buffer]; E --> F[Sweep Circuit]; F --> G[AM/FM Modulator]; G --> E;
```

Block	Function
Frequency Control	Sets oscillator frequency (typically 0.1Hz to 20MHz)
Waveform Generator	Produces basic waveforms (sine, square, triangle)
Mode Selector	Selects output waveform type
Amplifier & Attenuator	Controls output amplitude
Output Buffer	Provides low output impedance
Sweep Circuit	Automatically varies frequency over range
AM/FM Modulator	Modifies signal for modulation functions

**Block Diagram:**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; C --> D[Amplifier \& Attenuator]; B --> D; D --> E[Output Buffer]; F[Sweep Circuit] --> G[AM/FM Modulator]; F --> D; G --> E;
```

**Mermaid Diagram (Code)**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; C --> D[Amplifier \& Attenuator]; B --> D; D --> E[Output Buffer]; F[Sweep Circuit] --> G[AM/FM Modulator]; F --> D; G --> E;
```

**Block Diagram:**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; C --> D[Amplifier \& Attenuator]; B --> D; D --> E[Output Buffer]; F[Sweep Circuit] --> G[AM/FM Modulator]; F --> D; G --> E;
```

**Mermaid Diagram (Code)**

```
graph LR; A[Frequency Control] --> B[Waveform Generator]; C[Mode Selector] --> B; C --> D[Amplifier \& Attenuator]; B --> D; D --> E[Output Buffer]; F[Sweep Circuit] --> G[AM/FM Modulator]; F --> D; G --> E;
```

**Working Principle:**

- Generates sine wave using RC oscillator or DDS
- Shape converters transform sine into square and triangle
- Output amplitude controlled by attenuator circuit
- Modern generators use digital synthesis techniques

**Applications:** Circuit testing, signal injection, filter characterization

**Mnemonic**

“FWMASO - Frequency Waveform Mode Amplitude Sweep Output”