

# Fundamentals of Electronics (4311102) - Summer 2023 Solution

Milav Dabgar

July 31, 2023

## Question 1(a) [3 marks]

Define Active and Passive components.

### Solution

Answer:

**Table 1.** Active vs Passive Components

Active Components	Passive Components
Require external power source to operate.	Do not need external power source.
Can amplify and process electrical signals.	Cannot amplify or process signals.
<b>Examples:</b> transistors, diodes, ICs.	<b>Examples:</b> resistors, capacitors, inductors.

## Question 1(b) [4 marks]

State types of capacitors based on materials used.

### Solution

Answer:

**Table 2.** Types of Capacitors Based on Materials

Material Type	Capacitor Type	Typical Applications
<b>Ceramic</b>	Ceramic disc, multilayer	Bypass, coupling, high frequency
<b>Plastic Film</b>	Polyester, Polypropylene, Teflon	Timing, filtering, precision
<b>Electrolytic</b>	Aluminum, Tantalum	Power supply, DC blocking, high capacitance
<b>Paper</b>	Paper dielectric	Old equipment, not common now
<b>Mica</b>	Silvered mica	High precision RF circuits
<b>Glass</b>	Glass dielectric	High voltage applications

## Question 1(c) [7 marks]

Explain resistor color coding technique with example.

**Solution****Answer:**

The resistor color code uses colored bands to indicate resistance value, tolerance, and reliability.


**Table 3.** Standard Resistor Color Code

Color	Digit	Multiplier	Tolerance
Black	0	$\times 10^0$ (1)	-
Brown	1	$\times 10^1$ (10)	$\pm 1\%$
Red	2	$\times 10^2$ (100)	$\pm 2\%$
Orange	3	$\times 10^3$ (1k)	-
Yellow	4	$\times 10^4$ (10k)	-
Green	5	$\times 10^5$ (100k)	$\pm 0.5\%$
Blue	6	$\times 10^6$ (1M)	$\pm 0.25\%$
Violet	7	$\times 10^7$ (10M)	$\pm 0.1\%$
Grey	8	$\times 10^8$	$\pm 0.05\%$
White	9	$\times 10^9$	-
Gold	-	$\times 0.1$	$\pm 5\%$
Silver	-	$\times 0.01$	$\pm 10\%$

**Figure 1.** Resistor Color Bands

Example 1: Red-Violet-Orange-Gold

$$27 \times 10^3 \Omega \pm 5\% = 27k\Omega$$

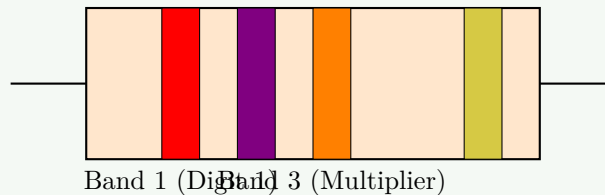**Example 1:** Red-Violet-Orange-Gold

- 1st (Red) = 2, 2nd (Violet) = 7, 3rd (Orange) =  $\times 1k$ , 4th (Gold) =  $\pm 5\%$
- Value:  $27k\Omega \pm 5\%$

**Example 2:** Brown-Black-Yellow-Silver


- 1st (Brown) = 1, 2nd (Black) = 0, 3rd (Yellow) =  $\times 10k$ , 4th (Silver) =  $\pm 10\%$
- Value:  $100k\Omega \pm 10\%$

**Question 1(c) OR [7 marks]**

Explain construction, working Characteristic and application of LDR.

**Solution****Answer:****Light Dependent Resistor (LDR)****Table 4.** LDR Details

Aspect	Description
<b>Construction</b>	Semiconductor material (cadmium sulfide) deposited in zigzag pattern on ceramic substrate. Packaged in transparent case with two terminals.
<b>Working Principle</b>	Photoconductivity: When light falls on material, photons release electron-hole pairs, increasing conductivity and decreasing resistance.
<b>Characteristics</b>	High resistance in dark ( $M\Omega$ ). Low resistance in light ( $100-5000\Omega$ ). Inverse non-linear relationship. Slow response time.
<b>Applications</b>	Automatic street lights, camera light meters, burglar alarms, display brightness control.

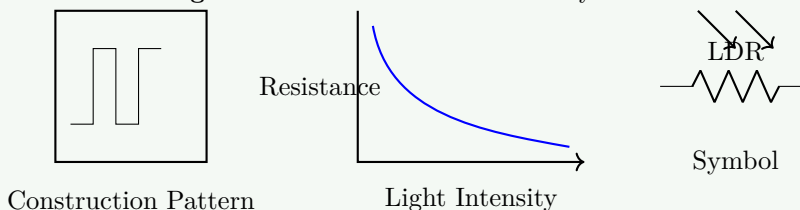**Figure 2.** LDR Characteristics and Symbol**Question 2(a) [3 marks]**

Classify Resistors based on materials.

**Solution****Answer:****Table 5.** Resistor Classification

Material Type	Characteristics	Examples
<b>Carbon Composition</b>	Low cost, noisy, poor tolerance.	General purpose.
<b>Carbon Film</b>	Better stability than composition.	Audio, general circuits.
<b>Metal Film</b>	Excellent stability, low noise.	Precision circuits.
<b>Metal Oxide</b>	Heat resistant, high stability.	Power supplies.
<b>Wire Wound</b>	High power, inductive.	Heating elements.
<b>Thick/Thin Film</b>	Small size (SMD).	Surface mount.

**Question 2(b) [4 marks]**

Calculate value of resistor for a given color code. – (i) Brown, Black, Yellow, Golden (ii) Yellow, Violet, Red, Silver

**Solution****Answer:****Part (i): Brown, Black, Yellow, Golden**


- Brown (1), Black (0), Yellow ( $\times 10^4$ ), Golden ( $\pm 5\%$ )
- $10 \times 10,000 = 100,000\Omega = 100k\Omega \pm 5\%$

**Part (ii): Yellow, Violet, Red, Silver**

- Yellow (4), Violet (7), Red ( $\times 10^2$ ), Silver ( $\pm 10\%$ )
- $47 \times 100 = 4,700\Omega = 4.7k\Omega \pm 10\%$

**Question 2(c) [7 marks]****Illustrate construction and operation of Electrolytic capacitors.****Solution****Answer:****Table 6.** Electrolytic Capacitor

Component	Description
<b>Anode</b>	Aluminum foil with oxide layer (dielectric).
<b>Cathode</b>	Electrolyte (liquid/paste) and metal foil.
<b>Separator</b>	Paper soaked in electrolyte.
<b>Operation</b>	Oxide layer gives high capacitance ( $C \propto A/d$ ) due to extreme thinness. Polarized (must connect correct +/-).

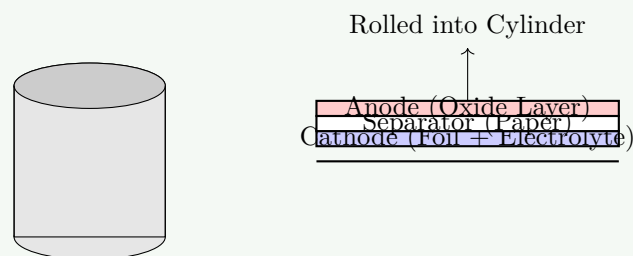**Figure 3.** Electrolytic Capacitor Construction**Question 2(a) OR [3 marks]****State the importance of filter circuit in rectifier.****Solution****Answer:**

- **Smoothing:** Converts pulsating DC from rectifier into steady DC.
- **Ripple Reduction:** Removes unwanted AC components (ripples).
- **Voltage Stabilization:** Maintains average output voltage.
- **device Protection:** Prevents damage to sensitive electronic components.

## Question 2(b) OR [4 marks]

Differentiate between P type semiconductor and N type semiconductor.

### Solution

Answer:

Table 7. P-type vs N-type

Feature	P-type	N-type
Dopant	Trivalent (B, Al, Ga)	Pentavalent (P, As, Sb)
Majority Carriers	Holes (+)	Electrons (-)
Minority Carriers	Electrons (-)	Holes (+)
Energy Level	Acceptor level near Valence band	Donor level near Conduction band

## Question 2(c) OR [7 marks]

Illustrate working of Bridge Rectifier with waveforms.


### Solution

Answer:

Operation:

- **Positive Half:** D1, D3 conduct. Current flows through load.
- **Negative Half:** D2, D4 conduct. Current flows through load in same direction.
- **Result:** Full wave rectification without center-tap transformer.

Figure 4. Bridge Rectifier Circuit and Waveforms

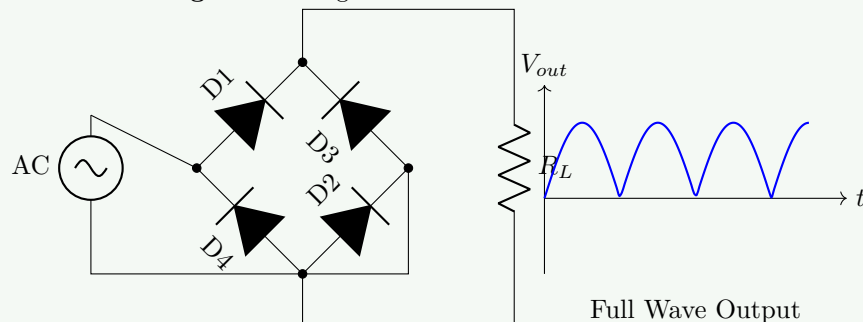

## Question 3(a) [3 marks]

Define (1) PIV (2) Ripple Factor.

**Solution****Answer:****Table 8.** PIV and Ripple Factor

Term	Definition
<b>PIV (Peak Inverse Voltage)</b>	Maximum voltage a diode can withstand in reverse bias. Must be higher than circuit's max reverse voltage to prevent breakdown.
<b>Ripple Factor (r)</b>	Ratio of RMS value of AC component to DC component in output. Lower r means better filtering.


**Formula:**  $r = \frac{V_{rms(ac)}}{V_{dc}}$

**Question 3(b) [4 marks]**

Illustrate VI characteristics of PN junction diode.

**Solution****Answer:****Table 9.** PN Junction Characteristics

Region	Behavior
<b>Forward Bias</b>	Conducts current easily after threshold (0.7V Si, 0.3V Ge). Exponential current rise.
<b>Reverse Bias</b>	Blocks current. Very small leakage ( $\mu A$ ). Breakdown at high reverse voltage.

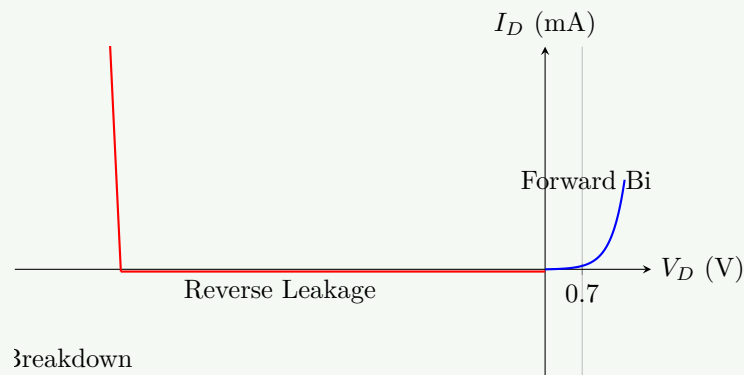**Figure 5.** VI Characteristics of PN Diode**Question 3(c) [7 marks]**


Explain the working of capacitor input and choke input filter with waveforms.

**Solution****Answer:****1. Capacitor Input Filter**

- Capacitor connected in parallel with load.
- Charges to peak, discharges slowly during dips.
- High DC voltage, but poor regulation.

**2. Choke Input Filter**

- Inductor (choke) in series, capacitor in parallel.
- Inductor opposes current change, smoothing current.
- Better regulation, lower DC voltage.

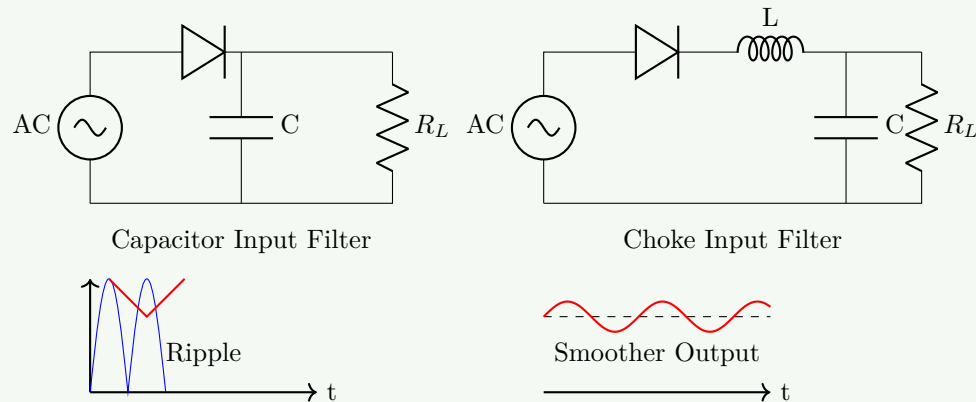**Figure 6.** Filter Circuits and Waveforms**Question 3(a) OR [3 marks]**

State the function and importance of Zener diode.

**Solution****Answer:****Table 10.** Zener Diode Functions


Function	Description
<b>Voltage Regulation</b>	Maintains constant output voltage.
<b>Voltage Reference</b>	Provides precise reference voltage.
<b>Protection</b>	Prevents voltage spikes from damaging circuits.
<b>Usage</b>	Operates in breakdown region.

**Question 3(b) OR [4 marks]**

Describe Light emitting diode (LED) with its characteristic.

**Solution****Answer:****Table 11.** LED Characteristics

Aspect	Description
<b>Principle</b>	Electroluminescence. Recombination of holes and electrons releases photons.
<b>Material</b>	Direct bandgap semiconductors (GaAs, GaP).
<b>Forward Voltage</b>	Red: 2V, Blue/White: 3V.
<b>Operation</b>	Works only in Forward Bias. Damaged by reverse bias ( $> 5V$ ).

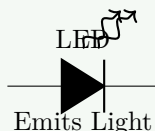**Figure 7.** LED Working**Question 3(c) OR [7 marks]**

Illustrate the working of capacitor input and choke input filter.

**Solution****Answer:**

(Refer to Question 3(c) for detailed waveforms and diagrams. This section provides component breakdown.)

**Table 12.** Capacitor vs Choke Filter

Parameter	Capacitor Input	Choke Input
<b>Components</b>	Capacitor in parallel.	Choke (series) + Cap (parallel).
<b>Output V</b>	Higher ( $\approx V_m$ ).	Lower ( $\approx 0.9V_m$ ).
<b>Regulation</b>	Poor (V drops with load).	Good (L opposes change).
<b>Diode Current</b>	High peak surges.	Continuous, lower peak.
<b>Cost/Size</b>	Low cost, small.	Heavy, bulky, expensive.

**Question 4(a) [3 marks]**

Discuss characteristics of PN junction diode.

**Solution****Answer:**

- **Forward Bias:** Low resistance, current flows after knee voltage.
- **Reverse Bias:** High resistance, only leakage current.
- **Breakdown:** Rapid current increase at Zener/Avalanche voltage.
- **Temp Effect:**  $V_f$  drops with heat,  $I_r$  doubles every  $10^\circ\text{C}$ .

**Question 4(b) [4 marks]**

Compare between P-N junction diode and Zener diode.



**Solution****Answer:****Table 13.** General Diode vs Zener Diode


Feature	PN Diode	Zener Diode
Symbol	Standard arrow	Arrow with 'Z' ends
Doping	Moderate	Heavy
Breakdown	Destructive	Non-destructive (Operating region)
Main Use	Rectification	Voltage Regulation

**Question 4(c) [7 marks]**

Illustrate the function of Zener diode as a voltage regulator.

**Solution****Answer:****Circuit Operation:**

- Zener diode connected in **Reverse Bias**.
- When  $V_{in} > V_z$ , Zener conducts and holds  $V_{out} = V_z$ .
- Series resistor  $R_s$  drops the excess voltage ( $V_{in} - V_z$ ).
- Changes in load current or input voltage are compensated by changing Zener current, keeping  $V_{out}$  steady.

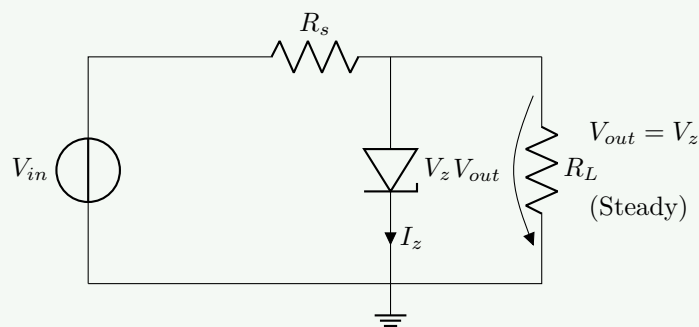**Figure 8.** Zener Regulator**Question 4(a) OR [3 marks]**

Discuss transistor in brief.

**Solution****Answer:**

- **Definition:** 3-terminal semiconductor device (Emitter, Base, Collector).
- **Types:** BJT (NPN, PNP), FET (JFET, MOSFET).
- **Function:** Amplifies weak signals, acts as a switch.
- **Control:** Current controlled (BJT) or Voltage controlled (FET).

**Question 4(b) OR [4 marks]**

Derive relation between  $\alpha$  and  $\beta$  for transistor amplifier.

**Solution****Answer:****Definitions:**

- $\alpha = \frac{I_C}{I_E}$  (Common Base current gain)
- $\beta = \frac{I_C}{I_B}$  (Common Emitter current gain)

**Derivation:**


1. Fundamental Equation:  $I_E = I_B + I_C$
2. Divide by  $I_C$ :  $\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$
3. Substitute definitions:  $\frac{1}{\alpha} = \frac{1}{\beta} + 1$
4. Rearrange:  $\frac{1}{\alpha} = \frac{1+\beta}{\beta}$
5. Therefore:  $\alpha = \frac{\beta}{1+\beta}$
6. Solving for  $\beta$ :  $\beta = \frac{\alpha}{1-\alpha}$

**Example:** If  $\alpha = 0.99$ ,  $\beta = \frac{0.99}{1-0.99} = 99$ .**Question 4(c) OR [7 marks]**

Explain in detail the construction of NPN and PNP transistor.

**Solution****Answer:****Table 14.** NPN vs PNP Construction

Aspect	NPN	PNP
Layers	N-P-N	P-N-P
Majority	Electrons	Holes
Doping	Emitter (Heavy), Base (Light), Collector (Moderate)	Same
Width	Base is very thin ( $< 10\mu m$ ) to reduce recombination	Same

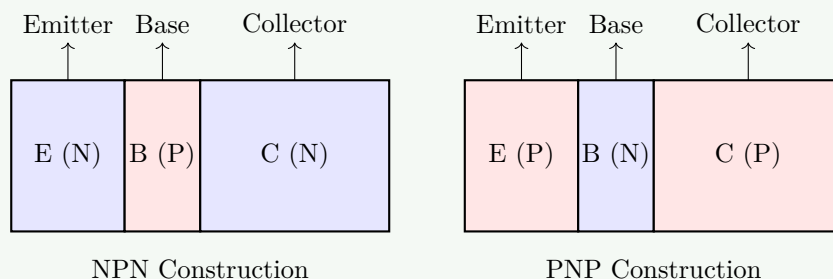**Figure 9.** Transistor Construction**Question 5(a) [3 marks]**

Explain e-waste in brief.

**Solution****Answer:****E-Waste (Electronic Waste):** Discarded electronic devices (phones, PCs, TVs).


- **Hazards:** Contains toxic lead, mercury, cadmium.
- **Value:** Contains recoverable gold, silver, copper.
- **Impact:** Environmental pollution if ended in landfill.
- **Need:** Proper recycling and disposal management.

**Question 5(b) [4 marks]**


Illustrate operation of NPN transistor with figure.

**Solution****Answer:****Working Principle:**

- **Forward Biased Base-Emitter:** Electrons injected from Emitter to Base.
- **Reverse Biased Base-Collector:** Electrons swept from Base to Collector.
- Small Base current ( $I_B$ ) controls large Collector current ( $I_C$ ).
- Equation:  $I_E = I_B + I_C$ .

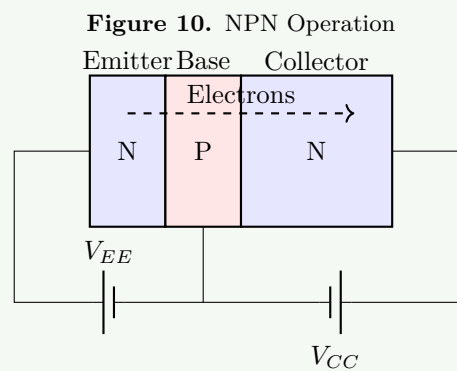**Question 5(c) [7 marks]**

Illustrate common emitter (CE) configuration of Transistor with input and output characteristics.

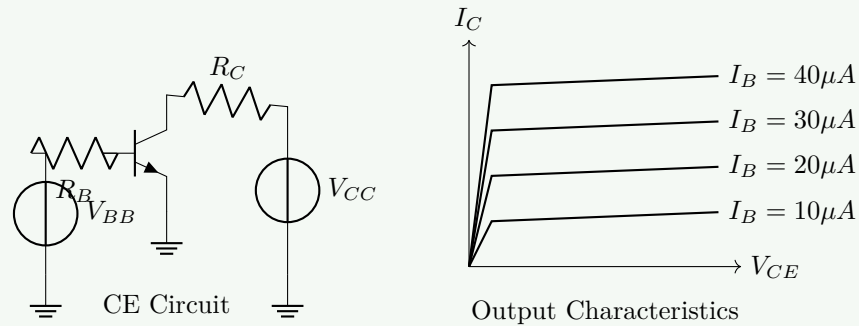**Solution****Answer:****CE Configuration:** Emitter is grounded (common). Input at Base, Output at Collector. High Gain.**Figure 11. CE Circuit and Characteristics**

- **Input Char:**  $I_B$  vs  $V_{BE}$ . Like a diode.
- **Output Char:**  $I_C$  vs  $V_{CE}$ . Saturation (steep rise), Active (flat), Cutoff (zero).

**Question 5(a) OR [3 marks]**

State types of e-waste.

**Solution****Answer:**


- **IT & Telecom:** Computers, phones, printers.
- **Consumer:** TVs, audio sets, cameras.
- **Appliances:** Fridges, washing machines.
- **Lighting:** Bulbs, LEDs.
- **Medical:** Scanners, monitors.

**Question 5(b) OR [4 marks]**

Illustrate different categories of Electronics waste.

**Solution****Answer:****Table 15.** E-Waste Categories

Category	Examples
Large Appliances	Washing machines, AC units
Small Appliances	Toasters, Irons
IT Equipment	PCs, Laptops, Mobile phones
Consumer Electronics	TVs, Stereos, Game consoles
Lighting	Fluorescent tubes
Tools	Drills, Saws

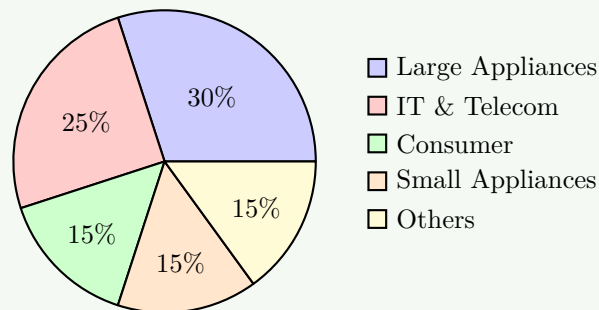**Figure 12.** E-Waste Composition**Question 5(c) OR [7 marks]****Explain transistor as a switch in cutoff and saturation region.****Solution****Answer:****Transistor Switch States:**

State	Region	Conditions
OFF (Open)	Cutoff	$V_{in} < 0.7V$ , $I_B = 0$ , $I_C = 0$ , $V_{CE} = V_{CC}$ .
ON (Closed)	Saturation	$V_{in} > 0.7V$ , $I_B$ max, $I_C$ max, $V_{CE} \approx 0.2V$ .

**Figure 13.** Transistor Switching