

# Subject Name Solutions

4331101 – Summer 2025

Semester 1 Study Material

*Detailed Solutions and Explanations*

## Question 1(a) [3 marks]

Define following terms. (i) Active elements (ii) Bilateral elements (iii) Linear elements

### Solution

Term	Definition
<b>Active elements</b>	Electronic components that can supply energy or power to a circuit (like batteries, generators, op-amps)
<b>Bilateral elements</b>	Components that allow current flow equally in both directions with same characteristics (like resistors, capacitors, inductors)
<b>Linear elements</b>	Components whose current-voltage relationship follows a straight line and obeys the principle of superposition (like resistors following Ohm's law)

### Mnemonic

“ABL: Active powers Batteries, Bilateral flows Both ways, Linear stays Lawful”

## Question 1(b) [4 marks]

Capacitors of 10 $\mu$ F, 20 $\mu$ F and 30 $\mu$ F are connected in series and supply of 200V DC is given. Find voltage across each capacitor.

### Solution

For series-connected capacitors:

1. Find equivalent capacitance:  $1/C_{eq} = 1/C_1 + 1/C_2 + 1/C_3$

1. Voltage division:  $V_C = (C_1/C) \times V$

**Calculation:**  $1/C_{eq} = 1/10 + 1/20 + 1/30 = 0.1 + 0.05 + 0.033 = 0.183$   $C_{eq} = 5.46 \text{ F}$

Capacitor	Formula	Calculation	Voltage
$C_1 = 10F$	$V_1 = (C_{eq}/C_1) \times V$	$(5.46/10) \times 200 = 109.2V$	109.2V
$C_2 = 20F$	$V_2 = (C_{eq}/C_2) \times V$	$(5.46/20) \times 200 = 54.6V$	54.6V
$C_3 = 30F$	$V_3 = (C_{eq}/C_3) \times V$	$(5.46/30) \times 200 = 36.4V$	36.4V

### Mnemonic

“Smaller Capacitors get Larger Voltages”

## Question 1(c) [7 marks]

Explain Node pair voltage method for graph theory.

### Solution

Node pair voltage method is a systematic approach to analyze electrical networks.

#### Procedure:

1. Select a reference node (ground)
2. Identify the node voltages (N-1 unknowns for N nodes)

3. Apply KCL at each non-reference node
4. Express branch currents in terms of node voltages
5. Solve the equations for node voltages

**Diagram:**

#### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Select reference node] --> B[Identify node voltages]
    B --> C[Apply KCL at each node]
    C --> D[Express branch currents using node voltages]
    D --> E[Solve equations for node voltages]
    E --> F[Calculate branch currents]
{Highlighting}
{Shaded}
```

**Key advantages:**

- **Fewer equations:** Only (n-1) equations for n nodes
- **Computational efficiency:** Reduces system complexity
- **Direct voltage solutions:** Provides node voltages directly
- **Systematic approach:** Works for any network topology

#### Mnemonic

“GARCS: Ground, Assign voltages, Relate with KCL, Calculate currents, Solve equations”

### Question 1(c) OR [7 marks]

Explain voltage division method with necessary equations.

#### Solution

Voltage division is a method to calculate how voltage distributes across series components.

**Principle:** In a series circuit, voltage divides proportionally to component resistances/impedances.

**Formula:** For a resistor  $R_1$  in a series circuit with total resistance  $RT$ :  $V_1 = (R_1/RT) \times VS$

**Diagram:**

```
+{--}{--}{--}+
VS {--}{--}{--}| {--}{--} R1 {--}{--}|}
+{--}{--}{--}+ |}
| V1
|
|
+{--}{--}{--}+ |}
| {--}{--} R2 {--}{--}|}
+{--}{--}{--}+
|
|
{--}{--}{--}{--}{--}
{--}{--}{--}
{--}
```

**Mathematical explanation:**

- For resistors:  $V_1 = (R_1/RT) \times VS$
- For capacitors:  $V_1 = (1/C_1)/(1/CT) \times VS = (CT/C_1) \times VS$
- For inductors:  $V_1 = (L_1/LT) \times VS$
- For complex impedances:  $V_1 = (Z_1/ZT) \times VS$

**Examples:**

1. Voltage across a  $1k\Omega$  resistor in series with  $4k\Omega$  with 5V source =  $(1/5) \times 5V = 1V$
1. Voltage across a 10 F capacitor in series with 40 F with 10V source =  $(1/10)/(1/8) \times 10V = 8V$