

# Electronic Circuits & Applications (4321103) - Winter 2024 Solution

Milav Dabgar

January 13, 2024

## Question 1 [a marks]

3 Explain amplifier parameters  $A_i$ ,  $R_i$  and  $R_o$  for CE configuration.

### Solution

#### CE Amplifier Parameters:

Table 1. CE Amplifier Parameters

Parameter	Definition	value
Current Gain ( $A_i$ )	Ratio of output current to input current	High (20-500)
Input Resistance ( $R_i$ )	Opposition to current flow at input	Medium (1-2 k $\Omega$ )
Output Resistance ( $R_o$ )	Opposition to current flow at output	High (40-50 k $\Omega$ )



### Mnemonic



CAR - CE has Current gain high, Average input resistance, and Robust output resistance.

## Question 1 [b marks]

4 Write short-note on heat sink.
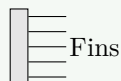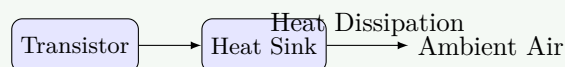
### Solution

**Heat Sink:** A device that absorbs and dissipates heat from electronic components to prevent overheating.



#### Types of Heat Sinks:

- **Passive:** Rely on natural convection (no fans).
- **Active:** Use fans for forced air convection.
- **Liquid-cooled:** Use liquid for better heat transfer.

#### Key Functions:

- **Thermal Conduction:** Draws heat away from the component.

- **Thermal Convection:** Transfers heat to the air.
- **Surface Area:** Fins increase area for maximum cooling.

### Mnemonic

CRAFT - Cooling through Radiation And Fins for Transistors.


## Question 1 [c marks]

7 Describe Thermal Runaway and Thermal Stability. How can overcome thermal run away in transistor?
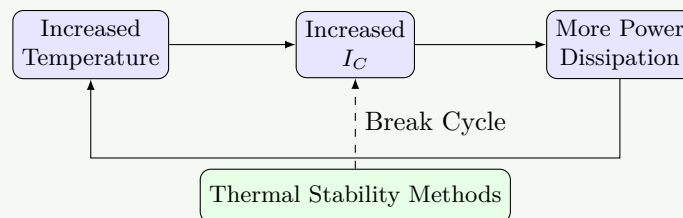
### Solution

**Thermal Runaway:** A self-reinforcing process where increased temperature causes more collector current, which generates more heat, further increasing temperature until the device fails.

**Thermal Stability:** The ability of a transistor circuit to maintain stable operation (constant Q-point) despite changes in temperature.



### Methods to Overcome Thermal Runaway:

- **Heat Sink:** Physically dissipates excess heat.
- **Negative Feedback:** Using an emitter resistor ( $R_E$ ) to stabilize current.
- **Bias Stabilization:** Using voltage divider biasing.
- **Temperature Compensation:** Using thermistors or diodes to counteract changes.

### Key Points:

- $I_C = I_{CBO}(1 + \beta) + \beta I_B$ .
- $I_{CBO}$  doubles for every  $10^\circ\text{C}$  rise.
- **Stability Factor S:** Lower S means better stability (Ideal  $S = 1$ ).

### Mnemonic

RENT - Reduce heat with sinks, Emitter resistors stabilize, Negative feedback helps, Temperature compensation.

## Question 1 [c marks]


7 Write down types of biasing methods. Explain the voltage divider biasing method in details.

### Solution

### Types of Biasing Methods:

- Fixed Bias
- Collector-to-Base Bias
- Voltage Divider Bias
- Emitter Bias
- Collector Feedback Bias

### Voltage Divider Bias Circuit:

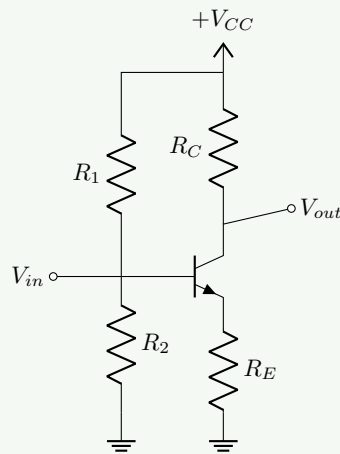**Operation:**

- **R1 and R2:** Form a voltage divider to provide a fixed voltage at the base.
- **RE:** Provides negative feedback for stability. If  $I_C$  increases, voltage drop across  $R_E$  increases, reducing  $V_{BE}$ , which reduces  $I_B$  and brings  $I_C$  back down.
- **Stable Bias Point:** The Q-point is almost independent of  $\beta$  variations.

**Advantages:**

- **Excellent Stability:** Very low stability factor ( $S \approx 1$ ).
- **Beta Independent:** Variations in transistor  $\beta$  do not affect the operating point significantly.
- **Widely Used:** Most common method for linear amplifiers.

**Mnemonic**

DIVE - Divider biasing Is Very Effective for stability.

## Question 2 [a marks]

### 3 Explain Stability Factor with features.

**Solution**

**Stability Factor (S):** A measure of the sensitivity of the collector current ( $I_C$ ) to changes in reverse saturation current ( $I_{CO}$ ) or temperature. Equation:  $S = \frac{\Delta I_C}{\Delta I_{CO}}$

**Table 2.** Stability Factors Comparison

Biasing Method	Stability Factor	Stability Level
Fixed Bias	$S = 1 + \beta$	Poor (Very High S)
Collector-to-Base	$S = \frac{\beta}{1 + \beta}$	Better
Voltage Divider	$S \approx 1$	Excellent (Lowest S)

**Features:**

- **Lower is Better:** An ideal stability factor is 1.
- **Temperature Resistance:** Indicates how well the circuit resists thermal drift.
- **Design Tool:** Used to select appropriate biasing components.

**Mnemonic**


SOS - Stability Of circuit Shows in its S-factor.

## Question 2 [b marks]

4 Describe direct coupling technique of cascading.
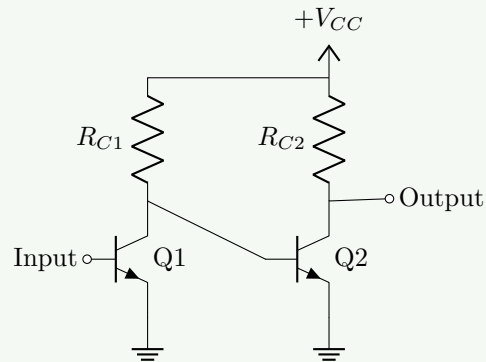
### Solution

**Direct Coupling:** The output of one stage is connected directly to the input of the next stage without any coupling capacitors or transformers.



#### Key Characteristics:

- **No Coupling Components:** Simple circuit.
- **Frequency Response:** Excellent low-frequency response (amplifies DC).
- **Level Shifting:** DC potentials increase stage by stage, requiring level shifting techniques.

**Applications:** Operational Amplifiers, Regulators.

### Mnemonic


DIRECT - DC signals Immediately REach Connecting Transistors.

## Question 2 [c marks]

7 Explain frequency response of two stage RC coupled amplifier.

### Solution

#### RC Coupled Amplifier Frequency Response:

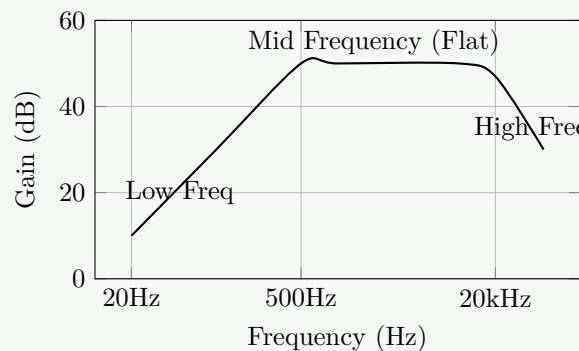

**Table 3.** Frequency Regions

Region	Frequency	Cause of Fall
Low	20Hz - 500Hz	Coupling Capacitors ( $C_C$ ) high reactance
Mid	500Hz - 20kHz	Constant Gain (Ideal operation)
High	> 20kHz	Transistor parasitic capacitances

**Two-Stage Effect:**

- **Bandwidth:** Reduces compared to single stage ( $BW_n = BW_1 \times \sqrt{2^{1/n} - 1}$ ).
- **Gain:** Product of individual stage gains ( $A_{total} = A_1 \times A_2$ ).

**Mnemonic**

LMH - Low frequencies by coupling caps, Mid frequencies flat, High frequencies by transistor caps.


**Question 2 [a marks]**

3 Briefly explain bandwidth and gain-bandwidth product of an amplifier.

**Solution**

**Bandwidth (BW):** The range of frequencies over which the amplifier gain is at least 70.7% (or -3dB) of its maximum value.  $BW = f_2 - f_1$

**Gain-Bandwidth Product (GBP):** The product of the voltage gain and the bandwidth is constant for a given amplifier.  $GBP = A_v \times BW = \text{Constant}$

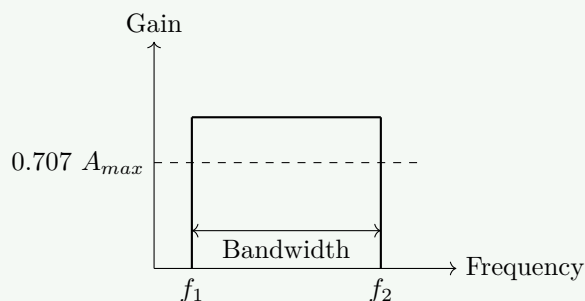**Mnemonic**

BAND - Bandwidth And gain Never Drop together.


**Question 2 [b marks]**

4 Explain effects of emitter bypass capacitor and coupling capacitor on frequency response of an amplifier.

**Solution****Capacitor Effects:**

**Table 4.** Capacitors

Capacitor	Function	Effect
Coupling ( $C_C$ )	Blocks DC, passes AC	Limits Low Frequency response (High reactance at low f)
Bypass ( $C_E$ )	Bypasses $R_E$	Increases Mid-band gain. If removed, gain drops due to negative feedback.

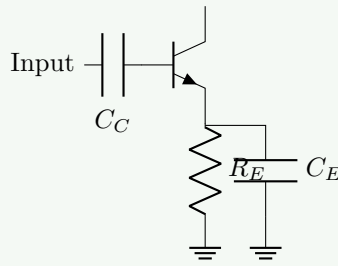**Mnemonic**

CELL - Coupling affects Extremely Low frequencies, bypass affects Low to high.

**Question 2 [c marks]**

7 Compare transformer coupled amplifier and RC coupled amplifier

**Solution**

**Comparison:**

**Table 5.** Transformer vs RC Coupled

Feature	Transformer Coupled	RC Coupled
Coupling	Transformer	Resistor-Capacitor
Impedance Matching	Excellent	Poor
Frequency Response	Poor (Resonant peaks)	Good (Flat over wide range)
Efficiency	High	Low
Size/Weight	Bulky/Heavy	Small/Light
Cost	Expensive	Inexpensive
Application	Power Amplifiers	Voltage Amplifiers

**Mnemonic**


TRIP - Transformers are Robust for Impedance matching, Problematic for bandwidth.

**Question 3 [a marks]**

3 Describe the transistor used as a tuned amplifier.

**Solution**

**Tuned Amplifier:** An amplifier that uses a parallel LC tank circuit as the collector load to amplify a specific narrow band of frequencies.

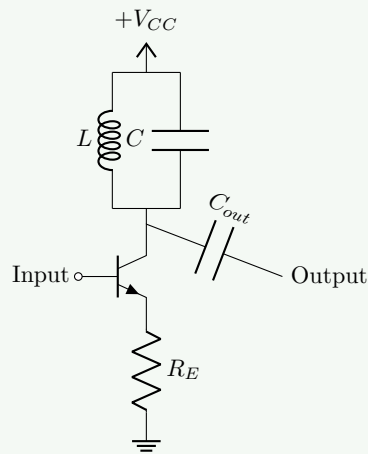**Key Components:**

- **LC Tank:** Determines resonant frequency  $f_r = \frac{1}{2\pi\sqrt{LC}}$ .
- **High Q:** Provides high selectivity.

**Applications:** Radio and TV receivers (IF amplifiers).

**Mnemonic**

TUNE - Transistors Using Narrowband Elements for frequency selection.

### Question 3 [b marks]

4 Explain in brief Direct coupled amplifier.

**Solution**

**Direct Coupled Amplifier:** (See Q2(b) for diagram) A multi-stage amplifier where the output of one stage is directly connected to the input of the next.

**Advantages:**

- Low cost (no capacitors/transformers).
- Amplifies DC signals (0 Hz to high frequency).

**Disadvantages:**

- Thermal drift issues (DC shift).
- Requires stable power supplies.

**Mnemonic**

DCAP - Direct Coupled Amplifier Passes all frequencies including DC.

### Question 3 [c marks]


7 Describe the importance of h parameters in two port networks. Draw h-parameters circuit for CE amplifier.

**Solution****Importance of h-parameters:**

- **Hybrid Nature:** Mix of impedance and admittance parameters.
- **Easy to Measure:**  $h_{11}, h_{21}$  measured with output shorted;  $h_{12}, h_{22}$  measured with input open.

- **Standard:** Manufacturers provide transistor specs in h-parameters.
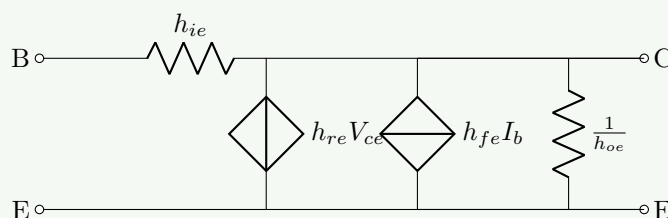
#### h-parameter Circuit for CE Amplifier:



#### Parameters:

1.  $h_{ie}$ : Input Impedance.
2.  $h_{re}$ : Reverse Voltage Ratio.
3.  $h_{fe}$ : Forward Current Gain ( $\beta$ ).
4.  $h_{oe}$ : Output Admittance.

#### Mnemonic

HIRE - h-parameters Include Resistance and current gain Effectively.

### Question 3 [a marks]

3 Compare transformer coupled amplifier and direct coupled amplifier.

#### Solution

##### Comparison:

Table 6. Comparison

Feature	Transformer Coupled	Direct Coupled
Frequency Response	Bandpass (Poor Low/High)	DC to High Frequency
Cost	High	Low
Size	Bulky	Compact
Impedance Matching	Excellent	Poor
DC Isolation	Yes	No

#### Mnemonic

TDC - Transformers provide DC isolation, Direct provides Complete frequency range.


### Question 3 [b marks]

4 Draw and Explain circuit diagram of common emitter amplifier.

#### Solution

##### Common Emitter (CE) Amplifier:

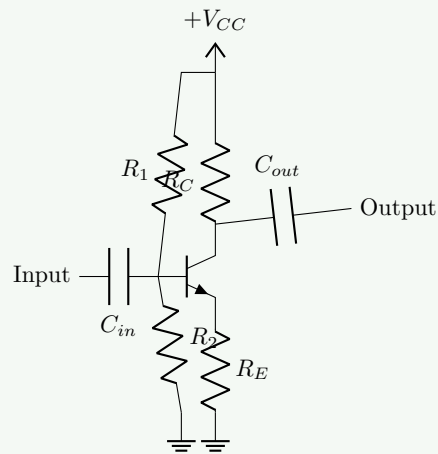

**Explanation:**

- **Input:** Applied to Base-Emitter.
- **Output:** Taken from Collector-Emitter.
- **Phase Shift:**  $180^\circ$  (Output is inverted).
- **Gain:** High voltage and current gain.

**Mnemonic**


CEA - Common Emitter Amplifies with signal inversion.

## Question 3 [c marks]

7 Draw Transistor Two Port Network and describe h-parameters for it. Write down advantages of hybrid parameters.

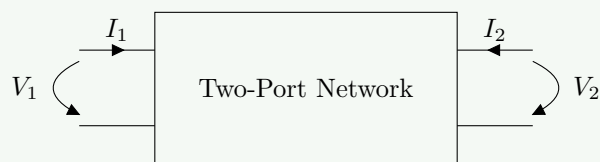**Solution**

**Two-Port Network:** (See Q3(c) above for h-parameter model explanation).



**Equations:**  $V_1 = h_{11}I_1 + h_{12}V_2$

$I_2 = h_{21}I_1 + h_{22}V_2$

**Advantages:**

- Real numbers at audio frequencies.
- Easily measured.
- Suitable for circuit analysis.

**Mnemonic**


HAEM - Hybrid parameters Are Easily Measured.

## Question 4 [a marks]

3 Explain Darlington pair and its applications.

**Solution**

**Darlington Pair:** Two transistors connected in cascade ( $CC - CC$ ) to behave like a single "super" transistor.

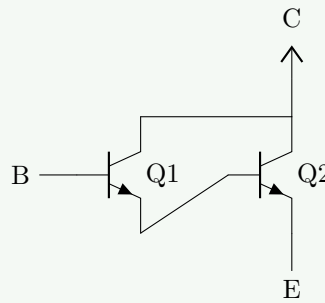**Features:**

- High Current Gain:  $\beta \approx \beta_1 \beta_2$ .
- High Input Impedance.

**Applications:** Power amplifiers, relay drivers, touch switches.

**Mnemonic**


DISH - Darlington Integrates Stages for High current gain.

**Question 4 [b marks]**

4 Describe the diode clamper circuit with necessary diagram.

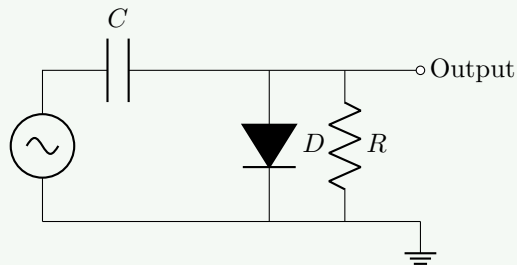**Solution**

**Diode Clamper:** A circuit that shifts the DC level of a waveform.




**Operation:** Capacitor charges to peak voltage, acting as a battery in series with the input signal, shifting it up or down. **Application:** TV Receivers (DC restoration).

**Mnemonic**

CLAMP - Circuit Levels Are Modified Precisely.

**Question 4 [c marks]**


7 Explain the construction, working and applications of OLED.

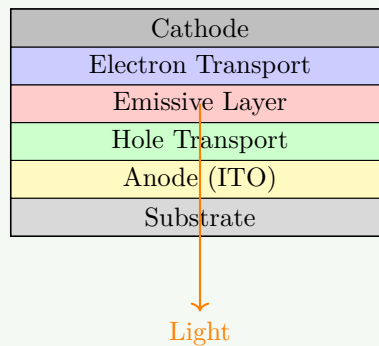**Solution****OLED (Organic Light Emitting Diode):****Working:**

- Charge carriers (holes and electrons) are injected from anode and cathode.
- They recombine in the emissive layer.
- Energy is released as light (Electroluminescence).


**Applications:** Curved screens, Flexible displays, High-end smartphones.**Mnemonic**

OLED - Organic Layers Emit Directly.

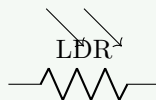**Question 4 [a marks]****3 Explain Short note on LDR.****Solution****LDR (Light Dependent Resistor):** A photoresistor made of Cadmium Sulfide (CdS) whose resistance decreases when light shines on it.**Logic:** Light Energy creates electron-hole pairs → Conductivity increases → Resistance decreases. **Use:** Street lights, alarms.**Mnemonic**

LORD - Light Oppositely Reduces the Device's resistance.

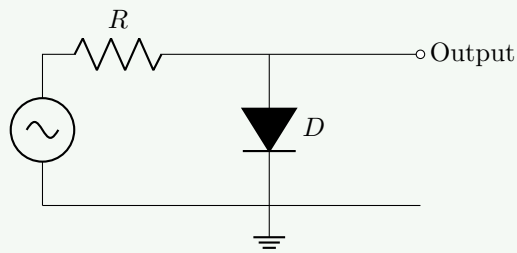**Question 4 [b marks]****4 Describe the diode clipper circuit with necessary diagram.****Solution****Diode Clipper:** Removes parts of a signal.



**Positive Clipper:** Diode points down (removes positive). **Negative Clipper:** Diode points up (removes negative).

#### Mnemonic

CLIP - Circuit Limits Input Peaks.


### Question 4 [c marks]

7 Explain Half Wave and Full wave Voltage Doubler.


#### Solution

**Voltage Doubler:** Produces DC voltage twice the peak AC input ( $2V_m$ ).

**Half-Wave Doubler:**

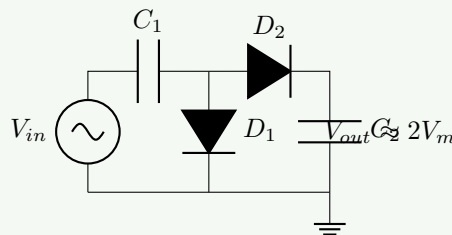

**Full-Wave Doubler:**

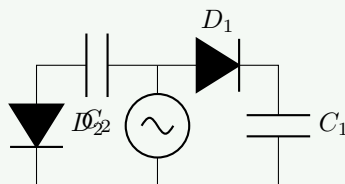


**Explanation:** Capacitors charge in alternate cycles and their voltages sum up.

#### Mnemonic

DOUBLE - Diodes Organize Unidirectional Boost.

### Question 5 [a marks]

3 Draw circuit diagram for +5 v Power Supply using its IC

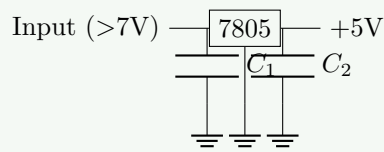**Solution****+5V Power Supply (7805):****Mnemonic**

FIVE - Fixed IC Voltage Efficiently provided.

**Question 5 [b marks]****4 Discuss load regulation and line regulation in reference to power supply.****Solution****Regulation:** Keeping output voltage constant.

1. **Line Regulation:** Ability to maintain constant  $V_{out}$  when Input Voltage ( $V_{in}$ ) changes.


$$\%Reg = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100$$

2. **Load Regulation:** Ability to maintain constant  $V_{out}$  when Load Current ( $I_L$ ) changes.

$$\%Reg = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

**Mnemonic**

LINE LOAD - Line Is Normal-input Efficiency, LOAD is Output Adjustment Defense.

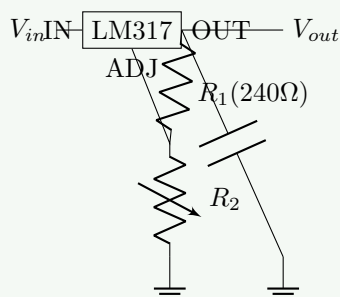**Question 5 [c marks]****7 Explain adjustable voltage regulator using LM317 with circuit diagram.****Solution****LM317 Adjustable Regulator:****Formula:**  $V_{out} = 1.25(1 + \frac{R_2}{R_1}) + I_{ADJ}R_2$ . **Use:** Bench power supplies.

**Mnemonic**


VARY - Voltage Adjustable Regulator Yields custom outputs.

**Question 5 [a marks]**

3 Draw circuit diagram for -15 v Power Supply using its IC

**Solution**

**-15V Power Supply (7915):**

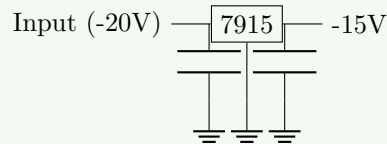

*Note: 79xx series is for negative voltage.*

**Mnemonic**


NINE - Negative IC Needs Efficient filtering.

**Question 5 [b marks]**

4 Explain working of UPS.

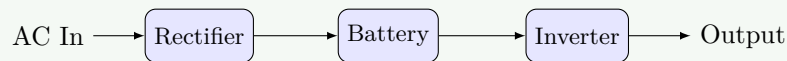**Solution**

**UPS (Uninterruptible Power Supply):** Provides emergency power.



**Operation:** 1. Rectifier charges battery. 2. Inverter converts DC to AC for load. 3. If power fails, battery continues to supply inverter.

**Mnemonic**


UPBEAT - Uninterruptible Power Backup.

**Question 5 [c marks]**

7 Draw and explain SMPS block diagram with its advantages and disadvantages.

**Solution**

**SMPS (Switch Mode Power Supply):**

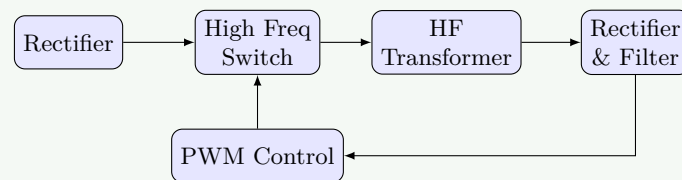

**Advantages:** High efficiency ( $> 80\%$ ), Compact size, Light weight. **Disadvantages:** High noise (EMI), Complex circuit.

### Mnemonic

SWITCH - Smaller Weight, Improved Thermal efficiency.