

Electronic Circuits & Applications (4321103) - Winter 2024 Solution

Milav Dabgar

January 13, 2024

Question 1 [a marks]

3 Explain amplifier parameters A_i , R_i and R_o for CE configuration.

Solution

CE Amplifier Parameters:

Table 1. CE Amplifier Parameters

Parameter	Definition	value
Current Gain (A_i)	Ratio of output current to input current	High (20-500)
Input Resistance (R_i)	Opposition to current flow at input	Medium (1-2 k Ω)
Output Resistance (R_o)	Opposition to current flow at output	High (40-50 k Ω)



Mnemonic

C


AR - CE has Current gain high, Average input resistance, and Robust output resistance.

Question 1 [b marks]

4 Write short-note on heat sink.

Solution

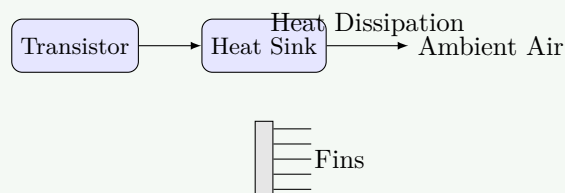Heat Sink: A device that absorbs and dissipates heat from electronic components to prevent overheating.



Types of Heat Sinks:

- **Passive:** Rely on natural convection (no fans).
- **Active:** Use fans for forced air convection.
- **Liquid-cooled:** Use liquid for better heat transfer.

Key Functions:

- **Thermal Conduction:** Draws heat away from the component.
- **Thermal Convection:** Transfers heat to the air.
- **Surface Area:** Fins increase area for maximum cooling.

Mnemonic

C

RAFT - Cooling through Radiation And Fins for Transistors.


Question 1 [c marks]

7 Describe Thermal Runaway and Thermal Stability. How can overcome thermal run away in transistor?

Solution

Thermal Runaway: A self-reinforcing process where increased temperature causes more collector current, which generates more heat, further increasing temperature until the device fails.

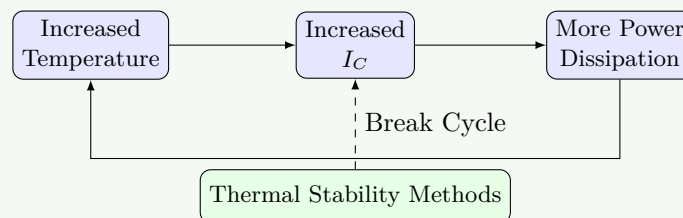Thermal Stability: The ability of a transistor circuit to maintain stable operation (constant Q-point) despite changes in temperature.



Methods to Overcome Thermal Runaway:

- **Heat Sink:** Physically dissipates excess heat.
- **Negative Feedback:** Using an emitter resistor (R_E) to stabilize current.
- **Bias Stabilization:** Using voltage divider biasing.
- **Temperature Compensation:** Using thermistors or diodes to counteract changes.

Key Points:

- $I_C = I_{CBO}(1 + \beta) + \beta I_B$.
- I_{CBO} doubles for every 10°C rise.
- **Stability Factor S:** Lower S means better stability (Ideal $S = 1$).

Mnemonic

R

ENT - Reduce heat with sinks, Emitter resistors stabilize, Negative feedback helps, Temperature compensation.

Question 1 [c marks]

7 Write down types of biasing methods. Explain the voltage divider biasing method in details.


Solution

Types of Biasing Methods:

- Fixed Bias
- Collector-to-Base Bias
- Voltage Divider Bias

- Emitter Bias
- Collector Feedback Bias

Voltage Divider Bias Circuit:

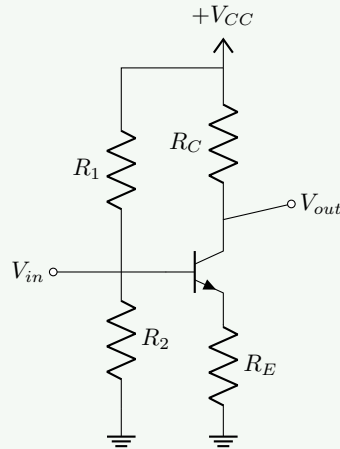

Operation:

- **R1 and R2:** Form a voltage divider to provide a fixed voltage at the base.
- **RE:** Provides negative feedback for stability. If I_C increases, voltage drop across R_E increases, reducing V_{BE} , which reduces I_B and brings I_C back down.
- **Stable Bias Point:** The Q-point is almost independent of β variations.

Advantages:

- **Excellent Stability:** Very low stability factor ($S \approx 1$).
- **Beta Independent:** Variations in transistor β do not affect the operating point significantly.
- **Widely Used:** Most common method for linear amplifiers.

Mnemonic

D

IVE - Divider biasing Is Very Effective for stability.

Question 2 [a marks]

3 Explain Stability Factor with features.

Solution

Stability Factor (S): A measure of the sensitivity of the collector current (I_C) to changes in reverse saturation current (I_{CO}) or temperature. Equation: $S = \frac{\Delta I_C}{\Delta I_{CO}}$

Table 2. Stability Factors Comparison

Biasing Method	Stability Factor	Stability Level
Fixed Bias	$S = 1 + \beta$	Poor (Very High S)
Collector-to-Base	$S = \frac{\beta}{1+\beta}$	Better
Voltage Divider	$S \approx 1$	Excellent (Lowest S)

Features:

- **Lower is Better:** An ideal stability factor is 1.
- **Temperature Resistance:** Indicates how well the circuit resists thermal drift.
- **Design Tool:** Used to select appropriate biasing components.

Mnemonic

S


OS - Stability Of circuit Shows in its S-factor.

Question 2 [b marks]

4 Describe direct coupling technique of cascading.

Solution

Direct Coupling: The output of one stage is connected directly to the input of the next stage without any coupling capacitors or transformers.

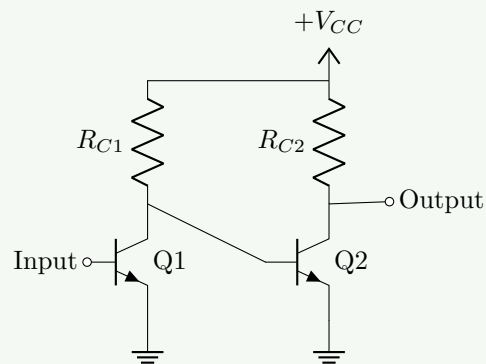**Key Characteristics:**

- **No Coupling Components:** Simple circuit.
- **Frequency Response:** Excellent low-frequency response (amplifies DC).
- **Level Shifting:** DC potentials increase stage by stage, requiring level shifting techniques.

Applications: Operational Amplifiers, Regulators.

Mnemonic

D

IRECT - DC signals Immediately REach Connecting Transistors.

Question 2 [c marks]

7 Explain frequency response of two stage RC coupled amplifier.

Solution

RC Coupled Amplifier Frequency Response:

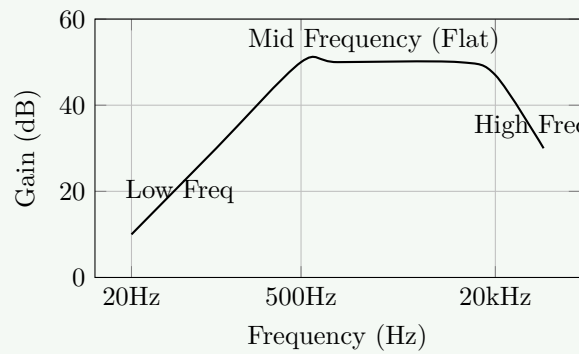


Table 3. Frequency Regions

Region	Frequency	Cause of Fall
Low	20Hz - 500Hz	Coupling Capacitors (C_C) high reactance
Mid	500Hz - 20kHz	Constant Gain (Ideal operation)
High	> 20kHz	Transistor parasitic capacitances

Two-Stage Effect:

- **Bandwidth:** Reduces compared to single stage ($BW_n = BW_1 \times \sqrt{2^{1/n} - 1}$).
- **Gain:** Product of individual stage gains ($A_{total} = A_1 \times A_2$).

Mnemonic

L

MH - Low frequencies by coupling caps, Mid frequencies flat, High frequencies by transistor caps.


Question 2 [a marks]

3 Briefly explain bandwidth and gain-bandwidth product of an amplifier.

Solution

Bandwidth (BW): The range of frequencies over which the amplifier gain is at least 70.7% (or -3dB) of its maximum value. $BW = f_2 - f_1$

Gain-Bandwidth Product (GBP): The product of the voltage gain and the bandwidth is constant for a given amplifier. $GBP = A_v \times BW = \text{Constant}$

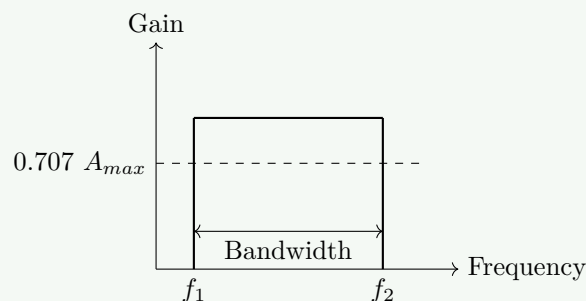**Mnemonic**

B

AND - Bandwidth And gain Never Drop together.

Question 2 [b marks]


4 Explain effects of emitter bypass capacitor and coupling capacitor on frequency response of an amplifier.

Solution

Capacitor Effects:

Table 4. Capacitors

Capacitor	Function	Effect
Coupling (C_C)	Blocks DC, passes AC	Limits Low Frequency response (High reactance at low f)
Bypass (C_E)	Bypasses R_E	Increases Mid-band gain. If removed, gain drops due to negative feedback.

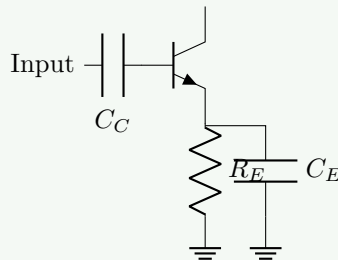

Mnemonic

C

ELL - Coupling affects Extremely Low frequencies, bypass affects Low to high.

Question 2 [c marks]

7 Compare transformer coupled amplifier and RC coupled amplifier

Solution

Comparison:

Table 5. Transformer vs RC Coupled

Feature	Transformer Coupled	RC Coupled
Coupling	Transformer	Resistor-Capacitor
Impedance Matching	Excellent	Poor
Frequency Response	Poor (Resonant peaks)	Good (Flat over wide range)
Efficiency	High	Low
Size/Weight	Bulky/Heavy	Small/Light
Cost	Expensive	Inexpensive
Application	Power Amplifiers	Voltage Amplifiers

Mnemonic

T


RIP - Transformers are Robust for Impedance matching, Problematic for bandwidth.

Question 3 [a marks]

3 Describe the transistor used as a tuned amplifier.

Solution

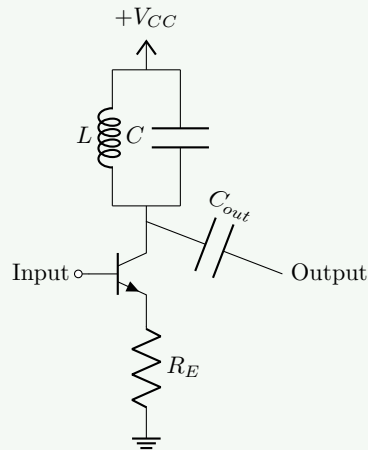Tuned Amplifier: An amplifier that uses a parallel LC tank circuit as the collector load to amplify a specific narrow band of frequencies.



Key Components:

- **LC Tank:** Determines resonant frequency $f_r = \frac{1}{2\pi\sqrt{LC}}$.
- **High Q:** Provides high selectivity.

Applications: Radio and TV receivers (IF amplifiers).

Mnemonic

T

UNE - Transistors Using Narrowband Elements for frequency selection.

Question 3 [b marks]

4 Explain in brief Direct coupled amplifier.

Solution

Direct Coupled Amplifier: (See Q2(b) for diagram) A multi-stage amplifier where the output of one stage is directly connected to the input of the next.

Advantages:

- Low cost (no capacitors/transformers).
- Amplifies DC signals (0 Hz to high frequency).

Disadvantages:

- Thermal drift issues (DC shift).
- Requires stable power supplies.

Mnemonic

D

CAP - Direct Coupled Amplifier Passes all frequencies including DC.

Question 3 [c marks]


7 Describe the importance of h parameters in two port networks. Draw h-parameters circuit for CE amplifier.

Solution

Importance of h-parameters:

- **Hybrid Nature:** Mix of impedance and admittance parameters.
- **Easy to Measure:** h_{11}, h_{21} measured with output shorted; h_{12}, h_{22} measured with input open.
- **Standard:** Manufacturers provide transistor specs in h-parameters.

h-parameter Circuit for CE Amplifier:

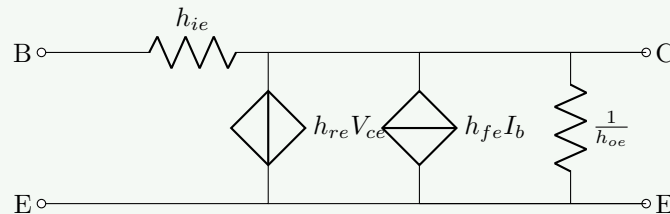

Parameters:

1. h_{ie} : Input Impedance.
2. h_{re} : Reverse Voltage Ratio.
3. h_{fe} : Forward Current Gain (β).
4. h_{oe} : Output Admittance.

Mnemonic

H

IRE - h-parameters Include Resistance and current gain Effectively.

Question 3 [a marks]

3 Compare transformer coupled amplifier and direct coupled amplifier.

Solution

Comparison:

Table 6. Comparison

Feature	Transformer Coupled	Direct Coupled
Frequency Response	Bandpass (Poor Low/High)	DC to High Frequency
Cost	High	Low
Size	Bulky	Compact
Impedance Matching	Excellent	Poor
DC Isolation	Yes	No

Mnemonic

T


DC - Transformers provide DC isolation, Direct provides Complete frequency range.

Question 3 [b marks]

4 Draw and Explain circuit diagram of common emitter amplifier.

Solution

Common Emitter (CE) Amplifier:

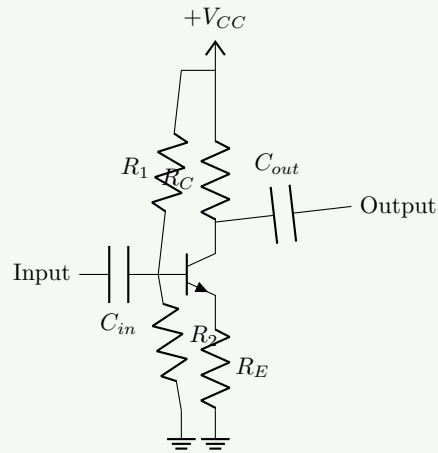

Explanation:

- **Input:** Applied to Base-Emitter.
- **Output:** Taken from Collector-Emitter.
- **Phase Shift:** 180° (Output is inverted).
- **Gain:** High voltage and current gain.

Mnemonic

C


EA - Common Emitter Amplifies with signal inversion.

Question 3 [c marks]

7 Draw Transistor Two Port Network and describe h-parameters for it. Write down advantages of hybrid parameters.

Solution

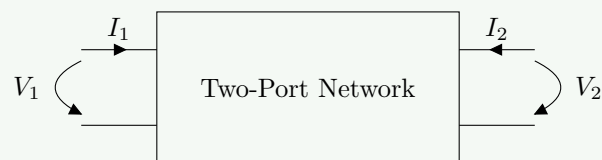Two-Port Network: (See Q3(c) above for h-parameter model explanation).



Equations: $V_1 = h_{11}I_1 + h_{12}V_2$

$I_2 = h_{21}I_1 + h_{22}V_2$


Advantages:

- Real numbers at audio frequencies.
- Easily measured.
- Suitable for circuit analysis.

Mnemonic

H

AEM - Hybrid parameters Are Easily Measured.

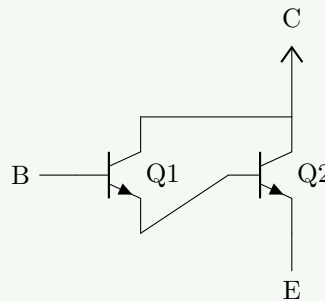
Question 4 [a marks]**3 Explain Darlington pair and its applications.****Solution****Darlington Pair:** Two transistors connected in cascade ($CC - CC$) to behave like a single "super" transistor.**Features:**

- High Current Gain: $\beta \approx \beta_1 \beta_2$.
- High Input Impedance.

Applications: Power amplifiers, relay drivers, touch switches.**Mnemonic**

D


ISH - Darlington Integrates Stages for High current gain.

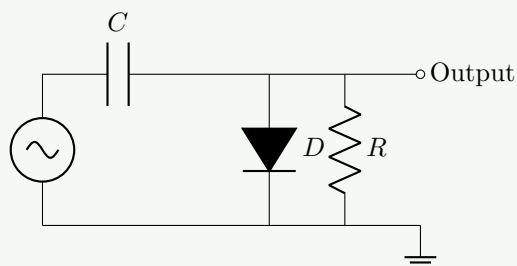Question 4 [b marks]**4 Describe the diode clamper circuit with necessary diagram.****Solution****Diode Clamper:** A circuit that shifts the DC level of a waveform.**Operation:** Capacitor charges to peak voltage, acting as a battery in series with the input signal, shifting it up or down. **Application:** TV Receivers (DC restoration).

Mnemonic

C

LAMP - Circuit Levels Are Modified Precisely.

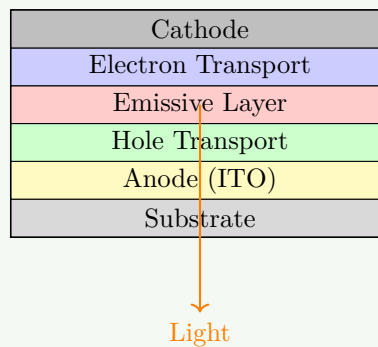
Question 4 [c marks]**7 Explain the construction, working and applications of OLED.****Solution****OLED (Organic Light Emitting Diode):****Working:**

- Charge carriers (holes and electrons) are injected from anode and cathode.
- They recombine in the emissive layer.
- Energy is released as light (Electroluminescence).

Applications: Curved screens, Flexible displays, High-end smartphones.**Mnemonic**

O


LED - Organic Layers Emit Directly.

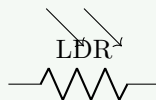Question 4 [a marks]**3 Explain Short note on LDR.****Solution****LDR (Light Dependent Resistor):** A photoresistor made of Cadmium Sulfide (CdS) whose resistance decreases when light shines on it.**Logic:** Light Energy creates electron-hole pairs → Conductivity increases → Resistance decreases. **Use:** Street lights, alarms.

Mnemonic



L

ORD - Light Oppositely Reduces the Device's resistance.

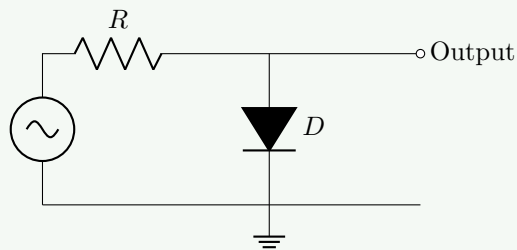Question 4 [b marks]**4 Describe the diode clipper circuit with necessary diagram.****Solution****Diode Clipper:** Removes parts of a signal.**Positive Clipper:** Diode points down (removes positive). **Negative Clipper:** Diode points up (removes negative).**Mnemonic**

C

LIP - Circuit Limits Input Peaks.

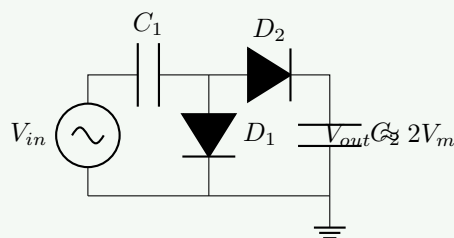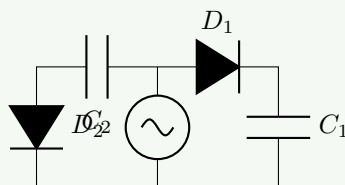Question 4 [c marks]**7 Explain Half Wave and Full wave Voltage Doubler.****Solution****Voltage Doubler:** Produces DC voltage twice the peak AC input ($2V_m$).**Half-Wave Doubler:****Full-Wave Doubler:**

Explanation: Capacitors charge in alternate cycles and their voltages sum up.

Mnemonic

D


OUBLE - Diodes Organize Unidirectional Boost.

Question 5 [a marks]

3 Draw circuit diagram for +5 v Power Supply using its IC

Solution

+5V Power Supply (7805):

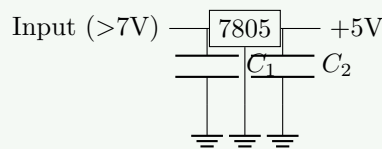

Mnemonic

F

IVE - Fixed IC Voltage Efficiently provided.

Question 5 [b marks]

4 Discuss load regulation and line regulation in reference to power supply.

Solution

Regulation: Keeping output voltage constant.

1. **Line Regulation:** Ability to maintain constant V_{out} when Input Voltage (V_{in}) changes.

$$\%Reg = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100$$

2. **Load Regulation:** Ability to maintain constant V_{out} when Load Current (I_L) changes.

$$\%Reg = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$


Mnemonic

L

INE LOAD - Line Is Normal-input Efficiency, LOAD is Output Adjustment Defense.

Question 5 [c marks]

7 Explain adjustable voltage regulator using LM317 with circuit diagram.

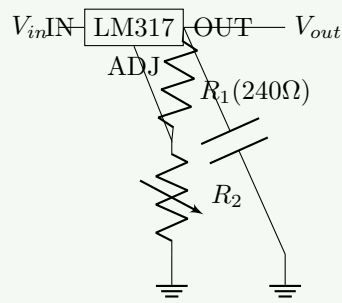
Solution**LM317 Adjustable Regulator:**

Formula: $V_{out} = 1.25(1 + \frac{R_2}{R_1}) + I_{ADJ}R_2$. **Use:** Bench power supplies.

Mnemonic

V

ARY - Voltage Adjustable Regulator Yields custom outputs.

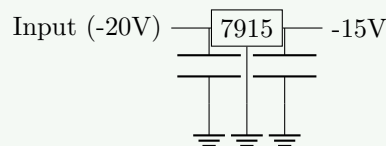Question 5 [a marks]**3 Draw circuit diagram for -15 v Power Supply using its IC****Solution****-15V Power Supply (7915):**

Note: 79xx series is for negative voltage.


Mnemonic

N

INE - Negative IC Needs Efficient filtering.

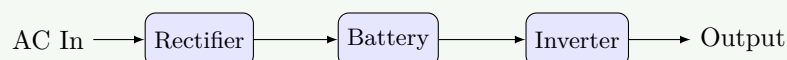Question 5 [b marks]**4 Explain working of UPS.****Solution**

UPS (Uninterruptible Power Supply): Provides emergency power.




Operation: 1. Rectifier charges battery. 2. Inverter converts DC to AC for load. 3. If power fails, battery continues to supply inverter.

Mnemonic

U

PBEAT - Uninterruptible Power Backup.

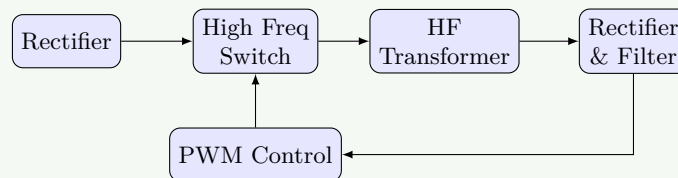Question 5 [c marks]**7 Draw and explain SMPS block diagram with its advantages and disadvantages.****Solution****SMPS (Switch Mode Power Supply):****Advantages:** High efficiency (> 80%), Compact size, Light weight. **Disadvantages:** High noise (EMI), Complex circuit.**Mnemonic**

S

WITCH - Smaller Weight, Improved Thermal efficiency.