

Subject Name Solutions

4341105 – Summer 2023

Semester 1 Study Material

Detailed Solutions and Explanations

Question 1(a) [3 marks]

Write advantages and disadvantages of negative feedback amplifier

Solution

Advantages

Increases bandwidth
Stabilizes gain
Reduces distortion
Increases input impedance (voltage series)
Decreases output impedance (voltage series)

Disadvantages

Reduces gain
Requires more components
Increases cost
May cause oscillations if improperly designed
Requires careful phase compensation

Mnemonic

“GRASS Grows Better Despite Dry Soil” (Gain Reduction, Amplifies Stability, Stops distortion, Better impedance)

Question 1(b) [4 marks]

Derive the equation of overall gain with negative feedback in amplifier and give application of negative feedback.

Solution

Derivation of overall gain with negative feedback:

flowchart LR

```
I[Input] --> S[SummingPoint]
S --> A[Amplifier]
A --> O[Output]
O --> F[FeedbackNetwork]
F --> S
```

- For an amplifier with gain A and feedback factor β :
 - Input signal = V_{in}
 - Feedback signal = $V_{out}\beta$
 - Actual input to amplifier = $V_{in} - V_{out}\beta$
 - Output = $A(V_{in} - V_{out}\beta)$
 - Therefore, $V_{out} = A(V_{in} - V_{out}\beta)$
 - $V_{out} + A\beta V_{out} = AV_{in}$
 - $V_{out}(1 + A\beta) = AV_{in}$
 - Overall gain = $V_{out}/V_{in} = A/(1 + A\beta)$**

Applications of negative feedback:

- Operational amplifiers
- Voltage regulators
- Audio amplifiers
- Instrumentation amplifiers

Mnemonic

“AVOI” (Amplifiers, Voltage regulators, Oscillation control, Instrumentation)

Question 1(c) [7 marks]

Draw and Explain current shunt type negative feedback amplifier and Derive the formula of input impedance and output impedance of it.

Solution

Current Shunt Negative Feedback Amplifier:

flowchart LR

I[Input] --> S[Current Sampling]

S --> A[Amplifier]


A --> O[Output]

O --> F[Feedback Network]

F --> Feedback Current S

In current shunt feedback, the output voltage is sampled and converted to a current that is subtracted from the input current.

Circuit Diagram:

 

Characteristics:

- **Feedback type:** Current sampling at output, shunt mixing at input
- **Samples:** Output voltage
- **Feedback to:** Input current

Derivation of Input Impedance:

- Without feedback: Z_{in}
- With current shunt feedback: $Z_{in}' = Z_{in}/(1 + A)$
- **Therefore, input impedance decreases by factor $(1 + A)$**

Derivation of Output Impedance:

- Without feedback: Z_o
- With current shunt feedback: $Z_o' = Z_o/(1 + A)$
- **Therefore, output impedance decreases by factor $(1 + A)$**

Mnemonic

“DISCO” (Decreased Impedances with Shunt Current Operation)

Question 1(c) OR [7 marks]

Draw and Explain voltage series type negative feedback amplifier and Derive the formula of input impedance and output impedance of it.

Solution

Voltage Series Negative Feedback Amplifier:


flowchart LR

```

    I[Input] --> S[VoltageSampling]
    S --> A[Amplifier]
    A --> O[Output]
    O --> F[FeedbackNetwork]
    F --> S
  
```

In voltage series feedback, the output voltage is sampled and fed back in series with the input voltage.

Circuit Diagram:

 

Characteristics:

- **Feedback type:** Voltage sampling at output, series mixing at input
- **Samples:** Output voltage
- **Feedback to:** Input voltage

Derivation of Input Impedance:

- Without feedback: Z_{in}
- With voltage series feedback: $Z_{in}' = Z_{in} \times (1 + A)$
- **Therefore, input impedance increases by factor $(1 + A)$**

Derivation of Output Impedance:

- Without feedback: Z_o
- With voltage series feedback: $Z_o' = Z_o / (1 + A)$
- **Therefore, output impedance decreases by factor $(1 + A)$**

Mnemonic

“ISDO” (Increased input impedance, Series feedback, Decreased output impedance, Output voltage sampled)

Question 2(a) [3 marks]

Draw and Explain the circuit diagram of UJT as a relaxation oscillator.

Solution

UJT Relaxation Oscillator:

```
flowchart TB
```

A[UJT Relaxation Oscillator]

```
A {-}{-}{-} B[Produces pulses withnRC charging circuit]}
```

```
A {-}{-}{-} C[UJT triggers whenncapacitor voltage reaches peak]}
```

```
A {-}{-} D[Simple timing circuit]}
```

Circuit Diagram:



In this circuit:

- C1 charges through R1
- When capacitor voltage reaches UJT's peak point, UJT turns on
- Capacitor discharges rapidly through UJT
- Process repeats creating oscillations

Mnemonic

“CURD” (Capacitor charges Until Reaching Discharge point)


Question 2(b) [4 marks]


Draw circuit diagram of Colpitts oscillator and explain in brief. Give the advantages and disadvantages of it.

Solution

Colpitts Oscillator:

Circuit Diagram:

 

 

Working:

- Uses LC tank circuit with capacitive voltage divider (C1 and C2)
- Transistor amplifies and provides energy to tank circuit
- Oscillation frequency: $f = \frac{1}{2\pi\sqrt{L \times (C1C2)/(C1 + C2)}}$

Advantages	Disadvantages
Good frequency stability	Requires two capacitors (C1, C2)
Works well at high frequencies	More difficult to tune than some oscillators
Lower harmonics	Sensitive to transistor parameters
Simple design	Limited frequency range

Mnemonic

“FAST Circuits” (Frequency stable, Appropriate for high frequencies, Simple design, Two capacitors needed)

Question 2(c) [7 marks]

Explain the Crystal Oscillator.

Solution

Crystal Oscillator:


flowchart TD

```

A[Crystal Oscillator] --> B[Uses piezoelectric crystal]
A --> C[Extremely stable frequency]
A --> D[High Q factor]
A --> E[Precise timing applications]

```

Circuit Diagram:

 

Working Principle:

- Based on piezoelectric effect of quartz crystal
- Crystal vibrates at natural resonant frequency when voltage applied

- Acts as very stable resonator with extremely high Q factor
- Provides feedback at precise frequency

Characteristics:

- **Resonant frequency:** Determined by crystal cut and dimensions
- **Q factor:** Typically 10,000-100,000 (much higher than LC circuits)
- **Frequency stability:** Typically 0.001% to 0.01%
- **Temperature coefficient:** Usually low, can be specially cut for zero temp coefficient

Applications:

- Clock generation in computers
- Frequency standards
- Radio transmitters/receivers
- Digital watches and clocks
- Microcontroller timing

Mnemonic

“STOP Precisely” (Stable, Temperature-resistant, Oscillates, Piezoelectric, Precisely)

Question 2(a) OR [3 marks]

Draw and explain the Hartley Oscillator.

Solution

Hartley Oscillator:


flowchart TB

A[Hartley Oscillator] --> B[Uses tapped inductor]

A --> C[LC tank circuit]

A --> D[RF applications]

Circuit Diagram:

 

Working:

- Uses LC tank circuit with tapped inductor (L1 and L2)
- Transistor amplifies and provides energy to tank circuit
- Oscillation frequency:

$$f = \frac{1}{2\pi\sqrt{L}} \text{ where } L = L1 + L2$$

- Feedback through inductive coupling

Mnemonic

“TIC” (Tapped inductor Circuit)

Question 2(b) OR [4 marks]

Draw and explain Wien Bridge oscillator.

Solution

Wien Bridge Oscillator:

flowchart TD


A[Wien Bridge Oscillator] --> B[Uses RC network]

A --> C[Audio frequency range]

A --> D[Low distortion]

A --> E[Stable output]

Circuit Diagram:

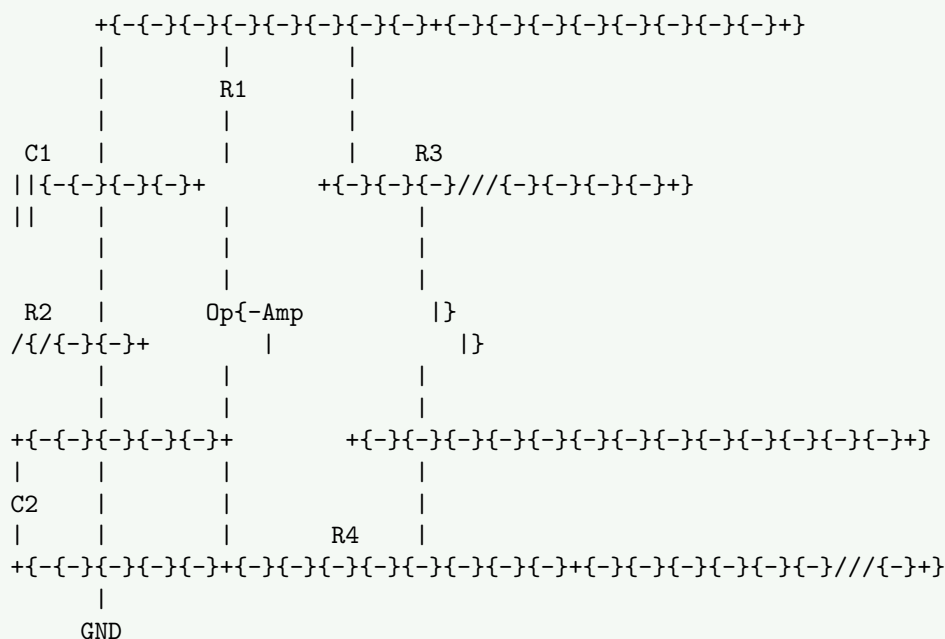

Working:

- Uses RC Wien bridge network as frequency-selective feedback
- $R_1=R_2$ and $C_1=C_2$ for simplest design
- Oscillation frequency: $f = 1/(2 RC)$
- Gain must be ≥ 3 for sustained oscillations
- Used for audio frequency generation with low distortion

Mnemonic

“FEAR” (Frequency selective, Equal RC components, Audio range, Reduced distortion)


Question 2(c) OR [7 marks]

Draw the Structure, symbol, equivalent circuit of UJT and explain in brief.


Solution

Unijunction Transistor (UJT):
Structure:


Base 2 (B2)

 

Symbol:

 

Equivalent Circuit:

 

Working Principle:

- UJT is a three-terminal device with one emitter and two bases
- N-type silicon bar with P-type emitter junction
- Forms a voltage divider with internal resistances R_{B1} and R_{B2}
- Emitter current starts flowing when $V_E > +V_D$
- Where η is intrinsic standoff ratio $= R_{B1}/(R_{B1}+R_{B2})$

Characteristics:

- **Intrinsic standoff ratio (η):** Typically 0.5 to 0.8
- **Negative resistance region:** Current increases as voltage decreases

- **Peak point:** Beginning of negative resistance region
- **Valley point:** End of negative resistance region

Applications:

- Relaxation oscillators
- Timing circuits
- Trigger generators
- SCR triggering circuits
- Sawtooth generators

Mnemonic

“NEVER” (Negative resistance, Emitter-triggered, Valley and peak points, Easily timed, Relaxation oscillator)

Question 3(a) [3 marks]

Differentiate between voltage and power amplifier.

Solution

Parameter	Voltage Amplifier	Power Amplifier
Purpose	Amplifies voltage	Delivers power to load
Output impedance	High	Low
Input impedance	High	Relatively low
Efficiency	Not important	Very important
Heat dissipation	Low	High (requires heat sink)
Position in circuit	Early stages	Final stage

Mnemonic

“PEHIP” (Power for Efficiency and Heat, Impedance matters, Position differs)

Question 3(b) [4 marks]

Explain class-B push pull power amplifier in detail.

Solution

Class-B Push-Pull Amplifier:


flowchart TB

```

A[Class-B Push-Pull] --> B[Uses two transistors]
A --> C[Each handles half cycle]
A --> D[Higher efficiency 78\%]
A --> E[Crossover distortion]

```

Circuit Diagram:

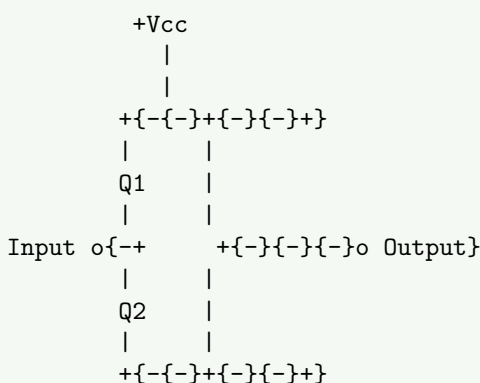

|
|
GND

Working:

- Uses two complementary transistors
- Q1 conducts during positive half-cycle
- Q2 conducts during negative half-cycle
- Each transistor conducts for 180° of input cycle
- Theoretical efficiency: 78.5%

Mnemonic

“ECHO” (Efficiency high, Crossover distortion, Half-cycle operation, Output high power)

Question 3(c) [7 marks]

Draw and Explain Complementary symmetry push-pull power amplifier in detail also list the disadvantages of it.

Solution


Complementary Symmetry Push-Pull Amplifier:

flowchart TD

```

A[Complementary Push-Pull] --> B[Uses NPN and PNP]
A --> C[Direct coupling possible]
A --> D[No center-tapped transformer]
A --> E[Class B or AB operation]
  
```

Circuit Diagram:

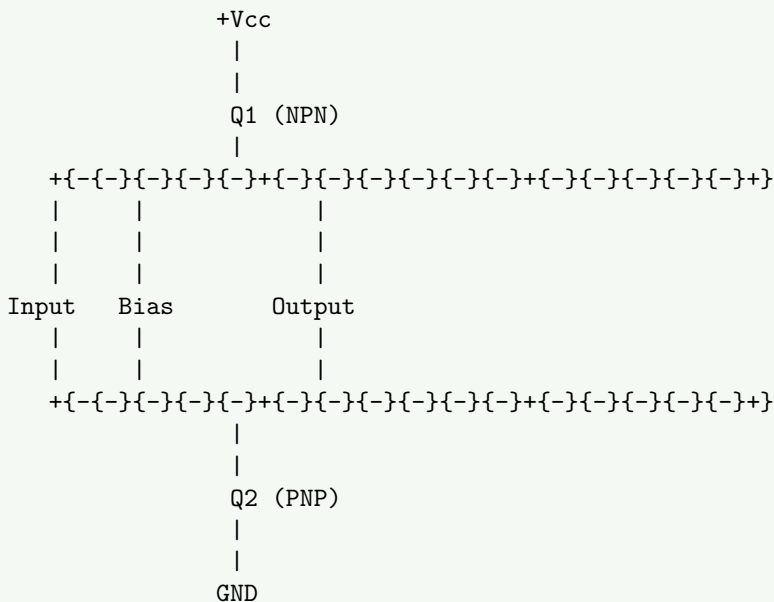

Working:

- Uses complementary pair (NPN and PNP transistors)
- No need for center-tapped transformer
- NPN handles positive half-cycle
- PNP handles negative half-cycle
- Biasing network reduces crossover distortion
- Direct coupling to speaker possible

Disadvantages:

- Thermal runaway if not properly biased
- Requires complementary matched transistors

- Crossover distortion in Class-B operation
- Needs both positive and negative power supplies
- Difficulty finding exact complementary pairs

Mnemonic

“MATCH Precisely” (Matched transistors, Avoids transformers, Thermal issues, Crossover distortion, Heat dissipation needed)

Question 3(a) OR [3 marks]

Define the terms related to power amplifier. i)Efficiency ii)Distortion iii)power dissipation capability

Solution

Term	Definition
Efficiency	Ratio of AC output power delivered to the load to the DC input power drawn from the supply. Mathematically: $\text{Efficiency} = \frac{P_{out}}{P_{in}} \times 100\%$. <i>High efficiency means less power wasted as heat.</i>
Distortion	Unwanted alteration of the output waveform compared to input waveform. Measured as Total Harmonic Distortion (THD). Includes harmonic, intermodulation, crossover, and amplitude distortion.
Power Dissipation Capability	Maximum power that can be dissipated by the amplifier without damage. Depends on heat sink, thermal resistance, and maximum junction temperature of transistors.

Mnemonic

“EDP” (Efficiency converts, Distortion deforms, Power capability protects)

Question 3(b) OR [4 marks]

Classify the power amplifier for mode of operation and explain working of different type power amplifier

Solution

Classification of Power Amplifiers:

flowchart TB

```

A[Power Amplifiers] --> B[Class A]
A --> C[Class B]
A --> D[Class AB]
A --> E[Class C]

```

Class	Conduction Angle	Working
Class A	360°	Amplifier conducts for entire input cycle. Output signal is exact replica of input but amplified. Linear but inefficient (25-30%).
Class B	180°	Two transistors each conduct for half cycle. One handles positive half, other handles negative half. More efficient (70-80%) but has crossover distortion.

Class AB $180^\circ - 360^\circ$

Class C $<180^\circ$

Compromise between Class A and B. Slight bias to reduce crossover distortion. Good efficiency (50-70%) with acceptable distortion. Conducts for less than half cycle. Very efficient ($>80\%$) but highly distorted. Used mainly in RF tuned amplifiers.

Mnemonic

“ABCE” (A-all cycle, B-both halves separately, C-compromise solution, E-efficiency with distortion)

Question 3(c) OR [7 marks]

Derive efficiency of class-B push pull power amplifier.

Solution

Derivation of Class-B Push-Pull Amplifier Efficiency:


flowchart TB

A[Class-B Efficiency] --> B[Based on power ratio]

A --> C[Each transistor conducts half cycle]

A --> D[Theoretical max efficiency: 78.5%]

Circuit Diagram:

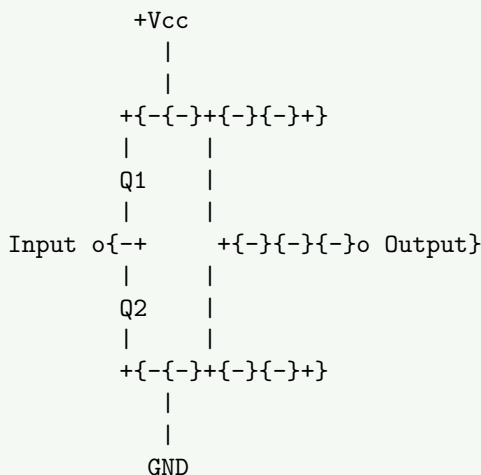

Efficiency Calculation:

1. DC power input calculation:

- Each transistor conducts for half cycle
- Average DC current: $I_{dc} = I_{max}/2$
- DC power input: $P_{dc} = V_{cc} \times I_{dc} = V_{cc} \times I_{max}/2$

2. AC power output calculation:

- RMS value of current: $I_{rms} = I_{max}/2$
- AC power output: $P_{ac} = (I_{rms})^2 \times R_L = (I_{max}/2)^2 \times R_L$
- For maximum power: $I_{max} \times R_L = V_{cc}$
- Therefore: $P_{ac} = (V_{cc})^2 / (2 \times R_L)$

3. Efficiency calculation:

- $= (P_{ac}/P_{dc}) \times 100\%$
- $= [(V_{cc})^2 / (2 \times R_L)] \div [V_{cc} \times I_{max}/2] \times 100\%$
- $= [(V_{cc})^2 / (2 \times R_L)] \div [V_{cc} \times V_{cc} / (2 \times R_L)] \times 100\%$
- $= [(V_{cc})^2 / (2 \times R_L)] \times [2 \times R_L / V_{cc}^2] \times 100\%$
- $= 1/4 \times 100\% \approx 78.5\%$

Maximum theoretical efficiency of Class-B push-pull amplifier is 78.5%

Mnemonic
“PIPE” (Power ratio, Input DC vs output AC, Pi in formula, Efficiency maximum 78.5%)

Mnemonic
“PIPE” (Power ratio, Input DC vs output AC, Pi in formula, Efficiency maximum 78.5%)

Question 4(a) [3 marks]

Draw pin diagram and Schematic symbol of IC 741 and explain it in detail.

Solution

IC 741 Op-Amp Pin Diagram and Symbol:

Pin Diagram:

Schematic Symbol:

Pin Description:

- Offset Null (NC1)
- Inverting Input (-)
- Non-inverting Input (+)
- Negative Supply (-Vcc)
- Offset Null (NC2)
- Output
- Positive Supply (+Vcc)
- NC (No Connection)

IC 741 Op-Amp Pin Diagram and Symbol:

Pin Diagram:

Schematic Symbol:

Pin Description:

- Offset Null (NC1)
- Inverting Input (-)
- Non-inverting Input (+)
- Negative Supply (-Vcc)
- Offset Null (NC2)
- Output
- Positive Supply (+Vcc)
- NC (No Connection)

IC 741 Op-Amp Pin Diagram and Symbol:

Pin Diagram:

Schematic Symbol:

Pin Description:

- Offset Null (NC1)
- Inverting Input (-)
- Non-inverting Input (+)
- Negative Supply (-Vcc)
- Offset Null (NC2)
- Output
- Positive Supply (+Vcc)
- NC (No Connection)

IC 741 Op-Amp Pin Diagram and Symbol:

Pin Diagram:

Schematic Symbol:

Pin Description:

- Offset Null (NC1)
- Inverting Input (-)
- Non-inverting Input (+)
- Negative Supply (-Vcc)
- Offset Null (NC2)
- Output
- Positive Supply (+Vcc)
- NC (No Connection)

- IC 741 Op-Amp Pin Diagram and Symbol:**
- Pin Diagram:**
-
- Schematic Symbol:**
-
- Pin Description:**
- Offset Null (NC1)
 - Inverting Input (-)
 - Non-inverting Input (+)
 - Negative Supply (-Vcc)
 - Offset Null (NC2)
 - Output
 - Positive Supply (+Vcc)
 - NC (No Connection)

Mnemonic
 “ON-INO” (Offset Null, Inverting input, Negative supply, Input non-inverting, Output, No connection)

Mnemonic
 “ON-INO” (Offset Null, Inverting input, Negative supply, Input non-inverting, Output, No connection)

Question 4(b) [4 marks]

Explain differential Amplifier using OPAMP.

Solution

Differential Amplifier Using Op-Amp:

```
graph TD
    A[Differential Amplifier] --> B[Amplifies difference]
    A --> C[Rejects common mode]
    A --> D[Four equal resistors]
    A --> E["Gain = R2/R1"]
```

Circuit Diagram:

Differential Amplifier Using Op-Amp:

```
graph TD
    A[Differential Amplifier] --> B[Amplifies difference]
    A --> C[Rejects common mode]
    A --> D[Four equal resistors]
    A --> E["Gain = R2/R1"]
```

Circuit Diagram:

Differential Amplifier Using Op-Amp:


```
graph TD
    A[Differential Amplifier] --> B[Amplifies difference]
    A --> C[Rejects common mode]
    A --> D[Four equal resistors]
    A --> E["Gain = R2/R1"]
```

Circuit Diagram:

Differential Amplifier Using Op-Amp:

```
graph TD
    A[Differential Amplifier] --> B[Amplifies difference]
    A --> C[Rejects common mode]
    A --> D[Four equal resistors]
    A --> E["Gain = R2/R1"]
```

Circuit Diagram:

 

Working:

- Output is proportional to difference between inputs
- If $R1 = R3$ and $R2 = R4$, then: $V_{out} = (R2/R1)(V2-V1)$
- Rejects signals common to both inputs (common-mode rejection)
- Used in instrumentation applications

Mnemonic

“CARE” (Common-mode rejection, Amplifies difference, Resistor matching important, Equal resistors for balance)

Question 4(c) [7 marks]


Explain the following parameters of an OP-Amp: 1) Input offset voltage 2) Output Offset Voltage 3) Input Offset Current 4) Input Bias Current 5) CMRR 6) Slew rate 7) Gain.

Solution

Parameters of an Op-Amp:

Parameter	Description	Typical Value for 741
Input Offset Voltage	Voltage needed at input to zero the output	1-5 mV
Output Offset Voltage	Output voltage when inputs are grounded	Depends on input offset and gain
Input Offset Current	Difference between input bias currents	3-30 nA
Input Bias Current	Average of the two input currents	30-500 nA
CMRR	Ability to reject common-mode signals	70-100 dB
Slew Rate	Maximum rate of output voltage change	0.5 V/ s
Gain (Aol)	Open-loop voltage gain	104-106 (80-120 dB)

Diagram for Input Offset Voltage:

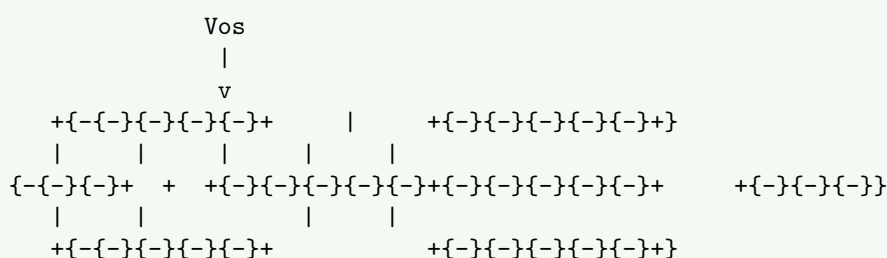

Mnemonic
 “VICS BGR” (Voltage offset at Input, Current offset, Slew rate, Bias current, Gain, Rejection ratio)

Mnemonic
 “VICS BGR” (Voltage offset at Input, Current offset, Slew rate, Bias current, Gain, Rejection ratio)

Question 4(a) OR [3 marks]

List characteristics of ideal op-amp.

Solution	
Characteristic	Ideal Value
Open-loop gain	Infinite
Input impedance	Infinite
Output impedance	Zero
Bandwidth	Infinite
CMRR	Infinite
Slew rate	Infinite
Offset voltage	Zero
Noise	Zero

Solution	
Characteristic	Ideal Value
Open-loop gain	Infinite
Input impedance	Infinite
Output impedance	Zero
Bandwidth	Infinite
CMRR	Infinite
Slew rate	Infinite
Offset voltage	Zero
Noise	Zero

Mnemonic
 “ZINC BOSS” (Zero offset, Infinite bandwidth, No noise, CMRR infinite, Bandwidth unlimited, Output impedance zero, Slew rate unlimited, Speed unlimited)

Mnemonic
 “ZINC BOSS” (Zero offset, Infinite bandwidth, No noise, CMRR infinite, Bandwidth unlimited, Output impedance zero, Slew rate unlimited, Speed unlimited)

Question 4(b) OR [4 marks]

Draw and explain the block diagram of the Operational Amplifier (OPAMP) in detail.

Solution

Op-Amp Block Diagram:

```

graph LR
    A[Input Stage] --> B[Intermediate Stage]
    B --> C[Output Stage]
    D[Biasing Circuit] --> A
    D --> B
    D --> C
    E[Compensation Network] --> B
  
```

Detailed Block Diagram:

The diagram illustrates the internal components of an operational amplifier. At the top, the 'Power Supply' is connected to a central node 'v'. Below this, the main signal path consists of an 'Input Pins' block, followed by a 'Differential Stage', a 'Gain Stage', a 'Voltage Stage', and finally the 'Output'. A 'Biasing Circuit' is connected to the 'Input Pins', 'Differential Stage', and 'Gain Stage'. A 'Compensation Network' is connected to the 'Gain Stage' and the 'Output'. The diagram uses various symbols to represent different types of components, such as resistors, capacitors, and active devices.

Solution

Op-Amp Block Diagram:

```

graph LR
    A[Input Stage] --> B[Intermediate Stage]
    B --> C[Output Stage]
    D[Biasing Circuit] --> A
    D --> B
    D --> C
    E[Compensation Network] --> B
  
```

Detailed Block Diagram:

The diagram illustrates the internal components of an operational amplifier. At the top, the 'Power Supply' is connected to a central node 'v'. Below this, the main signal path consists of an 'Input Pins' block, followed by a 'Differential Stage', a 'Gain Stage', a 'Voltage Stage', and finally the 'Output'. A 'Biasing Circuit' is connected to the 'Input Pins', 'Differential Stage', and 'Gain Stage'. A 'Compensation Network' is connected to the 'Gain Stage' and the 'Output'. The diagram uses various symbols to represent different types of components, such as resistors, capacitors, and active devices.

Solution

Op-Amp Block Diagram:

```

graph LR
    A[Input Stage] --> B[Intermediate Stage]
    B --> C[Output Stage]
    D[Biasing Circuit] --> A
    D --> B
    D --> C
    E[Compensation Network] --> B
  
```

Detailed Block Diagram:

The diagram illustrates the internal components of an operational amplifier. At the top, the 'Power Supply' is connected to a central node 'v'. Below this, the main signal path consists of an 'Input Pins' block, followed by a 'Differential Stage', a 'Gain Stage', a 'Voltage Stage', and finally the 'Output'. A 'Biasing Circuit' is connected to the 'Input Pins', 'Differential Stage', and 'Gain Stage'. A 'Compensation Network' is connected to the 'Gain Stage' and the 'Output'. The diagram uses various symbols to represent different types of components, such as resistors, capacitors, and active devices.

Solution

Op-Amp Block Diagram:

```

graph LR
    A[Input Stage] --> B[Intermediate Stage]
    B --> C[Output Stage]
    D[Biasing Circuit] --> A
    D --> B
    D --> C
    E[Compensation Network] --> B
  
```

Detailed Block Diagram:

The diagram illustrates the internal components of an operational amplifier. At the top, the 'Power Supply' is connected to a central node 'v'. Below this, the main signal path consists of an 'Input Pins' block, followed by a 'Differential Stage', a 'Gain Stage', a 'Voltage Stage', and finally the 'Output'. A 'Biasing Circuit' is connected to the 'Input Pins', 'Differential Stage', and 'Gain Stage'. A 'Compensation Network' is connected to the 'Gain Stage' and the 'Output'. The diagram uses various symbols to represent different types of components, such as resistors, capacitors, and active devices.

Solution


Op-Amp Block Diagram:

```

graph LR
    A[Input Stage] --> B[Intermediate Stage]
    B --> C[Output Stage]
    D[Biasing Circuit] --> A
    D --> B
    D --> C
    E[Compensation Network] --> B
  
```

Detailed Block Diagram:

The diagram illustrates the internal components of an operational amplifier. At the top, the **Power Supply** is connected to the **V** pin. Below this, the **Input Pins** are connected to the **Differential Stage**. The **Differential Stage** is connected to the **Gain Stage**, which is in turn connected to the **Voltage Stage**. The **Voltage Stage** is connected to the **Output**. A **Biasing Circuit** is connected to the **Input Pins**, **Differential Stage**, and **Gain Stage**. A **Compensation Network** is connected to the **Gain Stage**.

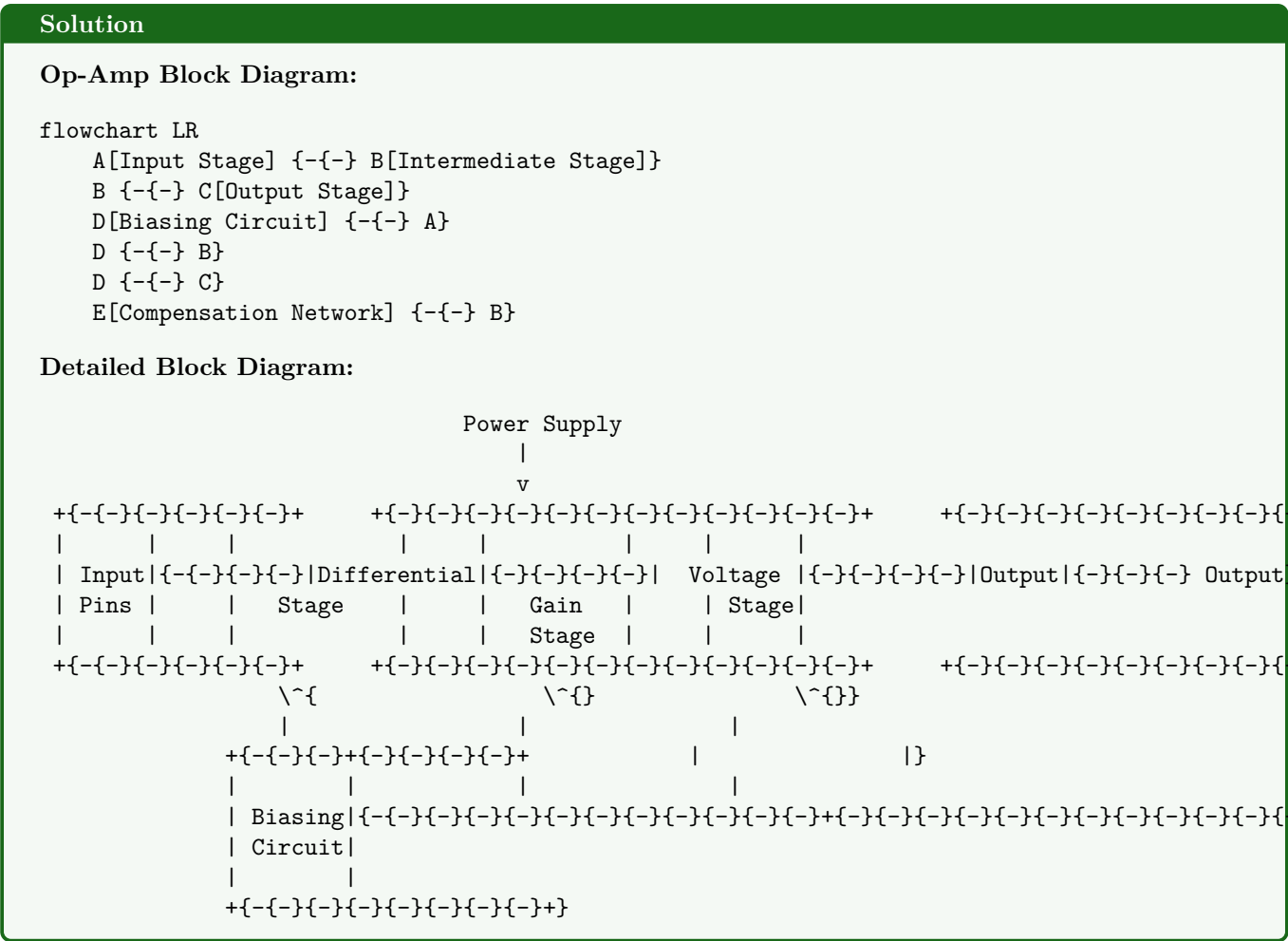

$\sqrt{}$
 |
 Power Supply

Working of Blocks:

1. **Input Stage:** Differential amplifier with high input impedance
2. **Intermediate Stage:** High-gain voltage amplifier with frequency compensation
3. **Output Stage:** Low output impedance buffer, provides current gain
4. **Biasing Circuit:** Provides proper DC levels to all stages
5. **Compensation Network:** Prevents oscillation, ensures stability

Mnemonic

“DISCO” (Differential stage Input, Second stage amplifies, Compensation network, Output buffer)

Question 4(c) OR [7 marks]

Draw & explain Inverting and Non-inverting Op-amp amplifier with the derivation of voltage gain.

Solution

Inverting Amplifier:


flowchart TB

A[Inverting Amplifier] --> B[Output 180° out of phase]

A --> C[Gain = $-R_f/R_{in}$]

A --> D[Virtual ground at inverting input]

Circuit Diagram:

 

Gain Derivation:

- Using virtual ground concept ($V_- \approx 0$)
- Current through R_{in} : $I_{in} = V_{in}/R_{in}$
- Current through R_f : $I_f = I_{in}$ (no current into op-amp input)
- Voltage across R_f : $V_{out} = -I_f \times R_f = -I_{in} \times R_f = -V_{in} \times R_f/R_{in}$
- Therefore, Gain = $V_{out}/V_{in} = -R_f/R_{in}$

Non-Inverting Amplifier:

flowchart TB


A[Non-Inverting Amplifier] --> B[Output in phase with input]

A --> C[Gain = $1 + R_f/R_{in}$]

A --> D[Higher input impedance than inverting]

Circuit Diagram:

R_f

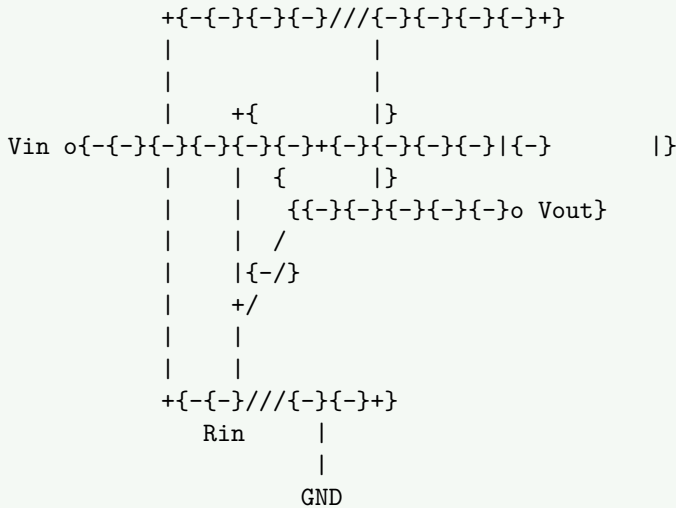

Gain Derivation:

- Due to negative feedback, $V_- \approx V_+ = V_{in}$
- Voltage across R_{in} : $V_- = V_{in}$
- Current through R_{in} : $I_{Rin} = V_- / R_{in} = V_{in} / R_{in}$
- Same current flows through R_f : $I_{Rf} = I_{Rin}$
- Voltage across R_f : $V_{Rf} = I_{Rf} \times R_f = V_{in} \times R_f / R_{in}$
- Output voltage: $V_{out} = V_- + V_{Rf} = V_{in} + V_{in} \times R_f / R_{in} = V_{in}(1 + R_f / R_{in})$
- Therefore, Gain = $V_{out} / V_{in} = 1 + R_f / R_{in}$

Comparison:

Parameter	Inverting Amplifier	Non-Inverting Amplifier
Gain formula	$-R_f / R_{in}$	$1 + R_f / R_{in}$
Phase shift	180°	0°
Input impedance	Equal to R_{in}	Very high ($\approx \text{infinite}$)
Min. possible gain	Can be < 1	Always ≥ 1

Mnemonic

“PING-PONG” (Phase Inverted Negative Gain vs Positive Output Non-inverted Gain)

Question 5(a) [3 marks]

Draw and explain integrator using Op-Amp.


Solution

Op-Amp Integrator:

flowchart TD

- A[Integrator] --> B[RC circuit in feedback]
- A --> C[Output is integral of input]
- A --> D[Acts as low-pass filter]

Circuit Diagram:

 

|
GND

Working:

- Output voltage is proportional to integral of input
- $V_{out} = -1/RC \int dt$
- Used in waveform generators, analog computers
- Acts as low-pass filter with -20dB/decade slope

Mnemonic

“TIME” (Takes Input and Makes integral over time Exactly)

Question 5(b) [4 marks]

Compare different types of power amplifier.

Solution

Parameter	Class A	Class B	Class AB	Class C
Conduction angle	360°	180°	180° – 360°	<180°
Efficiency	25-30%	70-80%	50-70%	>80%
Distortion	Very low	High (crossover)	Low	Very high
Biasing	Above cutoff	At cutoff	Slightly above cutoff	Below cutoff
Applications	High fidelity audio	General purpose	Audio amplifiers	RF amplifiers

Mnemonic

“CABINET” (Conduction angle, Amplification quality, Biasing, Ideal applications, Noise/distortion, Efficiency, Temperature concerns)

Question 5(c) [7 marks]

List applications of IC555 and explain any one in detail.

Solution

Applications of IC 555:

1. Astable multivibrator
2. Monostable multivibrator
3. Bistable multivibrator
4. Pulse width modulator
5. Sequential timer
6. Frequency divider
7. Tone generator

Astable Multivibrator Using IC 555:

flowchart TB

```

A[555 Astable] --> B[Free-running oscillator]
A --> C[No stable state]
A --> D[Output continuously switches]
A --> E[Frequency determined by R1, R2, C]


```

Circuit Diagram:

```

+Vcc
|
|
+---+---+---+---+---+---+---+---+---+

```

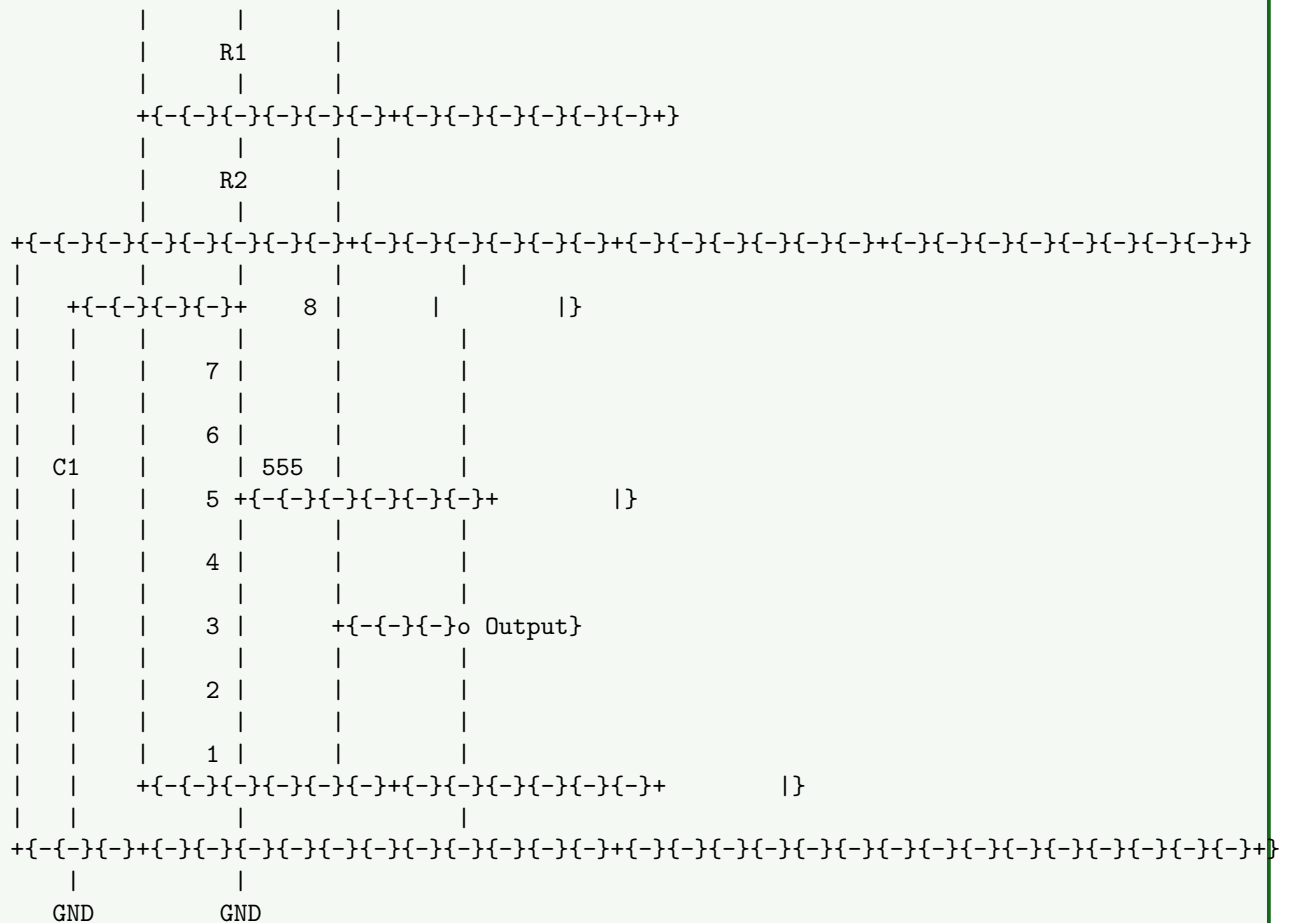

Working:

- R1, R2, and C determine frequency
- Output oscillates between HIGH and LOW
- Charging time: $t_1 = 0.693(R_1 + R_2)C$
- Discharging time: $t_2 = 0.693(R_2)C$
- Total period:
 $T = t_1 + t_2 = 0.693(R_1 + 2R_2)C$
- Frequency: $f = 1.44 / [(R_1 + 2R_2)C]$
- Duty cycle: $D = (R_1 + R_2) / (R_1 + 2R_2)$

Applications:

- LED flashers
- Clock generators
- Tone generators
- Pulse generation

Mnemonic

“FREE” (Frequency determined by Resistors and capacitor, Endless oscillation, Easy to configure)

Question 5(a) OR [3 marks]

Draw and explain summing amplifier using Op-Amp.

Solution

Summing Amplifier Using Op-Amp:


flowchart TB

A[Summing Amplifier] --> B[Adds multiple inputs]

A --> C[Weighted sum possible]

A --> D[Inverting configuration]

Circuit Diagram:

 

Working:

- Uses inverting configuration with multiple inputs
- Each input contributes to output based on its resistance
- If $R_1 = R_2 = R_3 = R$, and $R_f = R$, then $V_{out} = -(V_1 + V_2 + V_3)$
- If resistors differ, weighted sum is produced: $V_{out} = -R_f(V_1/R_1 + V_2/R_2 + V_3/R_3)$
- Virtual ground at inverting input simplifies analysis

Mnemonic

“SWIM” (Summing Weighted Inputs with Mixing)

Question 5(b) OR [4 marks]

Compare between push-pull amplifier and Complementary push-pull power amplifier.

Solution

Parameter	Push-Pull Amplifier	Complementary Push-Pull Amplifier
Transistors used	Same type (NPN or PNP)	Complementary pair (NPN and PNP)
Input transformer	Required (center-tapped)	Not required
Output transformer	Required	Not required
Circuit complexity	More complex	Simpler
Cost	Higher due to transformers	Lower
Frequency response	Limited by transformers	Better (wider range)
Phase distortion	Higher	Lower
Power supply	Single polarity	Dual polarity usually required

Mnemonic

“TONIC” (Transformers vs None, One type vs complementary, Nice frequency response, Improved distortion, Cost effectiveness)

Question 5(c) OR [7 marks]

Draw pin diagram and block diagram of IC555 and explain in detail.

Solution

IC 555 Timer:

Pin Diagram:

$$\begin{array}{ccccc}
& +\{-\{-\}\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}+ \\
1 & \circ\{-\{-\}\}\{-\}| & & & |\{-\}\{-\}\}\{-\}\circ 8\} \\
& | & & & | \\
2 & \circ\{-\{-\}\}\{-\}| & 555 & & |\{-\}\{-\}\}\{-\}\circ 7\} \\
& | & & & | \\
3 & \circ\{-\{-\}\}\{-\}| & & & |\{-\}\{-\}\}\{-\}\circ 6\} \\
& | & & & | \\
4 & \circ\{-\{-\}\}\{-\}| & & & |\{-\}\{-\}\}\{-\}\circ 5\} \\
& +\{-\{-\}\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}+
\end{array}$$

Pin Description:

1. Ground - Connected to circuit ground
2. Trigger - Starts the timing cycle when voltage falls below $1/3 V_{cc}$
3. Output - Provides the output signal, can source or sink up to 200mA
4. Reset - Terminates timing cycle when pulled low
5. Control Voltage - Allows access to internal voltage divider ($2/3 V_{cc}$)
6. Threshold - Ends timing cycle when voltage exceeds $2/3 V_{cc}$
7. Discharge - Connected to open collector of internal transistor
8. V_{cc} - Positive supply voltage (4.5V to 16V)

Block Diagram:

[illegible]

