

Fundamentals of Electronics (4311102) - Winter 2023 Solution

Milav Dabgar

January 24, 2023

Question 1(a) [3 marks]

Define Forward and reverse bias of diode.

Solution

Answer:

Forward Bias of Diode:

- **Connection Method:** P-type connected to positive terminal and N-type connected to negative terminal of battery
- **Barrier Width:** Barrier width decreases
- **Resistance:** Low resistance (typically $100-1000\Omega$)
- **Current Flow:** Allows current to flow easily through the diode

Reverse Bias of Diode:

- **Connection Method:** P-type connected to negative terminal and N-type connected to positive terminal
- **Barrier Width:** Barrier width increases
- **Resistance:** Very high resistance (typically several $M\Omega$)
- **Current Flow:** Blocks current flow (only small leakage current flows)

Diagram:

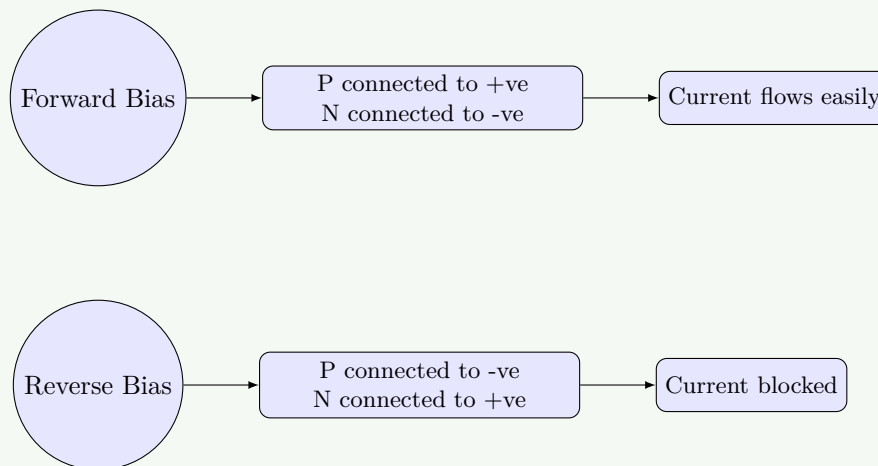


Figure 1. Forward and Reverse Bias Logic

Mnemonic

“PFNR: ”Positive to P Forward, Negative to P Reverse””

Question 1(b) [4 marks]

Explain construction and working of LDR.

Solution

Answer:

Construction of LDR:

- **Material:** Made of semiconductor material (Cadmium Sulfide)
- **Pattern:** Zigzag pattern of photosensitive material on ceramic base
- **Electrodes:** Metal electrodes at both ends
- **Package:** Encapsulated in transparent plastic or glass case

Working Principle:

- **Photoconductivity:** Based on photoconductivity principle
- **Dark Resistance:** High resistance ($M\Omega$ range) in dark conditions
- **Light Exposure:** When exposed to light, photons release electrons
- **Resistance Drop:** Resistance decreases ($k\Omega$ range) in bright light

Diagram:

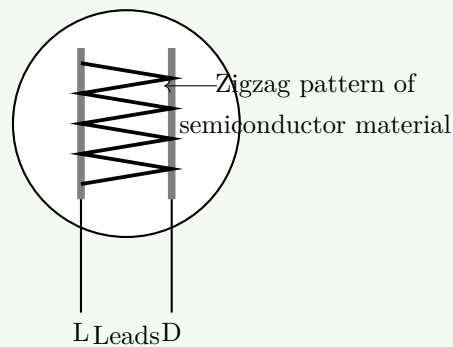


Figure 2. LDR Construction

Mnemonic

“MILD: ”More Illumination, Less Dark-resistance””

Question 1(c) [7 marks]

Explain the color band coding method of Resistor. Write color band of $47k\Omega \pm 5\%$ resistance.

Solution

Answer:

Color Band Coding Method:

Table 1. Resistor Color Code

| Color | Value | Multiplier | Tolerance |
|-----------|-------|------------|--------------|
| Black | 0 | 10^0 | - |
| Brown | 1 | 10^1 | $\pm 1\%$ |
| Red | 2 | 10^2 | $\pm 2\%$ |
| Orange | 3 | 10^3 | - |
| Yellow | 4 | 10^4 | - |
| Green | 5 | 10^5 | $\pm 0.5\%$ |
| Blue | 6 | 10^6 | $\pm 0.25\%$ |
| Violet | 7 | 10^7 | $\pm 0.1\%$ |
| Grey | 8 | 10^8 | $\pm 0.05\%$ |
| White | 9 | 10^9 | - |
| Gold | - | 10^{-1} | $\pm 5\%$ |
| Silver | - | 10^{-2} | $\pm 10\%$ |
| Colorless | - | - | $\pm 20\%$ |

4-Band Resistor Color Code:

- **First Band:** First significant digit
- **Second Band:** Second significant digit
- **Third Band:** Multiplier
- **Fourth Band:** Tolerance

For $47\text{k}\Omega \pm 5\%$:

- First digit: 4 = Yellow
- Second digit: 7 = Violet
- Multiplier: 10^3 = Orange (for k Ω)
- Tolerance: $\pm 5\%$ = Gold

Color bands for $47\text{k}\Omega \pm 5\%$: Yellow-Violet-Orange-Gold

Diagram:

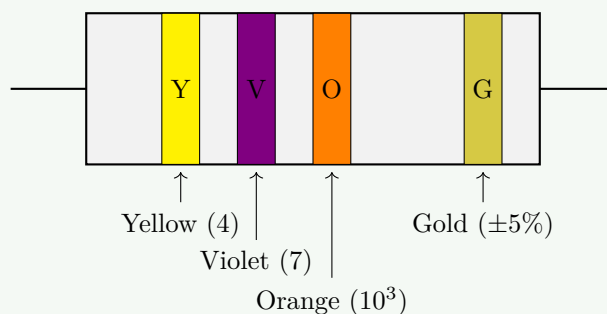


Figure 3. Resistor Color Bands: Yellow-Violet-Orange-Gold

Mnemonic

“BAND: ”Beginning digits, Amplify with Multiplier, Note tolerance with last band, Decode carefully”

Question 1(c OR) [7 marks]

Explain Aluminum Electrolytic wet type capacitor.

Solution**Answer:****Aluminum Electrolytic Wet Type Capacitor:****Construction:**


- **Plates:** Two aluminum foils (anode and cathode)
- **Dielectric:** Aluminum oxide layer on anode foil
- **Electrolyte:** Liquid electrolyte (boric acid, sodium borate, etc.)
- **Separator:** Paper separator soaked in electrolyte
- **Enclosure:** Aluminum can with rubber seal

Working Principle:

- **Oxide Layer:** Thin aluminum oxide layer acts as dielectric
- **Electrolyte:** Acts as cathode connection to second plate
- **Polarization:** Has defined polarity (+ and -) terminals

Characteristics:

- **Capacitance Range:** $1\mu\text{F}$ to $47,000\mu\text{F}$
- **Voltage Rating:** 6.3V to 450V
- **Polarity:** Polarized (must connect correctly)
- **Leakage Current:** Higher than other capacitor types
- **ESR:** Higher equivalent series resistance

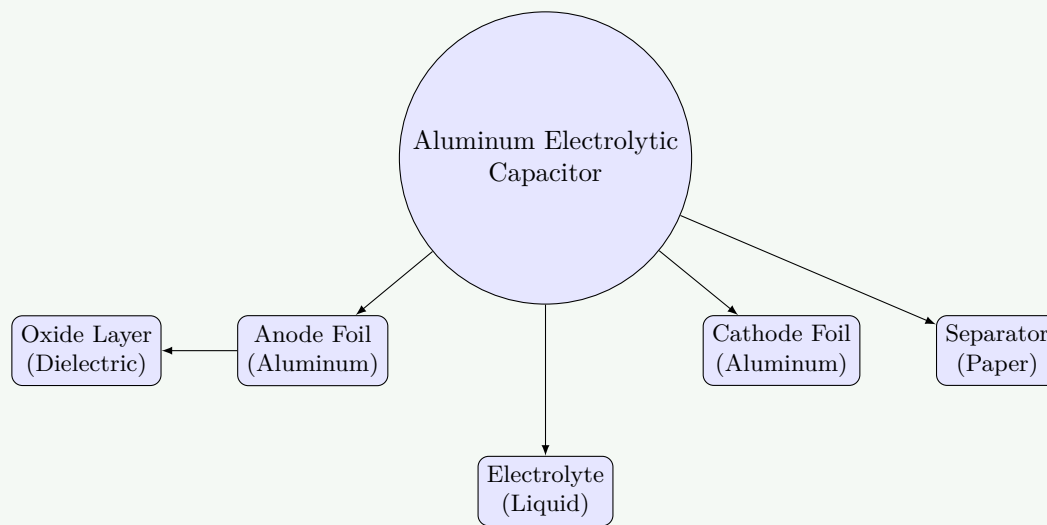Diagram:**Figure 4.** Aluminum Electrolytic Capacitor Components**Mnemonic**

“POLE: ”Polarized, Oxide layer, Liquid electrolyte, Enormous capacitance””

Question 2(a) [3 marks]

Draw the symbol of Schottkey diode, LED and Photo-diode.

Solution**Answer:****Symbols:**

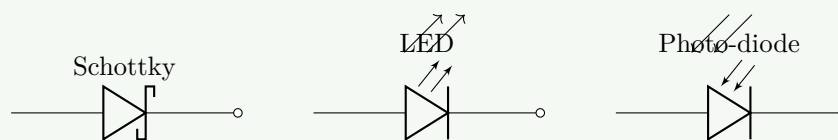


Figure 5. Symbols: Schottky Diode, LED, Photo-diode

Key Features:

- **Schottky Diode:** Standard diode symbol with curved bar (represents metal-semiconductor junction)
- **LED:** Standard diode symbol with two arrows pointing away (represents light emission)
- **Photo-diode:** Standard diode symbol with two arrows pointing toward diode (represents light detection)

Mnemonic

“SLP: ”Schottky has curve, LED emits, Photo-diode absorbs””

Question 2(b) [4 marks]

Define Active and Passive Components with example.

Solution

Answer:

Passive Components:

Table 2. Passive vs Active Components

| Characteristic | Description | Examples |
|---------------------------|------------------------------|--------------------------------------|
| Passive Components | | |
| Power | Cannot generate power | Resistors, Capacitors, Inductors |
| Signal | Cannot amplify signals | Transformers, Diodes |
| Control | No control over current flow | Connectors, Switches |
| Energy | Store or dissipate energy | Fuses, Filters |
| Active Components | | |
| Power | Can generate power | Transistors, ICs |
| Signal | Can amplify signals | Op-amps, Amplifiers |
| Control | Control current flow | SCRs, MOSFETs |
| Dependency | Require external power | Voltage regulators, Microcontrollers |

Diagram:

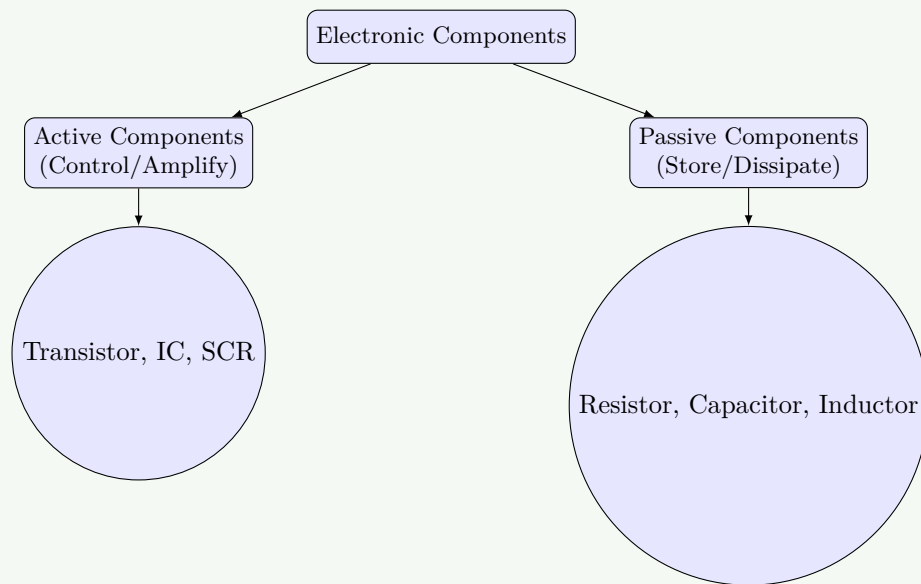


Figure 6. Classification of Electronic Components

Mnemonic

“PASS-ACT: ”Passive stores or dissipates, Active controls or amplifies””

Question 2(c) [7 marks]

Explain working of full wave bridge rectifier.

Solution

Answer:

Full Wave Bridge Rectifier:

Circuit Construction:

- **Diodes:** Four diodes arranged in bridge configuration
- **Input:** AC supply from transformer secondary
- **Output:** Pulsating DC across load resistor with filter capacitor

Working Principle:

- **Positive Half Cycle:** D1 and D3 conduct, D2 and D4 block
- **Negative Half Cycle:** D2 and D4 conduct, D1 and D3 block
- **Current Flow:** Always flows through load in same direction

Performance Parameters:

- **Ripple Frequency:** $2 \times$ input frequency (100 Hz for 50 Hz input)
- **Efficiency:** 81.2%
- **PIV:** $V_0(max)$ per diode
- **TUF:** 0.812 (Transformer Utilization Factor)

Diagram:

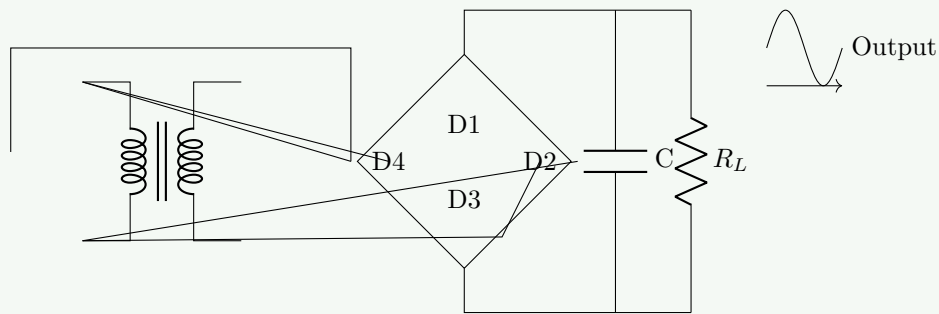


Figure 7. Full Wave Bridge Rectifier Circuit

Mnemonic

“BRIDGE: ”Better Rectification with Improved Diode Geometry Efficiency””

Question 2(a OR) [3 marks]

Explain construction and working of LED.

Solution

Answer:

Construction of LED:

- **Material:** Semiconductor (GaAs, GaP, AlGaInP, etc.)
- **Junction:** P-N junction with heavily doped semiconductors
- **Package:** Encased in transparent or colored epoxy lens
- **Cathode:** Identified by flat side on package or shorter lead

Working Principle:

- **Forward Bias:** Applied to P-N junction
- **Recombination:** Electrons and holes recombine at junction
- **Energy Release:** Energy released as photons (light)
- **Wavelength:** Determined by band gap of semiconductor material

Diagram:

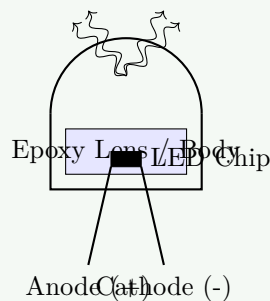


Figure 8. LED Construction

Mnemonic

“LEDS: ”Light Emits During electron-hole recombination in Semiconductor””

Question 2(b OR) [4 marks]

Explain composition type resistors.

Solution**Answer:****Composition Resistors:****Construction:**

- **Core Material:** Carbon particles mixed with insulating material (clay/ceramic)
- **Binding:** Resin binder forms solid cylindrical shape
- **Terminals:** Metal caps with leads attached to ends
- **Protection:** Coated with insulating paint or plastic

Characteristics:

- **Resistance Range:** 1Ω to $22M\Omega$
- **Power Rating:** $1/8W$ to $2W$
- **Tolerance:** $\pm 5\%$ to $\pm 20\%$
- **Temperature Coefficient:** -500 to $+500$ ppm/ $^{\circ}C$

Advantages & Limitations:

- **Cost:** Low cost
- **Noise:** Higher noise level
- **Stability:** Less stable with temperature
- **Applications:** General purpose, non-critical applications

Diagram:**Figure 9.** Carbon Composition Resistor Structure**Mnemonic**

"CCRI: "Carbon Composition Resistors are Inexpensive""

Question 2(c OR) [7 marks]

Explain working of full wave rectifier with two diodes.

Solution**Answer:****Full Wave Rectifier with Two Diodes (Center-tap):****Circuit Construction:**

- **Transformer:** Center-tapped transformer secondary
- **Diodes:** Two diodes connected to opposite ends of secondary
- **Output:** Taken between center tap and diode junction

Working Principle:

- **Positive Half Cycle:** Upper half of secondary positive, D1 conducts, D2 blocks
- **Negative Half Cycle:** Lower half of secondary positive, D2 conducts, D1 blocks
- **Current Flow:** Always flows through load in same direction

Performance Parameters:

- **Ripple Frequency:** $2 \times$ input frequency (100 Hz for 50 Hz input)
- **Efficiency:** 81.2%
- **PIV:** $2V_0(max)$ per diode (twice the center-tap rectifier)
- **TUF:** 0.693 (Transformer Utilization Factor)

Diagram:

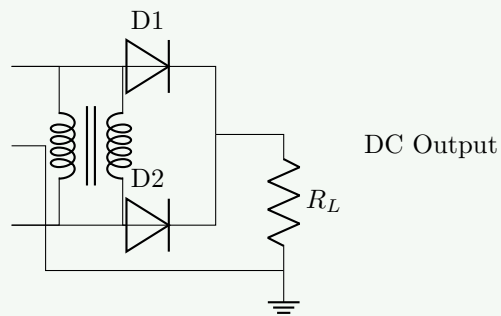


Figure 10. Center-Tap Full Wave Rectifier

Mnemonic

“CTFWR: ”Center Tap Facilitates Whole-cycle Rectification””

Question 3(a) [3 marks]

Explain working of schhotkey diode.

Solution

Answer:

Working of Schottky Diode:

- **Junction Type:** Metal-Semiconductor (M-S) junction instead of P-N
- **Charge Carriers:** Majority carrier device (electrons in N-type)
- **Barrier:** Schottky barrier formed at metal-semiconductor interface
- **Forward Voltage:** Lower forward voltage drop (0.2-0.4V vs 0.7V for Si diode)

Key Characteristics:

- **Switching Speed:** Very fast switching (no minority carrier storage)
- **Applications:** High-frequency circuits, power supplies
- **Recovery Time:** Negligible reverse recovery time

Diagram:

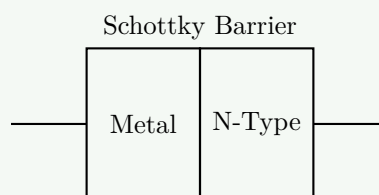


Figure 11. Schottky Structure

Mnemonic

“SFAM: ”Schottky’s Fast And Metal-based””

Question 3(b) [4 marks]


Explain N type semiconductor.

Solution**Answer:****N-type Semiconductor:****Formation:**

- **Base Material:** Intrinsic semiconductor (Silicon or Germanium)
- **Doping Element:** Pentavalent impurity (P, As, Sb)
- **Doping Process:** Thermal diffusion or ion implantation
- **Concentration:** Typically 1 part impurity to 10^8 parts silicon

Characteristics:

- **Majority Carriers:** Electrons (negative charge carriers)
- **Minority Carriers:** Holes
- **Conductivity:** Higher than intrinsic semiconductor
- **Fermi Level:** Closer to conduction band

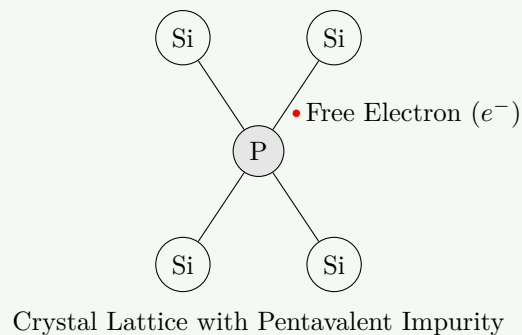Diagram:**Figure 12.** N-Type Doping**Mnemonic**

“PENT: ”Pentavalent Element makes N-Type with free electrons”

Question 3(c) [7 marks]

Explain construction and working of PN Junction Diode.

Solution**Answer:****Construction of PN Junction Diode:**

- **Materials:** P-type and N-type semiconductor regions
- **Junction:** Formed by diffusion or epitaxial growth
- **Depletion Region:** Forms at junction interface
- **Contacts:** Metal contacts attached to both regions
- **Packaging:** Sealed in glass, plastic, or metal case

Working Principle:

- **Depletion Region:** Forms due to diffusion of carriers
- **Barrier Potential:** Created across junction (0.7V for Si, 0.3V for Ge)
- **Forward Bias:** Current flows when forward voltage > barrier potential
- **Reverse Bias:** Only small leakage current flows until breakdown

Diagram:

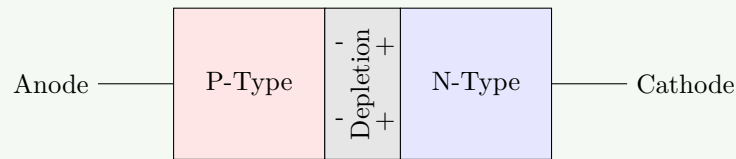


Figure 13. PN Junction Structure

Mnemonic

“BIRD: ”Barrier forms at Interface, Rectifies Direct current””

Question 3(a OR) [3 marks]

Explain working of photo diode.

Solution

Answer:

Working of Photo Diode:

- **Operation:** Always operated in reverse bias
- **Dark Current:** Small leakage current flows when no light incident (due to thermal generation)
- **Light Incidence:** When light falls on junction, energy breaks covalent bonds
- **Carrier Generation:** Electron-hole pairs generated in depletion region
- **Photocurrent:** Electric field sweeps carriers across junction, increasing reverse current
- **Proportionality:** Current increases linearly with light intensity

Diagram:

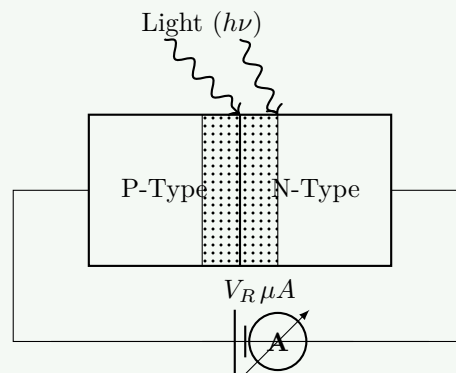


Figure 14. Photo Diode Operation

Mnemonic

“DARK: ”Dark current exists, Absorbs photons, Reverse bias, K-urrent increases””

Question 3(b OR) [4 marks]


Explain P type semiconductor.

Solution**Answer:****P-type Semiconductor:****Formation:**

- **Base Material:** Intrinsic semiconductor (Si or Ge)
- **Doping Element:** Trivalent impurity (Boron, Aluminum, Indium, Gallium)
- **Process:** Adding trivalent atoms creates vacancies (holes)

Characteristics:

- **Majority Carriers:** Holes (positive charge carriers)
- **Minority Carriers:** Electrons
- **Fermi Level:** Closer to valence band
- **Acceptor Ions:** Negative ions created when holes accept electrons

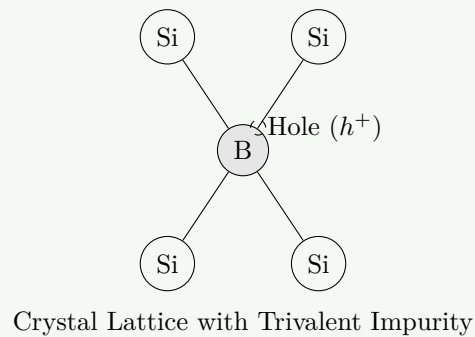Diagram:**Figure 15.** P-Type Doping**Mnemonic**

“TRIP: ”Trivalent Impurity produces Positive holes””

Question 3(c OR) [7 marks]

Compare half wave and full wave rectifier.

Solution**Answer:****Comparison of Rectifiers:****Table 3.** Rectifier Comparison

| Parameter | Half Wave | Full Wave (Center Tap) | Bridge Rectifier |
|----------------|--------------------|------------------------|---------------------------|
| No. of Diodes | 1 | 2 | 4 |
| Max Efficiency | 40.6% | 81.2% | 81.2% |
| Ripple Factor | 1.21 | 0.48 | 0.48 |
| Ripple Freq | f_{in} | $2f_{in}$ | $2f_{in}$ |
| PIV Rating | V_m | $2V_m$ | V_m |
| TUF | 0.287 | 0.693 | 0.812 |
| Output Voltage | $V_{dc} = V_m/\pi$ | $V_{dc} = 2V_m/\pi$ | $V_{dc} = 2V_m/\pi$ |
| Transformer | Simple | Center Tapped Required | Simple |
| Cost | Lowest | Medium | Highest (due to 4 diodes) |


Question 4(a) [3 marks]

Draw the symbol and construction of PNP and NPN transistor with proper labelling.


Solution

Answer:

Construction and Symbols:

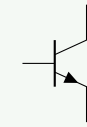

NPN Symbol

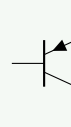

PNP Symbol

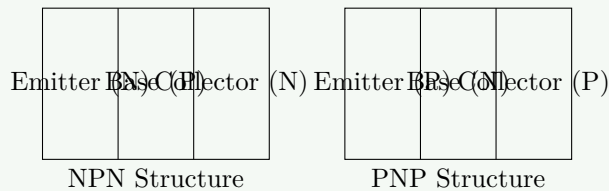


Figure 16. Transistor Symbols and Construction

Mnemonic

“P-POINT: ”PNP Points In, NPN Points Out”

Question 4(b) [4 marks]

Explain working of transistor amplifier.

Solution

Answer:

Transistor Amplifier Working:

- **Biasing:** Emitter-Base junction is forward biased, Collector-Base junction is reverse biased (Active Region)
- **Input:** Weak AC signal applied across Emitter-Base
- **Control:** Small variations in Base current (I_B) cause large variations in Collector current (I_C)
- **Gain:** Current Gain $\beta = \Delta I_C / \Delta I_B$ is typically large (50-300)
- **Output:** Amplified voltage developed across load resistor connected in collector circuit
- **Process:** I_E electrons injected into Base, most cross to Collector (due to reverse bias attraction), forming I_C

Diagram:

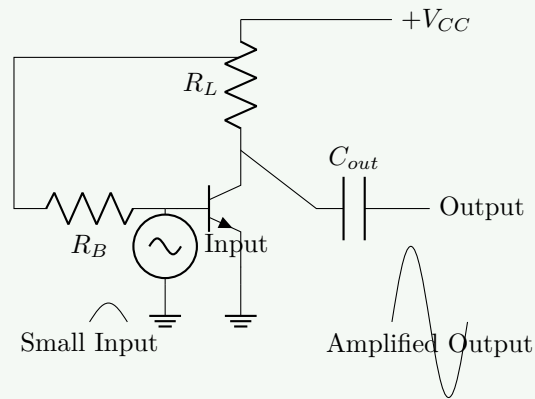


Figure 17. Common Emitter Amplifier Concept

Question 4(c) [7 marks]

Explain working of Zener diode.

Solution

Answer:

Zener Diode:

Construction:

- Heavily doped P-N junction diode
- Designed to operate in reverse breakdown region

Working Principle:

- **Forward Bias:** Acts like normal diode
- **Reverse Bias:** Blocks current up to breakdown voltage (V_Z)
- **Breakdown:** At V_Z , sharp increase in current occurs due to Zener effect (quantum tunneling) or Avalanche effect
- **Voltage Regulation:** Voltage across diode remains constant (V_Z) despite large changes in current

Applications:

- Voltage Regulator
- Reference voltage source
- Over-voltage protection

Characteristics Diagram:

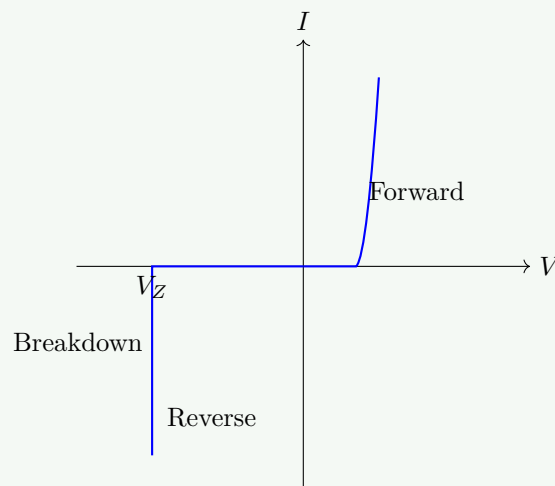


Figure 18. Zener V-I Characteristics

Mnemonic

“ZAP: ”Zener Always Provides constant voltage””

Question 4(a OR) [3 marks]

Explain transistor as a switch.

Solution

Answer:

Transistor as Switch: Operates in Cut-off and Saturation regions.

- **OFF State (Open Switch):**
 - Base current $I_B = 0$
 - Operates in **Cut-off Region**
 - Collector current $I_C \approx 0$
 - Output voltage $V_{CE} = V_{CC}$
- **ON State (Closed Switch):**
 - Sufficient Base current supplied
 - Operates in **Saturation Region**
 - Maximum Collector current flows (I_{sat})
 - Output voltage $V_{CE} \approx 0.2V$ (Saturation voltage)

Diagram:

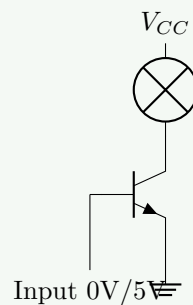


Figure 19. Transistor Switch Circuit

Mnemonic

“CO-SI: ”Cut-off is Open, Saturation is Closed””

Question 4(b OR) [4 marks]

Draw and explain characteristics of CE amplifier.

Solution

Answer:

Common Emitter Characteristics:

1. **Input Characteristics** (I_B vs V_{BE} at constant V_{CE}):
 - Resembles forward biased diode characteristic
 - Beyond knee voltage (0.7V for Si), I_B increases rapidly with small increase in V_{BE}
 - Increasing V_{CE} shifts curve slightly to right (Early effect - ignoring for basic explanation)
2. **Output Characteristics** (I_C vs V_{CE} at constant I_B):
 - **Cut-off Region:** $I_B = 0$, $I_C \approx 0$. Transistor OFF.

- **Active Region:** I_C is constant for given I_B , almost independent of V_{CE} . Used for amplification. Linear region.
- **Saturation Region:** V_{CE} is very low ($< 0.2V$). I_C increases rapidly with V_{CE} . Transistor ON.

Diagram:

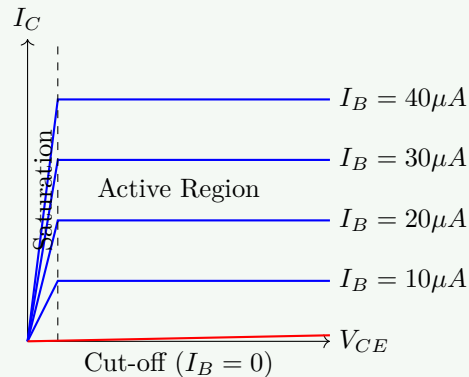


Figure 20. CE Output Characteristics

Question 4(c OR) [7 marks]

Explain working of varactor diode.

Solution

Answer:

Working of Varactor Diode:

- **Function:** Acts as a voltage-controlled variable capacitor
- **Operation:** Always operated in reverse bias
- **Principle:**
 - Reverse bias voltage increases width of depletion region
 - Depletion region acts as dielectric between P and N regions (acting as plates)
 - Capacitance $C = \epsilon A/d$ (where d is depletion width)
 - As Reverse Voltage (V_R) increases \rightarrow Width (d) increases \rightarrow Capacitance (C) decreases
- **Relationship:** $C_T \propto \frac{1}{\sqrt{V_R}}$
- **Application:** Tuning circuits (Radio/TV tuners), VCOs (Voltage Controlled Oscillators)

Diagram:

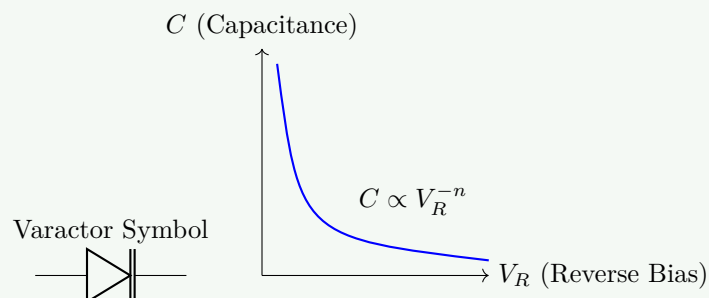


Figure 21. Varactor Diode Characteristics

Mnemonic

“VARY: ”Voltage Adjusts Reverse-bias Yielding capacitance””

Question 5(a) [3 marks]

Define Active, Saturation and Cut-Off region for transistor amplifier.

Solution

Answer:

- **Active Region:**
 - Emitter-Base junction: Forward Biased
 - Collector-Base junction: Reverse Biased
 - Use: Amplification
- **Saturation Region:**
 - Emitter-Base junction: Forward Biased
 - Collector-Base junction: Forward Biased
 - Use: ON Switch (Closed)
- **Cut-Off Region:**
 - Emitter-Base junction: Reverse Biased
 - Collector-Base junction: Reverse Biased
 - Use: OFF Switch (Open)

Question 5(b) [4 marks]

Check current gain α and β if $I_c = 10mA$ and $I_b = 100\mu A$.

Solution

Answer:

Given:

- $I_C = 10mA$
- $I_B = 100\mu A = 0.1mA$

Calculations:

1. Calculate β :

$$\beta = \frac{I_C}{I_B} = \frac{10mA}{0.1mA} = 100$$

2. Calculate Emitter Current I_E :

$$I_E = I_C + I_B = 10mA + 0.1mA = 10.1mA$$

3. Calculate α :

$$\alpha = \frac{I_C}{I_E} = \frac{10mA}{10.1mA} \approx 0.9901$$

Alternatively using relation:

$$\alpha = \frac{\beta}{1 + \beta} = \frac{100}{101} \approx 0.9901$$

Result:

- $\beta = 100$
- $\alpha = 0.99$

Question 5(c) [7 marks]

Discuss strategies for Electronic Waste management in small electronic industries.

Solution

Answer:

E-Waste Management Strategies:

1. **Inventory Management:** Keep track of all electronic equipment and lifespan to plan replacements efficiently.
2. **Reduce:** Minimize purchase of unnecessary equipment. Opt for upgradable modular devices instead of replacing entire units.
3. **Reuse:** refurbish old electronics for less demanding tasks (e.g., using older PCs for data entry or print servers).
4. **Recycle:** Partner with certified e-waste recyclers who safely extract valuable metals (Au, Ag, Cu) and dispose of hazardous materials (Pb, Hg).
5. **Segregation:** Set up separate bins for e-waste (batteries, cables, circuit boards) to prevent mixing with general waste.
6. **EPR Compliance:** Adhere to Extended Producer Responsibility (EPR) guidelines if involved in manufacturing.
7. **Employee Training:** Educate staff about proper disposal methods and data wiping before disposal.

Diagram:

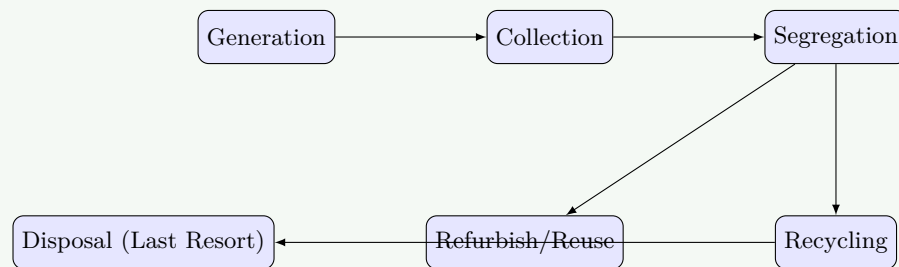


Figure 22. E-Waste Flow

Mnemonic

“3R: ”Reduce, Reuse, Recycle””

Question 5(a OR) [3 marks]

Draw circuit configuration of CB, CE and CC transistor.

Solution

Answer:

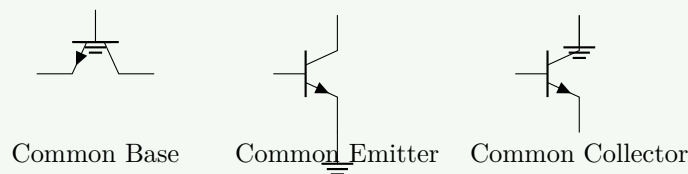


Figure 23. Transistor Configurations

Question 5(b OR) [4 marks]

Derive the relation between current gain α and β .

Solution**Answer:****Derivation:**

1. We know transistor currents:

$$I_E = I_C + I_B$$

2. Divide entire equation by I_C :

$$\frac{I_E}{I_C} = \frac{I_C}{I_C} + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

(Because $\alpha = I_C/I_E$ and $\beta = I_C/I_B$)3. Solve for α :

$$\frac{1}{\alpha} = \frac{\beta + 1}{\beta}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

4. Solve for β :

$$\frac{1}{\beta} = \frac{1}{\alpha} - 1 = \frac{1 - \alpha}{\alpha}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Conclusion:

$$\alpha = \frac{\beta}{1 + \beta}, \quad \beta = \frac{\alpha}{1 - \alpha}$$

Question 5(c OR) [7 marks]**Define E-waste and explain disposal of Electronic waste.****Solution****Answer:****Definition: E-Waste (Electronic Waste)** refers to discarded electrical or electronic devices such as computers, phones, printers, and appliances that have reached the end of their useful life.**Disposal Methods:**

1. **Landfilling:** Dumping waste in trenches. Least preferred method as toxic substances (Lead, Cadmium) leach into soil and groundwater.
2. **Incineration:** Controlled burning of waste. reduces volume but can release toxic gases into atmosphere if not filtered properly.
3. **Acid Bath:** Soaking circuits in acid to extract gold. Highly hazardous to workers and environment.
4. **Mechanical Recycling (Preferred):**
 - Shredding: Breaking devices into small pieces.
 - Separation: Using magnets and eddy currents to separate metals from plastic.
 - Recovery: Smelting metals for reuse.
5. **Reuse/Refurbishing:** Extending life by repairing. Best for environment.

Pyramid of E-Waste:

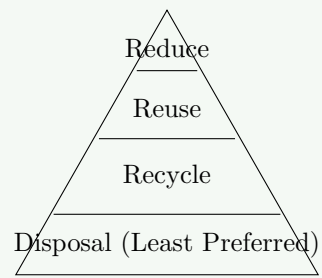


Figure 24. Waste Management Hierarchy