

Fundamentals of Electronics

DI01000051 – Winter 2024

Semester 1 Study Material

Detailed Solutions and Explanations

Question 1(a) [3 marks]

Define Active and Passive Components with example.

Solution

Table: Active vs Passive Components

| Type | Definition | Examples |
|---------|---|-------------------------------|
| Active | Components that can amplify signals and control current flow. Can provide power gain. | Transistor, Diode, IC, SCR |
| Passive | Components that cannot amplify signals. Consumes, stores, or releases energy. | Resistor, Capacitor, Inductor |

Key Difference: Active components require an external power source to operate; passive components do not.

Mnemonic

“Active Amplifies, Passive Preserves”

Question 1(b) [4 marks]


Explain construction and working of LDR.

Solution

Construction:

- Made of high resistance semiconductor material like Cadmium Sulfide (CdS).
- Material is deposited as a zig-zag (serpentine) track on a ceramic substrate to maximize length and reduce area.
- Encased in plastic/resin with a clear window.

Diagram:

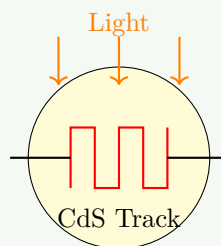

Working Principle (Photo-conductivity):

1. **Dark:** High Resistance ($M\Omega$ range). Few free carriers.
2. **Light:** Light energy breaks bonds, creating electron-hole pairs.
3. Conductivity increases \rightarrow Resistance decreases ($k\Omega$ range).

Mnemonic

“Light Low Resistance”

Question 1(c) [7 marks]

Define Capacitance and explain Aluminum Electrolytic wet type capacitor.

Solution


Capacitance: The ability of a system to store an electric charge. $C = Q/V$ (Unit: Farad).

Aluminum Electrolytic Capacitor:

- **Construction:**

- **Anode (+):** Pure aluminum foil with a thin oxide layer (Al_2O_3) acting as dielectric.
- **Cathode (-):** Second aluminum foil in contact with electrolyte.
- **Electrolyte:** Conductive liquid/gel soaked paper separator.

Diagram:

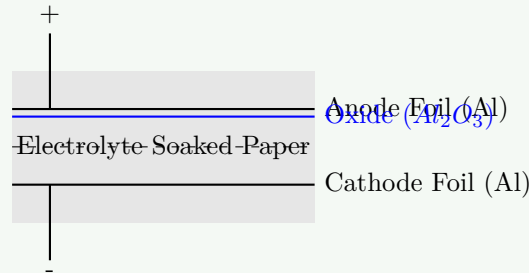

Features: High capacitance density, Polarized (must connect correctly), used in power supply filtering.

Mnemonic

“Aluminum Always Amplifies (Capacitance)”

Question 1(c OR) [7 marks]

Explain the color band coding method of Resistor. Write color band of $32\Omega \pm 10\%$ resistance.

Solution

Color Code Table:

| Color | Digit | Multiplier | Tolerance |
|--------|-------|------------|-----------|
| Black | 0 | 10^0 | - |
| Brown | 1 | 10^1 | 1% |
| Red | 2 | 10^2 | 2% |
| Orange | 3 | 10^3 | - |
| Yellow | 4 | 10^4 | - |
| Green | 5 | 10^5 | 0.5% |
| Blue | 6 | 10^6 | 0.25% |
| Violet | 7 | 10^7 | 0.1% |
| Gray | 8 | 10^8 | 0.05% |
| White | 9 | 10^9 | - |
| Gold | - | 0.1 | 5% |
| Silver | - | 0.01 | 10% |

Calculation for $32\Omega \pm 10\%$:

- Value: $32 = 32 \times 10^0$ or better 32×1 .
- Wait, standard bands usually form digit, digit, multiplier.
- $32\Omega = 3$ (Orange), 2 (Red) $\times 1$ (Black)? No, 32×1 .
- Actually, for low values, gold/silver multipliers are used often. But 32 fits standard:
- 1st Digit: 3 \rightarrow **Orange**
- 2nd Digit: 2 \rightarrow **Red**
- Multiplier: $10^0 = 1 \rightarrow$ **Black**
- Tolerance: $\pm 10\% \rightarrow$ **Silver**
- Bands: **Orange - Red - Black - Silver**

Note: The provided MDX used Gold/Silver multiplier example (3, 2, 0.1). $32 \times 0.1 = 3.2\Omega$. For 32Ω , it should be Black (x1). Let's stick to standard calculation: 3, 2, $\times 10^0$.

Mnemonic

“BBROYGBVGW” (Black Brown Red Orange Yellow Green Blue Violet Gray White)

Question 2(a) [3 marks]

Define following terms: 1) Rectifier 2) Ripple factor 3) Filter

Solution

1. **Rectifier:** An electronic circuit that converts alternating current (AC) into pulsating direct current (DC).
2. **Ripple Factor:** The ratio of the RMS value of the AC component to the DC component in the rectifier output. $\gamma = V_{ac,rms}/V_{dc}$. Low is better.
3. **Filter:** A circuit used to remove AC components (ripples) from the pulsating DC output of a rectifier to produce smooth DC.

Mnemonic


“Rectify Ripples, Filter Fixes”

Question 2(b) [4 marks]

Draw and explain positive clipper circuit with waveform.

Solution


Circuit Diagram:

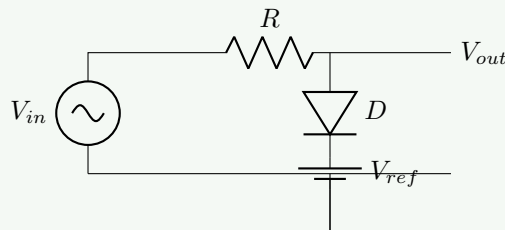

Working:

- When $V_{in} < V_{ref} + 0.7V$, diode is reverse biased (OPEN). $V_{out} = V_{in}$.
- When $V_{in} > V_{ref} + 0.7V$, diode is forward biased (SHORT). V_{out} is clipped at V_{ref} (ignoring diode drop).

Waveform:

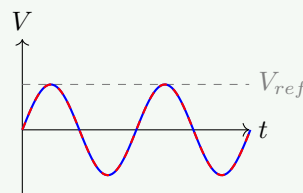


Question 2(c) [7 marks]

Explain working of full wave rectifier with two diodes.

Solution

Center-Tapped Full Wave Rectifier:

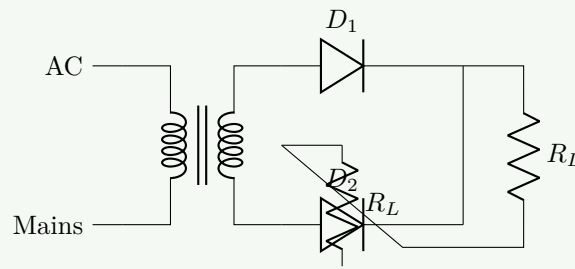

(Simplified drawing description for mental model: Center tap is ground reference. D_1 and D_2 feed R_L).

Working:

- **Positive Half Cycle:** Top of secondary positive. D_1 conducts, D_2 off. Current flows through R_L .
- **Negative Half Cycle:** Bottom of secondary positive. D_2 conducts, D_1 off. Current flows through R_L in same direction.

Result: Output is unidirectional pulsating DC with frequency $2f$. Efficiency $\eta = 81.2\%$.

Question 2(a OR) [3 marks]

Define rectifier and write its applications.

Solution

Definition: Device converting AC to DC.


Applications:

- DC Power supplies for electronic devices (TV, Computers).
- Battery Charging circuits.
- DC Motor drives.
- Detection of radio signals (demodulation).

Question 2(b OR) [4 marks]

Explain working of Pi(π) type capacitor filter.

Solution

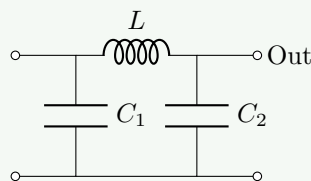

Working:

- C_1 : Bypasses most AC ripples to ground (low reactance to AC).
- L : Blocks AC components (high reactance) while passing DC.
- C_2 : Bypasses any remaining AC ripples.
- Result: Very smooth DC output. Known as CLC filter.

Question 2(c OR) [7 marks]

Compare half wave and full wave bridge rectifier.


Solution

| Parameter | Half Wave | Bridge Rectifier |
|---------------|-----------|------------------------------|
| No. of Diodes | 1 | 4 |
| Transformer | Basic | Basic (No center tap needed) |
| Efficiency | 40.6% | 81.2% |
| Ripple Factor | 1.21 | 0.48 |
| PIV Rating | V_m | V_m |
| Fout | f_{in} | $2f_{in}$ |

Question 3(a) [3 marks]

Draw the symbols of following: 1) Zener diode 2) LED 3) Varactor diode

Solution

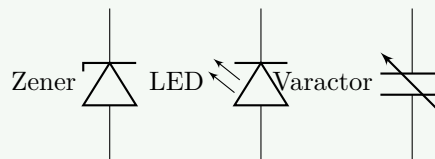

Note: Varactor symbol is a diode combined with a capacitor.

Question 3(b) [4 marks]

Explain construction and working of LED.

Solution

Construction: PN junction made from compound semiconductors (GaAs, GaP) instead of Si/Ge. Transparent casing.

Working:


- Operates in **Forward Bias**.
- Electrons from N-side recombine with holes in P-side.
- Energy released during recombination is emitted as photons (Light).
- Color depends on band gap energy of material.

Question 3(c) [7 marks]

Explain working characteristics of Zener diode.

Solution

V-I Characteristics:

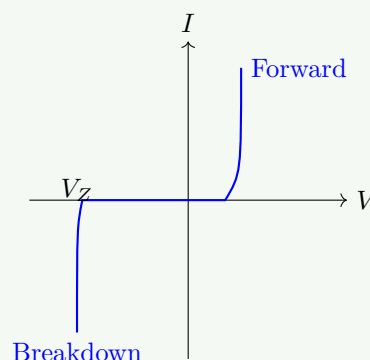

Regions:

- **Forward:** Acts like normal diode.
- **Reverse:** Blocks current until breakdown voltage V_Z .
- **Breakdown:** Current increases sharply while voltage remains constant at V_Z . This property is used for voltage regulation.

Question 3(a OR) [3 marks]

Enlist the applications of varactor diode.

Solution

- FM Radio transmitters (Modulation).
- TV Receivers (Electronic Tuning).
- Voltage Controlled Oscillators (VCOs).
- Adjustable Bandpass Filters.

Principle: Acts as a voltage-variable capacitor in reverse bias.

Question 3(b OR) [4 marks]

Explain working of photo diode.

Solution

Working:


- Operates in **Reverse Bias**.
- When light falls on junction, energy breaks bonds creating electron-hole pairs.
- These carriers are swept by electric field, creating a **Reverse Current**.
- Current is proportional to Light Intensity.

Question 3(c OR) [7 marks]

Explain Zener diode as a voltage regulator.

Solution

Circuit:

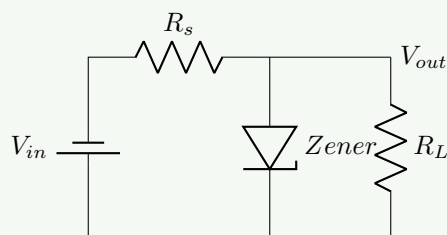

Operation:

- Zener connected in parallel with load, in reverse breakdown mode.
- If V_{in} increases, Zener current I_z increases, increasing drop across R_s , keeping V_{out} ($= V_z$) constant.
- If I_L changes, I_z adjusts to keep total current and drop across R_s such that V_{out} remains stable.

Question 4(a) [3 marks]

Draw the symbol and construction of PNP and NPN transistor with proper notation.

Solution



Construction:

- **NPN:** P-type base sandwiched between N-type collector/emitter.
- **PNP:** N-type base sandwiched between P-type collector/emitter.

Question 4(b) [4 marks]

Draw and Explain characteristics of CE amplifier.

Solution

Characteristics:

1. **Input:** I_B vs V_{BE} (constant V_{CE}). Looks like Forward Diode curve.
2. **Output:** I_C vs V_{CE} (constant I_B). Similar to FET curves but controlled by I_B .
 - **Active:** I_C constant for given I_B .
 - **Saturation:** V_{CE} very low, I_C rises fast.
 - **Cutoff:** $I_B = 0, I_C = 0$.

Question 4(c) [7 marks]

Derive relation between current gains α , β and γ .

Solution

Defs: $\alpha = I_C/I_E$, $\beta = I_C/I_B$, $\gamma = I_E/I_B$. We know $I_E = I_B + I_C$.

1. **β vs α :** Divide by I_C : $I_E/I_C = I_B/I_C + 1$ $1/\alpha = 1/\beta + 1 \Rightarrow 1/\alpha = (1 + \beta)/\beta$ $\alpha = \beta/(1 + \beta)$ OR $\beta = \alpha/(1 - \alpha)$.
2. **γ vs α :** $I_E = I_B + I_C \Rightarrow I_E = I_B + \alpha I_E$ $I_E(1 - \alpha) = I_B \Rightarrow I_E/I_B = 1/(1 - \alpha)$ $\gamma = 1/(1 - \alpha)$.
3. **γ vs β :** $\gamma = 1 + \beta$ (since $\gamma = I_E/I_B = (I_C + I_B)/I_B = \beta + 1$).

Question 4(a OR) [3 marks]

Define Active, Saturation and Cut-off region for transistor amplifier.

Solution

Operating Regions:

| Region | Base-Emitter | Base-Collector | State |
|-------------------|--------------|----------------|---------------|
| Active | Forward | Reverse | Amplification |
| Saturation | Forward | Forward | Switch ON |
| Cut-off | Reverse | Reverse | Switch OFF |

Question 4(b OR) [4 marks]

Explain working of Transistor as an amplifier.

Solution

Working Principle:

1. Transistor biased in **Active Region**.

2. Small AC signal applied to Base-Emitter (Low resistance).
3. Small change in Base connection causes Large change in Collector current ($I_C = \beta I_B$).
4. Output taken across high load resistance at Collector.
5. **Result:** Large amplified voltage/power at output.

Question 4(c OR) [7 marks]

Compare CB, CC, and CE amplifier configuration.


Solution

| Parameter | Common Base | Common Emitter | Common Collector |
|------------------|--------------------|-------------------|-------------------|
| In/Out | Emitter/Collector | Base/Collector | Base/Emitter |
| Input R_{in} | Very Low | Medium | Very High |
| Output R_{out} | Very High | Medium | Very Low |
| Current Gain | < 1 (α) | High (β) | High (γ) |
| Voltage Gain | High | High | ≈ 1 |
| Phase Shift | 0° | 180° | 0° |
| Application | RF, HF Apps | Audio/Voltage Amp | Buffer/Matching |

Question 5(a) [3 marks]

Draw the pin diagram of IC 555.

Solution

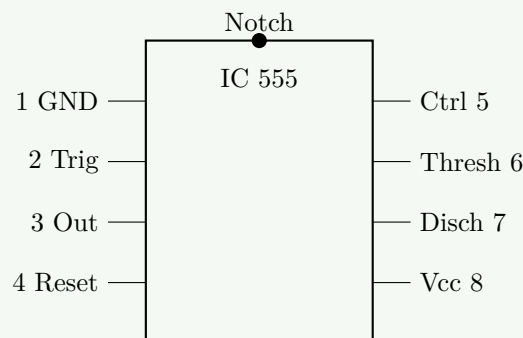

Question 5(b) [4 marks]

List out Features of 555 Timer IC.

Solution

- **Supply Voltage:** 5V to 18V DC.
- **Current Capability:** Can sink or source up to 200 mA.
- **Timing:** Microseconds to Hours.
- **Modes:** Monostable (One-shot) and Astable (Oscillator).
- **Stability:** High temperature stability ($\approx 0.005\%/^\circ\text{C}$).
- **Compatibility:** TTL and CMOS compatible.

Question 5(c) [7 marks]

Explain Mono stable multivibrator using 555 timer IC.

Solution

Circuit: Resistor R and Capacitor C connected. Pin 6 & 7 shorted and connected to RC junction. Trigger at Pin 2.

Working:

- Stable state: Output Low.
- Trigger (neg pulse) at pin 2 sets Flip-Flop. Output High. Discharge transistor OFF.
- Capacitor C charges via R .
- When V_c reaches $2/3V_{cc}$, threshold comparator resets Flip-Flop.
- Output Low. Capacitor discharges.
- **Pulse Width:** $T = 1.1RC$.

Question 5(a OR) [3 marks]

List out applications of IC 555.

Solution

1. **Timers:** Delay circuits, precision timing.
2. **Pulse Generation:** Square wave generation, PWM.
3. **Oscillators:** Tone generators, clocks.
4. **Others:** Missing pulse detector, Frequency divider, Traffic light controller.

Question 5(b OR) [4 marks]

Draw and explain the internal block diagram of IC 555.

Solution

Blocks:

- Voltage Divider (5k-5k-5k): Sets $1/3$ and $2/3 V_{cc}$.
- Comparators (2): Check Trigger and Threshold.
- SR Flip-Flop: Stores state.
- Discharge Transistor: Discharges timing cap.
- Output Driver: High current output.

Question 5(c OR) [7 marks]

Explain astable multivibrator using 555 timer IC.

Solution

Circuit: Pins 2 & 6 shorted. Resistors R_A, R_B and Capacitor C . **Working:**

- Charge: Through $R_A + R_B$. Time $t_{high} = 0.693(R_A + R_B)C$.
- Discharge: Through R_B . Time $t_{low} = 0.693R_B C$.
- Output oscillates between High and Low (Square wave).
- **Frequency:** $f = 1.44/((R_A + 2R_B)C)$.