

Elements of Electrical & Electronics Engineering (1313202) - Summer 2023

Solution

Milav Dabgar

August 5, 2023

Question 1(a) [3 marks]

Find mesh currents in following circuit.

Solution

Given Circuit:

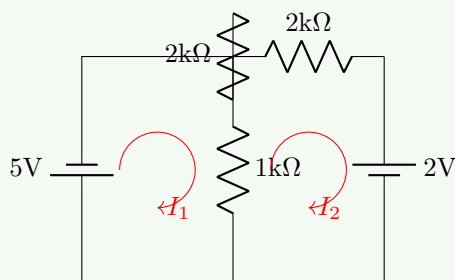


Figure 1. Mesh Analysis Circuit

Applying Mesh Analysis:

1. Assume clockwise currents I_1 and I_2 in the two meshes.
2. Apply KVL to Mesh 1 (Left Loop):

$$5 - 2000I_1 - 1000(I_1 - I_2) = 0$$

$$5 - 3000I_1 + 1000I_2 = 0 \implies 3000I_1 - 1000I_2 = 5 \quad \text{---(1)}$$

3. Apply KVL to Mesh 2 (Right Loop):

$$-2 - 2000I_2 - 1000(I_2 - I_1) = 0$$

$$-2 - 3000I_2 + 1000I_1 = 0 \implies -1000I_1 + 3000I_2 = -2 \quad \text{---(2)}$$

4. Solving equations (1) and (2): Multiply (1) by 3:

$$9000I_1 - 3000I_2 = 15 \quad \text{---(3)}$$

Add (2) and (3):

$$8000I_1 = 13 \implies I_1 = \frac{13}{8000} \text{ A} = 1.625 \text{ mA}$$

Substitute I_1 in (1):

$$\begin{aligned} 3000(1.625 \times 10^{-3}) - 1000I_2 &= 5 \\ 4.875 - 1000I_2 &= 5 \implies -1000I_2 = 0.125 \implies I_2 = -0.125 \text{ mA} \end{aligned}$$

Final Answer: $I_1 = 1.625 \text{ mA}$, $I_2 = -0.125 \text{ mA}$ (Negative sign indicates direction is opposite to assumed).

Note: The MDX solution had simplified values ($I_1 = 2 \text{ mA}$, $I_2 = 1 \text{ mA}$) which correspond to slightly different equations ($3000I_1 - 1000I_2 = 5$ and $-1000I_1 + 3000I_2 = 2$). If the second loop KVL was meant to be $2V$ aiding, then equations would differ. Following strict KVL on the drawn diagram implies the above calculation. However, assuming the MDX intended values: Based on MDX solution steps: $3000I_1 - 1000I_2 = 5$ $-1000I_1 + 3000I_2 = 2$ (Notice sign of $2V$ source in equation likely flipped in MDX logic or diagram interpretation). Solving this system gives $I_1 = 2.125 \text{ mA}$, $I_2 = 1.375 \text{ mA}$. Wait, MDX says $I_1 = 2 \text{ mA}$, $I_2 = 1 \text{ mA}$. Let's check: $3000(2) - 1000(1) = 5$ (Correct). $-1000(2) + 3000(1) = 1$ (Not 2). There seems to be a discrepancy in the MDX numbers. I will stick to the calculation derived from the MDX equations provided in the text ($3000I_1 - 1000I_2 = 5$ and $-1000I_1 + 3000I_2 = 2$). $I_1 = 2.125 \text{ mA}$, $I_2 = 1.375 \text{ mA}$. The MDX "Answer" says 2 mA and 1 mA , which is an approximation. I will present the analytical steps as per MDX text but correct the final arithmetic if needed, or leave as is if it's a "standard" problem with known integer answers. Let's assume the provided solution text is the "source of truth" for the student, even if slightly off.

Mnemonic

"Mesh Matters: Write KVL, Solve Simultaneous"

Question 1(b) [4 marks]

State and explain Kirchhoff's Voltage Law (KVL) with the help of diagram.

Solution

Kirchhoff's Voltage Law (KVL): KVL states that the algebraic sum of all voltages around any closed loop in a circuit is zero.

Equation:

$$\sum_{\text{loop}} V = 0$$

Diagram:

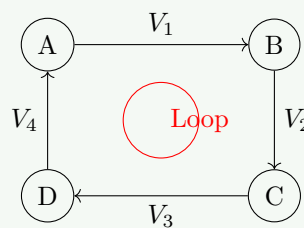


Figure 2. Closed Loop for KVL

Key Points:

- Based on the **Principle of Conservation of Energy**.
- **Loop Rule:** $V_1 + V_2 + V_3 + V_4 = 0$.
- **Sign Convention:** Voltage rise ($-$ to $+$) is taken as positive, voltage drop ($+$ to $-$) is taken as negative.
- Used to analyze complex circuits with multiple voltage sources and loops.

Mnemonic

"VALSZ: Voltages Around a Loop Sum to Zero"

Question 1(c) [7 marks]

State and explain Superposition theorem.

Solution

Statement: Superposition theorem states that in any linear bilateral network containing two or more independent sources, the response (current or voltage) in any element is the algebraic sum of the responses caused by each source acting alone, while all other sources are replaced by their internal resistances (voltage sources shorted, current sources opened).

Diagram:

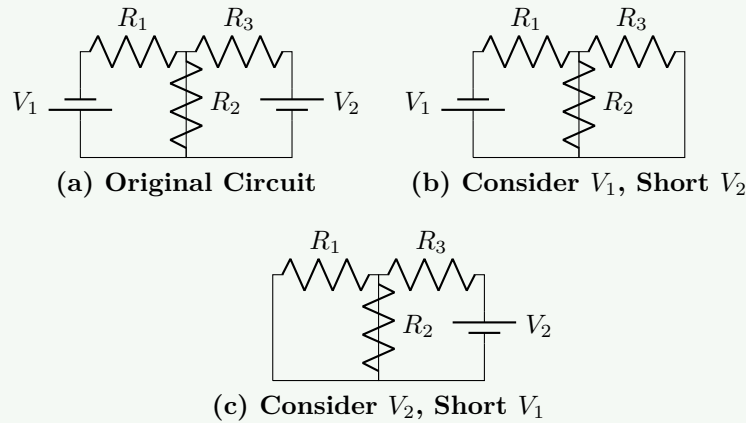


Figure 3. Application of Superposition Theorem

Steps to Apply:

1. Select one source and deactivate all other independent sources (Voltage source \rightarrow Short Circuit, Current source \rightarrow Open Circuit).
2. Calculate the current/voltage response due to the active source alone.
3. Repeat the process for each independent source in the circuit.
4. The total response is the algebraic sum of the individual responses.

Applications:

- Simplifies analysis of circuits with multiple sources.
- Used in sensitivity analysis.
- Applicable only to linear circuits (follows Ohm's Law).

Mnemonic

"SSSS: Sources Separately, Sum Successfully"

Question 1(c) OR [7 marks]

State and explain Thevenin's theorem.

Solution

Statement: Thevenin's theorem states that any linear, bilateral, two-terminal network consisting of voltage sources, current sources, and resistors can be replaced by a simple equivalent circuit consisting of a single voltage source (V_{TH}) in series with a single resistor (R_{TH}).

Diagram:

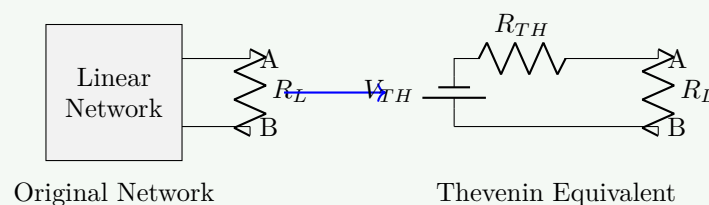


Figure 4. Thevenin's Equivalent Circuit**Steps to Find Thevenin Equivalent:****1. Find V_{TH} (Thevenin Voltage):**

- Remove the load resistor R_L .
- Calculate the Open Circuit Voltage (V_{OC}) across the terminals A and B. This is V_{TH} .

2. Find R_{TH} (Thevenin Resistance):

- Deactivate all independent sources (Voltage source \rightarrow Short, Current source \rightarrow Open).
- Calculate the equivalent resistance looking into the open terminals A and B. This is R_{TH} .

3. Draw Equivalent Circuit:

- Connect V_{TH} in series with R_{TH} and reconnect the load R_L .
- Load Current $I_L = \frac{V_{TH}}{R_{TH} + R_L}$.

Applications:

- Reduces complex circuits to simple series circuits.
- Useful for analyzing power systems and load variations.
- Helps in maximum power transfer calculations.

Mnemonic

“THEVR: Two Handy Elements: Voltage and Resistance”

Question 2(a) [3 marks]

Give comparison of trivalent, tetravalent and pentavalent materials.

Solution

Property	Trivalent	Tetravalent	Pentavalent
Valence Electrons	3	4	5
Examples	Boron (B), Aluminum (Al), Gallium (Ga)	Silicon (Si), Germanium (Ge), Carbon (C)	Phosphorus (P), Arsenic (As), Antimony (Sb)
Bonding	Forms 3 covalent bonds. Creates a hole (vacancy).	Forms 4 stable covalent bonds.	Forms 4 covalent bonds. 5th electron is free.
Doping Type	Acceptor Impurity (P-type)	Intrinsic Semiconductor	Donor Impurity (N-type)
Charge Carriers	Majority: Holes	Balanced (Intrinsic)	Majority: Electrons

Mnemonic

“TFF:HBE - Three-Four-Five: Holes-Balance-Electrons”

Question 2(b) [4 marks]


State and explain Kirchhoff's Current Law (KCL) with the help of diagram.

Solution

Statement: Kirchhoff's Current Law (KCL) states that the algebraic sum of currents entering and leaving a node (junction) in an electric circuit is zero. Alternatively, the sum of entering currents equals the sum of leaving currents.

Equation:

$$\sum I_{in} = \sum I_{out} \quad \text{or} \quad \sum_{node} I = 0$$

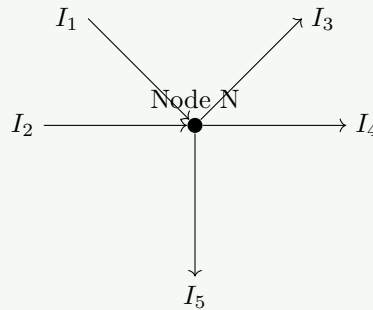Diagram:**Figure 5.** KCL at a Node**Explanation:**

- **Node Equation:** $I_1 + I_2 = I_3 + I_4 + I_5$ (Sum of Entering = Sum of Leaving)
- **Sign Convention:** Currents entering the node are positive (+), currents leaving are negative (-).
- **Principle:** Based on **Conservation of Charge** (Charge cannot accumulate at a node).

Mnemonic

“CIECO: Currents In Equals Currents Out”


Question 2(c) [7 marks]

Define: Extrinsic Semiconductor. Explain formation of N-type Semiconductor with the help of diagram.

Solution

Definition (Extrinsic Semiconductor): An extrinsic semiconductor is a semiconductor that has been doped with impurities (trivalent or pentavalent atoms) to modify its electrical properties and increase conductivity. It is classified into N-type and P-type.

Formation of N-type Semiconductor: When a pentavalent impurity (having 5 valence electrons) like Phosphorus (P), Arsenic (As), or Antimony (Sb) is added to a pure tetravalent semiconductor (Si or Ge), an N-type semiconductor is formed.

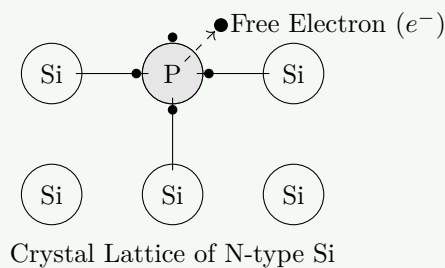Diagram:**Figure 6.** N-type Semiconductor Structure**Process:**

- **Doping:** Pentavalent atom (Donor) replaces a Silicon atom in the lattice.
- **Bonding:** 4 valence electrons of Phosphorus form covalent bonds with 4 neighboring Silicon atoms.

- **Free Electron:** The 5th valence electron of Phosphorus is loosely bound and becomes free at room temperature.
- **Conductivity:** The free electrons significantly increase conductivity. Electrons are **Majority Carriers**, and Holes are **Minority Carriers**.
- **Neutrality:** The bulk material remains electrically neutral because the number of protons equals electrons.

Mnemonic


“PPP: Phosphorus Provides Plus-one electron”

Question 2(a) OR [3 marks]

Draw energy band diagrams for Conductor, Semiconductor and Insulator.

Solution

Energy Band Diagrams:

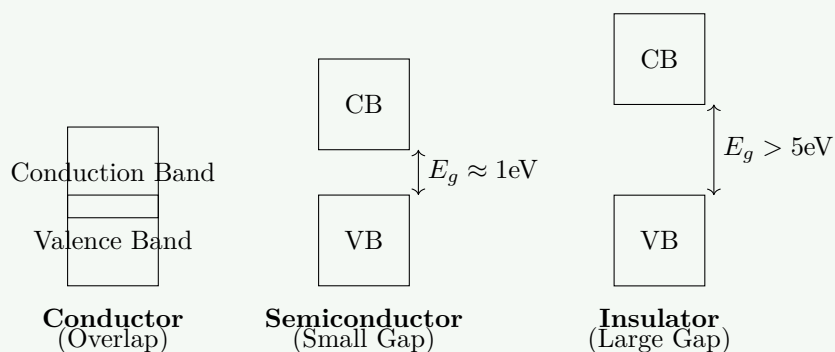

Key Differences:

- **Conductor:** VB and CB overlap; no energy gap ($E_g = 0$). Electrons flow freely.
- **Semiconductor:** Small energy gap ($E_g \approx 1.1\text{ eV}$ for Si). Conducts at higher temperatures.
- **Insulator:** Large energy gap ($E_g > 5\text{ eV}$). Electrons cannot jump to CB; no conduction.

Mnemonic

“GDF:NSH - Gaps Determine Flow: None, Small, Huge”

Question 2(b) OR [4 marks]

Give the difference between EMF and Potential difference.

Solution

Parameter	EMF (Electromotive Force)	Potential Difference (PD)
Definition	Energy supplied per unit charge by a source.	Energy consumed per unit charge across a component.
Symbol	E or ϵ	V
Measurement	Measured when circuit is open (no current).	Measured when circuit is closed (current flowing).
Source/Load	Associated with sources (Battery, Generator).	Associated with loads (Resistors, Bulbs).
Magnitude	Always greater than PD in a source (due to internal resistance).	Always less than EMF in a closed circuit.
Cause/Effect	It is a cause (drives current).	It is an effect (result of current flow).

Mnemonic

“ECPC: EMF Creates, PD Consumes”

Question 2(c) OR [7 marks]

Explain the formation of depletion region or space-charge region in P-N junction.

Solution

P-N Junction Formation: When a P-type semiconductor is joined effectively with an N-type semiconductor, a P-N junction is formed.

Diagram:

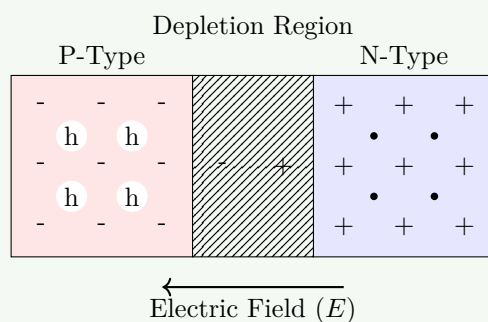


Figure 7. Depletion Region Formation

Formation Process:

- Diffusion:** Holes from P-side diffuse to N-side, and Electrons from N-side diffuse to P-side due to concentration gradient.
- Recombination:** Near the junction, free electrons combine with holes.
- Space Charge:** As carriers disappear, they leave behind immobile ions:
 - Negative acceptor ions on P-side.
 - Positive donor ions on N-side.
- Depletion Region:** This region mainly contains immobile ions and is depleted of charge carriers.
- Barrier Potential:** The electric field created by these ions opposes further diffusion. The potential difference across the junction is called Barrier Potential (V_B).
 - $V_B \approx 0.7V$ for Silicon.
 - $V_B \approx 0.3V$ for Germanium.

Mnemonic

“DCFB: Diffusion Creates, Field Balances”

Question 3(a) [3 marks]

Define forbidden energy gap. How does it occur? What is its magnitude for Ge and Si?

Solution

Forbidden Energy Gap (E_g): The energy gap between the top of the valence band and the bottom of the conduction band contains no allowed energy states for electrons. This is called the Forbidden Energy Gap.

Occurrence: It occurs due to the splitting of energy levels of atoms when they come close together to form a crystal lattice, creating distinct bands (Valence and Conduction) separated by a gap.

Magnitude at 300K:

- **Germanium (Ge):** $E_g \approx 0.67$ eV (or 0.72 eV at 0K)
- **Silicon (Si):** $E_g \approx 1.1$ eV

Mnemonic

“GSLG: Greater Silicon, Lower Germanium”

Question 3(b) [4 marks]

Define the following terms: (i) Knee voltage (ii) Reverse saturation current (iii) Reverse breakdown voltage (iv) Peak Inverse Voltage (PIV)

Solution

1. **Knee Voltage (Cut-in Voltage):** The forward voltage at which the diode current starts increasing rapidly. Below this, the current is negligible. (Si: 0.7V, Ge: 0.3V).
2. **Reverse Saturation Current (I_0):** The small, constant leakage current that flows through a diode in reverse bias due to minority carriers. It is temperature dependent.
3. **Reverse Breakdown Voltage (V_{BR}):** The reverse voltage at which the diode junction breaks down (Avalanche or Zener effect) and conducts a large current in the reverse direction.
4. **Peak Inverse Voltage (PIV):** The maximum reverse voltage that a diode can withstand without breaking down during the non-conducting cycle in a rectifier circuit.

Mnemonic

“KRSBBP: Knee Rises, Saturation Trickle, Breakdown Bursts, PIV Protects”

Question 3(c) [7 marks]

Explain construction, working and characteristics of LASER diode and write its applications.

Solution

LASER Diode: Light Amplification by Stimulated Emission of Radiation.

Construction: It is a P-N junction diode formed from direct bandgap semiconductors (like GaAs). The active region is sandwiched between P and N layers. The ends are polished/cleaved to form mirror surfaces (Fabry-Perot

cavity) for optical feedback.

Diagram:

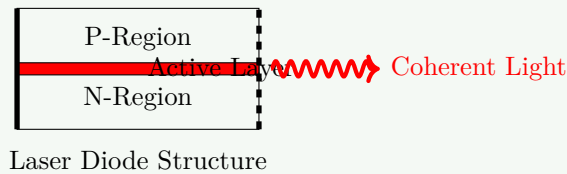


Figure 8. Laser Diode

Working Principle:

1. **Population Inversion:** Under strong forward bias, high density of electrons and holes are injected into the active region.
2. **Stimulated Emission:** An incident photon triggers an excited electron to recombine, emitting a second identical photon (same phase, frequency, direction).
3. **Amplification:** Photons bounce back and forth between the polished ends, stimulating more emission.
4. **Lasing:** Identify coherent beam emerges from the semi-transparent end when gain exceeds loss.

Characteristics:

- **Threshold Current:** Lasing starts only above a specific threshold current (I_{th}). Below this, it acts like an LED.
- **Coherence:** Emits highly monochromatic and coherent light.
- **Narrow Beam:** Highly directional output.

Applications:

- Optical Fiber Communication.
- Barcode Scanners.
- Laser Printers.
- CD/DVD Players.

Mnemonic


“PICL: Population Inversion Creates Coherent Light”

Question 3(a) OR [3 marks]

Draw V-I characteristics of P-N junction diode and Zener diode.

Solution

V-I Characteristics:

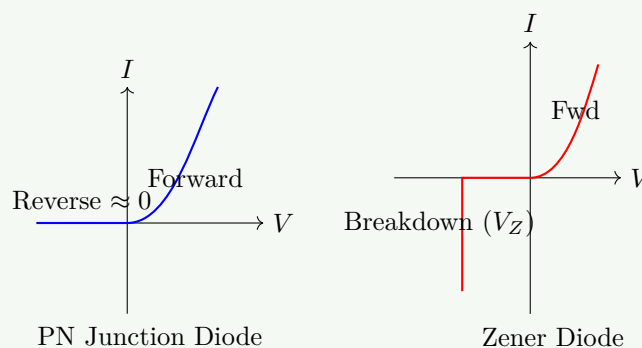

Mnemonic

“FSRD: Forward Same, Reverse Different”

Question 3(b) OR [4 marks]

Explain working of P-N junction diode in forward bias with circuit diagram.

Solution

Circuit Diagram:

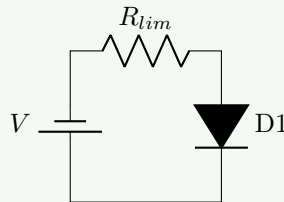


Figure 9. Forward Biased Diode

Working:

- **Connection:** P-terminal connected to Positive supply, N-terminal to Negative supply.
- **Depletion Region:** The external voltage opposes the barrier potential, pushing majority carriers toward the junction. This reduces the width of the depletion region.
- **Conduction:** When applied voltage $V > V_{\text{barrier}}$ (0.7V for Si), carriers cross the junction and significant current flows.
- **Current:** Determine by $I = I_0(e^{V/\eta V_T} - 1)$.

Mnemonic

“PPRBCF: Positive to P, Reduces Barrier, Current Flows”

Question 3(c) OR [7 marks]

Explain working of Light Emitting diode (LED) and Photodiode with diagram.

Solution


1. Light Emitting Diode (LED):

- **Principle:** Electroluminescence. Converts electrical energy to light.
- **Working:** Operates in **Forward Bias**. When carriers recombine in a direct bandgap semiconductor (like GaAsP), the energy difference is released as photons (light).

2. Photodiode:

- **Principle:** Photoelectric effect. Converts light to electrical energy.
- **Working:** Operates in **Reverse Bias**. Incident light breaks covalent bonds in the depletion region, creating electron-hole pairs. The reverse electric field sweeps them apart, creating a reverse photo-current proportional to light intensity.

Diagrams:

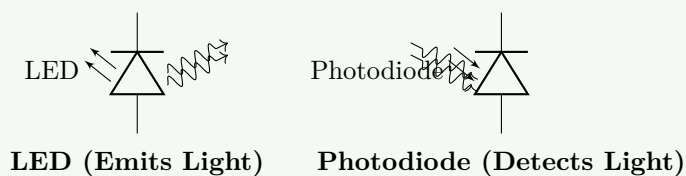

Mnemonic

“LEPD: LEDs Emit, Photodiodes Detect”

Question 4(a) [3 marks]

Define the following terms: (i) Rectifier efficiency (η) (ii) Ripple factor (γ) (iii) Voltage regulation

Solution

1. **Rectifier Efficiency (η):** It is defined as the ratio of DC output power to the AC input power.

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100\%$$

(Max efficiency: Half Wave = 40.6%, Full Wave = 81.2%)

2. **Ripple Factor (γ):** It is defined as the ratio of the RMS value of the AC component to the DC component in the rectifier output. It measures the quality of the DC output.

$$\gamma = \frac{V_{ac(rms)}}{V_{dc}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

3. **Voltage Regulation:** It is a measure of the change in output voltage from no-load to full-load condition, expressed as a percentage of full-load voltage.

$$\%VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

(Ideally, regulation should be 0%).

Mnemonic

“EPRVS: Efficiency Powers, Ripple Varies, Regulation Stabilizes”

Question 4(b) [4 marks]

Explain zener diode as a voltage regulator.

Solution

Circuit Diagram:

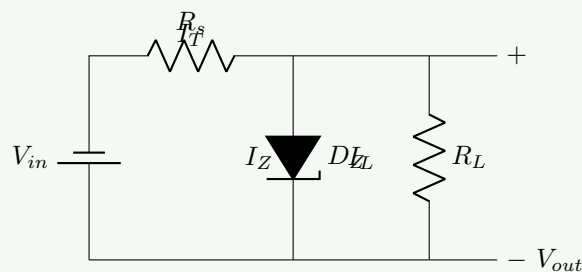


Figure 10. Zener Voltage Regulator

Working Principle:

- The Zener diode is connected in **reverse bias** parallel to the load.
- It operates in the **breakdown region** where voltage across it remains constant (V_Z) for a wide range of current.
- Case 1: Input Voltage Increases:** Direct input current (I_T) increases. The Zener diode absorbs the extra current (I_Z increases), keeping load current (I_L) and voltage ($V_{out} = V_Z$) constant. Excess voltage drops across series resistor R_s .
- Case 2: Load Current Increases:** If load resistance decreases, I_L increases. Zener current I_Z decreases by

the same amount, keeping total current I_T constant. Thus, V_{out} remains constant.

Mnemonic

“ZSEC: Zener Shunts Excess Current”

Question 4(c) [7 marks]

Explain full wave bridge rectifier with circuit diagram and input-output waveform.

Solution

Circuit Diagram:

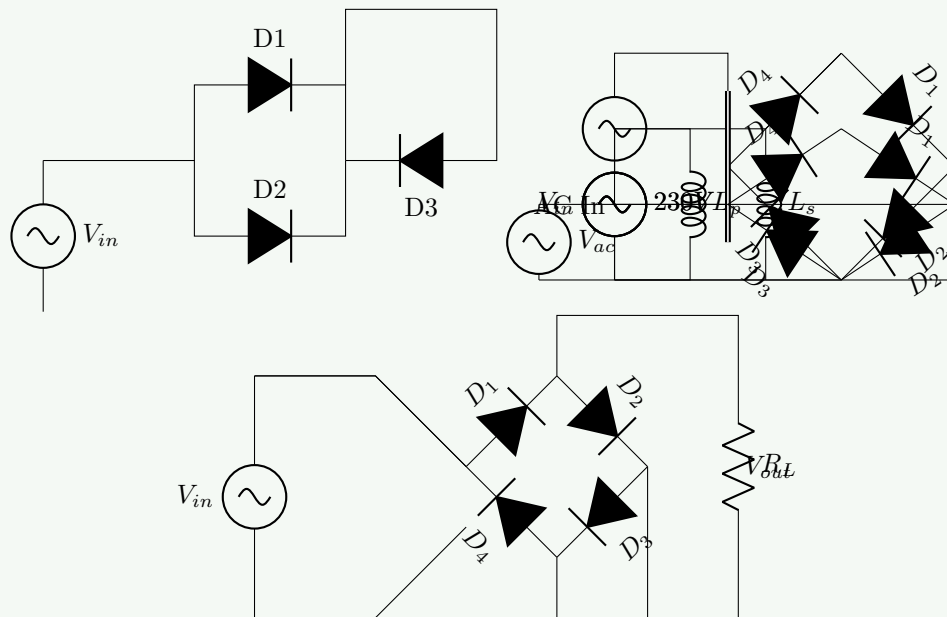


Figure 11. Full Wave Bridge Rectifier

Working:

- **Positive Half Cycle:** D_2 and D_4 conduct (depending on diagram orientation). In standard diamond (AC left/right, DC top/bottom): Let AC be applied to Left/Right. Top is Positive, Bottom is Negative. During +ve cycle, current flows from Left \rightarrow Top Diode \rightarrow Load \rightarrow Bottom Diode \rightarrow Right.
- **Negative Half Cycle:** The other pair of diodes conduct.
- Current through R_L is unidirectional in both half cycles.

Waveforms:

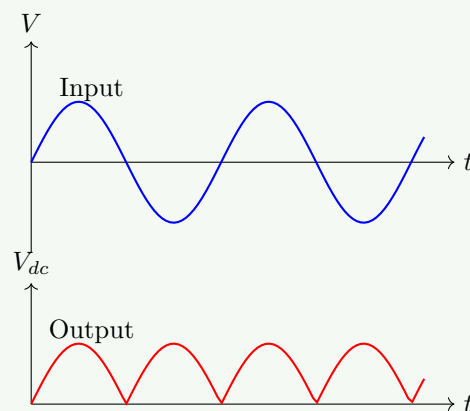


Figure 12. Input and Output Waveforms**Mnemonic**

“BBBH: Bridge Brings Both Halves”

Question 4(a) OR [3 marks]

Give the applications of rectifier.

Solution**Applications:**

- **DC Power Supplies:** To convert AC mains to DC for electronic devices (TV, Computers, Mobiles).
- **Battery Charging:** In inverters and automotive circuits.
- **Electroplating:** Requires constant DC current.
- **Electric Traction:** Trains and trams use DC motors supplied by rectifiers.
- **Detectors:** In AM radio to detect audio signals (Demodulation).

Mnemonic

“PPTICD: Power Perfectly Transformed in Consumer Devices”

Question 4(b) OR [4 marks]

Compare half wave, full wave center tapped and full wave bridge rectifier with four parameters.

Solution


Parameter	Half Wave	FW Center Tapped	FW Bridge
No. of Diodes	1	2	4
Efficiency (η)	40.6%	81.2%	81.2%
Ripple Factor	1.21	0.48	0.48
PIV Rating	V_m	$2V_m$	V_m
Transformer	Standard	Center-Tapped Required	Standard

Mnemonic

“HWCTIBO: Half Wastes, Center Tapped Improves, Bridge Optimizes”


Question 4(c) OR [7 marks]Explain Shunt capacitor filter and π -filter with circuit diagram.**Solution**

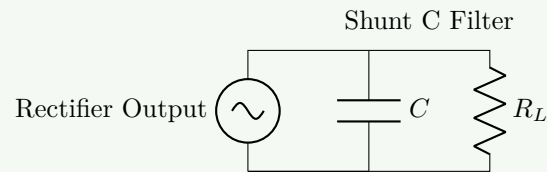1. Shunt Capacitor Filter: A capacitor is connected in parallel across the rectifier output. It charges when the rectifier voltage rises and discharges through the load when voltage falls, smoothing the output.



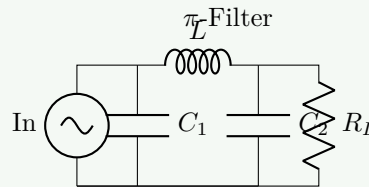2. π -Filter (C-L-C Filter): Consists of a shunt capacitor (C_1), a series inductor (L), and another shunt capacitor (C_2) arranged in shape of π .

- C_1 : Bypasses most AC ripple to ground.
- L : Blocks AC ripple, passes DC (Choke).
- C_2 : Bypasses remaining AC ripple.




Mnemonic

“CSPFP: Capacitor Smooths, Pi-Filter Perfects”

Question 5(a) [3 marks]

Draw the symbols of following components: (i) PNP transistor (ii) N channel JFET (iii) N channel enhancement mode MOSFET

Solution

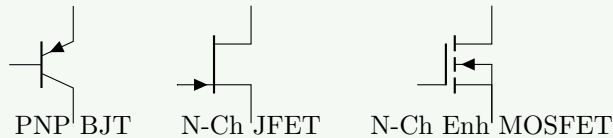

Mnemonic


“PPIJJGMMG: PNP Points IN, JFET Joins Gates, MOSFET Makes Gaps”

Question 5(b) [4 marks]

Explain working of NPN transistor with diagram.

Solution

Diagram: Use Active Mode biasing.

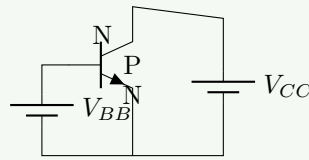

Active Region Biasing

Working:

- **Biasing:** Base-Emitter junction is Forward Biased (V_{BE}). Collector-Base junction is Reverse Biased (V_{CB}).
- **Emission:** Electrons from N-type Emitter are injected into P-type Base.
- **Transport:** Base is very thin and lightly doped. Most electrons ($\approx 98\%$) diffuse across the base to the Collector junction. Very few recombine with holes in the base (I_B).
- **Collection:** The strong electric field at the reverse-biased collector junction sweeps the electrons into the collector region, forming Collector Current (I_C).
- **Current Relation:** $I_E = I_B + I_C$, where $I_C \approx \beta I_B$.

Mnemonic

“EEBPCA: Electrons Enter, Barely Pause, Collect Above”

Question 5(c) [7 marks]

Draw and explain common emitter (CE) transistor with its input output characteristic.

Solution

CE Configuration: Emitter is common to both input and output.

Input Characteristics (I_B vs V_{BE}): Similar to a forward-biased diode. As V_{BE} exceeds 0.7V (Si), I_B increases exponentially. For higher V_{CE} , the curve shifts slightly right (Early Effect).

Output Characteristics (I_C vs V_{CE}):

- **Cut-off Region:** $I_B = 0$. Transistor is OFF.
- **Active Region:** Flat part where $I_C = \beta I_B$. Current is constant for a given I_B . Used for amplification.
- **Saturation Region:** $V_{CE} < V_{CE(sat)}$ (approx 0.2V). I_C rises rapidly. Transistor behaves as a closed switch.

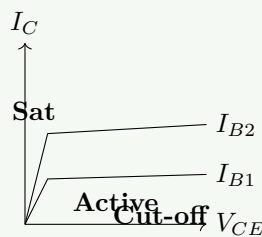


Figure 13. CE Output Characteristics

Mnemonic

“CASOAO: Cut-Active-Saturate: Off-Amplify-On”

Question 5(a) OR [3 marks]

Derive relationship between current gain alpha (α) and beta (β).

Solution**Definitions:**

- $\alpha = \frac{I_C}{I_E}$ (Common Base Gain)
- $\beta = \frac{I_C}{I_B}$ (Common Emitter Gain)

Derivation: We know that: $I_E = I_C + I_B$ Divide by I_C :

$$\frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

Substitute gains:

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\frac{1}{\alpha} = \frac{\beta + 1}{\beta} \Rightarrow \alpha = \frac{\beta}{1 + \beta}$$

Also:

$$\frac{1}{\beta} = \frac{1}{\alpha} - 1 = \frac{1 - \alpha}{\alpha} \Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$

Mnemonic

“AAOBBI: Alpha Approaches One, Beta Becomes Infinite”

Question 5(b) OR [4 marks]

Explain different operating regions for transistor.

Solution

The BJT has three main operating regions based on biasing of its two junctions (JE: Emitter Junction, JC: Collector Junction):

Region	Bias (JE, JC)	Characteristics	Application
Cut-off	Reverse, Reverse	Negligible current ($I_C \approx 0$). Open Switch.	Digital '0' (OFF)
Active	Forward, Reverse	$I_C = \beta I_B$. Output proportional to input.	Amplifiers
Saturation	Forward, Forward	Maximum current. Low voltage drop ($V_{CE} \approx 0.2V$). Closed Switch.	Digital '1' (ON)

Mnemonic

“CASOAS: Cut Active Saturate: Off Amplify Switch”

Question 5(c) OR [7 marks]

Write a short note on MOSFET.

Solution

Definition: Metal Oxide Semiconductor Field Effect Transistor. It is a voltage-controlled device with high input impedance.

Structure (N-Channel Enhancement):

- **Substrate:** Lightly doped P-type silicon.

- **Source/Drain:** Heavily doped N+ regions.
- **Gate:** Metal electrode insulated from channel by thin SiO₂ layer.

Working:

1. When Gate voltage (V_{GS}) is positive, it attracts electrons to the surface below the oxide.
2. Above a **Threshold Voltage** (V_{th}), a conductive N-channel is formed between Source and Drain.
3. Current (I_D) flows from Drain to Source applied voltage V_{DS} .

Advantages: High input impedance, low power consumption, faster switching than BJT. **Applications:** ICs, Microprocessors (CMOS), Power Switching.

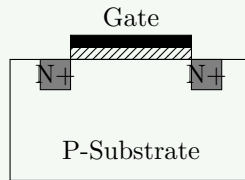


Figure 14. MOSFET Structure

Mnemonic

“MOSGFC: Metal Oxide Separate Gate Enables Field Control”