

Subject Name Solutions

4321103 – Summer 2023

Semester 1 Study Material

Detailed Solutions and Explanations

Question 1(a) [3 marks]

Explain thermal runaway in details.

Solution

Thermal runaway is a destructive mechanism in BJT transistors where increased temperature creates a self-reinforcing cycle leading to device failure.

flowchart LR

```
A[Increase in Temperature] --> B[Increase in Ic]
B --> C[Increase in Power Dissipation]
C --> D[Further Increase in Temperature]
D --> A
```

- **Heat Generation:** Temperature rises from normal operation
- **Leakage Current:** Collector current I_c increases with temperature
- **Power Dissipation:** More power = Temperature rises further
- **Destructive Cycle:** Continuous cycle until transistor destroys itself

Mnemonic

“The Higher Temperature, The Higher Current”

Question 1(b) [4 marks]

Define amplifier with simple block diagram write down amplifier parameters.

Solution

An amplifier is an electronic device that increases the power, voltage or current of an input signal.

flowchart LR

```
A[Input Signal] -- Vin --> B[AMPLIFIER]
B -- Vout --> C[Output Signal]
D[Power Supply] --> B
```

Amplifier Parameter	Description
Voltage Gain (A_v)	Ratio of output voltage to input voltage
Current Gain (A_i)	Ratio of output current to input current
Power Gain (A_p)	Product of voltage gain and current gain
Bandwidth	Range of frequencies amplifier can handle
Input Impedance	Resistance seen by the input source
Output Impedance	Internal resistance of amplifier

Mnemonic

“VIPS-BIO” (Voltage, Input impedance, Power, Supply, Bandwidth, Impedance Output)

Question 1(c) [7 marks]

Define Biasing in transistor? Write down types of biasing methods. Explain the voltage divider biasing method in details.

Solution

Biasing is the process of establishing a stable operating point (Q-point) for a transistor by applying DC voltages.

Biasing Method	Key Features
Fixed Bias	Simple, poor stability
Collector Feedback	Self-adjusting, better stability
Voltage Divider	Best stability, widely used
Emitter Bias	Good stability, negative feedback

Voltage Divider Biasing:

flowchart LR

```
VCC((+VCC)) --> R1
R1 --> R2
R2 --> B((Base))
R2 --> GND
B --> C((Collector))
B --> E((Emitter))
C --> RC
RC --> VCC
E --> RE
RE --> GND
```

- **R1 & R2:** Form voltage divider to provide stable base voltage
- **RE:** Provides stabilization through negative feedback
- **RC:** Determines collector current and voltage gain
- **Stability:** Best stability against temperature variations

Mnemonic

“Divide Voltage Before Transistor Conducts”

Question 1(c) OR [7 marks]

Explain Heat sink.

Solution

A heat sink is a passive heat exchanger that transfers heat from electronic devices to the surrounding air.

flowchart LR

```
A[Heat Source/Transistor] --> B[Interface Material]
B --> C[Heat Sink Base]
C --> D[Heat Sink Fins]
D --> E[Ambient Air]
```

Component	Function
Base	Conducts heat from device
Fins	Increases surface area for heat dissipation
Thermal Interface Material	Improves contact between device and sink
Types	Extruded, Bonded, Folded, Die-cast

- **Thermal Resistance:** Lower is better for heat dissipation
- **Material:** Usually aluminum or copper for good conductivity
- **Surface Area:** More fins means better cooling
- **Air Flow:** Critical for efficient heat removal