

# Electronics Devices & Circuits (1323202) - Winter 2023 Solution

Milav Dabgar

January 24, 2024


## Question 1(a) [3 marks]

Explain the concept of dc load line with the help of neat diagram.

### Solution

DC load line is a straight line on output characteristics that shows all possible operating points of a transistor.

**Diagram:**

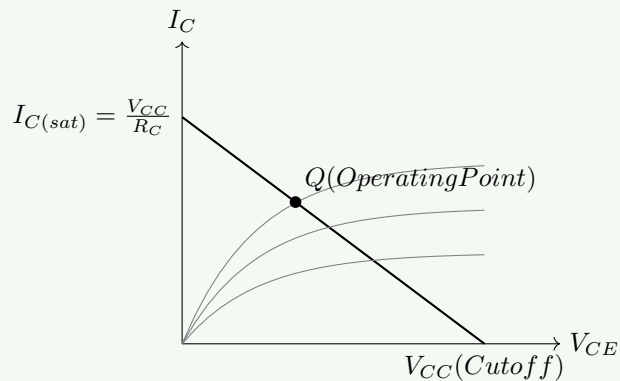

DC Load Line

- **Collector saturation current:** When  $V_{CE} = 0$ ,  $I_C = V_{CC}/R_C$
- **Cutoff voltage:** When  $I_C = 0$ ,  $V_{CE} = V_{CC}$
- **Q-point:** Operating point along load line

### Mnemonic

"LEVEL" - "Load line Establishes Voltage and current for Every Load condition"


## Question 1(b) [4 marks]

Explain thermal runaway in detail.

### Solution

Thermal runaway is a condition where heat causes transistor's collector current to increase, which generates more heat, leading to destruction.

**Diagram:**

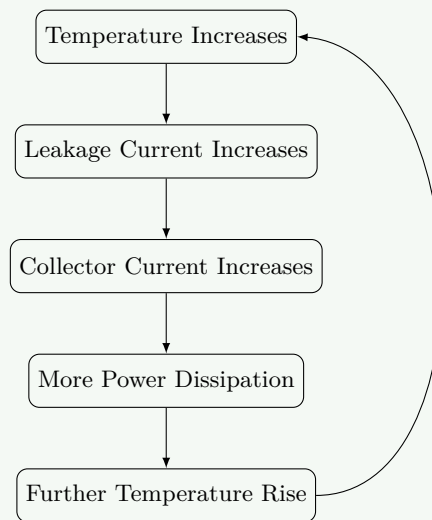

- **Heat generation:** Power dissipation =  $V_{CE} \times I_C$
- **Critical effect:** Increased junction temperature decreases  $V_{BE}$
- **Prevention:** Heat sinks, thermal stabilization circuits, proper biasing
- **Danger:** Can destroy transistor if not controlled

#### Mnemonic

"HEAT" - "Higher Emission Amplifies Temperature"


### Question 1(c) [7 marks]

Draw the circuit diagram and frequency response of a two stage R-C coupled amplifier. Explain the importance of each component.


#### Solution

R-C coupled amplifier uses capacitors to connect multiple transistor stages for higher gain.

**Circuit Diagram:**

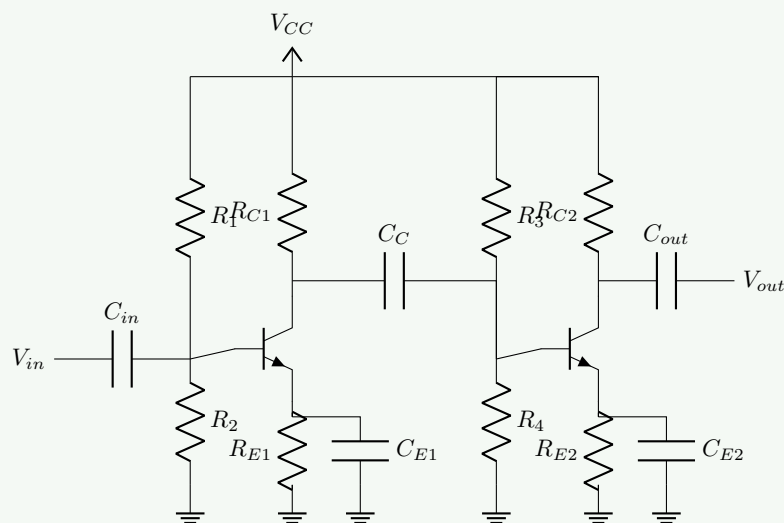

**Frequency Response:**

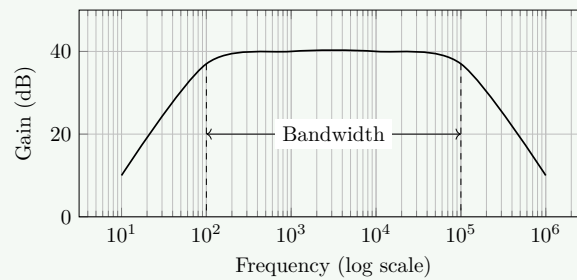

- **Coupling capacitors ( $C_C$ ):** Block DC, allow AC signal transfer between stages
- **Biasing resistors ( $R_1, R_2$ ):** Establish proper Q-point for transistor operation
- **Bypass capacitors ( $C_E$ ):** Prevent gain reduction from negative feedback across  $R_E$
- **Bandwidth:** Range between low ( $f_L$ ) and high ( $f_H$ ) cutoff frequencies

#### Mnemonic

"CARS" - "Coupling capacitors Allow Resistance Separation"

OR

### Question 1(c) [7 marks]

Compare negative and positive feedback in amplifier.

#### Solution

Feedback systems return a portion of output to the input with different effects based on polarity.

**Table 1.** Comparison of Feedback Types

Parameter	Negative Feedback	Positive Feedback
Gain	Decreases	Increases
Bandwidth	Increases	Decreases
Stability	Improves	Decreases
Distortion	Reduces	Increases
Noise	Reduces	Amplifies
Input/Output Impedance	Can be controlled	Unpredictable
Applications	Amplifiers, regulators	Oscillators, Schmitt triggers

- **Negative feedback:** Output is out of phase with input (180° shifted)
- **Positive feedback:** Output is in phase with input (0° shifted)
- **Barkhausen criteria:** Positive feedback with unity gain creates oscillation

#### Mnemonic

"SIGN" - "Stability Increases with Gain Negation"


### Question 2(a) [3 marks]

State and explain Barkhausen's criteria for oscillations.

**Solution**

Barkhausen's criteria define conditions for sustained oscillations in a feedback system.

**Diagram:**

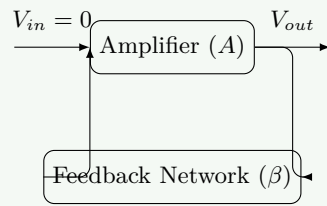

Conditions:

1. Loop Gain  $|A\beta| = 1$
2. Phase Shift  $\angle A\beta = 0^\circ$  or  $360^\circ$

- **Gain condition:** Loop gain ( $A \times \beta$ ) must equal 1 (unity)
- **Phase condition:** Total phase shift around the loop must be  $0^\circ$  or  $360^\circ$
- **Practical implementation:** Initial loop gain  $> 1$  to start, then stabilizes at 1 due to nonlinearity

**Mnemonic**

"LOOP" - "Loop's Overall Output Phase"

**Question 2(b) [4 marks]**

Compare Fixed bias, Collector to base bias & Voltage divider bias methods.

**Solution**

Different biasing techniques provide varying degrees of stability and temperature compensation.

**Table 2.** Comparison of Biasing Methods

Parameter	Fixed Bias	Collector-Base Bias	Voltage Divider Bias
Stability	Poor	Better	Excellent
Circuit Complexity	Simple	Medium	Complex
Temp Stability	Poor	Medium	Good
Components	1 Resistor	1 Resistor	3-4 Resistors
Stability Factor (S)	High (Unstable)	Medium	Low (Stable)

- **Fixed bias:** Single resistor from base to  $V_{CC}$
- **Collector-base bias:** Feedback resistor from collector to base provides negative feedback
- **Voltage divider:** Two resistors create stable reference voltage independent of  $\beta$

**Mnemonic**

"STORM" - "Stability Through Optimized Resistor Methods"


**Question 2(c) [7 marks]**

Write short note on Hartley oscillator.

**Solution**

Hartley oscillator is an LC oscillator with a tapped inductor for feedback.

**Circuit Diagram:**

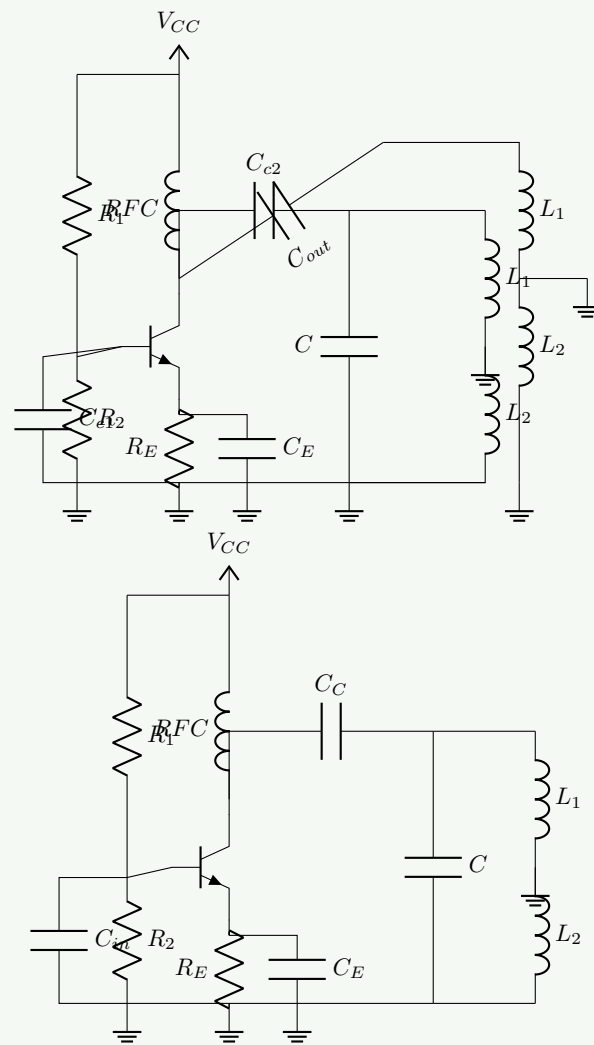

- **Circuit components:** Amplifier (CE Mode), Tank Circuit ( $L_1, L_2, C$ )
- **Frequency formula:**  $f = \frac{1}{2\pi\sqrt{L_{eq}C}}$  where  $L_{eq} = L_1 + L_2$
- **Feedback:** Voltage across  $L_2$  is fed back to base ( $180^\circ$  phase shift by tank +  $180^\circ$  by amp =  $360^\circ$ )
- **Applications:** RF signal generators, radio receivers

#### Mnemonic

"TILC" - "Tapped Inductor with LC Circuit"

OR


### Question 2(a) [3 marks]

Explain working of transistor as a switch.

#### Solution

Transistor switches between cutoff (OFF) and saturation (ON) regions for digital applications.

**Diagram:**

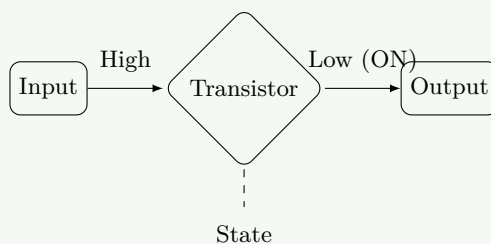

- **Cutoff region:**  $V_{BE} < 0.7V$ , acts as open switch,  $V_{CE} \approx V_{CC}$  (Output High)
- **Saturation region:**  $V_{BE} > 0.7V$ , acts as closed switch,  $V_{CE} \approx 0.2V$  (Output Low)
- **Switching time:** Limited by junction capacitance

#### Mnemonic

"COPS" - "Cutoff-On-Produces Switching"


## Question 2(b) [4 marks]

Define heat sink. List types of heat sink and give its applications.

#### Solution

Heat sink is a thermal conductor that transfers heat away from electronic components to prevent overheating.

**Diagram:**

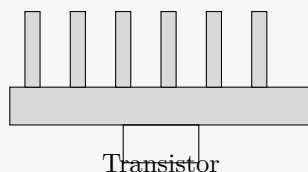

**Types of Heat Sinks:**

**Table 3.** Heat Sink Types and Applications

Type	Description	Application
Passive	No moving parts, natural convection	Low-power devices
Active	With fans or pumps	High-power amplifiers, CPUs
Liquid-cooled	Uses fluid for heat transfer	Supercomputers, high-end PCs
Finned	Multiple fins increase surface area	Power transistors

#### Mnemonic

"COOL" - "Conducting Out Of Local heat"


## Question 2(c) [7 marks]

Explain advantages and disadvantages of negative feedback in amplifiers in detail.

**Solution**

Negative feedback returns a portion of output signal to input with opposite phase to improve performance stability.

**Feedback Block Diagram:**

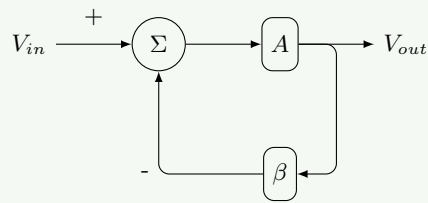

**Table 4.** Pros and Cons of Negative Feedback

Advantages	Disadvantages
Stabilizes gain against parameter changes	Reduces overall gain
Increases bandwidth	Requires more components
Reduces non-linear distortion	More power consumption in feedback circuit
Decreases noise	Complexity of design
Controls Input/Output Impedance	Potential for oscillation if phase margin low

**Mnemonic**

"STABLE" - "Stabilized Transmission And Bandwidth with Less Error"


**Question 3(a) [3 marks]**

**Draw symbol of SCR and explain working of SCR.**

**Solution**

Silicon Controlled Rectifier (SCR) is a four-layer PNPN device with three terminals.

**Symbol:**

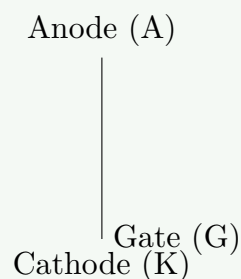

- **Structure:** P-N-P-N four-layer semiconductor device
- **Operation:** Remains OFF until gate triggered, then conducts until current falls below holding value
- **Terminals:** Anode (A), Cathode (K), Gate (G)

**Mnemonic**

"AGK" - "Anode-Gate controls Kathode current"


### Question 3(b) [4 marks]

Explain two transistor analogy of SCR with circuit diagram.

#### Solution

SCR can be represented as interconnected PNP and NPN transistors sharing semiconductor layers.

**Circuit Diagram:**

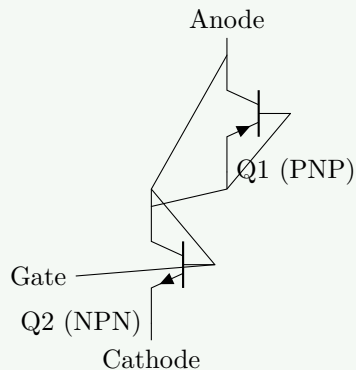

- **PNP section:** Upper transistor with collector connected to NPN base
- **NPN section:** Lower transistor with collector connected to PNP base
- **Regenerative Feedback:** Collector current of Q1 feeds Base of Q2; Collector current of Q2 feeds Base of Q1. Once triggered, the loop sustains standard conduction.

#### Mnemonic

"PNPN" - "Positive-Negative-Positive-Negative layers"


### Question 3(c) [7 marks]

Explain the working of TRIAC based fan regulator with circuit diagram.

#### Solution

TRIAC-based fan regulator controls AC power delivered to the load through phase control.

**Circuit Diagram:**

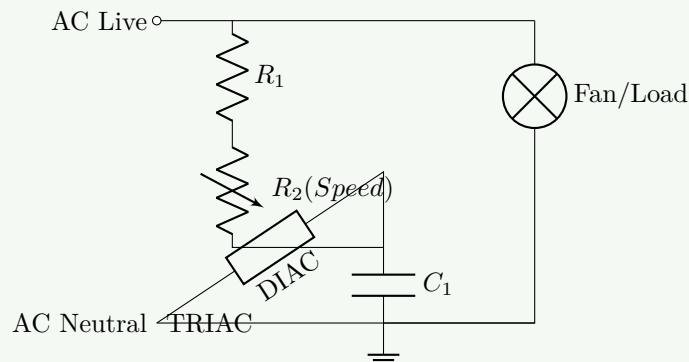

- **Phase control:** Varies firing angle of TRIAC to control effective RMS voltage
- **Diac:** Provides bidirectional triggering pulse for TRIAC
- **RC timing circuit:**  $R_1, R_2, C_1$  determine the delay angle; Changing  $R_2$  changes speed
- **Operation:** When capacitor voltage reaches DIAC breakover, TRIAC fires



**Mnemonic**

"TRIAC" - "Triggered Response In AC Circuits"



OR

### Question 3(a) [3 marks]

Draw V-I characteristics of DIAC and TRIAC.

**Solution**

DIACs and TRIACs are bidirectional devices with symmetrical forward and reverse characteristics.

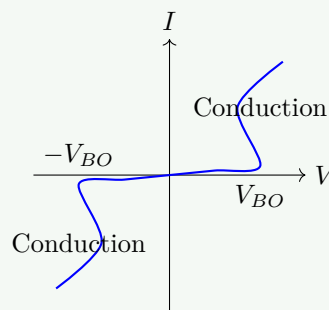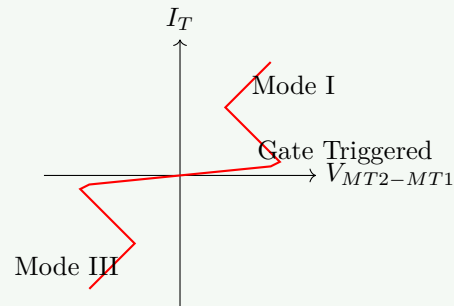**DIAC Characteristics:****TRIAC Characteristics:****Mnemonic**

"BIBO" - "Bidirectional In, Bidirectional Out"


### Question 3(b) [4 marks]

Explain the Gate triggering method of SCR.

**Solution**

Gate triggering applies a control signal to the gate terminal to turn on the SCR at a precise moment.

**Diagram:**

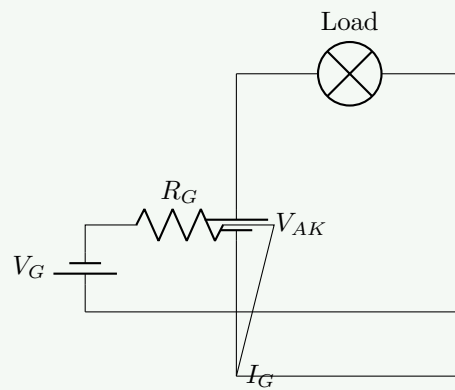

- **Gate pulse:** Positive current applied between gate and cathode
- **Timing:** Controls the firing angle ( $\alpha$ ) in AC circuits
- **Requirement:** Gate current must persist until anode current reaches latching current

#### Mnemonic

"GATE" - "Gain Activation Through Electron flow"


### Question 3(c) [7 marks]

Explain SCR application for DC power control.

#### Solution

SCR controls DC power by chopping the supply voltage using PWM or phase control techniques (if input is AC rectified). For pure DC, it needs a commutation circuit, but here we assume general DC control concept.

**Circuit Diagram:**

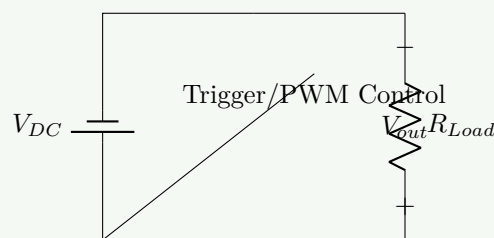

- **Chopping:** SCR acts as a switch, turning ON and OFF rapidly
- **Power Control:** Average output voltage  $V_{avg} = V_{in} \times \text{Duty Cycle}$
- **Commutation:** In DC circuits, SCR requires a forced commutation circuit to turn OFF (not shown for simplicity)

#### Mnemonic

"POWER" - "Pulse Operation With Electronic Regulation"

### Question 4(a) [3 marks]

List characteristics of Ideal OP-AMP.

**Solution**

Ideal operational amplifiers have perfect characteristics that real devices approximate.

**Table 5.** Ideal Op-Amp Characteristics

Characteristic	Ideal Value
Open Loop Gain ( $A_{OL}$ )	Infinite ( $\infty$ )
Input Impedance ( $Z_{in}$ )	Infinite ( $\infty$ )
Output Impedance ( $Z_{out}$ )	Zero ( $0\Omega$ )
Bandwidth ( $BW$ )	Infinite ( $\infty$ )
CMRR	Infinite ( $\infty$ )
Slew Rate	Infinite ( $\infty$ )
Offset Voltage	Zero ( $0V$ )

**Mnemonic**

"IBOCSS" - "Infinite Bandwidth, Open-loop gain, CMRR, Slew rate, and Sensitivity"


**Question 4(b) [4 marks]**

Explain working of differential amplifier using OP-AMP with circuit diagram.

**Solution**

Differential amplifier amplifies the voltage difference between two inputs while rejecting common signals.

**Circuit Diagram:**

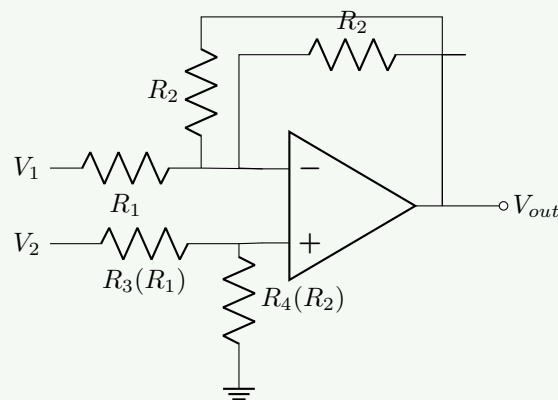

- **Gain formula:**  $V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$  (assuming  $R_3 = R_1, R_4 = R_2$ )
- **Common mode rejection:** Suppresses signals common to both inputs (noise)
- **Applications:** Instrumentation, medical equipment, audio balanced inputs

**Mnemonic**

"DIFF" - "Dual Input For Feedback"


**Question 4(c) [7 marks]**

Explain OP-AMP as an inverting amplifier (Closed loop) and derive the formula of voltage gain.

**Solution**

Inverting amplifier produces output that is inverted and amplified version of input.

**Circuit Diagram:**

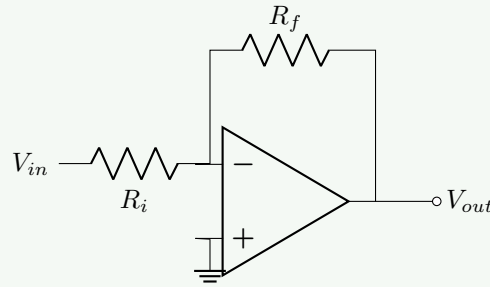

**Gain Derivation:**

- Apply KCL at inverting input (Virtual Ground Node  $V^-$ ):

$$I_1 + I_2 = 0$$

- Since Op-amp input impedance is infinite, current into terminals is zero.

$$I_1 = \frac{V_{in} - V^-}{R_i}, \quad I_2 = \frac{V_{out} - V^-}{R_f}$$

- Due to Virtual Ground concept ( $V^+ = 0$ ),  $V^- \approx 0$ .

$$\frac{V_{in}}{R_i} + \frac{V_{out}}{R_f} = 0$$

$$\frac{V_{out}}{R_f} = -\frac{V_{in}}{R_i}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$

**Mnemonic**

"VAIN" - "Virtual ground Amplification Inverts Negative"

**OR**

**Question 4(a) [3 marks]**

Define the following parameters of OPAMP: 1) CMRR, 2) Slew rate, 3) Gain Bandwidth Product

**Solution**

These parameters define key performance characteristics of operational amplifiers.

**Table 6.** Op-Amp Parameters

Parameter	Definition	Importance
CMRR	Ratio of differential gain to common-mode gain ( $A_d/A_{cm}$ )	High CMRR rejects noise
Slew Rate	Max rate of output voltage change ( $dV/dt$ ) in V/ $\mu$ s	Limits high-freq performance
Gain-Bandwidth	Product of Open Loop Gain and Frequency	Constant for a given op-amp

**Mnemonic**

"CSG" - "Common-mode rejection, Speed, and Gain"


**Question 4(b) [4 marks]**

Draw and explain summing amplifier using OP-AMP.

**Solution**

Summing amplifier produces output proportional to the weighted algebraic sum of input voltages.

**Circuit Diagram:**

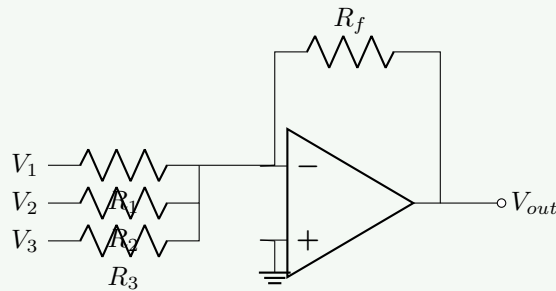

- **Output formula:**  $V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$
- **Averaging:** If  $R_1 = R_2 = R_3 = R$  and  $R_f = R/3$ , output is negative average
- **Applications:** Audio mixer, analog addition

**Mnemonic**

"SUM" - "Several Unified Multipliers"


**Question 4(c) [7 marks]**

Draw the pin diagram of IC 555 and explain Monostable multivibrator using IC555 with waveform.


**Solution**

IC 555 timer in monostable mode produces a single pulse of fixed duration ( $T$ ) when triggered.

**Pin Diagram:**

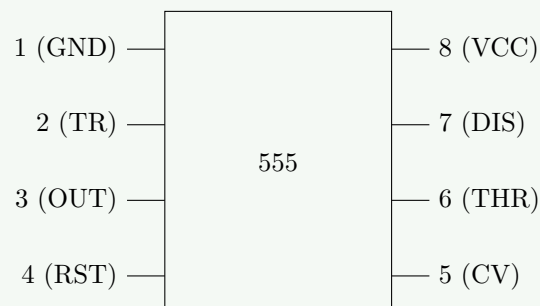

**Monostable Circuit & Waveforms:**

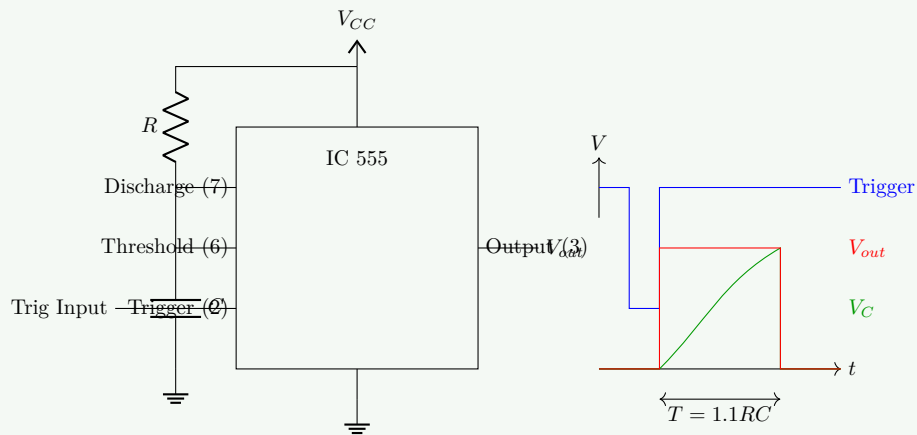

- **Operation:** Trigger (Pin 2) low pulse starts timing cycle. Output goes high. Capacitor charges via R.
- **End of Cycle:** When  $V_C = 2/3V_{CC}$ , output goes low, capacitor discharges.
- **Pulse Width:**  $T = 1.1 \times R \times C$  seconds.

#### Mnemonic

"TIMER" - "Triggered Input Makes Extended Response"


## Question 5(a) [3 marks]

Draw block diagram of SMPS and give its applications.

### Solution

Switch Mode Power Supply (SMPS) uses switching elements for efficient power conversion.

**Block Diagram:**

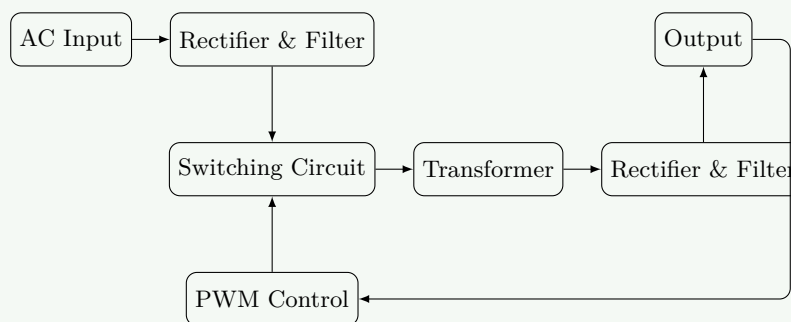

### Applications:

- Computer power supplies (ATX)
- Mobile phone chargers
- TV power supplies
- LED lighting drivers

#### Mnemonic

"SAFE" - "Switching Achieves Filtered Energy"


### Question 5(b) [4 marks]

Explain working of Regulated Power Supply with diagram.

#### Solution

Regulated power supply maintains constant output despite input or load variations.

**Block Diagram:**

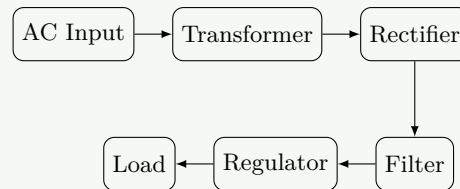

- **Transformer:** Steps down AC voltage to required level
- **Rectifier:** Converts AC to pulsating DC (diode bridge)
- **Filter:** Smooths DC ripple with capacitors
- **Regulator:** Stabilizes DC voltage (e.g., 7805, LM317)

#### Mnemonic

"TRFRO" - "Transform, Rectify, Filter, Regulate, Output"


### Question 5(c) [7 marks]

Explain basic block diagram of OP-AMP with diagram.

#### Solution

Operational amplifier consists of four cascaded stages performing specific functions.

**Block Diagram:**

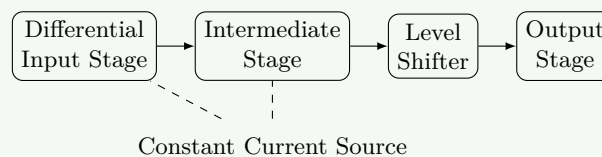

- **Differential Input Stage:** Provides high input impedance and CMRR (Dual Input Balanced Output)
- **Intermediate Stage:** Provides high voltage gain (Dual Input Unbalanced Output)
- **Level Shifter:** Shifts DC level to zero volts (Emitter Follower)
- **Output Stage:** Provides low output impedance and current drive (Push-Pull Amplifier)

#### Mnemonic

"DILO" - "Differential Input, Level shift, Output"

OR


### Question 5(a) [3 marks]

Explain adjustable voltage regulator using LM317 with diagram.

**Solution**

LM317 is a variable positive voltage regulator that adjusts output from 1.25V to 37V.

**Circuit Diagram:**

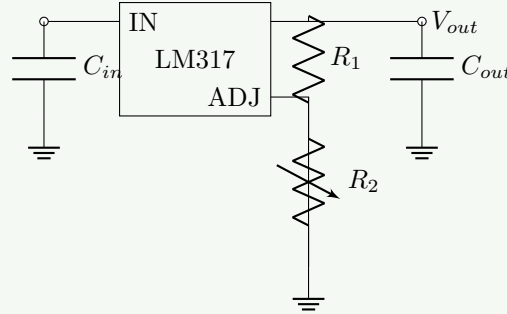

- **Formula:**  $V_{out} = 1.25V \times (1 + \frac{R_2}{R_1}) + I_{adj} R_2$  where 1.25V is reference voltage ( $V_{ref}$ )
- **Resistors:**  $R_1$  sets reference current,  $R_2$  adjusts output voltage
- **Protection:** Internal thermal overload and short circuit protection

**Mnemonic**

"AVR" - "Adjustable Voltage Regulation"

**Question 5(b) [4 marks]**

Give the difference between Fixed voltage regulator IC and Variable voltage regulator IC.

**Solution**

Comparison between fixed output regulators (like 78XX) and adjustable ones (like LM317).

**Table 7.** Fixed vs Variable Regulators

Parameter	Fixed Regulator	Variable Regulator
Output Voltage	Preset (e.g., 5V, 12V)	Adjustable Range (e.g., 1.2V-37V)
Components	Minimum (2 Capacitors)	More (Resistors + Capacitors)
Flexibility	Low (Fixed application)	High (Universal application)
Examples	7805, 7812, 7905	LM317, LM337, LM723
Cost	Generally Cheaper	Slightly Higher
Pin Config	In, Ground, Out	In, Adjust, Out

**Mnemonic**

"FOCUS" - "Fixed Output Compared to User-Set"

**Question 5(c) [7 marks]**

List applications of OP-AMP. Explain working operation of D to A converter with circuit diagram using OP-AMP.




## Solution

DAC converts digital binary input into equivalent analog voltage.

### Applications of OP-AMP:

1. Amplifiers (Inverting, Non-inverting, Differential)
2. Filters (Active Low Pass, High Pass)
3. Oscillators (Wein Bridge, Phase Shift)
4. Comparators and Schmitt Triggers
5. Mathematical Operations (Summing, Integrator, Differentiator)

### R-2R Ladder DAC Circuit:

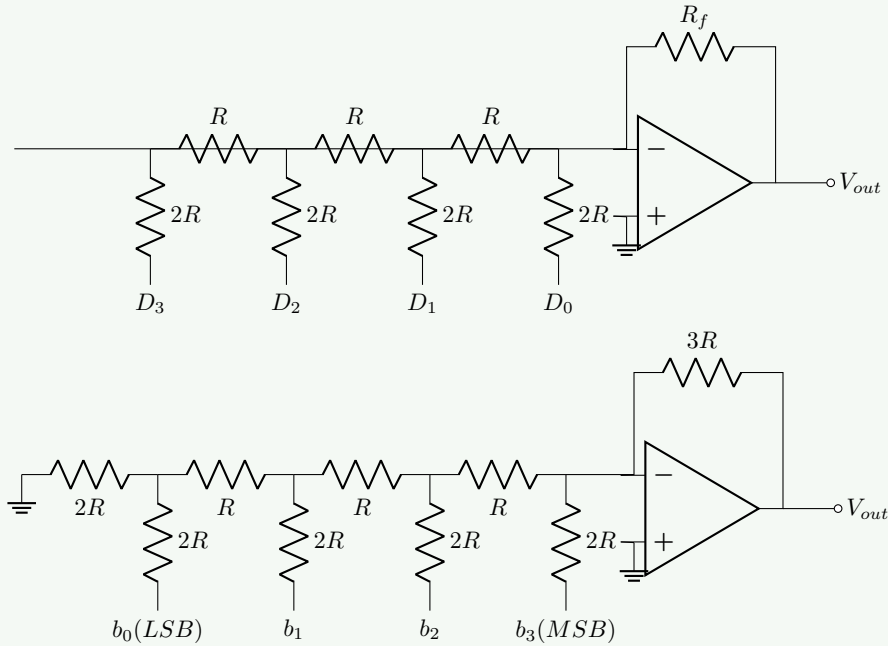

- **Principle:** Ladder network creates binary weighted currents
- **Output:**  $V_{out} \propto -(b_3 2^{-1} + b_2 2^{-2} + b_1 2^{-3} + b_0 2^{-4}) V_{ref}$
- **Advantages:** Only two resistor values ( $R, 2R$ ) needed, scalable

### Mnemonic

"DART" - "Digital to Analog Resistor Translation"