

Subject Name (SUBJECT001) - Sample Term Solution

Milav Dabgar

Month Day, Year

Contents

1 Question 1

1.1 Question 1(a) [3 marks]

Write a Java program to find the maximum of three numbers.

1.1.1 Solution

To find the **maximum** of three numbers, we use **conditional statements** (if-else) to compare values. The program takes three numbers as input and returns the *largest value* among them.

Listing 1: Find Maximum of Three Numbers

Java Program:

```
1 public class MaxOfThree {
2     public static void main(String[] args) {
3         int a = 25, b = 40, c = 15;
4         int max;
5
6         // Compare first two numbers
7         if (a > b) {
8             max = a;
9         } else {
10            max = b;
11        }
12
13        // Compare result with third number
14        if (c > max) {
15            max = c;
16        }
17
18        System.out.println("Maximum number is: " + max);
19    }
20 }
```

Output:

Maximum number is: 40

Key Points:

Logic: First compare **a** and **b**, store larger in **max**

Second Comparison: Compare **max** with **c** to get final maximum

Alternative: Can use `Math.max(a, Math.max(b, c))` for concise code

Mnemonic: *MAX: Compare in pairs, update Maximum At eXamination*

1.2 Question 1(b) [4 marks]

Calculate the cutoff frequency of an RC low-pass filter with $R = 1.5\text{ k}\Omega$ and $C = 100\text{ nF}$. Also find the output voltage if input is 10V at cutoff frequency.

1.2.1 Solution

Given Data:

- Resistance: $R = 1.5\text{ k}\Omega = 1500\text{ }\Omega$
- Capacitance: $C = 100\text{ nF} = 100 \times 10^{-9}\text{ F}$
- Input Voltage: $V_{in} = 10\text{ V}$

Step 1: Calculate Cutoff Frequency The **cutoff frequency** formula for RC low-pass filter is:

$$f_c = \frac{1}{2\pi RC}$$

Substituting values:

$$f_c = \frac{1}{2\pi \times 1500 \times 100 \times 10^{-9}}$$

$$f_c = \frac{1}{2\pi \times 1.5 \times 10^{-4}}$$

$$f_c = \frac{1}{9.42 \times 10^{-4}} = 1061.57\text{ Hz} \approx 1.06\text{ kHz}$$

Step 2: Calculate Output Voltage at Cutoff At cutoff frequency, output voltage is **0.707 times** (or $\frac{1}{\sqrt{2}}$) the input voltage:

$$V_{out} = 0.707 \times V_{in} = 0.707 \times 10 = 7.07\text{ V}$$

Results:

Cutoff Frequency: $f_c = 1.06\text{ kHz}$

Output Voltage: $V_{out} = 7.07\text{ V}$ at cutoff

Attenuation: -3 dB at cutoff frequency

Phase Shift: -45° at cutoff frequency

Mnemonic: *RC-Formula:* $f_c = \frac{1}{2\pi RC}$, $V_{out} = 0.707 \times V_{in}$ at f_c

1.3 Question 1(c) [7 marks]

Compare active and passive electronic components with suitable examples.

1.3.1 Solution

Electronic components are classified into **active** and **passive** categories based on their ability to control or amplify electrical energy.

Table 1: Active vs Passive Components Comparison

Characteristic	Active Components	Passive Components
Energy Source	Require external power source	Do not require external power
Control Ability	Can control/amplify current flow	Cannot amplify, only regulate
Directionality	Usually unidirectional	Bidirectional
Power Gain	Provide power gain (> 1)	Power gain is always ≤ 1
Examples	Transistors (BJT, FET), Diodes (LED, Zener), ICs (Op-Amp, 555), SCR	Resistors, Capacitors, Inductors, Transformers
Function	Amplification, switching, oscillation, rectification	Resistance, capacitance, inductance, filtering
Linearity	Can be linear or non-linear	Generally linear

Active Components in Detail:

Transistors: Used for amplification and switching. BJT uses current control, FET uses voltage control.

Diodes: Allow current in one direction. LED emits light, Zener regulates voltage.

ICs: Integrated circuits like 555 timer (oscillator), op-amps (amplifier).

Power Requirement: All active components need DC bias/supply to operate.

Passive Components in Detail:

Resistors: Oppose current flow, dissipate power as heat. Value in Ω .

Capacitors: Store energy in electric field. Value in Farads (F), blocks DC, passes AC.

Inductors: Store energy in magnetic field. Value in Henry (H), opposes AC changes.

Transformers: Transfer energy between circuits via magnetic coupling.

Capacitor Types: Capacitors include electrolytic (polarized, high capacitance), ceramic (small, stable), and film (precision) types.

Key Distinction: The fundamental difference is that active components can *inject power* into a circuit (amplification), while passive components can only *absorb or store* energy, never increase it.

Mnemonic: *ACTIVE = Amplify, Control, Transform; PASSIVE = Resist, Store, Filter*

1.4 Question 1(c) OR [7 marks]

Draw and explain the working of a half-wave rectifier circuit with input and output waveforms.

1.4.1 Solution

A **half-wave rectifier** converts AC voltage to pulsating DC by allowing only one half-cycle (positive or negative) of the input AC waveform to pass through.

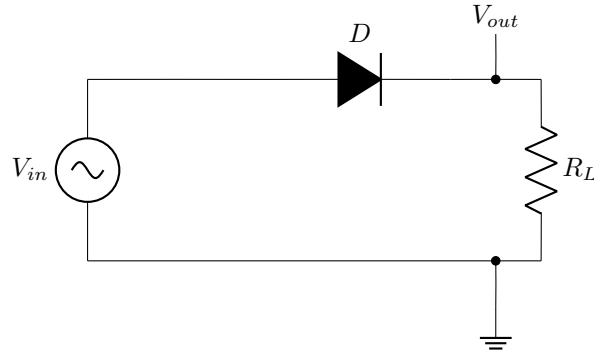


Figure 1: Half-Wave Rectifier Circuit

Circuit Diagram:**Working Principle:**

Positive Half-Cycle: When input AC is positive, diode is forward-biased (conducts). Current flows through load resistor R_L , producing output voltage.

Negative Half-Cycle: When input AC is negative, diode is reverse-biased (blocks). No current flows, output voltage is zero.

Result: Only positive half-cycles appear at output, creating pulsating DC.

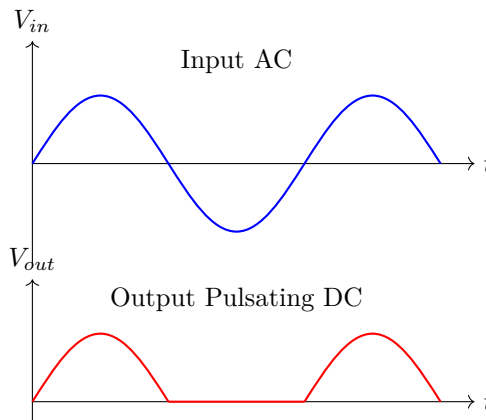


Figure 2: Input and Output Waveforms

Waveform Representation:**Key Parameters:**

Efficiency: $\eta = 40.6\%$ (theoretical maximum)

Ripple Factor: $r = 1.21$ (high ripple content)

Peak Inverse Voltage (PIV): $PIV = V_m$ (maximum reverse voltage across diode)

DC Output: $V_{DC} = \frac{V_m}{\pi} = 0.318V_m$ where V_m is peak AC voltage

Applications: Half-wave rectifiers are used in low-power applications like battery charging, signal demodulation, and voltage multipliers. They are *not suitable* for high-power applications due to poor efficiency.

Mnemonic: *HWR: Half-Wave = Half output, 40.6% efficiency, $PIV = V_m$*