

# Digital Electronics (4321102) - Summer 2023 Solution

Milav Dabgar

August 07, 2023

## Question 1(a) [3 marks]

Explain De-Morgan's theorem for Boolean algebra

### Solution

De-Morgan's theorem consists of two laws that show the relationship between AND, OR, and NOT operations:

**Law 1:** The complement of a sum equals the product of complements

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

**Law 2:** The complement of a product equals the sum of complements

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

**Table 1.** De-Morgan's Laws Verification

A	B	A+B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

### Mnemonic

"NOT over OR becomes AND of NOTs, NOT over AND becomes OR of NOTs"

## Question 1(b) [4 marks]

Convert following decimal number into binary and octal number (i) 215 (ii) 59

### Solution

#### Binary Conversion:

**For 215:**

- Divide by 2 repeatedly:  $215/2 = 107$  remainder 1
- $107/2 = 53$  remainder 1
- $53/2 = 26$  remainder 1
- $26/2 = 13$  remainder 0
- $13/2 = 6$  remainder 1
- $6/2 = 3$  remainder 0
- $3/2 = 1$  remainder 1

- $1/2 = 0$  remainder 1
- Therefore,  $(215)_{10} = (11010111)_2$

**For 59:**

- Divide by 2 repeatedly:  $59/2 = 29$  remainder 1
- $29/2 = 14$  remainder 1
- $14/2 = 7$  remainder 0
- $7/2 = 3$  remainder 1
- $3/2 = 1$  remainder 1
- $1/2 = 0$  remainder 1
- Therefore,  $(59)_{10} = (111011)_2$

**Octal Conversion:****For 215:**

- Divide by 8 repeatedly:  $215/8 = 26$  remainder 7
- $26/8 = 3$  remainder 2
- $3/8 = 0$  remainder 3
- Therefore,  $(215)_{10} = (327)_8$

**For 59:**

- Divide by 8 repeatedly:  $59/8 = 7$  remainder 3
- $7/8 = 0$  remainder 7
- Therefore,  $(59)_{10} = (73)_8$

**Table 2.** Number Conversion Summary

Decimal	Binary	Octal
215	11010111	327
59	111011	73

**Mnemonic**

"Divide by base, read remainders bottom-up"

**Question 1(c)(I) [2 marks]**

Write the base of decimal, binary, octal and hexadecimal number system

**Solution****Table 3.** Number System Bases

Number System	Base
Decimal	10
Binary	2
Octal	8
Hexadecimal	16

**Mnemonic**

"D-B-O-H: 10-2-8-16"

**Question 1(c)(II) [2 marks]**

$$(147)_{10} = (\underline{\hspace{2cm}})_2 = (\underline{\hspace{2cm}})_{16}$$

**Solution****Decimal to Binary conversion:**

- $147/2 = 73$  remainder 1
- $73/2 = 36$  remainder 1
- $36/2 = 18$  remainder 0
- $18/2 = 9$  remainder 0
- $9/2 = 4$  remainder 1
- $4/2 = 2$  remainder 0
- $2/2 = 1$  remainder 0
- $1/2 = 0$  remainder 1
- Therefore,  $(147)_{10} = (10010011)_2$

**Decimal to Hexadecimal conversion:**

- Group binary digits in sets of 4: 1001 0011
- Convert each group to hex: 1001 = 9, 0011 = 3
- Therefore,  $(147)_{10} = (93)_{16}$

**Table 4.** Conversion Result

Decimal	Binary	Hexadecimal
147	10010011	93

**Mnemonic**

"Group by 4 from right for hex"

**Question 1(c)(III) [3 marks]**

Convert following binary code into grey code (i) 1011 (ii) 1110

**Solution****Binary to Gray code conversion procedure:**

1. The MSB (leftmost bit) of the Gray code is the same as the MSB of the binary code
2. Other bits of the Gray code are obtained by XORing adjacent bits of the binary code

**For 1011:**

- MSB of Gray = MSB of Binary = 1
- Second bit =  $1 \oplus 0 = 1$
- Third bit =  $0 \oplus 1 = 1$
- Fourth bit =  $1 \oplus 1 = 0$
- Therefore,  $(1011)_2 = (1110)_{gray}$

**For 1110:**

- MSB of Gray = MSB of Binary = 1
- Second bit =  $1 \oplus 1 = 0$
- Third bit =  $1 \oplus 1 = 0$
- Fourth bit =  $1 \oplus 0 = 1$
- Therefore,  $(1110)_2 = (1001)_{gray}$

**Table 5.** Binary to Gray Code Conversion

Binary	Step-by-step	Gray Code
1011	$1, 1 \oplus 0 = 1, 0 \oplus 1 = 1, 1 \oplus 1 = 0$	1110
1110	$1, 1 \oplus 1 = 0, 1 \oplus 1 = 0, 1 \oplus 0 = 1$	1001

**Mnemonic**

"Keep first, XOR the rest"

**Question 1(c) [OR] (I) [2 marks]**

Write the full form of BCD and ASCII

**Solution****Table 6.** Full Forms of BCD and ASCII

Abbreviation	Full Form
BCD	Binary Coded Decimal
ASCII	American Standard Code for Information Interchange

**Mnemonic**

"Binary Codes Decimal values, American Standards Code Information"

**Question 1(c) [OR] (II) [2 marks]**

Write 1's and 2's complement of following binary numbers: (i) 1010 (ii) 1011

**Solution**

**1's Complement:** Invert all bits (change 0 to 1 and 1 to 0)

**2's Complement:** Take 1's complement and add 1

**For 1010:**

- 1's complement: 0101
- 2's complement:  $0101 + 1 = 0110$

**For 1011:**

- 1's complement: 0100
- 2's complement:  $0100 + 1 = 0101$

**Table 7.** Complement Results

Binary	1's Complement	2's Complement
1010	0101	0110
1011	0100	0101

**Mnemonic**

"Flip all bits for 1's, Add one more for 2's"

**Question 1(c) [OR] (III) [3 marks]**

Perform subtraction using 2's complement method (i)  $(110110)_2 - (101010)_2$

**Solution**

To subtract using 2's complement method:

1. Find 2's complement of subtrahend
2. Add it to the minuend
3. Discard any carry beyond the bit width

**Subtraction:**  $(110110)_2 - (101010)_2$

**Step 1:** Find 2's complement of 101010

- 1's complement of 101010 = 010101
- 2's complement =  $010101 + 1 = 010110$

**Step 2:** Add  $110110 + 010110$

```

  1 1 1 1 1
  1 1 0 1 1 0
+ 0 1 0 1 1 0
-----
  0 0 1 1 0 0

```

**Step 3:** Result is  $001100 = (12)_{10}$

**Table 8.** Subtraction Process

Step	Operation	Result
1	2's complement of 101010	010110
2	Add $110110 + 010110$	001100
3	Final result (decimal)	12

**Mnemonic**

"Complement the subtracted, add them up, carry goes away"

**Question 2(a) [3 marks]**

Draw logic circuit of AND, OR and NOT gate using NAND gate only

**Solution**

**AND gate using NAND gates:**


- AND gate = NAND gate followed by NOT gate (NAND gate)

**OR gate using NAND gates:**

- OR gate = Apply NOT (NAND gate) to both inputs, then NAND those results

**NOT gate using NAND gate:**

- NOT gate = NAND gate with both inputs tied together

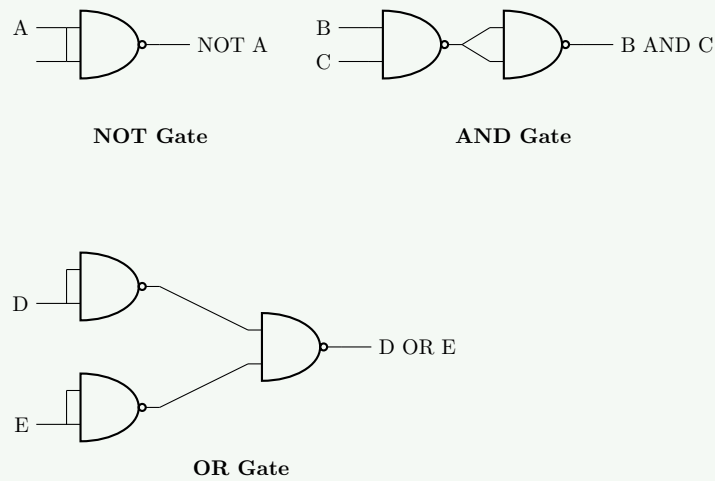**Mnemonic**

"NAND alone for NOT, NAND twice for AND, NAND each then NAND again for OR"


**Question 2(b) [4 marks]**

Draw/Write logic symbol, truth table and equation of following logic gates (i) XOR gate  
(ii) OR gate

**Solution**

**XOR Gate:**

**Logic Symbol:**

 


**Truth Table:**

A	B	Y ( $A \oplus B$ )
0	0	0
0	1	1
1	0	1
1	1	0

**Boolean Equation:**  $Y = A \oplus B = A'B + AB'$

**OR Gate:**

**Logic Symbol:**

 

**Truth Table:**

A	B	Y (A+B)
0	0	0
0	1	1
1	0	1
1	1	1

**Boolean Equation:**  $Y = A + B$

### Mnemonic

"XOR: Exclusive OR - one or the other but not both; OR: one or the other or both"

## Question 2(c)(I) [3 marks]

Simplify the Boolean expression using algebraic method  $Y = A + B[AC + (B + \overline{C})D]$

### Solution

**Step-by-step simplification:**

$$Y = A + B[AC + (B + \overline{C})D]$$

$$Y = A + B[AC + BD + \overline{C}D]$$

$$Y = A + BAC + BBD + B\overline{C}D$$

$$Y = A + ABC + BD + B\overline{C}D \quad (\text{Since } BB = B)$$

$$Y = A + AC + BD + B\overline{C}D \quad (\text{Absorption: } A + AB = A)$$

$$Y = A + BD + B\overline{C}D \quad (\text{Absorption: } A + AC = A)$$

$$Y = A + BD(1 + \overline{C})$$

$$Y = A + BD \quad (\text{Since } 1 + X = 1)$$

**Final expression:**  $Y = A + BD$

**Table 9.** Simplification Steps

Step	Expression	Law Applied
1	$A + B[AC + (B + \overline{C})D]$	Initial
2	$A + B[AC + BD + \overline{C}D]$	Distributive
3	$A + BAC + BBD + B\overline{C}D$	Distributive
4	$A + ABC + BD + B\overline{C}D$	Idempotent ( $BB = B$ )
5	$A + AC + BD + B\overline{C}D$	Absorption
6	$A + BD + B\overline{C}D$	Absorption ( $A + AC = A$ )
7	$A + BD(1 + \overline{C})$	Factoring
8	$A + BD$	Identity law

### Mnemonic

"Always look for idempotence, absorption, and complement patterns"

## Question 2(c)(II) [4 marks]

Simplify the Boolean expression using Karnaugh Map  $F(A,B,C) = \Sigma m(0, 2, 3, 4, 5, 6)$

### Solution

**K-map for  $F(A, B, C) = \Sigma m(0, 2, 3, 4, 5, 6)$ :**

		BC			
A		00	01	11	10
	0	1	0	0	1
	1	1	1	0	1

**Group the 1s:**

- Group 1:  $m(0,4)$  - corresponds to  $B'C'$
- Group 2:  $m(2,6)$  - corresponds to  $BC'$
- Group 3:  $m(4,5)$  - corresponds to  $AB'$

**Simplified expression:**  $F(A, B, C) = B'C' + BC' + AB'$

**Result:**  $F = C'(B' + B) + AB' = C' + AB'$

### Mnemonic

"Group adjacent 1s in powers of 2"

## Question 2 [OR] (a) [3 marks]

Draw logic circuit of AND, OR and NOT gate using NOR gate only

### Solution

**NOT gate using NOR gate:**

- NOT gate = NOR gate with both inputs tied together


**AND gate using NOR gates:**

- AND gate = Apply NOT (NOR gate) to both inputs, then NOR those results again

**OR gate using NOR gates:**

- OR gate = NOR gate followed by NOT gate (NOR gate)

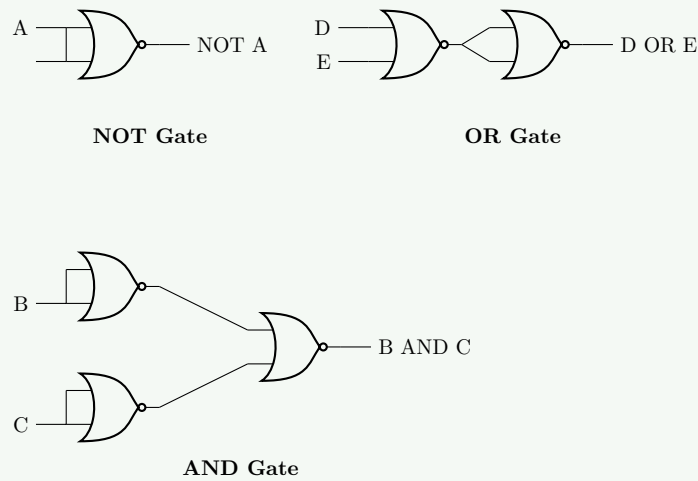

**Figure 2.** Universal Gates implementation (NOR)**Mnemonic**


"NOR alone for NOT, NOT each then NOR for AND, Double NOR for OR"

**Question 2 [OR] (b) [4 marks]**

Draw/Write logic symbol, truth table and equation of following logic gates (i) NOR gate  
(ii) AND gate

**Solution**

**NOR Gate:**  
**Logic Symbol:**

 


**Truth Table:**

A	B	Y (A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

**Boolean Equation:**  $Y = (A + B)' = A'B'$

**AND Gate:**  
**Logic Symbol:**

 

**Truth Table:**

A	B	Y (A·B)
0	0	0
0	1	0
1	0	0
1	1	1

**Boolean Equation:**  $Y = A \cdot B$

### Mnemonic

"NOR: NOT OR - neither one nor the other; AND: both must be 1"

## Question 2 [OR] (c) [7 marks]

Write the Boolean expression of Q for above logic circuit. Simplify the Boolean expression of Q and draw the logic circuit of simplified circuit using AND-OR-Invert method

### Solution

**Step 1:** Write Boolean expression from the circuit:  $Q = (A + B) \cdot (B + C \cdot ((B + C)'))$

$$Q = (A + B) \cdot (B + C \cdot (B' \cdot C'))$$

$$Q = (A + B) \cdot (B + C \cdot B' \cdot C')$$

**Step 2:** Simplify the expression:

- Note that  $C \cdot C' = 0$
- Therefore,  $C \cdot B' \cdot C' = 0$
- So  $Q = (A + B) \cdot (B + 0) = (A + B) \cdot B = A \cdot B + B \cdot B = A \cdot B + B = B + A \cdot B = B(1 + A) = B$

**Step 3:** Final simplified expression:  $Q = B$

**Step 4:** AND-OR-Invert implementation of  $Q = B$ :

- This is simply a wire from input B to output Q

B ————— Q

**Table 10.** Simplification Steps

Step	Expression	Simplification
1	$(A + B) \cdot (B + C \cdot ((B + C)'))$	Original expression
2	$(A + B) \cdot (B + C \cdot B' \cdot C')$	Applying De Morgan's
3	$(A + B) \cdot (B + 0)$	$C \cdot C' = 0$
4	$(A + B) \cdot B$	Simplifying
5	$A \cdot B + B \cdot B$	Distributive property
6	$A \cdot B + B$	Idempotent property ( $B \cdot B = B$ )
7	$B(1 + A)$	Factoring
8	$B$	$1 + A = 1$

### Mnemonic

"When complementary variables multiply, they zero out"

## Question 3(a) [3 marks]

Define combinational circuit. Give two examples of combinational circuits

**Solution**

**Combinational circuit:** A digital circuit whose output depends only on the current input values and not on previous inputs or states. In combinational circuits, there is no memory or feedback.

**Key characteristics:**

- Output depends only on current inputs
- No memory elements
- No feedback paths

**Examples of combinational circuits:**

1. Multiplexers (MUX)
2. Decoders
3. Adders/Subtractors
4. Encoders
5. Comparators

**Table 11.** Combinational vs Sequential Circuits

Characteristic	Combinational Circuit	Sequential Circuit
Memory	No	Yes
Feedback	No	Usually
Output depends on	Current inputs only	Current and previous inputs
Examples	Multiplexers, Adders	Flip-flops, Counters

**Mnemonic**


"Combinational circuits: Current In, Current Out - no memory about"

**Question 3(b) [4 marks]**

**Explain half adder using logic circuit and truth table**

**Solution**

**Half Adder:** A combinational circuit that adds two binary digits and produces sum and carry outputs.

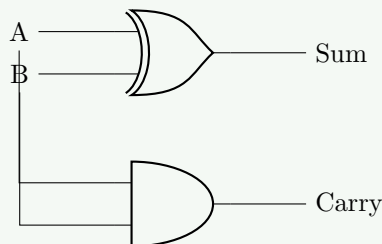**Logic Circuit:****Truth Table:**

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

**Boolean Equations:**

- $\text{Sum} = A \oplus B = A'B + AB'$
- $\text{Carry} = A \cdot B$

**Limitations:**

- Cannot add three binary digits
- Cannot accommodate carry input from previous stage

**Mnemonic**

"XOR for Sum, AND for Carry"

**Question 3(c)(I) [3 marks]**

**Explain multiplexer in brief**

**Solution**


**Multiplexer (MUX):** A combinational circuit that selects one of several input signals and forwards it to a single output line based on select lines.

**Key features:**

- Acts as a digital switch
- Has  $2^n$  data inputs,  $n$  select lines, and 1 output
- Select lines determine which input is connected to output

**Common multiplexers:**

- 2:1 MUX (1 select line)
- 4:1 MUX (2 select lines)
- 8:1 MUX (3 select lines)

 **Basic structure:****Applications:**

- Data routing
- Data selection
- Parallel to serial conversion
- Implementation of Boolean functions

**Mnemonic**

"Many In, Selection picks, One Out"

**Question 3(c)(II) [4 marks]**

**Design 8:1 multiplexer. Write its truth table and draw its logic circuit**


**Solution****8:1 Multiplexer Design:**

- 8 data inputs ( $I_0$  to  $I_7$ )
- 3 select lines ( $S_2, S_1, S_0$ )
- 1 output (Y)

**Truth Table:**

$S_2$	$S_1$	$S_0$	Output Y
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

**Boolean Equation:**  $Y = S_2' S_1' S_0' I_0 + S_2' S_1' S_0 I_1 + S_2' S_1 S_0' I_2 + S_2' S_1 S_0 I_3 + S_2 S_1' S_0' I_4 + S_2 S_1' S_0 I_5 + S_2 S_1 S_0' I_6 + S_2 S_1 S_0 I_7$

 **Logic Circuit:****Mnemonic**


"Eight inputs, three selects, decode and OR to output"

**Question 3 [OR] (a) [3 marks]**

Draw the block diagram of 4-bit binary parallel adder

**Solution**

**4-bit Binary Parallel Adder:** A circuit that adds two 4-bit binary numbers and produces a 4-bit sum and a carry output.

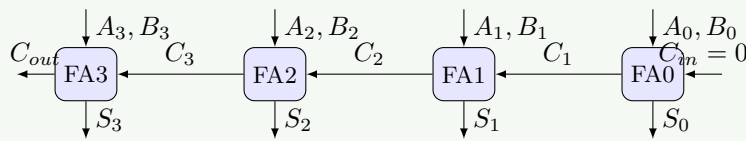**Components:**

- Four full adders (FA) connected in cascade
- Each FA adds corresponding bits and the carry from previous stage
- Initial carry-in ( $C_{in}$ ) is typically 0

**Mnemonic**

"Four FAs linked, carries ripple through"


### Question 3 [OR] (b) [4 marks]

Explain full adder using logic circuit and truth table

**Solution**

**Full Adder:** A combinational circuit that adds three binary digits (two inputs and a carry-in) and produces sum and carry outputs.

**Logic Circuit:**

 

**Truth Table:**

A	B	$C_{in}$	Sum	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Boolean Equations:**

- $\text{Sum} = A \oplus B \oplus C_{in}$
- $C_{out} = AB + C_{in}(A \oplus B)$

**Mnemonic**

"XOR all three for Sum, OR the ANDs for Carry"


**Question 3 [OR] (c)(I) [3 marks]**

Explain 4:1 multiplexer using logic circuit and truth table

**Solution**

**4:1 Multiplexer:** A digital switch that selects one of four input lines and connects it to the output based on two select lines.

**Logic Circuit:**

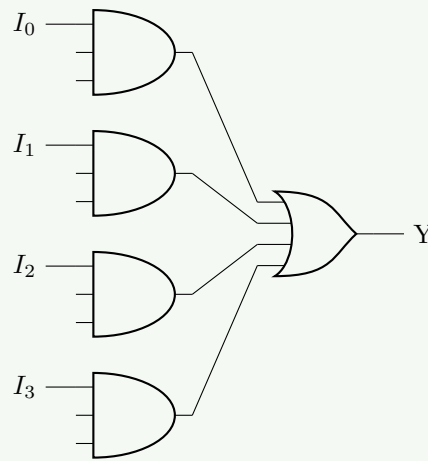

**Truth Table:**

$S_1$	$S_0$	Output Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

**Boolean Equation:**  $Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$

**Mnemonic**

"Two select lines choose one of four inputs"

**Question 3 [OR] (c)(II) [4 marks]**


Design 8:1 multiplexer using two 4:1 multiplexer.

**Solution**

**Design approach:** Use two 4:1 MUXes and one 2:1 MUX to create an 8:1 MUX.

1. First 4:1 MUX handles inputs  $I_0 - I_3$  using select lines  $S_0, S_1$
2. Second 4:1 MUX handles inputs  $I_4 - I_7$  using select lines  $S_0, S_1$
3. 2:1 MUX selects between outputs of the two 4:1 MUXes using  $S_2$

**Block Diagram:**

 

**Truth Table:**

$S_2$	$S_1$	$S_0$	Output Y
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

#### Mnemonic

"S0,S1 select from each 4:1 MUX, S2 selects between them"

## Question 4(a) [3 marks]

Define sequential circuit. Give two examples of it

#### Solution

**Sequential Circuit:** A digital circuit whose output depends not only on the current inputs but also on the past sequence of inputs (history/previous states).

**Key characteristics:**

- Contains memory elements (flip-flops)
- Output depends on both current inputs and previous states
- Usually incorporates feedback paths
- Requires clock signals for synchronization (for synchronous circuits)

**Examples of sequential circuits:**

1. Flip-flops (SR, JK, D, T)
2. Registers (shift registers)
3. Counters (binary, decade, ring counters)
4. State machines
5. Memory units

**Table 12.** Sequential vs Combinational Circuits



Characteristic	Sequential Circuit	Combinational Circuit
Memory	Yes	No
Feedback	Usually	No
Output depends on	Current & previous inputs	Current inputs only
Clock required	Usually	No
Examples	Flip-flops, Counters	Multiplexers, Adders

**Mnemonic**

"Sequential remembers history, combinational only knows now"

**Question 4(b) [4 marks]****Design decade counter****Solution**

**Decade Counter:** A sequential circuit that counts from 0 to 9 (decimal) and then resets to 0.

**Design using JK flip-flops:**

- Requires 4 JK flip-flops ( $Q_3, Q_2, Q_1, Q_0$ ) to represent 4-bit binary number
- Counts from 0000 to 1001 (0-9 decimal) then resets


**J-K Input Equations:**

- $J_0 = K_0 = 1$  (toggle on every clock)
- $J_1 = K_1 = Q_0 \cdot \overline{Q_3}$
- $J_2 = K_2 = Q_1 \cdot Q_0$
- $J_3 = K_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$  (Simplified for BCD)

*Note: Standard asynchronous (ripple) or synchronous design can be used. Ripple is simpler: Asynchronous*

**Decade Counter Logic:**

- Cascade 4 JK FFs.
- Reset condition: When count reaches 10 (1010), clear all FFs.
- NAND gate connected to CLR inputs, inputs to NAND are  $Q_3$  and  $Q_1$ .

 **Block Diagram (Asynchronous/Ripple):****Mnemonic**

"Count BCD, reset after 9"


**Question 4(c)(I) [3 marks]**

Explain S-R flip-flop using NOR gate. Draw its logic symbol and write its truth table.


**Solution**

**S-R Flip-flop using NOR gates:** A basic flip-flop constructed from two cross-coupled NOR gates that can store one bit of information.

**Logic Circuit:**

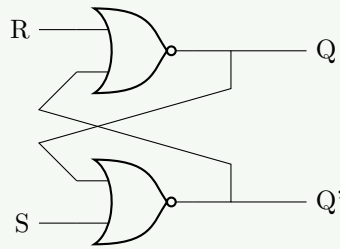

**Logic Symbol:**

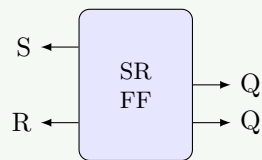

**Truth Table:**

S	R	Q (next)	Q' (next)	Operation
0	0	Q (prev)	Q' (prev)	Memory (no change)
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Invalid (avoid)

**Mnemonic**

"S sets to 1, R resets to 0, both active gives invalid state"


**Question 4(c)(II) [4 marks]**

**Explain S-R flip-flop using NAND gate. Write the limitation of SR flip flop**

**Solution**

**S-R Flip-flop using NAND gates:** A basic flip-flop constructed from two cross-coupled NAND gates.

**Logic Circuit:**

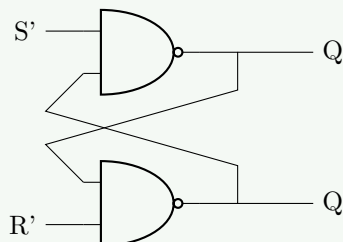

**Limitations of SR Flip-flop:**

1. **Invalid state:** When both  $S=1$ ,  $R=1$  (for NOR) or  $S=0$ ,  $R=0$  (for NAND), the output is unpredictable
2. **Race condition:** When inputs change simultaneously, the final state can be unpredictable
3. **No clocking mechanism:** Cannot synchronize with other digital components
4. **Not edge-triggered:** Cannot respond to brief pulses reliably
5. **Unwanted toggling:** May respond to noise or glitches

**Table 13.** NAND vs NOR SR Flip-flop

Characteristic	NAND SR Flip-flop	NOR SR Flip-flop
Active inputs	Low (0)	High (1)
Inactive inputs	High (1)	Low (0)
Invalid state	S=0, R=0	S=1, R=1

**Mnemonic**

"NAND: active-low inputs, NOR: active-high inputs; both have an invalid state"

**Question 4 [OR] (a) [3 marks]**

Write the definition of flip-flop. List the types of flip-flops

**Solution**

**Flip-flop:** A basic sequential digital circuit that can store one bit of information and has two stable states (0 or 1). It serves as a basic memory element in digital systems.

**Key characteristics:**

- Bistable multivibrator (two stable states)
- Can maintain its state indefinitely until directed to change
- Forms the basic building block for registers, counters, and memory circuits
- Can be triggered by clock signals (synchronous) or level changes (asynchronous)

**Types of Flip-flops:**

Flip-flop Type	Description
SR (Set-Reset)	The most basic flip-flop with set and reset inputs
JK	Improved version of SR that eliminates invalid state
D (Data)	Stores the value at input D, used for data storage
T (Toggle)	Changes state when triggered, useful for counters
Master-Slave	Two-stage flip-flop that prevents race conditions

**Mnemonic**

"Storing a Single Step: SR, JK, D, T"

**Question 4 [OR] (b) [4 marks]**

Design 3-bit ring counter


**Solution**

**Ring Counter:** A circular shift register where only one bit is set (1) and all others are reset (0). The single set bit "rotates" around the register when clocked.

**Design using D flip-flops:**

- Requires 3 D flip-flops for 3-bit counter
- Initial state: 100, then cycles through 010, 001, and back to 100

**Block Diagram:**

 

Note: Diagram simplified.  $Q_2$  output connects back to  $D_0$  input.

### Mnemonic

"One hot bit travels in a circle"


## Question 4 [OR] (c)(I) [3 marks]

Explain J-K flip-flop using its logic symbol and truth table

### Solution

**J-K Flip-flop:** An improved version of SR flip-flop that eliminates the invalid state and provides predictable behavior in all input combinations.

**Logic Symbol:**

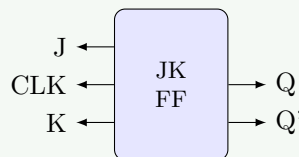

**Truth Table:**

J	K	Q (next)	Operation
0	0	Q (prev)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q' (prev)	Toggle

### Mnemonic

"J sets, K resets, Both toggle, None remember"

## Question 4 [OR] (c)(II) [4 marks]


Draw logic circuit of D flip-flop and T flip-flop using J-K flip-flop

### Solution


**D Flip-flop using JK Flip-flop:**

- Connect D input to J
- Connect D' (NOT D) to K

**Logic Circuit:**

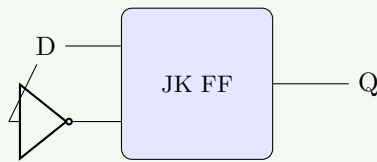**T Flip-flop using JK Flip-flop:**

- Connect T input to both J and K

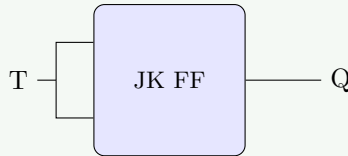**Logic Circuit:****Mnemonic**

"D directly follows, T toggles when true"

**Question 5(a) [3 marks]****Compare RAM and ROM****Solution****RAM (Random Access Memory) vs ROM (Read-Only Memory):****Table 14.** RAM vs ROM Comparison

Characteristic	RAM	ROM
Full form	Random Access Memory	Read-Only Memory
Data retention	Volatile (loses data when power off)	Non-volatile (retains data without power)
Read/Write capability	Both read and write operations	Primarily read-only (except in PROM, EPROM, EEPROM)
Speed	Faster	Slower
Cost per bit	Higher	Lower
Applications	Temporary data storage, active program execution	Boot instructions, firmware, permanent data
Types	SRAM, DRAM	Mask ROM, PROM, EPROM, EEPROM, Flash

**Mnemonic**

"RAM Reads And Modifies (but forgets), ROM Remembers On shutdown (but fixed)"

**Question 5(b) [4 marks]****Explain Serial In Serial Out shift register**

**Solution**

**Serial In Serial Out (SISO) Shift Register:** A sequential circuit that shifts data one bit at a time both at input and output.

**Operation:**

- Data enters serially one bit at a time
- Each bit shifts through the register on each clock pulse
- Data exits serially one bit at a time
- First-in, first-out operation

**Block Diagram:****Applications:**

- Data transmission between digital systems
- Serial-to-serial data conversion
- Time delay circuits

**Mnemonic**

"Bits enter line, march through chain, exit in sequence"

**Question 5(c) [7 marks]**

Write short note on logic families

**Solution**

**Logic Families:** Groups of digital integrated circuits with similar electrical characteristics, fabrication technology, and logic implementations.

**Major Logic Families:****1. TTL (Transistor-Transistor Logic):**

- Based on bipolar junction transistors
- Standard series: 7400
- Supply voltage: 5V
- Moderate speed and power consumption
- High noise immunity

**2. CMOS (Complementary Metal-Oxide-Semiconductor):**

- Based on MOSFETs (P-type and N-type)
- Standard series: 4000, 74C00
- Wide supply voltage range (3-15V)
- Very low power consumption
- High noise immunity

**3. ECL (Emitter-Coupled Logic):**

- Based on differential amplifier with emitter-coupled transistors
- Extremely high speed (fastest logic family)
- High power consumption

**Table 15.** Comparison of Logic Families

Parameter	TTL	CMOS	ECL
Speed	Medium	Low to High	Very High
Power consumption	Medium	Very Low	High
Noise immunity	High	Very High	Low
Fan-out	10	50+	25
Supply voltage	5V	3-15V	-5.2V

**Mnemonic**

"TTL Takes Transistors, CMOS Conserves More Operational Supply, ECL Executes Calculations Lightning-fast"

**Question 5 [OR] (a) [3 marks]**

**Compare SRAM and DRAM**

**Solution**

**SRAM (Static RAM) vs DRAM (Dynamic RAM):**

**Table 16.** SRAM vs DRAM Comparison

Characteristic	SRAM	DRAM
Full form	Static Random Access Memory	Dynamic Random Access Memory
Storage element	Flip-flop	Capacitor
Refreshing	Not required	Required periodically (ms)
Speed	Faster	Slower
Density	Lower	Higher
Cost per bit	Higher	Lower
Applications	Cache memory	Main memory (RAM)

**Mnemonic**

"Static Stays steady with Six Transistors, Dynamic Drains and needs regular refreshing"

 
 
 
**Question 5 [OR] (b) [4 marks]**

**Explain 8:3 encoder**

**Solution**

**8:3 Encoder:** A combinational circuit that converts 8 input lines to 3 output lines, essentially converting an active input line to its binary position.

**Logic Circuit:**

**Boolean Equations:**

- $Y_0 = I_1 + I_3 + I_5 + I_7$
- $Y_1 = I_2 + I_3 + I_6 + I_7$
- $Y_2 = I_4 + I_5 + I_6 + I_7$

**Mnemonic**

"Eight Inputs become their position in Three bits"

**Question 5 [OR] (c) [7 marks]**

Define (i) Fan-in (ii) Fan-out (iii) Noise margin (iv) Propagation delay (v) Power dissipation for logic families

**Solution****Key Parameters of Logic Families:**

1. **Fan-in:** Maximum number of inputs a logic gate can accept. Determines complexity.
2. **Fan-out:** Maximum number of similar gates that one gate output can drive reliably.
3. **Noise margin:** The ability of a gate to tolerate electrical noise on its inputs without changing output state.
4. **Propagation delay:** The time delay between input change and corresponding output change. Measures speed (lower is better).
5. **Power dissipation:** The amount of power consumed by the gate (usually in mW). Lower is better for battery operation.

**Mnemonic**

"Fan in/out loads, Noise ignores, Delay waits, Power burns"