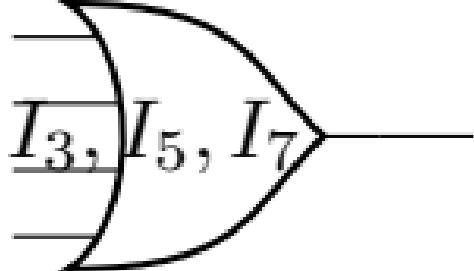
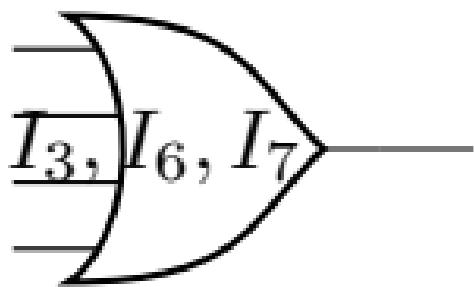


Inputs  $I_1, I_3, \underline{I_5}, I_7$  —  $Y_0$



Inputs  $I_2, I_3, \underline{I_6}, I_7$  —  $Y_1$



Inputs  $I_4, I_5, \underline{I_6}, I_7$  —  $Y_2$

