

# Subject Name Solutions

4311101 – Winter 2023

Semester 1 Study Material

*Detailed Solutions and Explanations*

## Question 1(a) [3 marks]

Define Power & Energy.

### Solution

- **Power:** Rate of doing work or energy consumption per unit time. Measured in Watts (W).
- **Energy:** Ability to do work or the work done. Measured in Joules (J) or Watt-hours (Wh).

Table 1: Power vs Energy

Parameter	Definition	Formula	Unit
Power	Rate of energy transfer	$P = W/t$	Watt (W)
Energy	Capacity to do work	$E = P \times t$	Joule (J) or Watt-hour (Wh)

### Mnemonic

“Power Performs, Energy Endures”

## Question 1(b) [4 marks]

Define current and electrical potential.

### Solution

#### Diagram:

flowchart LR

A[Electron Flow] --> B[Current]

C[Potential Energy] --> D[Voltage]

- **Current:** Flow of electric charge per unit time. Measured in Amperes (A).
- **Electrical Potential:** Work done per unit charge to move a charge from one point to another. Measured in Volts (V).

### Mnemonic

“Current Charges, Potential Pushes”


## Question 1(c) [7 marks]

Explain KCL and KVL with examples.

### Solution

#### Diagram:

```
+{--}{--}{--}{--}+      i1}
  |          ↓
  |      R1
+{--}{--}{--}{--}///{--}{--}{--}{--}+
  |          |
```

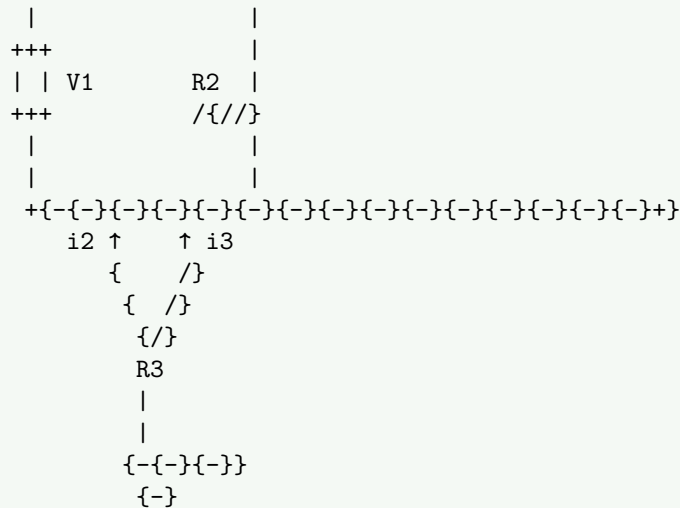

#### Kirchhoff's Current Law (KCL):

- Sum of currents entering a node equals sum of currents leaving it.
- Example: At node X,  $i1 + i2 = i3$

#### Kirchhoff's Voltage Law (KVL):

- Sum of voltage drops around any closed loop equals zero.
- Example:  $V1 - V(R1) - V(R2) = 0$

#### Mnemonic

"Currents Come-Leave, Voltages Voyage-Loop"

### Question 1(c) OR [7 marks]

Explain different types of connections for Resistors.

#### Solution

##### Diagram:

##### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    subgraph "Series Connection"
        A[R1] --> B[R2]
        B --> C[R3]
    end
    subgraph "Parallel Connection"
        D[R1]
        E[R2]
        F[R3]
        G --> D & E & F
        H
    end
{Highlighting}
{Shaded}
```

Table 2: Series vs Parallel Connection

Parameter	Series Connection	Parallel Connection
Total Resistance	$R_{eq} = R1 + R2 + R3 + \dots$	$1/R_{eq} = 1/R1 + 1/R2 + 1/R3 + \dots$
Current	Same through all resistors	Divides through each path
Voltage	Divides across resistors	Same across all resistors
Application	Voltage dividers	Current division

Mnemonic
“Series Sum, Parallel Parts”

Mnemonic
“Series Sum, Parallel Parts”

Question 2(a) [3 marks]

**Define Resistance and Resistivity. Also state their unit of measurement.**

**Solution**

- **Resistance:** Opposition to current flow, measured in Ohms ( $\Omega$ ).  $R = V/I$ .
- **Resistivity:** Material property indicating resistance per unit dimension, measured in Ohm-meter ( $\Omega \cdot m$ ).  $R = \rho L/A$ .

- Solution**

  - **Resistance:** Opposition to current flow, measured in Ohms ( $\Omega$ ).  $R = V/I$ .
  - **Resistivity:** Material property indicating resistance per unit dimension, measured in Ohm-meter ( $\Omega \cdot m$ ).  $R = \rho L/A$ .

**Mnemonic**  
“Resistance Restricts, Resistivity Relates to material”

**Mnemonic**  
“Resistance Restricts, Resistivity Relates to material”

Question 2(b) [4 marks]

**Define cell and write names of different types of cell.**

**Solution**

**Diagram:**

Battery

- **Cell:** Device that converts chemical energy into electrical energy creating a voltage.

**Types of Cells:**

1. **Primary cells:** Dry cell, Alkaline cell, Mercury cell
2. **Secondary cells:** Lead-acid, Nickel-Cadmium, Lithium-ion

**Solution**

**Diagram:**

Battery

- **Cell:** Device that converts chemical energy into electrical energy creating a voltage.

**Types of Cells:**

1. **Primary cells:** Dry cell, Alkaline cell, Mercury cell
2. **Secondary cells:** Lead-acid, Nickel-Cadmium, Lithium-ion

**Solution**

**Diagram:**

Battery

- **Cell:** Device that converts chemical energy into electrical energy creating a voltage.

**Types of Cells:**

1. **Primary cells:** Dry cell, Alkaline cell, Mercury cell
2. **Secondary cells:** Lead-acid, Nickel-Cadmium, Lithium-ion

- Solution**
- Diagram:**
- 
- Battery
- **Cell:** Device that converts chemical energy into electrical energy creating a voltage.
- Types of Cells:**
1. **Primary cells:** Dry cell, Alkaline cell, Mercury cell
  2. **Secondary cells:** Lead-acid, Nickel-Cadmium, Lithium-ion

**Solution**

**Diagram:**

Battery

- **Cell:** Device that converts chemical energy into electrical energy creating a voltage.

**Types of Cells:**

1. **Primary cells:** Dry cell, Alkaline cell, Mercury cell
2. **Secondary cells:** Lead-acid, Nickel-Cadmium, Lithium-ion

- Solution**
- Diagram:**
- 
- Battery
- **Cell:** Device that converts chemical energy into electrical energy creating a voltage.
- Types of Cells:**
1. **Primary cells:** Dry cell, Alkaline cell, Mercury cell
  2. **Secondary cells:** Lead-acid, Nickel-Cadmium, Lithium-ion

**Mnemonic**  
“Primary Produces once, Secondary Serves repeatedly”

**Mnemonic**  
“Primary Produces once, Secondary Serves repeatedly”

Question 2(c) [7 marks]

Calculate total equivalent resistance of the above circuit if  $R_1=5\Omega$ ,  $R_2=3\Omega$ ,  $R_3=4\Omega$ ,  $R_4=1\Omega$ ,  $R_5=2\Omega$ .

**Solution**

**Diagram:**

```

graph TD
    R1["R1  
/{ // }"]
    R1 --- N1["+{-}{-}{-}{-}{-}{-}+"]
    R1 --- N2["+{(-){(-){(-){(-){(-){(-)}}}}+"]
    N1 --- R2["R2 /{"]
    N1 --- R3["R3 ///"]
    N2 --- R5["R5 }"]
    N2 --- R4["R4 /}"]
    R2 --- N3["{/"]
    R4 --- N4["}/"]
    N3 --- R2
    N4 --- R4
  
```

**Solution**

**Diagram:**

```

graph TD
    R1["R1  
/{ // }"]
    R1 --- N1["+{-}{-}{-}{-}{-}{-}+"]
    R1 --- N2["+{(-){(-){(-){(-){(-){(-)}}}}+"]
    N1 --- R2["R2 /{"]
    N1 --- R3["R3 ///"]
    N2 --- R4["R4 /}"]
    N2 --- R5["R5 }"]
    R2 --- N3["{/"]
    R4 --- N4["}/"]
    N3 --- R2
    N4 --- R4
    
```

**Solution**

**Diagram:**

```

graph TD
    R1["R1  
/{ // }"]
    R1 --- N1["+{-}{-}{-}{-}{-}{-}+"]
    R1 --- N2["+{(-){(-){(-){(-){(-){(-)}}}}+"]
    N1 --- R2["R2 /{"]
    N1 --- R3["R3 ///"]
    N2 --- R4["R4 /}"]
    N2 --- R5["R5 }"]
    R2 --- N3["{ /"]
    R4 --- N4["} /"]
    N3 --- N5["|"]
    N4 --- N6["|"]
    N5 --- N7["|"]
    N286 --- N288["|"]
```

$$\begin{array}{c}
 +\{-\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\}+ \quad | \} \\
 \quad \quad \quad | \\
 \quad \quad \quad R4 \\
 \quad \quad \quad / \{ \{ \{ \quad | \} \\
 +\{-\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\}+ \quad +\{-\}\{-\}\{-\}\{-\}\{-\}\}+ \\
 | \quad \quad \quad | \\
 +\{-\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\{-\}\}+
 \end{array}$$

**Step-by-step solution:**

1. R2 and R3 are in series:  $R_{23} = R_2 + R_3 = 3\Omega + 4\Omega = 7\Omega$
2. R23 and R4 are in parallel:  $1/R_{234} = 1/7 + 1/1 = (1+7)/7 = 8/7$  Therefore,  $R_{234} = 7/8 = 0.875\Omega$
3. R1, R234, and R5 are in series:  $R_{eq} = R_1 + R_{234} + R_5 = 5\Omega + 0.875\Omega + 2\Omega = 7.875\Omega$

**Therefore, equivalent resistance = 7.875Ω**

**Mnemonic**

“Series-Sum, Parallel-Product over Sum”

**Question 2(a) OR [3 marks]**

Find the cost of energy if 100W bulb operated 10 hours daily for 30 days. Rate of energy is Rupees 5/unit.

Solution		
Table 3: Energy Calculation		
Parameter	Value	Calculation
Power	100W = 0.1kW	Given
Operating hours	10 hours/day × 30days = 300hours	Given
Energy consumed	0.1kW × 300h = 30kWh = 30units	E = P × t
Rate	Rs. 5/unit	Given
Total cost	30 units × Rs.5/unit = Rs.150	Cost = Units × Rate

Therefore, cost of energy = Rs. 150

**Mnemonic**

“Energy × Rate = Electric bill fate”

**Question 2(b) OR [4 marks]**

State ohm’s law and explain the use ohm’s law to calculate current in any circuit.

Solution
<p><b>Diagram:</b></p> <p style="text-align: center;">Mermaid Diagram (Code)</p> <pre> {Shaded} {Highlighting}[] graph LR     A[Voltage] {-{-}{-}} "V = IR"  B[Current]}     C[Resistance] {-{-}{-}} B} {Highlighting} {Shaded} </pre> <p><b>Ohm’s Law:</b> Current flowing through a conductor is directly proportional to voltage and inversely proportional to resistance.</p> <p><b>Formula:</b> <math>V = IR</math> or <math>I = V/R</math> or <math>R = V/I</math></p>

**Application:** To find current in a circuit, measure voltage across a component and divide by its resistance ( $I = V/R$ ).

**Mnemonic**

“Volts Invite current, Resistance Restricts”

Question 2(c) OR [7 marks]

Show that the current in a purely capacitive circuit leads the applied voltage by  $90^\circ$  and the current in a purely inductive circuit lags the applied voltage by  $90^\circ$ .

### Solution

Diagrams:

### Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    subgraph "Capacitive Circuit"
        A[Voltage] --{-}{-} B["Voltage = V sin(t)"]
        C[Current] --{-}{-} D["Current = I sin(t + 90°)"]
    end
    subgraph "Inductive Circuit"
        E[Voltage] --{-}{-} F["Voltage = V sin(t)"]
        G[Current] --{-}{-} H["Current = I sin(t {-} 90°)"]
    end
{Highlighting}
{Shaded}
```

**For Capacitive Circuit:**

- **Voltage equation:**  $v = V \sin(t)$
- **Current:**  
 $i = C \times dv/dt = CV \cos(t) = I \sin(t + 90^\circ)$
- **Current leads voltage by  $90^\circ$**

**For Inductive Circuit:**

- **Voltage equation:**  

$$v = L \times di/dt = LI \cos(t) = V \sin(t + 90^\circ)$$
- **Current:**  $i = I \sin(t)$
- **Current lags voltage by  $90^\circ$**

### Mnemonic

“ELI the ICE man” - In EL (inductor), I lags E; in ICE (capacitor), I leads E

Question 3(a) [3 marks]

Define cycle, form factor and amplitude.

#### Solution

Diagram:

Diagram.

$$\begin{array}{c}
 \backslash \sim \{ \} \\
 | \quad \quad / \{ \quad \quad / \} \\
 | \quad / \quad \{ \quad \quad / \quad \} \\
 A \{ - \{ - \} \{ - \} | \{ - \} \{ - \} / \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} / \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \} \\
 | \quad / \quad \quad \quad \{ / \quad \quad \} \\
 | / \quad \quad \quad \{ \} \\
 + \{ - \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \} \\
 | \{ - \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} \{ - \} | \}
 \end{array}$$

cycle

- Cycle: One complete repetition of a waveform.
- Form Factor: Ratio of RMS value to average value. For sine wave = 1.11.
- Amplitude: Maximum displacement of a waveform from its mean position.

#### Mnemonic

“Cycles Complete, Form Factors Find ratio, Amplitude Achieves maximum”

### Question 3(b) [4 marks]

Define RMS and Average value. Write expression of RMS and average value of sinusoidal waveform.

#### Solution

Table 4: RMS vs Average Value

Parameter	Definition	Formula for Sine Wave
RMS Value	Square root of mean of squared values	$V_{rms} = V_m / \sqrt{2} = 0.707 V_m$
Average Value	Mean of all instantaneous values over half cycle	$V_{avg} = 2V_m / \pi = 0.637 V_m$

- RMS (Root Mean Square): Equivalent DC value that produces same heating effect.
- Average Value: Mean of all instantaneous values over a half cycle.

#### Mnemonic

“RMS Relates to heating, Average Adds and divides”

### Question 3(c) [7 marks]

Explain the terms Apparent power, True Power and Reactive power. State their unit of measurement.

#### Solution

Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    subgraph "Power Triangle"
        A[True Power P] --- B[Apparent Power S]
        C[Reactive Power Q] --- B
    end
end
{Highlighting}
{Shaded}
```

Table 5: Types of Power

Power Type	Definition	Formula	Unit
Apparent Power (S)	Total power supplied	$S = VI$	VA (Volt-Ampere)
True Power (P)	Actual power consumed	$P = VI \cos$	W (Watt)
Reactive Power (Q)	Power oscillating between source and load	$Q = VI \sin$	VAR (Volt-Ampere Reactive)



## Solution

Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    subgraph "Star Connection"
        A1[R] --{-}{-}{-} D[Neutral]}
        B1[Y] --{-}{-}{-} D}
        C1[B] --{-}{-}{-} D}
    end

    subgraph "Delta Connection"
        A2[R] --{-}{-}{-} B2[Y]}
        B2 --{-}{-}{-} C2[B]}
        C2 --{-}{-}{-} A2}
    end
{Highlighting}
{Shaded}
```

Table 7: Star vs Delta Connection

Parameter	Star (Y) Connection	Delta ( $\Delta$ ) Connection
Line Voltage (VL)	$\sqrt{3} \times \text{Phase Voltage}$	Same as Phase Voltage
Line Current (IL)	Same as Phase Current	$\sqrt{3} \times \text{Phase Current}$
Neutral Wire	Present	Absent
Application	Unbalanced loads, Residential	Balanced loads, Industrial

## Mnemonic

“Star Shows neutral, Delta Delivers higher current”

## Question 4(a) [3 marks]

Calculate the peak to peak value of a sinusoidal voltage if RMS value is 230V.

## Solution

Table 8: Calculation Steps

Parameter	Formula	Calculation
RMS Value	Given	230V
Peak Value	$V_m = \sqrt{2} \times V_{rms}$	$V_m = \sqrt{2} \times 230 = 325.27V$
Peak-to-Peak Value	$V_{p-p} = 2 \times V_m$	$V_{p-p} = 2 \times 325.27 = 650.54V$

Therefore, peak-to-peak value = 650.54V

## Mnemonic

“RMS to Peak - multiply by  $\sqrt{2}$ , Peak to Peak – double it”

## Question 4(b) [4 marks]

An alternating current is given by  $i = 142.14 \sin 628t$  find frequency and time period.



### Solution

Table 9: Calculation Steps

Parameter	Formula	Calculation
Given equation	$i = 142.14 \sin(628t)$	$= 628 \text{ rad/s}$
Frequency	$f = \omega / (2\pi)$	$f = 628 / (2\pi) = 100 \text{ Hz}$
Time Period	$T = 1/f$	$T = 1/100 = 0.01 \text{ s} = 10 \text{ ms}$

Therefore, frequency = 100 Hz and time period = 0.01 s

### Mnemonic

“Frequency From omega divide 2 , Time takes inverse”


### Question 4(c) [7 marks]

State and explain Fleming’s left hand rule and right hand rule.


### Solution

Diagram:

Left Hand Rule

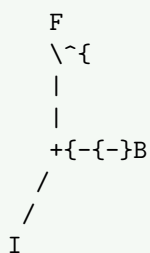

Right Hand Rule

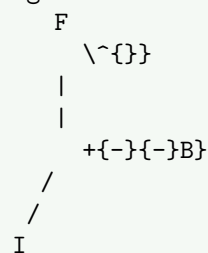

Fleming’s Left Hand Rule (Motor):

- Used to determine direction of force on a current-carrying conductor in a magnetic field.
- Hold left hand with thumb, fore and middle fingers at right angles.
- Thumb: Motion (Force)
- Forefinger: Magnetic field
- Middle finger: Current

Fleming’s Right Hand Rule (Generator):

- Used to determine direction of induced current when a conductor moves in a magnetic field.
- Hold right hand with thumb, fore and middle fingers at right angles.
- Thumb: Motion of conductor
- Forefinger: Magnetic field
- Middle finger: Induced current

### Mnemonic

“Left Lifts motors, Right Raises generators”

### Question 4(a) OR [3 marks]

A conductor of length 1 metre moves with speed of 30m/s in magnetic field of 0.6 Tesla making angle of  $30^\circ$  with the field. Calculate dynamically EMF induced in it. (use  $\sin 30^\circ = 0.5$ )

### Solution

Table 10: Given Parameters



**Mnemonic**

“Static Stays but flux Changes, Dynamic Drives through field”

Question 5(a) [3 marks]

### Explain PV Cell.

## Solution

Diagram:

```
Sun Rays  
|||  
vvv  
+{-}{-}{-}{-}{-}{-}{-}+}  
| N |  
|{-}{-}{-}{-}{-}{-}{-}| {-} P{-}N Junction}  
| P |  
+{-}{-}{-}{-}{-}{-}{-}+}  
| |  
| |  
Load
```

- PV Cell: Device that converts sunlight directly into electricity using photovoltaic effect.
- Working: Sunlight excites electrons in semiconductor material, creating voltage difference.
- Material: Typically made from silicon with P-N junction.

- **PV Cell:** Device that converts sunlight directly into electricity using photovoltaic effect.
- **Working:** Sunlight excites electrons in semiconductor material, creating voltage difference.
- **Material:** Typically made from silicon with P-N junction.

**Mnemonic**

“Photons Visit, Current Created”

Question 5(b) [4 marks]

**Explain the solar PV panel and arrays.**

### Solution

Diagram:

**Mermaid Diagram (Code)**

```
{Shaded}
{Highlighting}[]
graph LR
    A[Solar Cell] {-{-}{}}|"Multiple cells in series"| B[Solar Panel]}
    B {-{-}{}}|"Multiple panels connected"| C[Solar Array]}
{Highlighting}
{Shaded}
```

Table 12: Solar System Hierarchy

Component	Description
PV Cell	Basic unit that converts sunlight to electricity (0.5V - 0.6V)
PV Panel	Multiple cells connected in series/parallel (typically 12V, 24V)
PV Array	Multiple panels connected to achieve required voltage/current

### Mnemonic

“Cells Combine into Panels, Panels Produce Arrays”

### Question 5(c) [7 marks]

Draw and explain block diagram of wind power system.

#### Solution

Diagram:

flowchart LR

```
A[Wind Turbine] -- "Mechanical energy" --> B[Gearbox]
B -- "High speed rotation" --> C[Generator]
C -- "AC power" --> D[Power Electronics]
D -- "Controlled output" --> E[Transformer]
E -- "Grid-compatible power" --> F[Grid/Load]
G[Control System] -. "A & C & D" .-> A
```

Components of Wind Power System:

1. **Wind Turbine:** Converts wind energy to mechanical energy
2. **Gearbox:** Increases rotational speed for generator
3. **Generator:** Converts mechanical energy to electrical energy
4. **Power Electronics:** Controls and regulates electrical output
5. **Transformer:** Steps up/down voltage for transmission/distribution
6. **Control System:** Monitors and optimizes overall operation

### Mnemonic

“Wind Turns Gears, Generating Electrical Returns”

### Question 5(a) OR [3 marks]

State the benefits of green energy.

#### Solution

Table 13: Benefits of Green Energy

Benefit Category	Examples
Environmental	Reduces pollution, Minimizes carbon footprint
Economic	Creates jobs, Reduces energy dependency
Health	Improves air quality, Reduces health issues
Sustainability	Renewable, Inexhaustible sources

### Mnemonic

“Clean Energy Creates Economic Salvation”

### Question 5(b) OR [4 marks]

Explain Solar PV applications in brief.

#### Solution

Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting} []
```

```
graph TD
    A[Solar PV Applications] --> B[Residential]
    A --> C[Commercial]
    A --> D[Industrial]
    A --> E[Utility Scale]
    A --> F[Off-grid]
    {Highlighting}
    {Shaded}
```

#### Solar PV Applications:

1. Residential: Rooftop systems, Solar water heaters
2. Commercial: Building integrated PV, Solar parking
3. Industrial: Process heating, Power generation
4. Utility Scale: Solar farms, Grid support
5. Off-grid: Rural electrification, Remote applications

#### Mnemonic

“Residences, Commerce, Industry Utilize Solar”

### Question 5(c) OR [7 marks]

Explain different types of Green energy.

#### Solution

Table 14: Types of Green Energy

Type	Source	Applications
Solar	Sun	PV systems, Thermal plants
Wind	Moving air	Wind turbines, Windmills
Hydro	Flowing water	Dams, Run-of-river systems
Biomass	Organic matter	Combustion, Biogas production
Geothermal	Earth's heat	Direct heating, Power plants
Tidal	Ocean tides	Barrage systems, Tidal turbines

#### Diagram:

```
pie title "Green Energy Sources"
    "Solar" : 30
    "Wind" : 25
    "Hydro" : 20
    "Biomass" : 15
    "Geothermal" : 7
    "Tidal" : 3
```

#### Mnemonic

“Sun, Wind, Hydro, Biomass, Geothermal, Tidal - Simple Ways Humans Build Green Tomorrow”