

Elements of Electrical & Electronics Engineering (1313202) - Winter 2023

Solution

Milav Dabgar

January 17, 2024

Question 1(a) [3 marks]

Explain difference between Active and passive network.

Solution

| Active Network | Passive Network |
|---|--|
| Contains at least one energy source | Contains no energy source |
| Can deliver power to other elements | Cannot deliver power to other elements |
| Examples: Transistors, Op-amps, Batteries | Examples: Resistors, Capacitors, Inductors |

Mnemonic

“Active Adds Power, Passive Pulls Power”

Question 1(b) [4 marks]

State and explain Kirchhoff's voltage law (KVL).

Solution

Kirchhoff's Voltage Law (KVL): The algebraic sum of all voltages around any closed path (loop) in a circuit is zero.

Mathematical Form: $\sum V = 0$ or $V_1 + V_2 + V_3 + V_4 = 0$

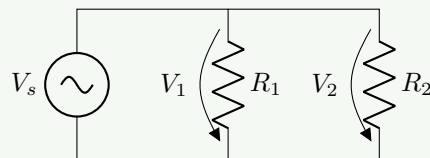


Figure 1. Closed Loop for KVL

- **Circuit Application:** When moving around a loop, voltage rises (batteries) are positive and voltage drops (components) are negative.
- **Physical Meaning:** Total energy in a closed loop is conserved.

Mnemonic

“Voltage Loop Sum Zero”

Question 1(c) [7 marks]

Define the following terms: (1) Charge (2) Current (3) Potential (4) E.M.F. (5) Inductance (6) Capacitance (7) Frequency.

Solution

| Term | Definition |
|--------------------|--|
| Charge | The basic electrical quantity measured in coulombs (C); flow of electrons creates electricity. |
| Current | The rate of flow of electric charge, measured in amperes (A); $I = dQ/dt$. |
| Potential | Electric potential energy per unit charge, measured in volts (V). |
| E.M.F. | Electromotive force, energy supplied by source per unit charge, measured in volts (V). |
| Inductance | Property of a conductor to oppose change in current, measured in henry (H). |
| Capacitance | Ability of a component to store electric charge, measured in farad (F). |
| Frequency | Number of cycles per second of an alternating quantity, measured in hertz (Hz). |

Mnemonic

“Careful Currents Pass Easily Into Circuit Frequently”

Question 1(c) OR [7 marks]

State Ohm’s law. Write its application and limitation.

Solution

Ohm’s Law: The current flowing through a conductor is directly proportional to the potential difference across it and inversely proportional to its resistance.

Mathematical Form: $I = V/R$

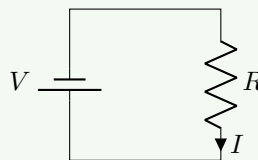


Figure 2. Ohm’s Law Circuit

Applications of Ohm’s Law:

- Computing current, voltage, resistance in circuits.
- Design of electrical networks.
- Power calculations ($P = VI = I^2R = V^2/R$).
- Voltage division and current division.

Limitations of Ohm’s Law:

- Not valid for non-linear elements (diodes, transistors).
- Not applicable at very high frequencies.
- Not valid for non-metallic conductors like semiconductors.
- Not applicable for vacuum tubes and gaseous devices.

Mnemonic

“Voltage Drives, Resistance Restricts”

Question 2(a) [3 marks]

Draw and explain energy band diagrams for insulator, conductor and Semiconductor.

Solution

Energy Band Diagrams:

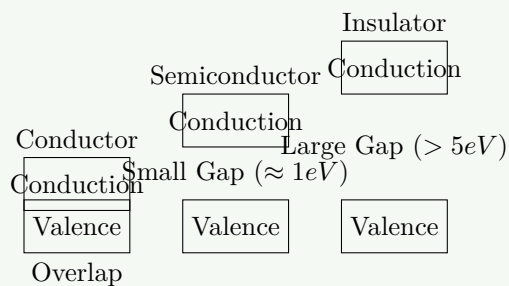


Figure 3. Energy Band Diagrams

- **Conductor:** Valence and conduction bands overlap, allowing easy electron flow.
- **Semiconductor:** Small energy gap ($\approx 1 \text{ eV}$) between bands; electrons can jump with thermal energy.
- **Insulator:** Large energy gap ($> 5 \text{ eV}$) prevents electron movement between bands.

Mnemonic


“Conductors Connect, Semiconductors Sometimes, Insulators Impede”

Question 2(b) [4 marks]

Write statement of Maximum power transfer theorem and reciprocity theorem.

Solution

| Theorem | Statement |
|---------------------------------------|--|
| Maximum Power Transfer Theorem | Maximum power is transferred from source to load when load resistance equals the source internal resistance ($R_L = R_S$). |
| Reciprocity Theorem | In a linear passive network with a single source, if the source is moved from position A to B, the current at A due to source at B will equal the current at B when source was at A. |

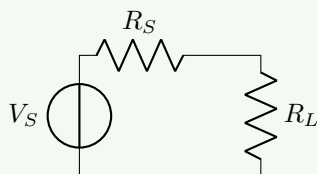

Max Power when $R_L = R_S$

Mnemonic

“Match Resistance to Maximize Power; Switch Source and Sink, Current Stays Same”

Question 2(c) [7 marks]

Explain the formation and conduction of N-type materials.

Solution

N-type Semiconductor Formation:

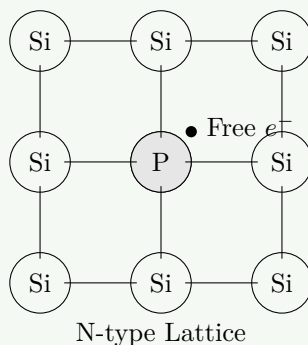


Figure 4. Pentavalent Doping (N-type)

- **Doping Process:** Silicon/Germanium (4 valence e^-) doped with pentavalent elements (P, As, Sb).
- **Extra Electron:** Each dopant atom provides 1 extra electron after covalent bonding.
- **Conduction Mechanism:**
 - **Majority Carriers:** Free electrons (negative charge carriers).
 - **Minority Carriers:** Holes (very few).
- **Electrical Properties:** Increased conductivity and negative charge carriers.

Mnemonic


“Pentavalent Provides Plus one Electron, Negative-type”

Question 2(a) OR [3 marks]

Define valence band, conduction band and forbidden gap.

Solution

| Term | Definition |
|------------------------|--|
| Valence Band | The highest energy band filled with electrons, where electrons are bound to atoms. |
| Conduction Band | The band above valence band where electrons move freely and contribute to electrical conduction. |
| Forbidden Gap | The energy range between valence and conduction bands where no electron states exist. |

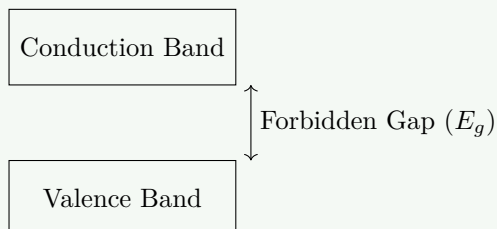

Mnemonic

“Valence Holds, Forbidden Blocks, Conduction Flows”

Question 2(b) OR [4 marks]

Define the terms active power, reactive power and power factor with power triangle.

Solution**Power Terms in AC Circuits:**

| Term | Definition |
|---------------------------|--|
| Active Power (P) | Actual power consumed, measured in watts (W); $P = VI \cos \theta$. |
| Reactive Power (Q) | Power oscillating between source and load, measured in VAR; $Q = VI \sin \theta$. |
| Power Factor (PF) | Ratio of active power to apparent power; $PF = \cos \theta$. |

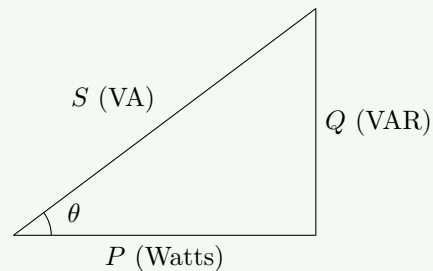
Power Triangle:

Figure 5. Power Triangle

- **Apparent Power (S):** Vector sum of active and reactive power.
- **Power Factor:** $\cos \theta = P/S$ (0 to 1).

Mnemonic

“Active Power Works, Reactive Power Waits”

Question 2(c) OR [7 marks]

Explain the structure of atom of trivalent, tetravalent and pentavalent elements.

Solution**Atomic Structures:**

| Element Type | Valence Electrons | Examples | Electronic Configuration |
|--------------------|-------------------|-------------------------------|--------------------------------|
| Trivalent | 3 | Boron, Aluminum, Gallium | 3 electrons in outermost shell |
| Tetravalent | 4 | Carbon, Silicon, Germanium | 4 electrons in outermost shell |
| Pentavalent | 5 | Nitrogen, Phosphorus, Arsenic | 5 electrons in outermost shell |

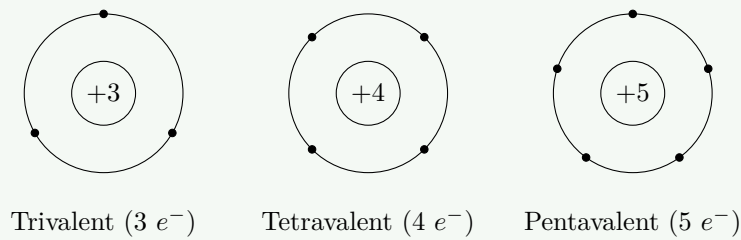


Figure 6. Valence Shell Electrons

- **Trivalent Elements:** Used as p-type dopants in semiconductors.
- **Tetravalent Elements:** Form semiconductor base materials.
- **Pentavalent Elements:** Used as n-type dopants in semiconductors.

Mnemonic


“Three Tries to Bond, Four Forms Full bonds, Five Frees an Electron”

Question 3(a) [3 marks]

Draw the symbol of photodiode and state it's application.

Solution

Photodiode Symbol:

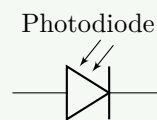

Applications of Photodiode:

- Light sensors and detectors.
- Optical communication systems.
- Camera exposure controls.
- Barcode scanners.
- Medical instruments.
- Solar cells.

Mnemonic

“Photons Produce Current”

Question 3(b) [4 marks]

Write a Short note on LED.

Solution

LED (Light Emitting Diode):

| Parameter | Description |
|------------------|--|
| Structure | p-n junction with special doping materials. |
| Working | Electrons recombine with holes, releasing energy as photons. |
| Materials | GaAs (red), GaP (green), GaN (blue), etc. |
| Voltage | Forward voltage typically 1.8V to 3.3V depending on color. |

Advantages:

- High efficiency (low power consumption).
- Long life (50,000+ hours).
- Small size and durability.
- Various colors available.

Applications:

- Indicators and displays.
- Lighting systems.
- TV/monitor backlights.
- Traffic signals.

Mnemonic

“Light Emits when Diode conducts”

Question 3(c) [7 marks]

Draw and explain VI characteristic of PN junction diode.

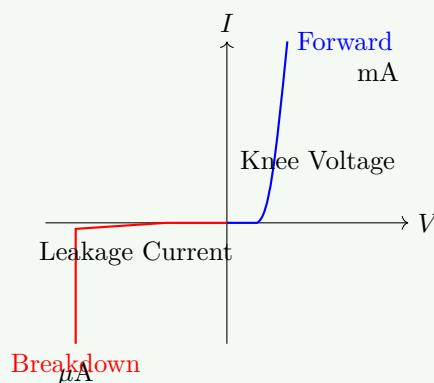
Solution**P-N Junction Diode V-I Characteristic:**

Figure 7. V-I Characteristics

Forward Bias Region:

- **Knee Voltage:** 0.3V (Ge), 0.7V (Si) where current starts flowing.
- **Current Equation:** $I = I_s(e^{qV/kT} - 1)$.
- **Conductivity:** High (low resistance).

Reverse Bias Region:

- **Leakage Current:** Very small reverse current (micro-amps).
- **Breakdown Region:** Sharp increase in current at breakdown voltage.
- **Conductivity:** Very low (high resistance).

Key Points:

- **Barrier Potential:** Decreases in forward bias, increases in reverse bias.
- **Diode Resistance:** Dynamic resistance changes with applied voltage.
- **Temperature Effect:** Voltage drop decreases with temperature increase.

Mnemonic

“Forward Flows Freely, Reverse Resists”

Question 3(a) OR [3 marks]

List the applications of PN junction diode.

Solution**Applications of PN Junction Diode:**

| Application Category | Examples |
|---------------------------|---|
| Rectification | Half-wave rectifier, Full-wave rectifier, Bridge rectifier. |
| Signal Processing | Signal demodulation, Clipping circuits, Clamping circuits. |
| Protection | Voltage spike protection, Reverse polarity protection. |
| Logic Gates | Diode logic circuits, Switching applications. |
| Voltage Regulation | Zener diodes for voltage references. |
| Light Applications | LEDs, Photodiodes, Solar cells. |

Mnemonic

“Rectify, Process, Protect, Logic, Regulate, Light”

Question 3(b) OR [4 marks]

Explain the formation of depletion region in unbiased P-N junction.

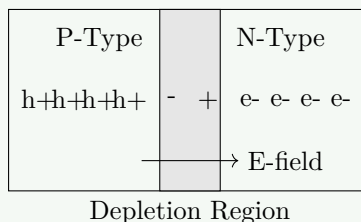
Solution**Depletion Region Formation:**

Figure 8. Depletion Region

Process:

- **Diffusion:** Electrons from n-side diffuse to p-side; holes from p-side diffuse to n-side.
- **Recombination:** Electrons and holes recombine at the junction.
- **Immobile Ions:** Exposed positive ions in n-region, negative ions in p-region.
- **Electric Field:** Forms between positive and negative ions, opposing further diffusion.
- **Equilibrium:** Diffusion current equals drift current; no net current flows.

Properties of Depletion Region:

- No free charge carriers.
- Acts as insulator.
- Width depends on doping levels.
- Contains built-in potential barrier.

Mnemonic

“Diffusion Depletes Carriers, Creating Electric barrier”

Question 3(c) OR [7 marks]

Explain construction, working and applications of PN junction diode.

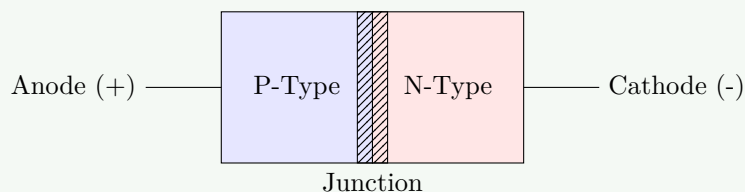
Solution**Construction of PN Junction Diode:**

Figure 9. PN Junction Construction

- **P-Type Region:** Silicon/Germanium doped with trivalent impurities (boron, aluminum).
- **N-Type Region:** Silicon/Germanium doped with pentavalent impurities (phosphorus, arsenic).
- **Junction:** Interface between p and n regions with depletion layer.
- **Terminals:** Anode (p-side) and Cathode (n-side).

Working Principle:

| Bias Condition | Behavior |
|----------------|---|
| Forward Bias | Depletion region narrows, current flows when $V > 0.7V$ (Si). |
| Reverse Bias | Depletion region widens, only small leakage current flows. |

Applications:

- Rectification in power supplies.
- Signal demodulation in radios.
- Voltage regulation (Zener).
- Signal clipping and clamping.
- Logic gates and switching.
- Light emission and detection.

Mnemonic

“Forward Flow, Reverse Restrict, Convert AC to DC”

Question 4(a) [3 marks]

Define: (1) Ripple frequency (2) Ripple factor (3) PIV of a diode.

Solution

| Term | Definition |
|--|--|
| Ripple Frequency | The frequency of AC component present in rectified DC output; for half-wave $f = f_{in}$, for full-wave $f = 2f_{in}$. |
| Ripple Factor (γ) | Ratio of RMS value of AC component to DC component in rectifier output; $\gamma = V_{ac(rms)}/V_{dc}$. |
| PIV of Diode | Peak Inverse Voltage - maximum reverse voltage a diode can withstand without breakdown. |

Mnemonic

“Ripples Per second, Ripple Proportion, Reverse Peak Voltage”

Question 4(b) [4 marks]

Give comparison between full wave rectifier with two diodes and full wave bridge rectifier.

Solution

| Parameter | Center-Tapped Full Wave | Bridge Rectifier |
|----------------|-------------------------|----------------------|
| Diodes Used | 2 diodes | 4 diodes |
| Transformer | Center-tapped required | No center tap needed |
| PIV of Diode | $2V_m$ | V_m |
| Output Voltage | $V_{dc} = 0.637V_m$ | $V_{dc} = 0.637V_m$ |
| Ripple Factor | 0.48 | 0.48 |
| Efficiency | 81.2% | 81.2% |
| TUF | 0.693 | 0.812 |

Mnemonic

“Bridge Beats Tap with Lower PIV but Needs More Diodes”

Question 4(c) [7 marks]

Explain zener diode as voltage regulator.

Solution

Zener Diode Voltage Regulator:

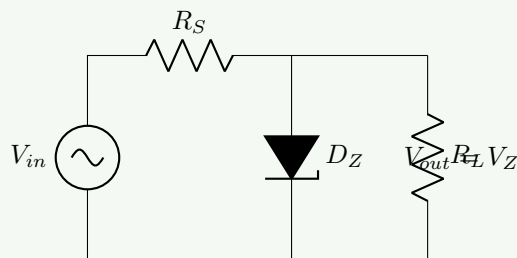


Figure 10. Zener Voltage Regulator

Working Principle:

- **Reverse Biased:** Zener operates in breakdown region.
- **Constant Voltage:** Maintains fixed voltage (V_Z) across its terminals.
- **Current Regulation:** Series resistor (R_S) limits current.
- **Load Changes:** When load current changes, Zener current changes to maintain constant output voltage.

Design Equations:

- $R_S = (V_{in} - V_Z)/(I_L + I_Z)$.
- Power rating of Zener: $P_Z = V_Z \times I_{Z(max)}$.

Mnemonic

“Zener Stays at breakdown Voltage despite Current changes”


Question 4(a) OR [3 marks]

What is rectifier? Explain full wave rectifier with waveforms.

Solution

Rectifier: A circuit that converts AC voltage to pulsating DC voltage by allowing current flow in one direction only.

Full Wave Rectifier (Center-Tapped):

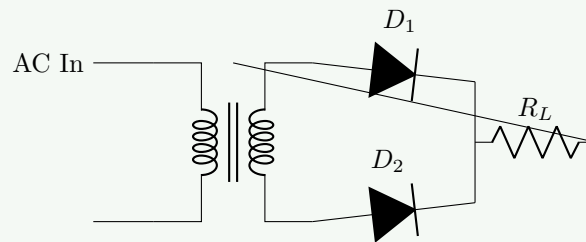

Waveforms:

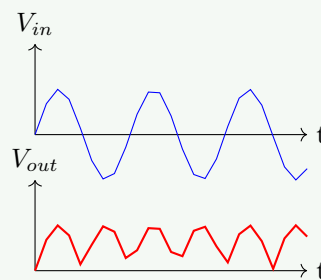


Figure 11. Full Wave Rectifier Waveforms

- **Operation:** Both half cycles of AC input are converted to same polarity.
- **Frequency:** Output ripple frequency is twice the input frequency.
- **Voltage:** $V_{dc} = 0.637V_m$.

Mnemonic

“Full Wave Forms Full Output”

Question 4(b) OR [4 marks]

Why filter is required in rectifier? State the different types of filter and explain any one type of filter.


Solution

Need for Filters: Rectifiers produce pulsating DC with large ripples; filters smooth this output to provide steady DC voltage.

Types of Filters:

- Capacitor (C) filter.

- Inductor (L) filter.
- LC filter.
- π (Pi) filter.
- RC filter.

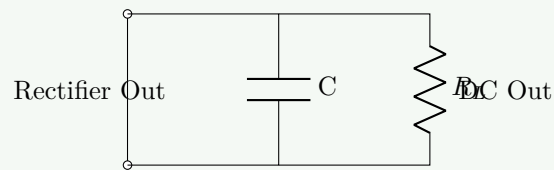Capacitor Filter:**Figure 12.** Capacitor Filter**Working Principle:**

- Capacitor charges during voltage rise to peak.
- Discharges slowly through load during voltage fall.
- Reduces ripple by providing discharge path with time constant RC .

Mnemonic


“Capacitor Catches Charge and Releases Slowly”

Question 4(c) OR [7 marks]

Write the need of rectifier. Explain bridge rectifier with circuit diagram and draw its input and output waveforms.

Solution**Need for Rectifiers:**

- Convert AC to DC for electronic devices.
- Power supplies and battery charging.
- Signal demodulation.

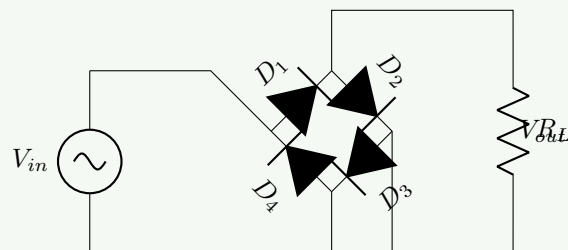Bridge Rectifier Circuit:**Figure 13.** Bridge Rectifier**Working Principle:**

- **Positive Half Cycle:** D_1 and D_3 conduct.
- **Negative Half Cycle:** D_2 and D_4 conduct.
- **Result:** Unidirectional current through R_L .

Waveforms: Input is sine wave, Output is pulsating DC (full-wave rectified).

Mnemonic

“Bridge Brings Both halves to Direct Current”

Question 5(a) [3 marks]

Explain causes of electronic waste.

Solution

| Causes of Electronic Waste: | Cause | Description |
|-----------------------------|-------------------------|--|
| | Rapid Technology Change | Frequent upgrades and obsolescence of electronics. |
| | Short Lifecycle | Devices designed with limited useful life. |
| | Consumer Behavior | Preference for new gadgets over repair. |
| | Manufacturing Issues | Poor quality leading to early failures. |
| | Marketing Strategies | Promoting new models through planned obsolescence. |

Mnemonic

“Upgrade, Use, Throw, Repeat”

Question 5(b) [4 marks]

Compare PNP and NPN transistors.

Solution

| Parameter | PNP Transistor | NPN Transistor |
|-------------------|----------------------------|----------------------------|
| Majority Carriers | Holes | Electrons |
| Current Flow | Emitter to Collector | Collector to Emitter |
| Biasing | Emitter +ve, Collector -ve | Collector +ve, Emitter -ve |
| Switching Speed | Slower | Faster |
| Usage | Less common | More common |

Mnemonic

“PNP: Positive-Negative-Positive; NPN: Negative-Positive-Negative”

Question 5(c) [7 marks]

Draw the symbol, explain the construction and working of MOSFET.

Solution

MOSFET (N-Channel Enhancement):

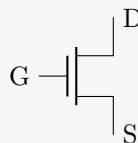


Figure 14. MOSFET Symbol

Construction:

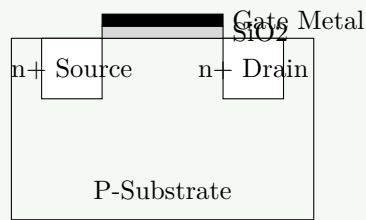


Figure 15. MOSFET Construction

Working Principle (Enhancement Mode):

- No channel exists initially.
- When positive voltage applied to Gate ($V_{GS} > V_{Th}$), electrons are attracted to surface.
- An N-channel is formed connecting Source and Drain, allowing current flow.

Mnemonic

“Gate Voltage Controls Electron Channel”

Question 5(a) OR [3 marks]

Explain methods to handle electronic waste.

Solution**Methods to Handle E-Waste:**

- **Reduce:** Designing long-lasting products.
- **Reuse:** Refurbishing used electronics.
- **Recycle:** Recovering materials.
- **Recover:** Extracting energy/metals.

**Mnemonic**

“Reduce, Reuse, Recycle, Recover Resources”

Question 5(b) OR [4 marks]

Derive the relationship between α_{dc} and β_{dc} .

Solution**Given:**

- $\alpha_{dc} = I_C / I_E$
- $\beta_{dc} = I_C / I_B$

Derivation: From KCL: $I_E = I_C + I_B$ Divide by I_C :

$$\frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\frac{1}{\alpha} = \frac{\beta + 1}{\beta}$$

Similarly,

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Mnemonic

“Alpha approaches One as Beta approaches Infinity”

Question 5(c) OR [7 marks]

Explain common collector configuration with its input and output characteristics.

Solution

Common Collector (Emitter Follower):

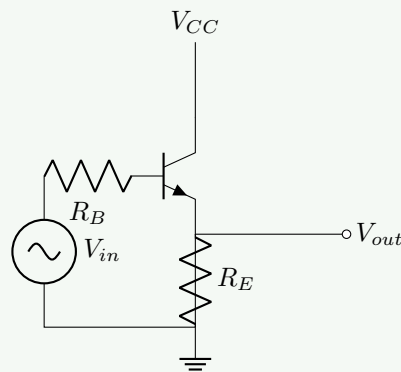


Figure 16. Common Collector Circuit

Characteristics:

- **Input:** Plot of I_B vs V_{BC} . High input impedance.
- **Output:** Plot of I_E vs V_{CE} . Low output impedance.
- **Voltage Gain:** ≈ 1 .
- **Current Gain:** High ($\beta + 1$).

Mnemonic

“Collector Common, Current amplifies, Voltage follows”