

Subject Name Solutions

4331101 – Winter 2022

Semester 1 Study Material

Detailed Solutions and Explanations

Question 1(a) [3 marks]

Define: 1) Branch 2) Junction 3) Mesh

Solution

- **Branch:** A branch is a single circuit element or a combination of elements connected between two nodes of a network.
- **Junction:** A junction (or node) is a point in a circuit where two or more circuit elements are connected together.
- **Mesh:** A mesh is a closed path in a network where no other closed path exists inside it.

Mnemonic

“BJM: Branches Join at junctions to Make meshes”

Question 1(b) [4 marks]

Write voltage division and current division rule with necessary circuit diagram

Solution

Voltage Division Rule: In a series circuit, voltage across any component is proportional to its resistance.

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((+)) --- B[R1] --- C[R2] --- D((-))
    E[V1] --- B
    F[V2] --- C
    G[VS] --- A
{Highlighting}
{Shaded}
```

- **Formula:** $V_1 = VS \times (R_1 / (R_1 + R_2))$
- **Application:** Used to find individual voltage drops across series components

Current Division Rule: In a parallel circuit, current through any branch is inversely proportional to its resistance.

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((+)) --- B[ ] --- C((-))
    B --- D[R1] --- E[ ]
    E --- F[R2] --- C
    F[I1] --- D
    G[I2] --- E
    H[IS] --- A
{Highlighting}
{Shaded}
```

- **Formula:** $I_1 = IS \times (R_2 / (R_1 + R_2))$
- **Key concept:** Current takes path of least resistance

Mnemonic

“VoSe CuPa: Voltage divides in Series, Current divides in Parallel”

Question 1(c) [7 marks]

Draw Graph and Tree for a network shown in fig(1). Show link currents on a graph. Also write Tie-set schedule for a tree of network shown in fig. (1)

Solution

Graph of the Network:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((A)) --- B((B))
    A --- C((C))
    A --- D((D))
    B --- C
    B --- D
    C --- D
    A --- 1[1] --- B
    A --- 3[3] --- C
    B --- 2[2] --- D
    C --- 5[5] --- D
    B --- 6[6] --- C
    A --- 7[7] --- D
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
    style D fill:#f9f,stroke:#333,stroke-width:2px
{Highlighting}
{Shaded}
```

Tree of the Network (shown with bold edges):

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((A)) --- B((B))
    A --- C((C))
    C --- D((D))
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
    style D fill:#f9f,stroke:#333,stroke-width:2px
    linkStyle 0 stroke-width:4px,stroke:green
    linkStyle 1 stroke-width:4px,stroke:green
    linkStyle 2 stroke-width:4px,stroke:green
{Highlighting}
{Shaded}
```

Link Currents (shown on remaining branches that are not part of the tree):

- Link 1: Branch 2 (BD)

- Link 2: Branch 6 (BC)
- Link 3: Branch 7 (AD)
- Link 4: Branch 5 (CD)

Tie-set Schedule:

Link/Tree Branch	Branch 1 (AB)	Branch 3 (AC)	Branch 4 (CD)	Branch 2 (BD)	Branch 6 (BC)	Branch 7 (AD)	Branch 5 (CD)
Link 1 (BD)	1	0	0	1	0	0	0
Link 2 (BC)	1	1	0	0	1	0	0
Link 3 (AD)	0	0	1	0	0	1	0
Link 4 (CD)	0	0	1	0	0	0	1

Mnemonic

“TGLT: Trees Generate Link-current Tie-sets”

Question 1(c) OR [7 marks]

Draw Graph and Tree for a network shown in fig(1). Show branch voltages on tree. Also write cut-set schedule for a tree of network shown on fig.(1)

Solution

Graph of the Network:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((A)) --- B((B))
    A --- C((C))
    A --- D((D))
    B --- C
    B --- D
    C --- D
    A --- 1[1] --- B
    A --- 3[3] --- C
    B --- 2[2] --- D
    C --- 5[5] --- D
    B --- 6[6] --- C
    A --- 7[7] --- D
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
    style D fill:#f9f,stroke:#333,stroke-width:2px
{Highlighting}
{Shaded}
```

Tree of the Network (shown with bold edges and branch voltages):

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((A)) ---|V1| B((B))
    A ---|V3| C((C))
    C ---|V4| D((D))
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
    style D fill:#f9f,stroke:#333,stroke-width:2px
```

```

style D fill:#f9f,stroke:#333,stroke-width:2px}
linkStyle 0 stroke-width:4px,stroke:green}
linkStyle 1 stroke-width:4px,stroke:green}
linkStyle 2 stroke-width:4px,stroke:green}
{Highlighting}
{Shaded}

```

Cut-set Schedule:

Cut-set/Branch	Branch 1 (AB)	Branch 3 (AC)	Branch 4 (CD)	Branch 2 (BD)	Branch 6 (BC)	Branch 7 (AD)	Branch 5 (CD)
Cut-set 1 (AB)	1	0	0	-1	-1	0	0
Cut-set 2 (AC)	0	1	0	0	1	-1	0
Cut-set 3 (CD)	0	0	1	1	0	1	1

Mnemonic

“CGVS: Cut-sets Generate Voltage Sources”

Question 2(a) [3 marks]

Define: 1) Active and passive network 2) Unilateral and Bilateral network.

Solution

- **Active Network:** A network containing one or more sources of EMF (voltage/current sources) that supply energy to the circuit.
- **Passive Network:** A network containing only passive elements like resistors, capacitors, and inductors with no energy sources.
- **Unilateral Network:** A network in which the properties and performance change when input and output terminals are interchanged.
- **Bilateral Network:** A network in which the properties and performance remain unchanged when input and output terminals are interchanged.

Diagram:

Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph LR
    subgraph "Network Types"
        A[Active: Contains sources]
        B[Passive: No sources]
        C[Unilateral: Diodes/Transistors]
        D[Bilateral: R, L, C elements]
    end
{Highlighting}
{Shaded}

```

Mnemonic

“APUB: Active Provides energy, Unilateral Blocks reversal”

Question 2(b) [4 marks]

Write equation for Z parameter and derive Z₁₁, Z₁₂, Z₂₁, Z₂₂ from that equation.

Solution

Z-parameters define the relationship between port voltages and currents in a two-port network:

Equations:

- $V_1 = Z_{11}I_1 + Z_{12}I_2$
- $V_2 = Z_{21}I_1 + Z_{22}I_2$

Derivation:

- $Z_{11} = V_1/I_1(\text{with } I_2 = 0)$: Input impedance with output port open – circuited
- $Z_{12} = V_1/I_2(\text{with } I_1 = 0)$: Reverse transfer impedance with input port open – circuited
- $Z_{21} = V_2/I_1(\text{with } I_2 = 0)$: Forward transfer impedance with output port open – circuited
- $Z_{22} = V_2/I_2(\text{with } I_1 = 0)$: Output impedance with input port open – circuited

Mnemonic

“Z Impedance: Open circuit gives correct Parameters”

Question 2(c) [7 marks]

Derive equation of characteristic impedance(Z_{OT}) for a standard T network.

Solution

For a standard T-network:

Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph LR
    A((Port{-1})) --- B[Z1] --- C((Junction))
    C --- D[Z2] --- E((Port{-2}))
    C --- F[Z3] --- G((Ground))
{Highlighting}
{Shaded}

```

Derivation Steps:

1. For a symmetric T-network, $Z_1 = Z_2$
1. Under matched condition, input impedance equals characteristic impedance
2. $Z_{0t} = Z_1 + (Z_{13})/(Z_1 + Z_3)$
2. For balanced T-network where $Z_1 = Z_2 = Z/2$ and $Z_3 = Z$:
2. $Z_{0t} = Z/2 + (Z/2)/(Z/2 + Z)$
2. $Z_{0t} = Z/2 + (Z^2/2)/(Z + Z/2)$
2. $Z_{0t} = Z/2 + (Z^2/2)/(3Z/2)$
2. $Z_{0t} = Z/2 + Z^2/3Z$
2. $Z_{0t} = Z/2 + Z/3$
2. $Z_{0t} = (3Z + 2Z)/6$
2. $Z_{0t} = \sqrt{Z_1(Z_1 + 2Z_3)}$

Final Equation: $Z_{0t} = \sqrt{Z_1(Z_1 + 2Z_3)}$

Mnemonic

“TO Impedance: Two arms Over middle branch”

Question 2(a) OR [3 marks]

Define: 1) Driving point impedance 2) Transfer impedance

Solution

- **Driving Point Impedance:** The ratio of voltage to current at the same port/pair of terminals when all other independent sources are set to zero.
- **Transfer Impedance:** The ratio of voltage at one port to the current at another port when all other

independent sources are set to zero.

Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    subgraph "Impedance Types"
        A["Driving Point:  $V_{1/I_{1}}$  or  $V_{2/I_{2}}$ "]
        B["Transfer:  $V_{2/I_{1}}$  or  $V_{1/I_{2}}$ "]
    end
end
{Highlighting}
{Shaded}
```

Mnemonic

“DTSS: Driving at Terminal Same, Transfer at Separate”

Question 2(b) OR [4 marks]

Explain Kirchhoff’s voltage law with example.

Solution

Kirchhoff’s Voltage Law (KVL): The algebraic sum of all voltages around any closed loop in a circuit is zero.

Mathematically: $\sum V = 0$ (around a closed loop)

Circuit Example:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((+)) -- "10V" --> B
    B -- " $R_1 = 2\Omega$ " --> C
    C -- " $R_2 = 3\Omega$ " --> D
    D -- " $R_3 = 5\Omega$ " --> A
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
    style D fill:#f9f,stroke:#333,stroke-width:2px
end
{Highlighting}
{Shaded}
```

If $I = 1A$, then:

- $V_1 = 1A \times 2 = 2V$
- $V_2 = 1A \times 3 = 3V$
- $V_3 = 1A \times 5 = 5V$

Applying KVL: $10V - 2V - 3V - 5V = 0$

Mnemonic

“VACZ: Voltages Around Closed loop are Zero”

Question 2(c) OR [7 marks]

Derive equation to convert π network into T network.

Solution

Network to T Network Conversion:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    subgraph " Network"
        A1((A)) --- B1((B))
        A1 --- Y1[Ya] --- C1
        B1 --- Y2[Yb] --- C1
        A1 --- Y3[Yc] --- B1
        C1((C))
    end

    subgraph "T Network"
        A2((A)) --- Z1[Za] --- D2((D))
        B2((B)) --- Z2[Zb] --- D2
        D2 --- Z3[Zc] --- C2((C))
    end
{Highlighting}
{Shaded}
```

Conversion Equations:

1. $Z_a = (Y_a \times Y_c) / Y$
1. $Z_b = (Y_b \times Y_c) / Y$
1. $Z_c = (Y_a \times Y_b) / Y$

Where $Y = Y_a + Y_b + Y_c$

Derivation:

1. Start with Y-parameters of -network
2. Express Y-parameters in terms of branch admittances
3. Convert to Z-parameters using matrix inversion
4. Express T-network impedances in terms of Z-parameters
5. Simplify to get the conversion formulas above

Mnemonic

“PIE to TEA: Product over sum for opposite branch”

Question 3(a) [3 marks]

Explain Kirchhoff's current law with example.

Solution

Kirchhoff's Current Law (KCL): The algebraic sum of all currents entering and leaving a node must equal zero.

Mathematically: $\sum I = 0$ (at any node)

Circuit Example:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    A[I_1 = 5A] --- B((Node))
    C[I_2 = 2A] --- B
    B --- D[I_3 = 3A]
    B --- E[I_4 = 4A]
    style B fill:#f9f,stroke:#333,stroke-width:2px
{Highlighting}
{Shaded}
```

Applying KCL at node B:

- Currents entering: $I_1 + I_2 = 5A + 2A = 7A$
- Currents leaving: $I_3 + I_4 = 3A + 4A = 7A$
- Therefore: $I_1 + I_2 - I_3 - I_4 = 5 + 2 - 3 - 4 = 0$

Mnemonic

“CuNoZ: Currents at Node are Zero”

Question 3(b) [4 marks]

Explain mesh analysis with required equations.

Solution

Mesh Analysis: A circuit analysis technique that uses mesh currents as variables to solve a circuit with multiple loops.

Steps:

1. Identify all meshes (closed loops) in the circuit
2. Assign a mesh current to each mesh
3. Apply KVL to each mesh
4. Solve the resulting system of equations

Example Circuit:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((A)) -- R_1 --> B((B))
    B -- R_3 --> C((C))
    A -- R_2 --> C
    A -- V_1 --> D
    D --> A
    C -- V_2 --> E
    E --> C
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
{Highlighting}
{Shaded}
```

Equations:

- Mesh 1: $V_1 = I_1 R_1 + I_1 R_2 - I_2 R_2$
- Mesh 2: $V_2 = I_2 R_2 + I_2 R_3 - I_1 R_2$

Mnemonic

“MILK: Mesh Is Loop with KVL”

Question 3(c) [7 marks]

State and explain Thevenin's theorem.

Solution

Thevenin's Theorem: Any linear network with voltage and current sources can be replaced by an equivalent circuit consisting of a voltage source (V_{TH}) in series with a resistance (R_{TH}).

Mermaid Diagram (Code)

```
{Shaded}
```



```

{Highlighting}[]
graph TD
    subgraph "Original Network"
        A((A)) --{}{} B[Complex Network] --{}{} C((B))
    end
    subgraph "Thevenin Equivalent"
        D((A)) --{}{} E[VTH] --{}{} F(({}+))
        F --{}{} G[RTH] --{}{} H((B))
    end
{Highlighting}
{Shaded}

```

Steps to Find Thevenin Equivalent:

1. Remove the load from the terminals of interest
2. Calculate the open-circuit voltage (VOC) across these terminals (= VTH)
3. Calculate the resistance looking back into the circuit with all sources replaced by their internal resistances (= RTH)
4. The Thevenin equivalent consists of VTH in series with RTH

Example Application:

- Original complex circuit with load RL
- Remove RL and find VOC = VTH
- Deactivate sources and find RTH
- Reconnect RL to simplified Thevenin equivalent

Mnemonic

“TORV: Thevenin’s Open-circuit Resistance and Voltage”

Question 3(a) OR [3 marks]

State and explain reciprocity theorem.

Solution

Reciprocity Theorem: In a linear, bilateral network, if a voltage source in one branch produces a current in another branch, then the same voltage source, if placed in the second branch, will produce the same current in the first branch.

Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph LR
    subgraph "Original Circuit"
        direction LR
        A((A)) --{}{} B[V] --{}{} C((B))
        C --{}{} D[Network] --{}{} E((C))
        E --{}{} F[Ammeter] --{}{} A
    end

    subgraph "Reciprocal Circuit"
        direction LR
        G((A)) --{}{} H[Ammeter] --{}{} I((B))
        I --{}{} J[Network] --{}{} K((C))
        K --{}{} L[V] --{}{} G
    end
{Highlighting}
{Shaded}

```

Mathematically: If a voltage V_1 in branch 1 produces current I_2 in branch 2, then voltage V_1 in branch 2 will produce current I_2 in branch 1.

Limitations: Applies only to networks with:

- Linear elements

- Bilateral elements (no diodes, transistors)
- Single independent source

Mnemonic

“RESWAP: REciprocity SWAPs Position with identical results”

Question 3(b) OR [4 marks]

Explain nodal analysis with required equations.

Solution

Nodal Analysis: A circuit analysis technique that uses node voltages as variables to solve a circuit.

Steps:

1. Choose a reference node (ground)
2. Assign voltage variables to remaining nodes
3. Apply KCL at each non-reference node
4. Solve the resulting system of equations

Example Circuit:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((Node 1)) -- G1 --- B((Ground))
    C((Node 2)) -- G2 --- B
    A -- G3 --- C
    A -- I1 --- B
    C -- I2 --- B
    style A fill:#f9f,stroke:#333,stroke-width:2px
    style C fill:#f9f,stroke:#333,stroke-width:2px
    style B fill:#f9f,stroke:#333,stroke-width:2px
{Highlighting}
{Shaded}
```

Equations:

- Node 1: $I_1 = V_1 G_1 + (V_1 - V_2) G_3$
- Node 2: $I_2 = V_2 G_2 + (V_2 - V_1) G_3$

Mnemonic

“NKCVC: Nodal uses KCL with Voltage variables”

Question 3(c) OR [7 marks]

State and prove maximum power transfer theorem.

Solution

Maximum Power Transfer Theorem: A load connected to a source will extract maximum power when its resistance equals the internal resistance of the source.

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A((+)) --- B[VS]
    C((X)) --- D[RS]
    E((Y)) --- F[RL]
    G((Z))
{Highlighting}
{Shaded}
```

```
G {-}{-} A}
style C fill:#f9f,stroke:#333,stroke-width:2px}
style E fill:#f9f,stroke:#333,stroke-width:2px}
{Highlighting}
{Shaded}
```

Proof:

1. Current in the circuit: $I = VS/(RS + RL)$
 2. Power delivered to load:

$$P = I^2 RL = (VS^2 RL)/(RS + RL)^2$$
 3. For maximum power, $dP/dRL = 0$
 4. Solving: $(VS^2(RS + RL)^2 - VS^2 RL 2(RS + RL))/(RS + RL)^4 = 0$
 4. Simplifying: $(RS + RL)^2 = 2RL(RS + RL)$
 4. Further simplifying: $RS + RL = 2RL$
 5. Therefore: $RS = RL$
- Maximum Power:** $P_{max} = VS^2/(4RS)$

Mnemonic

“MaRLRS: Maximum power when load Resistance equals Source Resistance”

Question 4(a) [3 marks]

Why series resonance circuit act as voltage amplifier and parallel resonance circuit act as current amplifier?

Solution

Series Resonance as Voltage Amplifier:

- At resonance, series circuit impedance is minimum (just R)
- Voltage across L or C can be much larger than source voltage
- Voltage magnification factor = $Q = XL/R = 1/R\sqrt{L/C}$
- Voltage across L or C = $Q \times \text{Source voltage}$

Parallel Resonance as Current Amplifier:

- At resonance, parallel circuit impedance is maximum
- Current in L or C can be much larger than source current
- Current magnification factor = $Q = R/XL = R\sqrt{C/L}$
- Current through L or C = $Q \times \text{Source current}$

Table:

Circuit Type	Impedance at Resonance	Amplification
Series	Minimum (R only)	Voltage (V_L or $V_C = Q$)
Parallel	Maximum (R^2/r)	Current (I_L or $I_C = Q$)

Mnemonic

“SeVoPa: Series Voltage, Parallel current amplification”

Question 4(b) [4 marks]

Derive equation of Q of coil.

Solution

Q-factor of a Coil:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
```

```

A((A)) {-}{-}{-} B[R] {-}{-}{-} C((B))}
C {-}{-}{-} D[L] {-}{-}{-} A}
style C fill:#f9f,stroke:#333,stroke-width:2px}
{Highlighting}
{Shaded}

```

Derivation:

1. Q-factor is defined as: $Q = \text{Energy stored} / \text{Energy dissipated per cycle}$
2. Energy stored in inductor $= (1/2)LI^2$
2. Power dissipated in resistor $= I^2 R$
2. Energy dissipated per cycle $= \text{Power} \times \text{Timeperiod} = I^2 R \times (1/f)$
2. Therefore: $Q = ((1/2)LI^2) / (I^2 R \times (1/f))$
2. Simplifying: $Q = 2 \times (1/2)LI^2 \times f / (I^2 R)$
2. $Q = 2 f \times L / R$

$$R = L / Q$$

Final Equation: $Q = L / R = 2 fL / R = XL / R$

Mnemonic

“QualityEDR: Quality equals Energy stored Divided by energy lost per Radian”

Question 4(c) [7 marks]

Derive equation of series resonance frequency for series R-L-C circuit.

Solution

Series R-L-C Circuit:

Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph LR
    A((Input)) {-}{-}{-} B[R] {-}{-}{-} C[L] {-}{-}{-} D[C] {-}{-}{-} E((Output))}
    style A fill:#f9f,stroke:#333,stroke-width:2px}
    style E fill:#f9f,stroke:#333,stroke-width:2px}
{Highlighting}
{Shaded}

```

Derivation:

1. Impedance of series RLC circuit: $Z = R + j(XL - XC)$
2. Where: $XL = L$ and $XC = 1/C$
3. At resonance, $XL = XC$ (inductive and capacitive reactances are equal)
4. Therefore: $L = 1/C$
5. Solving for : $^2 = 1/LC$
5. Resonant frequency: $\omega_0 = 1/\sqrt{LC}$
5. In terms of frequency f: $f_0 = 1/(2\sqrt{LC})$

Characteristics at Resonance:

- Impedance is minimum (purely resistive: $Z = R$)
- Current is maximum ($I = V/R$)
- Power factor is unity (circuit appears resistive)
- Voltages across L and C are equal and opposite

Mnemonic

“RES: Reactances Equal at Series resonance”

Question 4(a) OR [3 marks]

What is coupled circuits? Define self-inductance and mutual inductance.

Solution

Coupled Circuits: Two or more circuits that are magnetically linked such that energy can be transferred between them through their mutual magnetic field.

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    subgraph "Primary"
        A((A)) --{} B[L1] --{} C((B))
    end

    subgraph "Secondary"
        D((C)) --{} E[L2] --{} F((D))
    end

    G[M] --{} B
    G --{} E
{Highlighting}
{Shaded}
```

Self-inductance (L): The property of a circuit whereby a change in current produces a self-induced EMF in the same circuit. $L = \Phi/I$ (ratio of magnetic flux to the current producing it)

Mutual inductance (M): The property of a circuit whereby a change in current in one circuit induces an EMF in another circuit. $M = \Phi_{21}/I_1$ (ratio of flux in circuit 2 due to current in circuit 1)

Mnemonic

“SiMu: Self in Mine, Mutual in Yours”

Question 4(b) OR [4 marks]

Derive equation for co-efficient of coupling (K).

Solution

Coefficient of Coupling (k):

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    subgraph "Coupled Coils"
        A((A)) --{} B[L1] --{} C((B))
        D((C)) --{} E[L2] --{} F((D))
        G[M] --{} B
        G --{} E
    end
{Highlighting}
{Shaded}
```

Derivation:

1. The mutual inductance (M) between two coils depends on:
 - Self-inductances of the coils (L_1 and L_2)
 - Physical arrangement (proximity and orientation)
2. Maximum possible mutual inductance: $M_{max} = \sqrt{L_1 L_2}$
2. Coefficient of coupling is defined as: $k = M/M_{max}$
2. Therefore: $k = M/\sqrt{L_1 L_2}$

Characteristics:

- k ranges from 0 (no coupling) to 1 (perfect coupling)

- k depends on geometry, orientation, and medium
- Typical transformers: $k = 0.95$ to 0.99
- Air-core coils: $k = 0.01$ to 0.5

Mnemonic

“KMutual: K Measures Mutual linkage proportion”

Question 4(c) OR [7 marks]

A series RLC circuit has $R=30\Omega$, $L=0.5H$, and $C=5\mu F$. Calculate (i) series resonance frequency (2) Q Factor (3)BW

Solution

Given:

- Resistance, $R = 30\Omega$
- Inductance, $L = 0.5H$
- Capacitance,
 $C = 5\mu F = 5 \times 10^{-6} F$

Calculations:

(i) Series Resonance Frequency:

- $f_0 = 1/(2\sqrt{LC})$
- $f_0 = 1/(2\sqrt{0.5 \times 5 \times 10^{-6}})$
- $f_0 = 1/(2\sqrt{2.5 \times 10^{-6}})$
- $f_0 = 1/(2 \times 1.58 \times 10^{-3})$
- $f_0 = 1/(9.9 \times 10^{-3})$
- $f_0 = 100.76 Hz$
- $f_0 \approx 100 Hz$

(ii) Q Factor:

- $Q = (1/R)\sqrt{L/C}$
- $Q = (1/30)\sqrt{0.5/(5 \times 10^{-6})}$
- $Q = (1/30)\sqrt{100,000}$
- $Q = (1/30) \times 316.23$
- $Q = 10.54$

(iii) Bandwidth (BW):

- $BW = f_0/Q$
- $BW = 100.76/10.54$
- $BW = 9.56 Hz$

Table:

Parameter	Formula	Value
Resonant Frequency (f_0)	$1/(2\sqrt{LC})$	100 Hz
Quality Factor (Q)	$(1/R)\sqrt{L/C}$	10.54
Bandwidth (BW)	f_0/Q	9.56 Hz

Mnemonic

“RQB: Resonance Quality determines Bandwidth”

Question 5(a) [3 marks]

Classify various types of attenuators.

Solution

Attenuators: Network of resistors designed to reduce (attenuate) signal level without distortion.

Types of Attenuators:

Mermaid Diagram (Code)

```

{Shaded}
{Highlighting}[]
graph TD
    A[Attenuators] --{-}{-} B[Fixed Attenuators]}
    A --{-}{-} C[Variable Attenuators]}
    B --{-}{-} D[T{-}type]}
    B --{-}{-} E[{-}type]}
    B --{-}{-} F[Bridged{-}T]}
    B --{-}{-} G[Lattice]}
    C --{-}{-} H[Step Attenuators]}
    C --{-}{-} I[Continuously Variable]}
{Highlighting}
{Shaded}

```

Based on configuration:

- **T-type:** Three resistor T-shaped configuration
- **-type:** Three resistor -shaped configuration
- **Bridged-T:** T-type with a resistor bridging across
- **Lattice:** Balanced configuration with four resistors

Based on symmetry:

- **Symmetrical:** Equal input and output impedance
- **Asymmetrical:** Different input and output impedance

Mnemonic

“ATP Fixed: Attenuator Types include Pad, Tee, Lattice”

Question 5(b) [4 marks]

Derive relation between attenuator and neper.

Solution

Relationship between Attenuation and Neper:

- **Attenuation ():** Ratio of input voltage (or current) to output voltage (or current), expressed in different units.
- **Neper (Np):** Natural logarithmic unit of ratios, used mainly in transmission line theory.

Derivation:

1. For a voltage ratio V_1/V_2 :
 - Attenuation in Nepers = $\ln(V_1/V_2)$
 - Attenuation in Decibels = $20\log_{10}(V_1/V_2)$
2. For a power ratio P_1/P_2 :
 - Attenuation in Nepers = $(1/2)\ln(P_1/P_2)$
 - Attenuation in Decibels = $10\log_{10}(P_1/P_2)$
3. Relationship between dB and Neper:
 - 1 Neper = 8.686 dB
 - 1 dB = 0.115 Neper

Table:

Unit	Voltage Ratio	Power Ratio
Neper (Np)	$\ln(V_1/V_2)$	$(1/2)\ln(P_1/P_2)$
Decibel (dB)	$20\log_{10}(V_1/V_2)$	$10\log_{10}(P_1/P_2)$

Mnemonic


“NED: Neper Equals Decibel divided by 8.686”

Question 5(c) [7 marks]


Derive equations of R1 and R2 for symmetrical T attenuator.

Solution	<div data-bbox="158 174 523 203">Symmetrical T Attenuator:</div> <div data-bbox="620 230 971 262">Mermaid Diagram (Code)</div> <pre data-bbox="158 288 914 631"> {Shaded} {Highlighting}[] graph LR A((Input)) --{--}{--} B[R1] --{--}{--}{--} C((Junction)) C --{--}{--}{--} D[R1] --{--}{--}{--} E((Output)) C --{--}{--}{--} F[R2] --{--}{--}{--} G((Ground)) style A fill:#f9f,stroke:#333,stroke-width:2px style E fill:#f9f,stroke:#333,stroke-width:2px style C fill:#f9f,stroke:#333,stroke-width:2px {Highlighting} {Shaded} </pre> <div data-bbox="158 663 306 689">Derivation:</div> <ol data-bbox="191 694 1003 1135" style="list-style-type: none"> For a symmetrical T-attenuator with characteristic impedance Z_0 : <ul style="list-style-type: none"> Input and output impedance must both equal Z_0 Attenuation ratio $N = V_1/V_2 = I_2/I_1$ From circuit analysis: <ul style="list-style-type: none"> $Z_0 = R_1 + (R_2(R_1))/(R_2 + R_1)$ $N = (R_1 + R_2 + R_1)/R_2 = (2R_1 + R_2)/R_2$ Solving for R_1 and R_2 : <ul style="list-style-type: none"> $R_1 = Z_0(N - 1)/(N + 1)$ $R_2 = 2Z_0N/(N^2 - 1)$ For attenuation in dB (): <ul style="list-style-type: none"> $N = 10^{(/20)}$ $R_1 = Z_0 \tanh(/2)$ $R_2 = Z_0 / \sinh()$ <div data-bbox="158 1142 376 1167">Final Equations:</div> <ul data-bbox="191 1173 515 1232" style="list-style-type: none"> $R_1 = Z_0(N - 1)/(N + 1)$ $R_2 = 2Z_0N/(N^2 - 1)$
Mnemonic	<div data-bbox="158 1332 831 1364">“TSR: T-attenuator Symmetry Requires equal R1 values”</div>



```
{          /\}
{              /\}
R2 {          /\}
    {        / R2\}
      {\     /\}
       \{\   /\}
         \/\}/
           \| }
            \| }
             \| }
R1 /         \| }
```

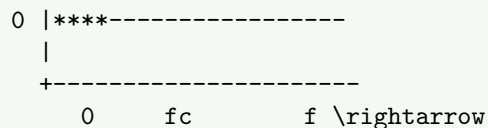

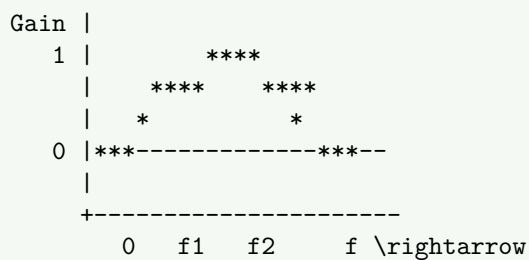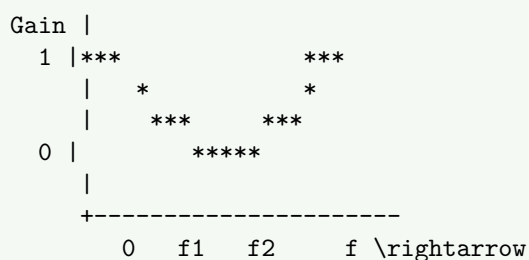3. **Band Pass Filter:** Passes frequencies within a specific band



4. **Band Stop Filter:** Rejects frequencies within a specific band



Mnemonic


“LHBBA: Low High Band-pass Band-stop All-pass”

Question 5(c) OR [7 marks]


Draw the circuit for T-section and π -section constant-K low pass filter and Derive equation of cut-off frequency.

Solution

T-section Constant-K Low Pass Filter:

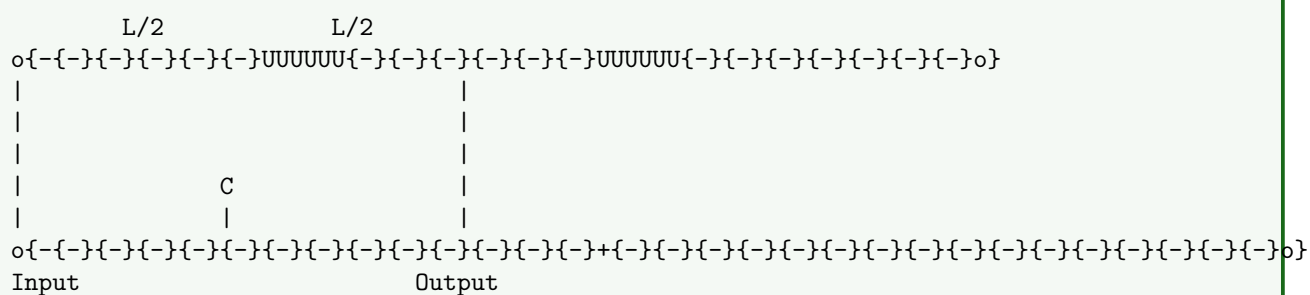

π -section Constant-K Low Pass Filter:

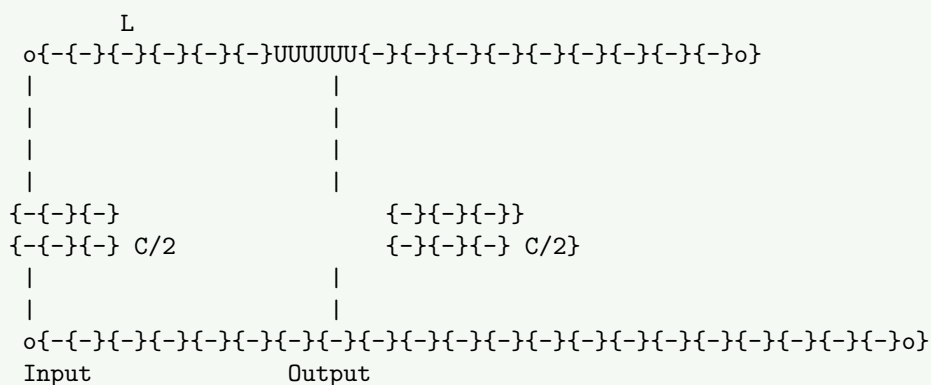

Derivation of Cutoff Frequency:

1. For a constant-K filter:
 - $Z_1 \times Z_2 = R_0^2$ (characteristic impedance squared)
 - $Z_1 = jL$ (series impedance)
 - $Z_2 = 1/jC$ (shunt impedance)
2. Therefore:
 - $R_0^2 = Z_1 \times Z_2 = jL \times 1/jC = L/C$
 - $R_0 = \sqrt{L/C}$
3. Pass band condition:
 - $-1 < Z_1/4Z_2 < 0$
 - $-1 < jL/(4 \times 1/jC) < 0$
 - $-1 < -^2LC/4 < 0$
4. At cutoff frequency:
 - $^2LC/4 = 1$
 - $c^2 = 4/LC$
 - $c = 2/\sqrt{LC}$
 - $f_c = c/2 = 1/\sqrt{LC}$

Final Equation:

- Cutoff frequency $f_c = 1/\sqrt{LC}$

Mnemonic

“KCLP: Konstant-k Cutoff in Low Pass depends on L and C product”