

# VLSI Technology (4361102) - Summer 2024 Solution

Milav Dabgar

May 16, 2024

## Question 1(a) [3 marks]

Draw the structure of FinFET and write its advantages.

### Solution

Structure of FinFET showing Source, Drain, and Gate wrapping around the fin.

 


Figure 1. FinFET Structure

### Advantages:

Advantage	Description
Better Control	Multiple gates provide superior channel control
Reduced Leakage	Lower off-state current due to 3D structure
Improved Performance	Higher drive current and faster switching

Table 1. FinFET Advantages

### Mnemonic

“BCR - Better Control Reduces leakage”


## Question 1(b) [4 marks]

Explain depletion and inversion of MOS structure under external bias

### Solution

Table: MOS Bias Conditions

Bias Type	Gate Voltage	Channel State	Charge Carriers
<b>Depletion</b>	Slightly Positive	Depleted	Holes pushed away
<b>Inversion</b>	High Positive	Inverted	Electrons attracted

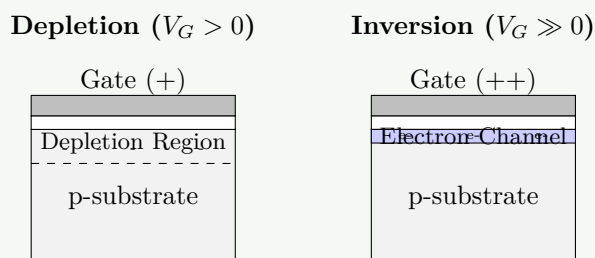**Table 2.** MOS Bias Conditions**Figure 2.** MOS Depletion and Inversion Layers

- **Depletion:** Positive gate voltage creates electric field pushing holes away, leaving immobile negative ions.
- **Inversion:** Higher voltage attracts electrons to surface, forming a conducting n-channel.

**Mnemonic**

“DI - Depletion Inverts to conducting channel”

**Question 1(c) [7 marks]**

Explain n-channel MOSFET with the help of its Current-Voltage characteristics.

**Solution****Table: MOSFET Operating Regions**

Region	Condition	Drain Current	Characteristics
<b>Cut-off</b>	$V_{GS} < V_{TH}$	$I_D \approx 0$	No conduction
<b>Linear</b>	$V_{DS} < V_{GS} - V_{TH}$	$I_D \propto V_{DS}$	Resistive behavior
<b>Saturation</b>	$V_{DS} \geq V_{GS} - V_{TH}$	$I_D \propto (V_{GS} - V_{TH})^2$	Current independent of $V_{DS}$

**Table 3.** MOSFET Operating Regions

 


Figure 3. MOSFET IV Characteristics

**Key Equations:**

- **Linear:**  $I_D = \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{TH})V_{DS} - \frac{V_{DS}^2}{2}]$
- **Saturation:**  $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$

**Mnemonic**

“CLS - Cut-off, Linear, Saturation regions”

**Question 1(c OR) [7 marks]**

Define scaling. Compare full voltage scaling with constant voltage scaling. Write the disadvantages of scaling.

**Solution**

**Definition:** Scaling reduces device dimensions to increase density and performance.

**Table: Scaling Comparison**

Parameter	Full Voltage Scaling	Constant Voltage Scaling
Voltage	Reduced by $\alpha$	Remains constant
Power Density	Constant	Increases by $\alpha$
Electric Field	Constant	Increases by $\alpha$
Performance	Better	Moderate improvement

Table 4. Scaling Comparison

**Disadvantages:**

- **Short Channel Effects:** Channel length modulation increases.
- **Hot Carrier Effects:** High electric fields damage devices.
- **Quantum Effects:** Tunneling currents increase significantly.

**Mnemonic**

“SHQ - Short channel, Hot carriers, Quantum effects”

## Question 2(a) [3 marks]

Draw two input NAND gate using CMOS.

### Solution

CMOS NAND gate uses two parallel pMOS transistors and two series nMOS transistors.

 


Figure 4. 2-Input CMOS NAND Gate

Table: NAND Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Table 5. NAND Truth Table

### Mnemonic

“PP-SS: Parallel PMOS, Series NMOS”

## Question 2(b) [4 marks]

Explain noise immunity and noise margin for nMOS inverter.

### Solution

Table: Noise Parameters

Parameter	Definition	Formula
NMH	High noise margin	$V_{OH} - V_{IH}$
NML	Low noise margin	$V_{IL} - V_{OL}$
Noise Immunity	Ability to reject noise	$\text{Min}(\text{NMH}, \text{NML})$

Table 6. Noise Parameters

 


Figure 5. Noise Margins

- $V_{IL}$ : Maximum low input voltage recognized as logic 0.
- $V_{IH}$ : Minimum high input voltage recognized as logic 1.
- **Good noise immunity**: Large noise margins prevent false switching due to noise.

## Mnemonic

“HILOL - High/Low Input/Output Levels”

## Question 2(c) [7 marks]


Explain Voltage Transfer Characteristics (VTC) of CMOS inverter.

## Solution

Table: VTC Regions

Region	Input Range	Output	Transistor States
A	0 to $V_{TN}$	$V_{DD}$	pMOS ON, nMOS OFF
B	$V_{TN}$ to $V_{DD}/2$	Transition	Both ON (Sat/Lin)
C	$V_{DD}/2$ (Threshold)	Rapid Drop	Both Saturation
D	$V_{DD}/2$ to $V_{DD} -  V_{TP} $	Transition	Both ON (Lin/Sat)
E	$V_{DD} -  V_{TP} $ to $V_{DD}$	0V	pMOS OFF, nMOS ON

Table 7. VTC Regions

 

**Figure 6.** CMOS Inverter VTC

**Key Features:**

- **Sharp transition:** Ideal switching behavior at  $V_{th}$ .
- **High gain:** Large slope in transition region (Region C).
- **Rail-to-rail:** Output swings full supply range (0 to  $V_{DD}$ ).

**Mnemonic**


“ASH - A-region, Sharp transition, High gain”

## Question 2(a OR) [3 marks]

Implement NOR2 gate using depletion load nMOS.

**Solution**

Depletion load NOR2 uses a depletion nMOS as load and two parallel nMOS as drivers.

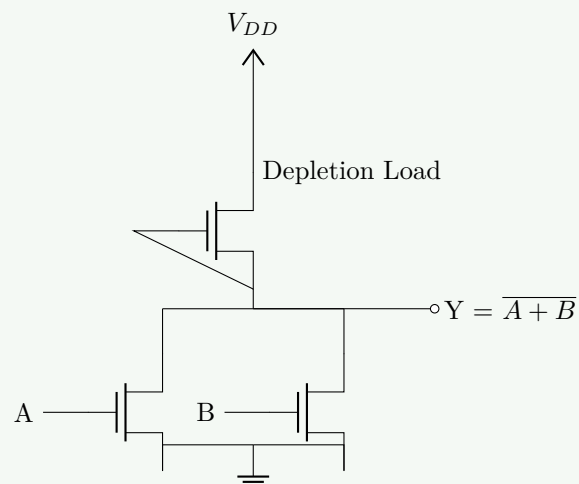

**Figure 7.** Depletion Load NOR2

Table: NOR2 Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Table 8. NOR2 Truth Table

## Mnemonic

“DPN - Depletion load, Parallel NMOS”

## Question 2(b OR) [4 marks]

Differentiate between enhancement load inverter and Depletion load inverter.

## Solution

Table: Load Inverter Comparison

Parameter	Enhancement Load	Depletion Load
Threshold Voltage	$V_T > 0$	$V_T < 0$
Gate Connection	$V_{GS} = V_{DS}$	$V_{GS} = 0$
Logic High ( $V_{OH}$ )	$V_{DD} - V_T$	$V_{DD}$
Power Consumption	Higher	Lower
Switching Speed	Slower	Faster

Table 9. Inverter Load Types Comparison

## Mnemonic

“EPDLH - Enhancement Positive, Depletion Lower power, Higher speed”

## Question 2(c OR) [7 marks]

Explain Depletion load nMOS inverter with its VTC.

## Solution

## Circuit Operation:

- **Load transistor:** Always conducting ( $V_{GS} = 0, V_T < 0$ ). Acts as a constant current source.
- **Driver transistor:** Controlled by input voltage ( $V_{in}$ ).
- **Output:** Determined by voltage divider action between load and driver resistances.

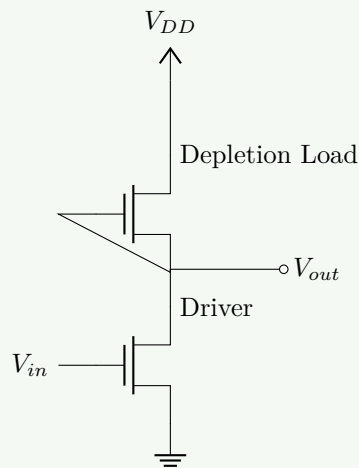


Figure 8. Depletion Load Inverter

Table: Operating Points

Input State	Driver	Load	Output
$V_{in} = 0$	OFF	ON (Linear)	$V_{DD}$
$V_{in} = V_{DD}$	ON (Linear)	ON (Sat)	$\approx 0V$

Table 10. Inverter Operating Points

**VTC Characteristics:**

- $V_{OH}$ : Reaches full  $V_{DD}$  (unlike enhancement load which drops  $V_T$ ).
- $V_{OL}$ : Low voltage close to  $0V$ .
- **Transition**: Sharp switching due to better load characteristics.

**Mnemonic**

“DLB - Depletion Load gives Better high output”


**Question 3(a) [3 marks]**

Implement EX-OR using Depletion load nMOS.

**Solution**

To implement XOR ( $Y = A \oplus B = A\bar{B} + \bar{A}B$ ) using depletion load nMOS logic (which implements  $\overline{\text{Pull-Down}}$ ), we organize the pull-down network to realize the complement of XOR, which is XNOR ( $AB + \bar{A}\bar{B}$ ). A standard implementation uses 4 transistors in the pull-down network to realize  $Y = \overline{(A + \bar{B})(\bar{A} + B)} = A \oplus B$ .



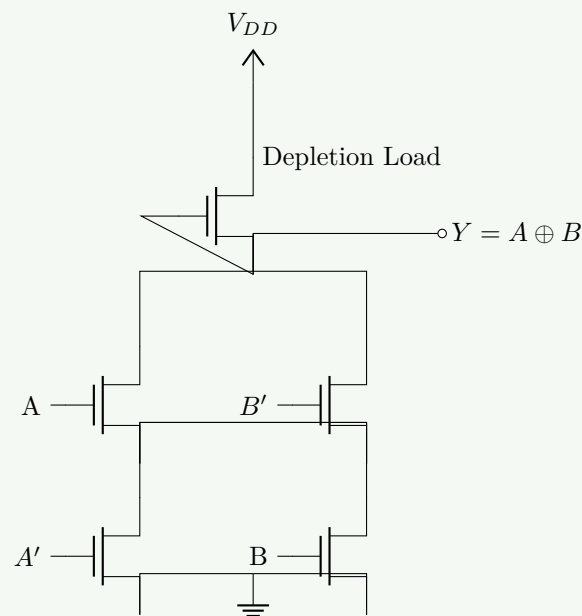

**Figure 9.** Depletion Load NMOS EX-OR Gate

**Logic Equation:**  $Y = \overline{(A + \bar{B})} \cdot (\bar{A} + B) = \overline{A\bar{A} + AB + \bar{B}\bar{A} + \bar{B}B} = \overline{0 + AB + \bar{A}\bar{B} + 0} = \overline{A\odot B} = A \oplus B$

#### Mnemonic

“XOR - eXclusive OR, different inputs give 1”

### Question 3(b) [4 marks]


Explain design hierarchy with example.

#### Solution

**Table: Hierarchy Levels**

Level	Component	Example
<b>System</b>	Complete chip	Microprocessor
<b>Module</b>	Functional blocks	ALU, Memory
<b>Gate</b>	Logic gates	NAND, NOR
<b>Transistor</b>	Individual devices	MOSFET

**Table 11.** Design Hierarchy Levels

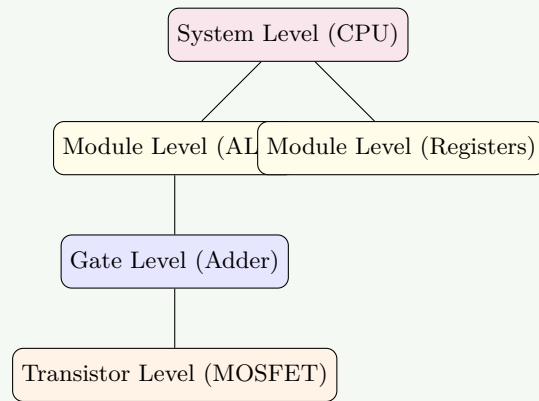

**Figure 10.** Design Hierarchy Tree

**Benefits:**

- **Modularity:** Independent design and testing of blocks.
- **Reusability:** Common blocks (like adders) used multiple times.
- **Maintainability:** Easy debugging and modification.

**Mnemonic**


“SMG-T: System, Module, Gate, Transistor levels”

## Question 3(c) [7 marks]

Draw and explain Y chart design flow.

**Solution**

The Y-chart represents the three domains of VLSI design: Behavioral, Structural, and Physical.

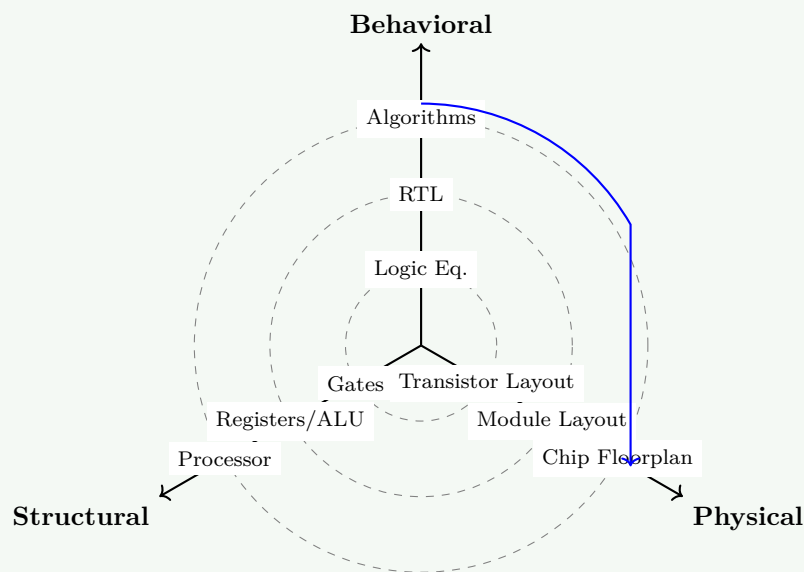

**Figure 11.** Gajski-Kuhn Y-Chart

Table: Y-Chart Domains

Domain	Description	Examples
Behavioral	What system does	Algorithms, RTL
Structural	How it's organized	Architecture, Gates
Physical	Where components placed	Floorplan, Layout

Table 12. Y-Chart Domains

**Design Flow:**

- **Top-down:** Behavioral  $\rightarrow$  Structural  $\rightarrow$  Physical.
- **Bottom-up:** Physical constraints influence upper levels.

**Mnemonic**

“BSP - Behavioral, Structural, Physical domains”

**Question 3(a OR) [3 marks]**

Implement NAND2 - SR latch using CMOS

**Solution**

NAND SR Latch consists of two cross-coupled NAND gates.

 


Figure 12. CMOS NAND SR Latch

**Table: SR Latch Operation**

S	R	Q	Q'	State
0	0	1	1	Invalid
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q	Q'	Hold

Table 13. NAND SR Latch Truth Table (Active Low Inputs)

**Mnemonic**

“SR-HRI: Set, Reset, Hold, Invalid states”


**Question 3(b OR) [4 marks]**

Which method is used to transfer pattern or mask on the silicon wafer? Explain it with

neat diagrams

### Solution

**Method: Photolithography** is used to transfer geometric shapes on a mask to the surface of a silicon wafer.

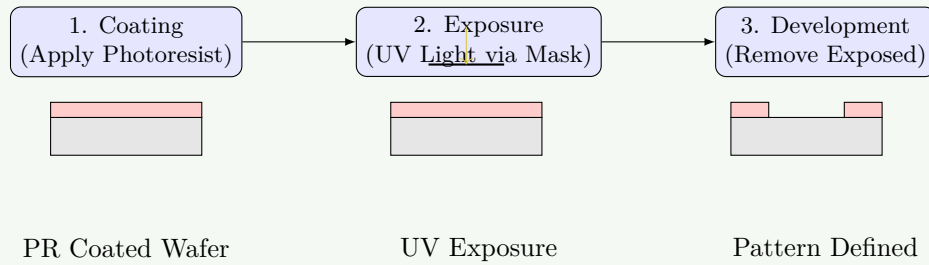

**Figure 13.** Photolithography Process

### Process Steps:

- **Coating:** Applying a thin layer of photoresist.
- **Exposure:** Exposing resist to UV light through a mask.
- **Development:** Dissolving the exposed (positive) or unexposed (negative) resist.

### Mnemonic

“CED - Coating, Exposure, Development”

## Question 3(c OR) [7 marks]

Which are the methods used to deposit metal in MOSFET fabrication? Explain deposition in detail with proper diagram.


### Solution

**Table: Metal Deposition Methods**

Method	Technique	Application
<b>PVD</b>	Sputtering, Evaporation	Aluminum, Copper
<b>CVD</b>	CVD, PECVD	Tungsten, Titanium
<b>Electroplating</b>	Electrochemical	Copper interconnects

**Table 14.** Metal Deposition Methods

**Sputtering Process:** In sputtering, ions from a plasma are accelerated towards a target material, ejecting atoms which settle on the wafer.

 

**Figure 14.** Sputtering System

**Advantages:**

- **Uniform thickness:** Excellent step coverage.
- **Low temperature:** Preserves device integrity.
- **Variety:** Can deposit alloys and compounds.

**Mnemonic**

“IBE-DC: Ion Bombardment Ejects atoms for Deposition Control”

## Question 4(a) [3 marks]

Implement  $Z = ((A+B+C) \cdot (D+E+F) \cdot G)'$  with depletion nMOS load.

**Solution**

The logic function  $Z = \overline{(A+B+C) \cdot (D+E+F) \cdot G}$  is implemented using a depletion load and a pull-down network. The pull-down network consists of three series blocks corresponding to the AND operations: 1. Parallel inputs A, B, C (OR) 2. Parallel inputs D, E, F (OR) 3. Single input G. Since these are ANDed, the blocks are in series.

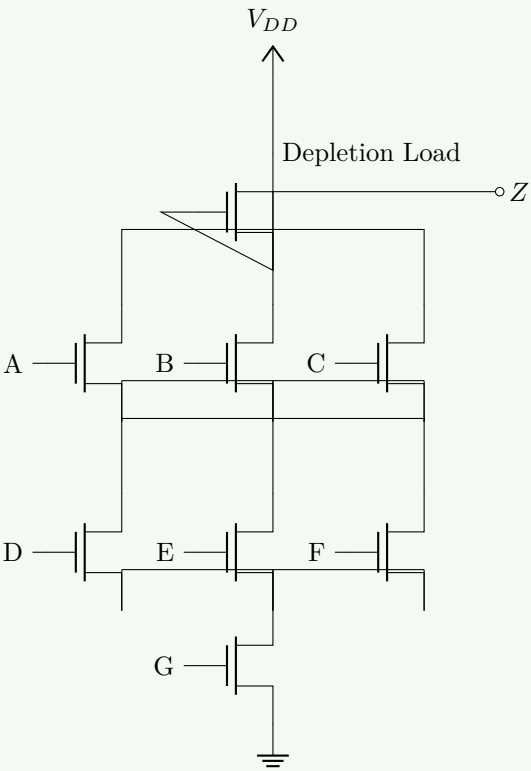


Figure 15. Logic Implementation of Z

Mnemonic

“POI - Parallel OR, Inversion at output”

Question 4(b) [4 marks]

List and explain the design styles used in VERILOG.

Solution

Table: Verilog Design Styles

Style	Description	Use Case	Example
Behavioral	Algorithm description	High-level modeling	<code>always</code> blocks
Dataflow	Boolean expressions	Combinational logic	<code>assign</code> statements
Structural	Component instantiation	Hierarchical design	module connections
Gate-level	Primitive gates	Low-level design	<code>and</code> , <code>or</code> , <code>not</code> gates

Table 15. Verilog Design Styles

Characteristics:

- **Behavioral:** Describes what circuit does (functionality).
- **Structural:** Shows how components connect (netlist).
- **Mixed:** Combines multiple styles for complex ideas.

**Mnemonic**

“BDSG - Behavioral, Dataflow, Structural, Gate-level”

**Question 4(c) [7 marks]**

Implement NAND2 SR latch using CMOS and also implement NOR2 SR latch using CMOS.

**Solution****NAND2 SR Latch (Verilog):**

```

1 module nand_sr_latch(
2     input S, R,
3     output Q, Q_bar
4 );
5     nand(Q, S, Q_bar);
6     nand(Q_bar, R, Q);
7 endmodule

```

**NOR2 SR Latch (Verilog):**

```

1 module nor_sr_latch(
2     input S, R,
3     output Q, Q_bar
4 );
5     nor(Q_bar, R, Q);
6     nor(Q, S, Q_bar);
7 endmodule

```

**Comparison:**

- **NAND:** Set/Reset with low inputs (Active Low).
- **NOR:** Set/Reset with high inputs (Active High).

**Mnemonic**

“NAND-Low, NOR-High active”

**Question 4(a OR) [3 marks]**

Implement  $Y = (ABC + DE + F)'$  with depletion nMOS load.

**Solution**

The logic function  $Y = \overline{(ABC) + (DE) + F}$  implements Sum of Products (ORing of AND terms). The pull-down network consists of three parallel branches: 1. A, B, C in Series (AND) 2. D, E in Series (AND) 3. F Single

 


Figure 16. Logic Implementation of Y

**Mnemonic**

“SSS-I: Series-Series-Single with Inversion”

**Question 4(b OR) [4 marks]**

Write Verilog Code to implement full adder.

**Solution**

```

1 module full_adder(
2     input a, b, cin,
3     output sum, cout
4 );
5     assign sum = a ^ b ^ cin;
6     assign cout = (a & b) | (cin & (a ^ b));
7 endmodule

```

**Logic Functions:**

- **Sum:** Triple XOR operation ( $A \oplus B \oplus C_{in}$ )
- **Carry:** Majority function of inputs ( $AB + BC_{in} + AC_{in}$ )

**Mnemonic**

“XOR-Sum, Majority-Carry”

**Question 4(c OR) [7 marks]**

Implement  $Y = (S1'S0'I0 + S1'S0 I1 + S1 S0' I2 + S1 S2 I3)$  using depletion load



## Solution

**4:1 Multiplexer Verilog Code** (Assuming S2 corresponds to S0 in context of 4-input):

```

1 // 4:1 Multiplexer implementation
2 module mux_4to1(
3     input [1:0] sel, // S1, S0
4     input [3:0] data, // I3, I2, I1, I0
5     output Y
6 );
7     assign Y = (sel == 2'b00) ? data[0] :
8               (sel == 2'b01) ? data[1] :
9               (sel == 2'b10) ? data[2] :
10                  data[3];
11 endmodule

```

**Table: Multiplexer Selection**

S1	S0	Selected Input	Output
0	0	I0	$Y = I0$
0	1	I1	$Y = I1$
1	0	I2	$Y = I2$
1	1	I3	$Y = I3$

**Table 16.** Multiplexer Selection

## Mnemonic

“DAO - Decoder, AND gates, OR combination”

## Question 5(a) [3 marks]

Implement the logic function  $G = (PQR + U(S+T))'$  using CMOS

## Solution

The function  $G = \overline{(PQR) + U(S+T)}$  requires a CMOS implementation. **Pull-Down Network (PDN)**: Implements  $(PQR) + U(S+T)$  via nMOS.

- $P, Q, R$  in Series (AND).
- $S, T$  in Parallel (OR) is correct for  $(S+T)$ .
- $U$  in Series with  $(S||T)$ .
- The block  $(P - Q - R)$  is in Parallel with  $(U - (S||T))$ .

**Pull-Up Network (PUN)**: Implements dual via pMOS.

- $P, Q, R$  in Parallel.
- $S, T$  in Series.
- $U$  in Parallel with  $(S - T)$ .
- The block  $(P||Q||R)$  is in Series with  $(U||(S - T))$ .

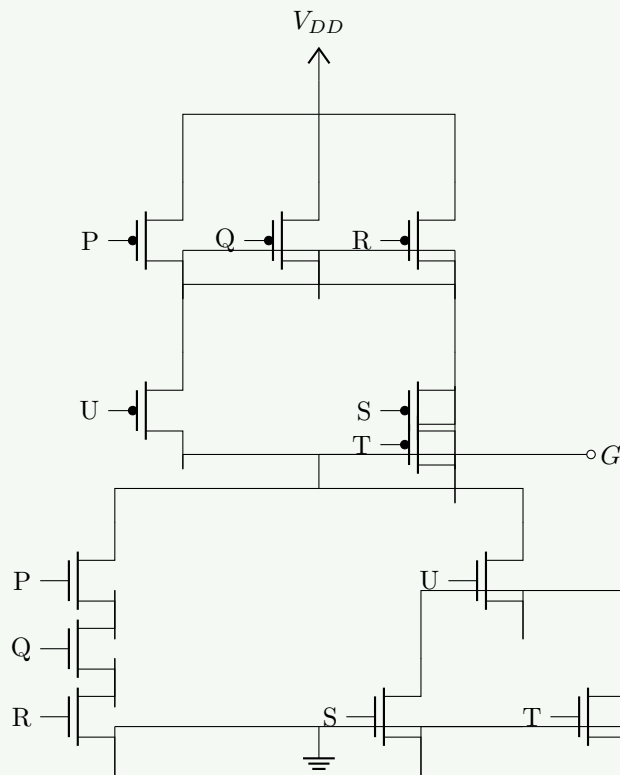


Figure 17. CMOS Implementation of Logic G

**Mnemonic**

“PSSP - Parallel Series Series Parallel”

**Question 5(b) [4 marks]**

Implement 8x1 multiplexer using Verilog

**Solution**

```

1 module mux_8to1(
2     input [2:0] sel,      // 3-bit select
3     input [7:0] data,    // 8 data inputs
4     output reg Y         // Output
5 );
6     always @(*) begin
7         case(sel)
8             3'b000: Y = data[0];
9             3'b001: Y = data[1];
10            3'b010: Y = data[2];
11            3'b011: Y = data[3];
12            3'b100: Y = data[4];
13            3'b101: Y = data[5];
14            3'b110: Y = data[6];
15            3'b111: Y = data[7];
16        endcase
17    end
18 endmodule

```

Table: 8:1 MUX Selection

S2	S1	S0	Output
0	0	0	data[0]
0	0	1	data[1]
1	0	0	data[4]
1	1	1	data[7]

Table 17. 8:1 MUX Truth Table (Partial)

**Mnemonic**

“Case-Always: Use case statement in always block”

**Question 5(c) [7 marks]**

Implement 4 bit full adder using structural modeling style in Verilog.

**Solution****Verilog Code (Structural):**

```

1  module full_adder(
2      input a, b, cin,
3      output sum, cout
4  );
5      assign sum = a ^ b ^ cin;
6      assign cout = (a & b) | (cin & (a ^ b));
7  endmodule
8
9  module full_adder_4bit(
10     input [3:0] a, b,
11     input cin,
12     output [3:0] sum,
13     output cout
14 );
15     wire c1, c2, c3;
16
17     // Instantiating 4 Full Adders
18     full_adder fa0(.a(a[0]), .b(b[0]), .cin(cin),
19                   .sum(sum[0]), .cout(c1));
20     full_adder fa1(.a(a[1]), .b(b[1]), .cin(c1),
21                   .sum(sum[1]), .cout(c2));
22     full_adder fa2(.a(a[2]), .b(b[2]), .cin(c2),
23                   .sum(sum[2]), .cout(c3));
24     full_adder fa3(.a(a[3]), .b(b[3]), .cin(c3),
25                   .sum(sum[3]), .cout(cout));
26 endmodule

```

**Table: Ripple Carry Addition**

Stage	Inputs	Carry In	Sum	Carry Out
<b>FA0</b>	A[0], B[0]	Cin	S[0]	C1
<b>FA1</b>	A[1], B[1]	C1	S[1]	C2
<b>FA2</b>	A[2], B[2]	C2	S[2]	C3
<b>FA3</b>	A[3], B[3]	C3	S[3]	Cout

Table 18. Ripple Carry Structure

**Mnemonic**

“RCC - Ripple Carry Chain connection”

**Question 5(a OR) [3 marks]**

Implement logic function  $Y = ((AF(D + E)) + (B + C))'$  using CMOS.

**Solution**

Function:  $Y = \overline{(A \cdot F \cdot (D + E)) + (B + C)}$ . **PDN (Implementation of Function):**

- Block 1:  $B, C$  in Parallel (OR).
- Block 2:  $D, E$  in Parallel (OR)  $\rightarrow$  Series with  $A, F$  (AND).
- Top level: Block 1 || Block 2.

**PUN (Implementation of Dual):**

- Block 1:  $B, C$  in Series.
- Block 2:  $D, E$  in Series  $\rightarrow$  Parallel with  $A, F$ .
- Top level: Block 1 - Block 2 (Series).

 


Figure 18. CMOS Implementation of Y

**Mnemonic**

“PNAI - PMOS Network Applies Inversion”

**Question 5(b OR) [4 marks]**

Implement 4 bit up counter using Verilog

**Solution**

```

1  module counter_4bit_up(
2      input clk, reset,
3      output reg [3:0] count
4  );
5      always @(posedge clk or posedge reset) begin
6          if (reset)
7              count <= 4'b0000;
8          else
9              count <= count + 1;
10     end
11 endmodule

```

**Table: Counter Sequence**

Clock	Reset	Count	Next Count
↑	1	X	0000
↑	0	0000	0001
↑	0	1111	0000

**Table 19.** Counter Sequence

**Mnemonic**

“SRA - Synchronous Reset with Auto rollover”

**Question 5(c OR) [7 marks]**

Implement 3:8 decoder using behavioral modeling style in Verilog.

**Solution**

```

1  module decoder_3to8(
2      input [2:0] select,
3      input enable,
4      output reg [7:0] out
5  );
6      always @(*) begin
7          if (enable) begin
8              case(select)
9                  3'b000: out = 8'b00000001;
10                 3'b001: out = 8'b00000010;
11                 3'b010: out = 8'b00000100;
12                 3'b011: out = 8'b00001000;
13                 3'b100: out = 8'b00010000;

```

```
14         3'b101: out = 8'b00100000;  
15         3'b110: out = 8'b01000000;  
16         3'b111: out = 8'b10000000;  
17         default: out = 8'b00000000;  
18     endcase  
19 end else begin  
20     out = 8'b00000000;  
21 end  
22 end  
23 endmodule
```

**Applications:**

- **Memory addressing:** Chip select generation.
- **Data routing:** Channel selection.
- **Control logic:** State machine outputs.

**Mnemonic**

“BEOH - Behavioral Enable One-Hot decoder”