

Subject Name Solutions

1333201 – Winter 2023

Semester 1 Study Material

Detailed Solutions and Explanations

Question 1(a) [3 marks]

Define: (A) Amplitude Modulation, (B) Frequency Modulation, and (C) Phase Modulation

Solution

Table 1: Types of Modulation Techniques

Modulation Type	Definition
Amplitude Modulation (AM)	Process where amplitude of carrier signal is varied according to the instantaneous value of modulating signal while frequency remains constant
Frequency Modulation (FM)	Process where frequency of carrier signal is varied according to the instantaneous value of modulating signal while amplitude remains constant
Phase Modulation (PM)	Process where phase of carrier signal is varied according to the instantaneous value of modulating signal while amplitude remains constant

Mnemonic

“A-F-P: Amplitude changes, Frequency shifts, Phase adjusts”

Question 1(b) [4 marks]

Explain the need for modulation.

Solution

Table 2: Need for Modulation

Need	Explanation
Practical Antenna Size	Reduces antenna size by increasing frequency (Antenna length = $\lambda/4$)
Interference Reduction	Allows multiple signals to be transmitted simultaneously on different frequencies
Range Extension	Higher frequency signals travel farther in atmosphere
Multiplexing	Enables multiple signals to share communication medium

Diagram:

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph TD
    A[Need for Modulation] --> B[Practical Antenna Size]
    A --> C[Interference Reduction]
    A --> D[Range Extension]
    A --> E[Multiplexing]
{Highlighting}
{Shaded}
```

Mnemonic

“PIRM: Practical antennas, Interference reduction, Range extension, Multiplexing”

Question 1(c) [7 marks]

A modulating signal has amplitude of 3 V and frequency of 1 KHz is amplitude modulated by a carrier of amplitude 10 V and frequency 30KHz. Find modulation index, frequencies of sideband components and their amplitudes. Also draw the spectrum of AM wave.

Solution


Table 3: Given Information

Parameter	Modulating Signal	Carrier Signal
Amplitude	3 V	10 V
Frequency	1 kHz	30 kHz

Calculations:

- Modulation Index (m) = $A_m/A_c = 3/10 = 0.3$
- Sideband Frequencies = $f_c \pm f_m = 30 \pm 1 = 29\text{kHz and } 31\text{kHz}$
- Sideband Amplitudes = $m \times A_c/2 = 0.3 \times 10/2 = 1.5\text{V}$

Diagram: AM Spectrum

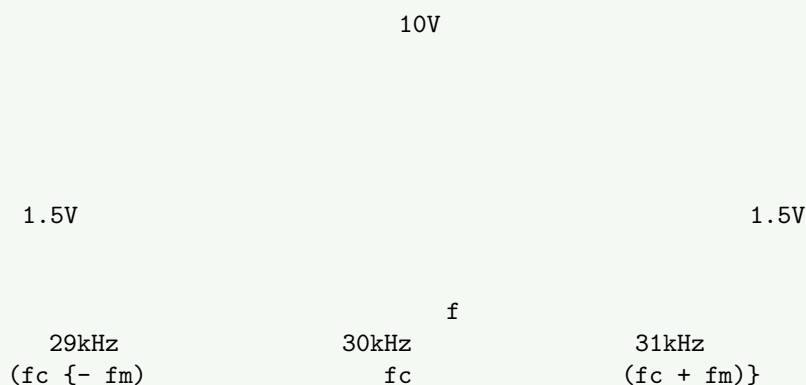

Mnemonic

“LSB-C-USB: Lower sideband, Carrier, Upper sideband at 29-30-31”

Question 1(c) OR [7 marks]

Derive mathematical relation between carrier powers, and modulated signal power for AM.

Solution

Mathematical Relation:

- Carrier signal: $c(t) = A_c \cos(2 f_c \cdot t)$
- Modulating signal: $m(t) = A_m \cos(2 f_m \cdot t)$
- AM signal: $s(t) = A_c[1 + m \cdot \cos(2 f_m \cdot t)] \cdot \cos(2 f_c \cdot t)$

Table 4: Power Distribution in AM

Component	Expression	In Terms of P_c
Carrier Power (P_c)	$A_c^2/2$	P_c
Total Sideband Power (P_s)	$m^2 A_c^2/4$	$m^2 P_c/2$
Total AM Power (P_t)	$P_c(1 + m^2/2)$	$P_c(1 + m^2/2)$

Diagram: Power Distribution

```
pie
    title "Power Distribution in AM (m=1)"
    "Carrier Power" : 66.7
    "Sideband Power" : 33.3
```

- Modulation Efficiency** = $P_s/P_t = (m^2/2)/(1 + m^2/2) \times 100\%$

Mnemonic

“Total Power = Carrier Power $\times (1 + m^2/2)$ ”

Question 2(a) [3 marks]

Compare AM and FM.

Solution

Table 5: Comparison between AM and FM

Parameter	AM	FM
Modulation Parameter	Amplitude varies	Frequency varies
Bandwidth	$2 \times f_m$	$2 \times (f + f_m)$
Noise Immunity	Poor	Excellent
Power Efficiency	Low	High
Circuit Complexity	Simple	Complex

Mnemonic

“ABNPC: Amplitude/Bandwidth/Noise/Power/Complexity differences”

Question 2(b) [4 marks]

Explain envelope detector with the help of circuit diagram.

Solution

Diagram: Envelope Detector Circuit

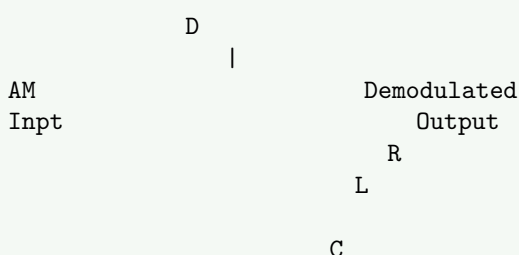


Table 6: Envelope Detector Components

Component	Function
Diode (D)	Rectifies AM signal to extract positive half cycles
Capacitor (C)	Charges to peak of input, holds charge between peaks
Resistor (RL)	Discharges capacitor at rate suitable for envelope extraction

Time Constant Selection:

- $1/f_m \ll RC \ll 1/f_c$ (for proper envelope detection)

Mnemonic

“DCR: Diode rectifies, Capacitor charges, Resistor discharges”

Question 2(c) [7 marks]

Draw and explain the block diagram of Superheterodyne receiver.

Solution**Diagram: Superheterodyne Receiver****Mermaid Diagram (Code)**

```
{Shaded}
{Highlighting}[]
graph LR
    A[Antenna] --> B[RF Amplifier]
    B --> C[Mixer]
    D[Local Oscillator] --> C
    C --> E[IF Amplifier]
    E --> F[Detector]
    F --> G[AF Amplifier]
    G --> H[Speaker]
{Highlighting}
{Shaded}
```

Table 7: Functions of Superheterodyne Receiver Blocks

Block	Function
RF Amplifier	Amplifies weak RF signal, provides selectivity, rejects image frequency
Local Oscillator	Generates frequency $f_o = f_{RF} + f_{IF}$ for mixing
Mixer	Combines RF signal with local oscillator to produce IF (Intermediate Frequency)
IF Amplifier	Provides most of the receiver gain and selectivity at fixed frequency
Detector	Extracts the modulating signal from the IF signal
AF Amplifier	Amplifies recovered audio to drive speaker

Mnemonic

“RLMIDS: RF, Local oscillator, Mixer, IF, Detector, Speaker”

Question 2(a) OR [3 marks]

Define the followings terms: (A) Sensitivity, and (B) Selectivity

Solution

Table 8: Receiver Characteristics

Term	Definition
Sensitivity	Ability of receiver to detect and amplify weak signals; measured as minimum input signal strength (μV) needed for standard output
Selectivity	Ability of receiver to separate desired signal from adjacent channels; measured as ratio of response at resonant frequency to off-resonant frequency

Diagram: Selectivity Curve

Response

f1 fc f2 Frequency

Mnemonic

“SS: Signal Strength for Sensitivity, Signal Separation for Selectivity”

Question 2(b) OR [4 marks]

Describe the block diagram of general communication system.

Solution

Diagram: General Communication System

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Information Source] --> B[Transmitter]
    B --> C[Channel]
    C --> D[Receiver]
    D --> E[Destination]
    F[Noise Source] --> C
{Highlighting}
{Shaded}
```

Table 9: Components of Communication System

Component	Function
Information Source	Generates message to be communicated (voice, data, video)
Transmitter	Converts message into signals suitable for transmission
Channel	Medium through which signals travel (wire, fiber, air)
Receiver	Extracts original message from received signals
Destination	Entity for which message is intended
Noise Source	Unwanted signals that interfere with the message

Mnemonic

“I-T-C-R-D: Information Travels Carefully, Reaches Destination”

Question 2(c) OR [7 marks]

Solution

Diagram: Superheterodyne FM Receiver

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Antenna] --> B[RF Amplifier]
    B --> C[Mixer]
    D[Local Oscillator] --> C
    C --> E[IF Amplifier]
    E --> F[Limiter]
    F --> G[FM Discriminator]
    G --> H[De-emphasis]
    H --> I[AF Amplifier]
    I --> J[Speaker]
{Highlighting}
{Shaded}
```

Table 10: Additional Components in FM Receiver

Component	Function
Limiter	Removes amplitude variations, provides constant amplitude signal
FM Discriminator	Converts frequency variations to amplitude variations (demodulation)
De-emphasis	Attenuates higher frequencies boosted at transmitter

Unique Aspects of FM Receiver:

- Uses wider bandwidth IF amplifier (200 kHz vs 10 kHz for AM)
- Requires limiter stage for noise reduction
- Employs specialized discriminator for FM demodulation

Mnemonic

“MILD: Mixer, IF, Limiter, Discriminator - key components in FM reception”


Question 3(a) [3 marks]

Solution

Table 11: Impulse and Pulse Characteristics

Signal	Time Domain	Frequency Domain
Impulse	Infinitely narrow spike with infinite amplitude	Flat spectrum with all frequencies equally present
Pulse	Rectangular shape with finite width and height	Sinc function $(\sin(x)/x)$ shape

Diagram: Impulse and Pulse

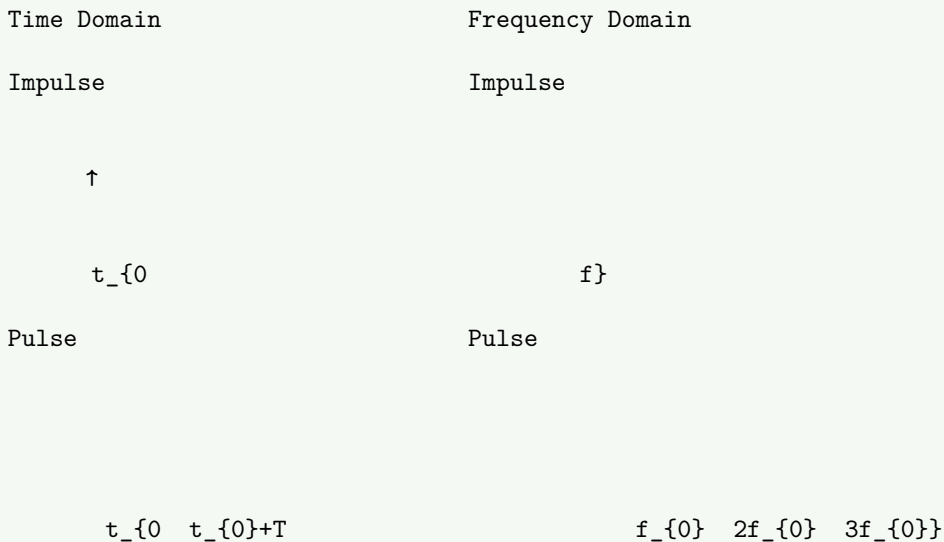

Mnemonic

“I-P: Impulse is a Pinpoint spike, Pulse has Persistent width”

Question 3(b) [4 marks]

Solution

Table 12: Types of Sampling

Type of Sampling	Description	Effect
Under Sampling	Sampling frequency $f_s < 2f_m$ (less than Nyquist rate)	Aliasing occurs; signal cannot be recovered
Critical Sampling	Sampling frequency $f_s = 2f_m$ (exactly Nyquist rate)	Theoretically perfect reconstruction possible
Over Sampling	Sampling frequency $f_s > 2f_m$ (exceeds Nyquist rate)	Better reconstruction, easier filtering

Diagram: Under Sampling vs Critical Sampling

Under Sampling ($f_s < 2f_m$)

↑ ↑ ↑ ↑ ↑

Aliasing occurs {- samples too far apart}

Critical Sampling ($f_s = 2f_m$)

↑ ↑ ↑ ↑ ↑ ↑ ↑ ↑

Just enough samples to reconstruct

Mnemonic

“UCO: Under ($f_s < 2f_m$), Critical ($f_s = 2f_m$), Over ($f_s > 2f_m$)”

Question 3(c) [7 marks]

Solution

Table 13: Pulse Modulation Techniques

Technique	Description	Signal Parameter Varied
PAM (Pulse Amplitude Modulation)	Amplitude of pulses varies according to modulating signal	Amplitude
PWM (Pulse Width Modulation)	Width/duration of pulses varies according to modulating signal	Pulse width
PPM (Pulse Position Modulation)	Position/timing of pulses varies according to modulating signal	Pulse position

Diagram: PAM, PWM, PPM Waveforms

Modulating Signal

/ {}
/ {}
/ { /}
/ { / }
/ { / }
/ { / }
{/ }

PAM

PWM

PPM

Mnemonic

“APP: Amplitude, Position, Pulse-width change respectively”

Question 3(a) OR [3 marks]

Solution


Sampling Theorem Statement: “A band-limited continuous-time signal can be completely represented by and reconstructed from its samples, if the sampling frequency is at least twice the highest frequency component in the signal.”

Table 14: Key Elements of Sampling Theorem


Term	Description
Nyquist Rate	Minimum sampling frequency (f_s) required = $2f_m$
Nyquist Interval	Maximum time between samples = $1/(2f_m)$
Band-limited Signal	Signal with finite highest frequency component

Diagram: Proper Sampling

Original Signal

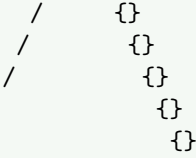

Sampled at $f_s = 2f_m$

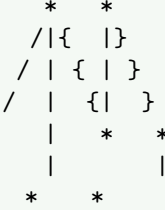

Mnemonic

“2F: Frequency must be sampled at least Twice its highest Frequency”

Question 3(b) OR [4 marks]

Solution


Table 15: Quantization Concepts

Term	Description
Quantization	Process of converting continuous amplitude values into discrete levels
Quantization Levels	Total number of discrete values used (usually 2^n)
Quantization Step Size	Voltage difference between adjacent levels ($Q = V_{max}/2^n$)
Quantization Error	Difference between actual signal value and quantized value

Diagram: Quantization Process

Continuous Signal

Quantized Signal

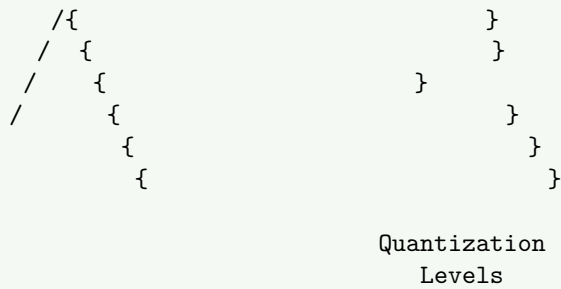

Mnemonic

“LSED: Levels, Step size, Error, Discrete values”

Question 3(c) OR [7 marks]

Solution

Table 16: Companding Concepts

Term	Description
Companding	COMpressing + exPANDING; non-linear quantization technique
Compression	Reduces amplitude range of signal before transmission
Expansion	Restores original amplitude range at receiver
Purpose	Improves SNR for weak signals while maintaining dynamic range
Types	-law (North America, Japan), A-law (Europe)

Diagram: Companding Process

Mermaid Diagram (Code)

```

graph LR
    A[Input Signal] --> B[Compressor]
    B --> C[Uniform Quantizer]
    C --> D[Digital Transmission]
    D --> E[Digital Reception]
    E --> F[Expander]
    F --> G[Output Signal]
  
```

Companding Laws:

- **-law:** $y = \text{sgn}(x) \times \ln(1 + |x|) / \ln(1 + \frac{1}{A})$ where $A = 255$ in USA
- **A-law:** $y = \text{sgn}(x) \times A|x| / (1 + \ln(A))$ for $|x| < 1/A$; $y = \text{sgn}(x) \times (1 + \ln(A|x|)) / (1 + \ln(A))$ for $1/A \leq |x| \leq 1$

Mnemonic

“CEQS: Compress, Encode, Quantize, Send; then Decode, Expand, Recover”


Question 4(a) [3 marks]

Solution

Table 17: Delta Modulation Concepts

Concept	Description
Delta Modulation	Simplest form of DPCM where only 1-bit quantization is used
Step Size	Fixed increment/decrement in approximating signal
Output	Binary stream (1 for increase, 0 for decrease)
Advantages	Simple implementation, low bandwidth

Diagram: Delta Modulation

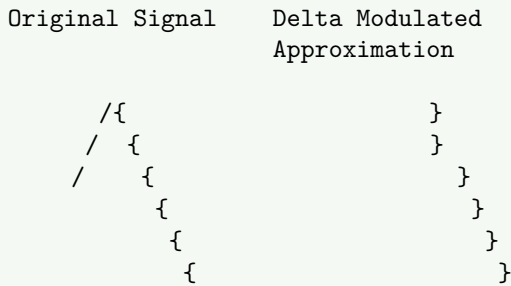

Binary Output: 1 1 1 1 0 0 0 0 0

Mnemonic

“1B1S: 1-Bit, 1-Step tracking”

Question 4(b) [4 marks]

Solution

Table 18: Advantages and Disadvantages of PCM

Advantages	Disadvantages
High noise immunity	Requires higher bandwidth
Better signal quality	Complex system implementation
Compatible with digital systems	Quantization noise present
Secure transmission possible	Synchronization required
Multiplexing capability	Higher power requirement

Diagram: PCM System Overview

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Analog Signal] --> B[Sampling]
    B --> C[Quantization]
    C --> D[Encoding]
    D --> E[Digital Transmission]
    E --> F[Decoding]
    F --> G[Reconstruction]
    G --> H[Analog Output]
{Highlighting}
{Shaded}
```

Mnemonic

“NCSMP: Noise immunity, Compatible with digital, Secure, Multiplexing, Processing benefits”

Question 4(c) [7 marks]

Solution

Diagram: PCM-TDM System

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    subgraph "Transmitter"
        A1[Analog Input 1] --> B1[Anti-aliasing Filter]
        B1 --> C1[Sample & Hold]
        A2[Analog Input 2] --> B2[Anti-aliasing Filter]
        B2 --> C2[Sample & Hold]
        A3[Analog Input 3] --> B3[Anti-aliasing Filter]
        B3 --> C3[Sample & Hold]
        C1 & C2 & C3 --> D[Multiplexer]
        D --> E[Quantizer]
        E --> F[Encoder]
        F --> G[Frame Generator]
    end

    G --> H[Transmission Channel]

    subgraph "Receiver"
        H --> I[Frame Synchronizer]
        I --> J[Decoder]
        J --> K[Demultiplexer]
        K --> L1[Reconstruction Filter 1]
        K --> L2[Reconstruction Filter 2]
        K --> L3[Reconstruction Filter 3]
        L1 --> M1[Output 1]
        L2 --> M2[Output 2]
        L3 --> M3[Output 3]
    end
end
{Highlighting}
{Shaded}
```

Table 19: PCM-TDM System Components

Component	Function
Anti-aliasing Filter	Limits signal bandwidth to avoid aliasing
Sample & Hold	Captures analog value and holds it for processing
Multiplexer	Combines multiple input channels into single time division multiplexed stream
Quantizer	Converts continuous samples to discrete values
Encoder	Converts quantized values to binary code
Frame Generator	Adds synchronization and control bits
Demultiplexer	Separates combined signal back into individual channels
Reconstruction Filter	Smooths the decoded signal to recover analog waveform

Mnemonic

“SAMPLER: Sample, Amplify, Multiplex, Process, Limit, Encode, Reconstruct”

Question 4(a) OR [3 marks]


Solution

Table 20: Slope Overload Error

Concept	Description
Slope Overload Error	Error occurring when input signal changes faster than DM step size can track
Cause	Fixed step size in Delta Modulation too small for steep input slopes
Effect	Distortion in reconstructed signal, particularly at high frequencies
Solution	Adaptive Delta Modulation (variable step size)

Diagram: Slope Overload Error

Original Signal vs DM Approximation

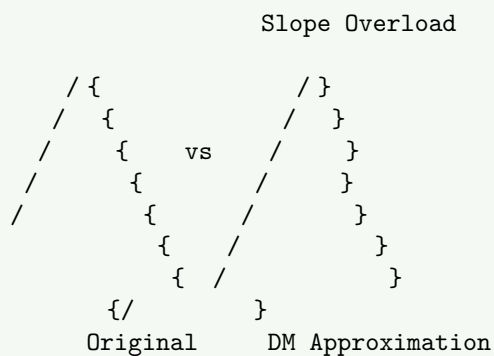

Mnemonic

“SOS: Signal Outpaces Steps when slope is steep”

Question 4(b) OR [4 marks]

Solution

Diagram: DPCM Transmitter

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Analog Input] --> B[Sample & Hold]
    B --> C[Difference Calculator]
    C --> D[Quantizer]
    D --> E[Encoder]
    E --> F[Digital Output]
    F --> G[Decoder]
    G --> H[Predictor]
    H --> C
```

{Highlighting}
{Shaded}

Table 21: DPCM Transmitter Components

Component	Function
Sample & Hold	Captures analog signal at regular intervals
Difference Calculator	Computes error between current sample and predicted value
Quantizer	Converts error signal to discrete levels
Encoder	Converts quantized values to binary code
Predictor	Estimates next sample based on previous values
Decoder	Same as in receiver, used in feedback loop

Key Advantage:

- Transmits only the difference between successive samples
- Reduces bit rate compared to standard PCM

Mnemonic

“SDQEP: Sample, Difference, Quantize, Encode, Predict”

Question 4(c) OR [7 marks]

Solution

Diagram: PCM Transmitter

Mermaid Diagram (Code)

```
graph LR
    A[Analog Input] --> B[Anti-aliasing Filter]
    B --> C[Sample & Hold]
    C --> D[Quantizer]
    D --> E[Encoder]
    E --> F[Digital Output]
```

Table 22: PCM Transmitter Components in Detail

Component	Function	Design Considerations
Anti-aliasing Filter	Limits input bandwidth to $f_s/2$	Cutoff frequency $< f_s/2$, sharp roll-off
Sample & Hold	Captures instantaneous signal value	Sampling rate $\geq 2f_m$, $aperture\ time \ll sampling\ period$
Quantizer	Approximates sample amplitudes to discrete levels	Levels = 2^n where n = bit depth, typically 8-16 bits
Encoder	Converts quantized values to digital codes	Uses coding schemes like NRZ, RZ, Manchester
Line Coder	Prepares binary sequence for transmission	May use regenerative repeaters for long distance

Signal Processing Details:

- **Time Domain:** Sampling at intervals $T_s = 1/f_s$
- **Amplitude Domain:** Quantizing continuous amplitudes into 2^n discrete levels
- **Code Domain:** Converting levels to n-bit binary code

Mnemonic

“SAFE-Q: Sample And Filter, then Encode after Quantizing”

Question 5(a) [3 marks]**Solution**

Table 23: Comparison of PCM and DM

Parameter	PCM	DM
Bit Rate	Higher (multiple bits per sample)	Lower (1 bit per sample)
Circuit Complexity	More complex	Simpler
Signal Quality	Better	Lower, suffers from slope overload & granular noise
Bandwidth	Wider	Narrower
Sampling Rate	At least $2f_m$	Much higher than $2f_m$

Mnemonic

“BCSBS: Bit rate, Complexity, Signal quality, Bandwidth, Sampling”

Question 5(b) [4 marks]**Solution**

Table 24: Antenna Terminology

Term	Definition
Antenna	Device that converts electrical signals into electromagnetic waves and vice versa
Radiation Pattern	Graphical representation of radiation properties of antenna as function of space coordinates
Directivity	Ratio of radiation intensity in a given direction to average radiation intensity
Polarization	Orientation of electric field vector of electromagnetic wave radiated by antenna

Diagram: Radiation Pattern

Mnemonic

“ARDP: Antennas Radiate with Directivity and Polarization”

Question 5(c) [7 marks]

Solution

0.0.1

Table 25: Smart Antenna Characteristics

0.0.2

Table 26: Parabolic Reflector Characteristics

Mnemonic

“PFHS: Parabolic Focus gives High Signal strength”

Question 5(a) OR [3 marks]

Solution

Table 27: Microstrip Antenna Characteristics

Feature	Description
Structure	Conductive patch on dielectric substrate with ground plane
Shape	Rectangular, circular, elliptical, triangular patches
Size	Typically $\lambda/2$ in length, very thin ($h \ll \lambda$)
Advantages	Low profile, lightweight, low cost, easy fabrication, compatible with PCB technology
Disadvantages	Low efficiency, narrow bandwidth, low power handling

Diagram: Microstrip Patch Antenna

Patch (Copper)

Dielectric Substrate
(FR4, PTFE, etc.)

Ground Plane (Copper)

Mnemonic

“PDGF: Patch on Dielectric with Ground plane gives Flat profile”

Question 5(b) OR [4 marks]

Solution

Table 28: EM Wave Spectrum and Applications

Band	Frequency Range	Wavelength	Applications
ELF	3 Hz - 30 Hz	10,000 - 100,000 km	Submarine communication
VLF	3 kHz - 30 kHz	10 - 100 km	Navigation, time signals
LF	30 kHz - 300 kHz	1 - 10 km	AM radio, maritime radio
MF	300 kHz - 3 MHz	100 m - 1 km	AM broadcasting
HF	3 MHz - 30 MHz	10 - 100 m	Shortwave radio, amateur radio
VHF	30 MHz - 300 MHz	1 - 10 m	FM radio, TV broadcasting
UHF	300 MHz - 3 GHz	10 cm - 1 m	TV, mobile phones, WiFi
SHF	3 GHz - 30 GHz	1 - 10 cm	Satellite, radar, 5G
EHF	30 GHz - 300 GHz	1 mm - 1 cm	Radio astronomy, security scanning
IR	300 GHz - 400 THz	750 nm - 1 mm	Thermal imaging, remote control
Visible	400 THz - 800 THz	380 - 750 nm	Optical communications

Diagram: EM Wave Spectrum

Mermaid Diagram (Code)

```
{Shaded}
{Highlighting}[]
graph LR
    A[Radio] --{} B[Microwave]}
    B --{} C[IR]}
    C --{} D[Visible]}
    D --{} E[UV]}
    E --{} F[X-Ray]}
    F --{} G[Gamma]}

    style A fill:#0077be
    style B fill:#00a2e8
    style C fill:#ff7f00
    style D fill:#ffff00
    style E fill:#8a2be2
    style F fill:#0f52ba
    style G fill:#800080
{Highlighting}
{Shaded}
```

Mnemonic

“RVMIXG: Radio, Visible, Microwave, Infrared, X-ray, Gamma”

Question 5(c) OR [7 marks]

Solution

0.0.3

Table 29: Space Wave Propagation Characteristics

0.0.4

Table 30: Ground Wave Characteristics

Mnemonic

“SHGM: Space waves go High, Ground waves hug Medium surface”