

Subject Name Solutions

4341101 – Winter 2024

Semester 1 Study Material

Detailed Solutions and Explanations

Question 1(a) [3 marks]

List Common features of Microcontrollers.

Solution

Feature	Purpose
CPU Core	Process instructions
Memory (RAM/ROM)	Store program and data
I/O Ports	Interface with external devices
Timers/Counters	Measure time intervals
Interrupts	Handle asynchronous events
Serial Communication	Transfer data with other devices

Mnemonic

“CRITICS: CPU ROM I/O Timers Interrupts Comm Serial”


Question 1(b) [4 marks]

Explain the functions of ALU.

Solution

Function	Description
Arithmetic Operations	Addition, subtraction, increment, decrement
Logical Operations	AND, OR, XOR, NOT, comparison
Data Movement	Transfer between registers and memory
Flag Setting	Update status flags based on operation results

Diagram:

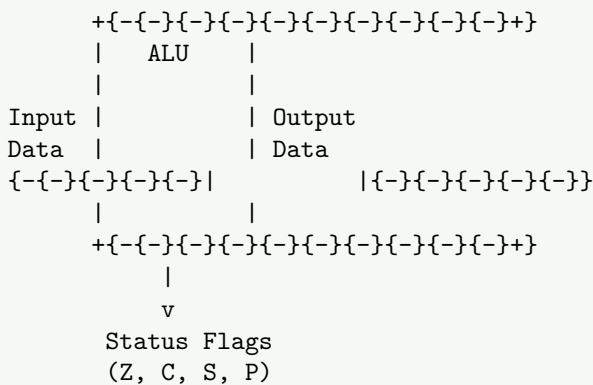

Mnemonic

“ALFS: Arithmetic Logic Flags Status”

Question 1(c) [7 marks]

Define: Memory, Operand, Instruction Cycle, Opcode, CU, Machine Cycle, CISC

Solution

Term	Definition
Memory	Storage unit that holds data and instructions
Operand	Data value or address used in an operation
Instruction Cycle	Complete process of fetching and executing an instruction
Opcode	Operation code that specifies the instruction type
CU	Control Unit that coordinates processor operations
Machine Cycle	Basic operation cycle consisting of T-states
CISC	Complex Instruction Set Computer with rich instruction set

- **Memory:** Organized array of storage cells with unique addresses
- **Operand:** Data elements that instructions operate upon
- **Instruction Cycle:** Fetch-decode-execute sequence for each instruction
- **Opcode:** Binary code that tells processor what operation to perform

Diagram:

Instruction Cycle:

+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+	+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+	+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+
Fetch	{-}{-}{-} Decode	{-}{-}{-} Execute }
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+	+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+	+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+

Mnemonic

“MO-ICO-MC: Memory-Operand-Instruction-Control-Operation-Machine-Complex”

Question 1(c OR) [7 marks]

i) Define: Microprocessor. ii) Compare Von-Neumann and Harvard architecture.

Solution

i) Microprocessor Definition:

An integrated circuit containing the CPU functionality of a computer, capable of fetching, decoding, and executing instructions with ALU and control circuitry on a single chip.

ii) Von-Neumann vs Harvard Architecture:

Feature	Von-Neumann	Harvard
Memory	Single shared memory	Separate program & data memory
Bus	Single bus for data & instructions	Separate buses
Speed	Slower (memory bottleneck)	Faster (parallel access)
Complexity	Simpler design	More complex
Applications	General computing	Real-time systems

Diagram:

```

graph LR
    Fetch[Fetch] -- Fetch --> Decode[Decode]
    Decode -- Decode --> Execute[Execute]
    Execute -- Execute --> Fetch
    Fetch -- "Next Instruction Cycle" --> Fetch
    Decode -- "Next Instruction Cycle" --> Decode
    Execute -- "Next Instruction Cycle" --> Execute
  
```

Mnemonic


“FDE: First Get, Then Understand, Finally Do”

Question 2(c) [7 marks]

Describe block diagram of 8085 microprocessor with the help of neat diagram.

Solution	
Block	Function
ALU	Arithmetic & logical operations
Register Array	Temporary data storage
Instruction Register & Decoder	Hold & interpret instructions
Control & Timing Unit	Generate control signals
Address Buffer	Interface with address bus
Data Buffer	Interface with data bus
Serial I/O	Communication with SID/SOD
Interrupt Control	Handle interrupt requests

Diagram:

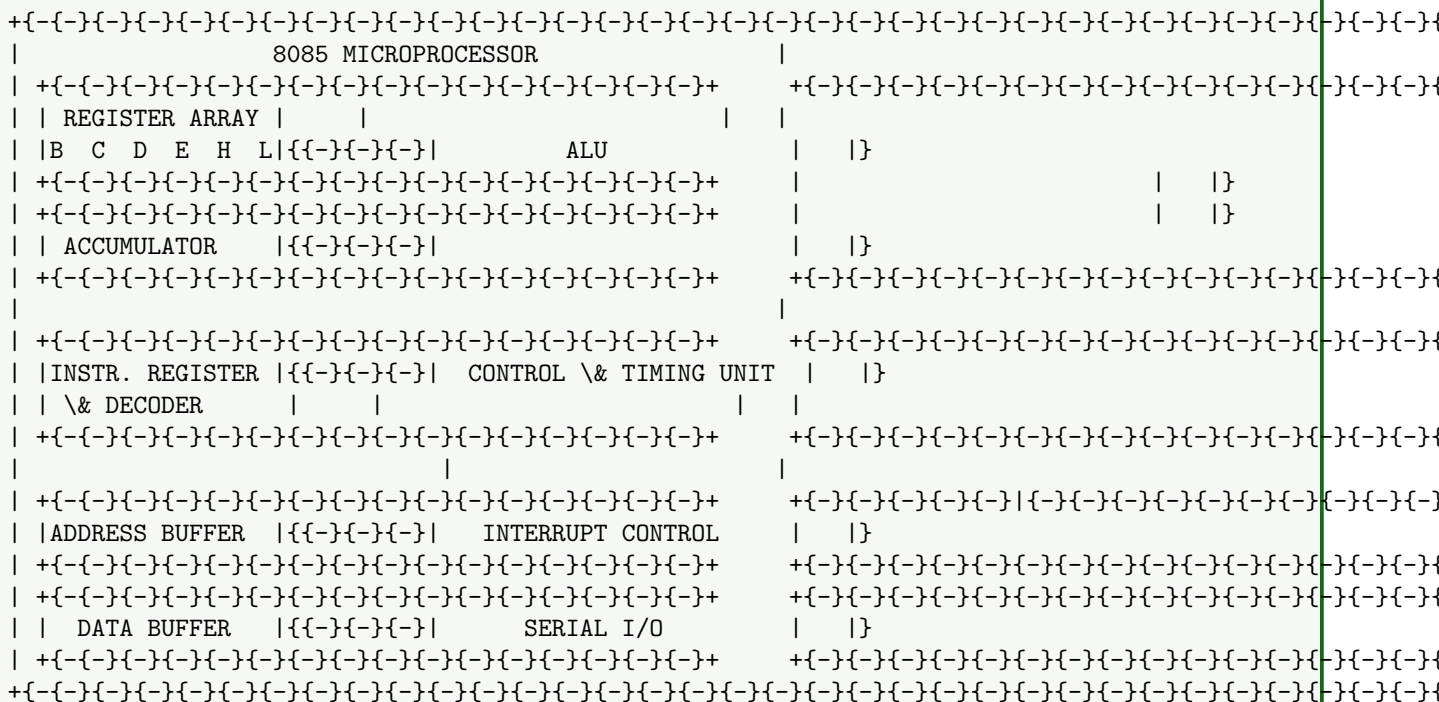

- **Core Components:** ALU and registers form processing core
- **Control Path:** Instructions flow through register, decoder, control unit
- **Data Path:** Data moves through buffers to/from external buses
- **Timing:** Synchronizes all operations via internal clock

Mnemonic

“RAID: Registers-ALU-Instructions-Decoders”

Question 2(a OR) [3 marks]

Compare Microprocessor & Microcontroller.

Solution

Feature	Microprocessor	Microcontroller
Design	CPU only	CPU + peripherals
Memory	External	Internal (RAM/ROM)
I/O ports	Limited	Many built-in
Applications	General computing	Embedded systems
Cost	Higher	Lower
Example	Intel 8085/8086	Intel 8051

Mnemonic

“Micro-P Processes, Micro-C Controls”


Question 2(b OR) [4 marks]

Explain De-multiplexing of Address and Data buses for 8085 Microprocessor.

Solution

Step	Action
1	ALE signal goes high
2	Lower address (A0-A7) appears on AD0-AD7
3	Latch captures address using ALE
4	ALE goes low, AD0-AD7 now carries data

Diagram:

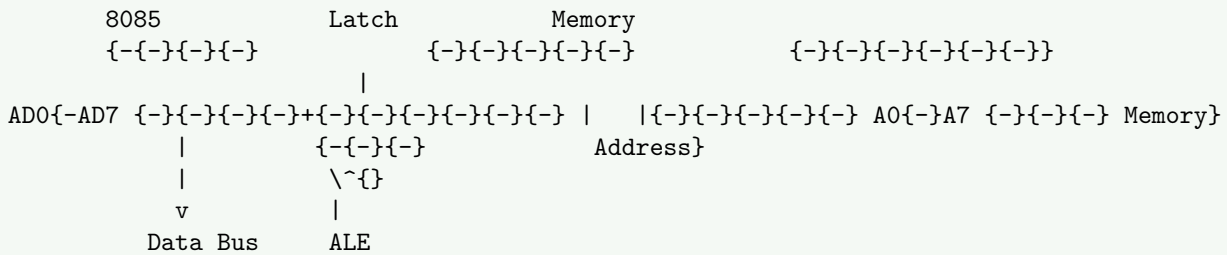

- **Multiplexing:** AD0-AD7 pins carry address and data at different times
- **ALE Signal:** Address Latch Enable controls when address is captured
- **8-bit Latch:** Holds lower address bits during entire machine cycle
- **Timing:** Address valid only during high state of ALE pulse

Mnemonic

“ALAD: ALE Latches Address before Data”

Question 2(c OR) [7 marks]

Describe Pin diagram of 8085 microprocessor with the help of neat diagram.

Solution

Pin Group	Function
Address/Data	Multiplexed AD0-AD7, A8-A15
Control	RD, WR, IO/M, S0, S1, ALE, CLK
Interrupts	INTR, RST 5.5-7.5, TRAP
DMA	HOLD, HLDA
Power	Vcc, Vss
Serial I/O	SID, SOD
Reset	RESET IN, RESET OUT

Diagram:

	X1	{-{-}-} 1	40 {-{-}-}	Vcc}
	X2	{-{-}-} 2	39 {-{-}-}	HOLD}
RESET	OUT	{-{-}-} 3	38 {-{-}-}	HLDA}
RESET	IN	{-{-}-} 4	37 {-{-}-}	CLK}
	IO/M	{-{-}-} 5	36 {-{-}-}	RESET IN}
	S1	{-{-}-} 6	35 {-{-}-}	READY}
	RD	{-{-}-} 7	34 {-{-}-}	IO/M}
	WR	{-{-}-} 8	33 {-{-}-}	S1}
ALE		{-{-}-} 9	32 {-{-}-}	RD}
	S0	{-{-}-} 10	31 {-{-}-}	WR}
A15		{-{-}-} 11	30 {-{-}-}	ALE}
A14		{-{-}-} 12	29 {-{-}-}	S0}
A13		{-{-}-} 13	28 {-{-}-}	A15}
A12		{-{-}-} 14	27 {-{-}-}	A14}
A11		{-{-}-} 15	26 {-{-}-}	A13}
A10		{-{-}-} 16	25 {-{-}-}	A12}
A9		{-{-}-} 17	24 {-{-}-}	A11}
A8		{-{-}-} 18	23 {-{-}-}	A10}
AD7		{-{-}-} 19	22 {-{-}-}	A9}
AD6		{-{-}-} 20	21 {-{-}-}	A8}
			+{-{-}-}{-{-}-}{-{-}-}{-{-}-}+	

- **Address Pins:** A8-A15 (8) and multiplexed AD0-AD7 (8) for 16-bit addressing
- **Control Pins:** Generate timing and control signals for peripheral devices
- **Interrupt Pins:** Hardware interrupt handling with priority levels
- **Clock:** X1, X2 for crystal connection, CLK for synchronization
- **Power:** Vcc (+5V) and Vss (Ground) for power supply

Mnemonic

“ACID-PS: Address-Control-Interrupt-DMA-Power-Serial”

Question 3(a) [3 marks]

Explain interrupts of 8051 microcontroller.

Solution

Interrupt	Vector	Priority	Source
External 0	0003H	1 (IP.0)	Pin INT0 (P3.2)
Timer 0	000BH	2 (IP.1)	Timer 0 overflow
External 1	0013H	3 (IP.2)	Pin INT1 (P3.3)
Timer 1	001BH	4 (IP.3)	Timer 1 overflow
Serial	0023H	5 (IP.4)	Serial port events

```
Diagram:
```

```
+{--}{--}{--}{--}{--}{--}+  
| 8051 |  
INT0 {--}{--}{--}|      |}  
|      |  
INT1 {--}{--}{--}|      | Interrupts are}  
|      | prioritized and  
TIMER0 {--}{--}|      | can be enabled/disabled}  
|      | individually  
TIMER1 {--}{--}|      |}  
|      |  
SERIAL {--}{--}|      |}  
+{--}{--}{--}{--}{--}{--}+
```

Mnemonic

“ETTES: External-Timer-Timer-External-Serial”

“ETTES: External-Timer-Timer-External-Serial”

Question 3(b) [4 marks]

Draw Pin diagram of 8051 microcontroller.

Solution

8051 Microcontroller		
+{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}+		
P1.0{--} 1	40	{--}{--}VCC}
P1.1{--} 2	39	{--}{--}P0.0/AD0}
P1.2{--} 3	38	{--}{--}P0.1/AD1}
P1.3{--} 4	37	{--}{--}P0.2/AD2}
P1.4{--} 5	36	{--}{--}P0.3/AD3}
P1.5{--} 6	35	{--}{--}P0.4/AD4}
P1.6{--} 7	34	{--}{--}P0.5/AD5}
P1.7{--} 8	33	{--}{--}P0.6/AD6}
RST {--} 9	32	{--}{--}P0.7/AD7}
P3.0/RXD 10	31	{--}{--}EA/VPP}
P3.1/TXD 11	30	{--}{--}ALE/PROG}
P3.2/INT0 12	29	{--}{--}PSEN}
P3.3/INT1 13	28	{--}{--}P2.7/A15}
P3.4/T0{- 14	27	{--}{--}P2.6/A14}
P3.5/T1{- 15	26	{--}{--}P2.5/A13}
P3.6/WR{- 16	25	{--}{--}P2.4/A12}
P3.7/RD{- 17	24	{--}{--}P2.3/A11}
XTAL2 {-{-} 18	23	{--}{--}P2.2/A10}
XTAL1 {-{-} 19	22	{--}{--}P2.1/A9}
VSS {-{-} 20	21	{--}{--}P2.0/A8}
{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}		

Pin Group	Function
P0	Port 0, multiplexed with address/data
P1	Port 1, general purpose I/O
P2	Port 2, upper address and I/O
P3	Port 3, special functions and I/O
XTAL	Crystal oscillator connections
Control	RST, EA, ALE, PSEN

Mnemonic

“PORT 0123: Data-General-Address-Special”

“PORT 0123: Data-General-Address-Special”

Question 3(c) [7 marks]

Explain Internal RAM Organization of 8051 microcontroller.

Solution

RAM Area	Address Range	Usage
Register Banks	00H-1FH	R0-R7 (4 banks)
Bit-addressable	20H-2FH	128 bits (0-7FH)
Scratch Pad	30H-7FH	General purpose
SFRs	80H-FFH	Control registers

Diagram:

8051 Internal RAM (128 bytes):

```
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 00H)
| Register Bank 0|
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 08H)
| Register Bank 1|
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 10H)
| Register Bank 2|
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 18H)
| Register Bank 3|
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 20H)
| Bit{addressable}|
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 30H)
|                               |
| Scratch Pad                   |
|                               |
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 80H)
```

Special Function Registers:

```
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ 80H}
|                                     |
| SFRs                             |
| (not all bytes                   |
| are used)                         |
|                                   |
+{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}{-}+ FFH}
```

- **Register Banks:** Four banks of 8 registers (R0-R7) selectable by PSW
- **Bit-addressable:** 16 bytes (128 bits) individually addressable as bits
- **General Purpose:** User variables and stack space
- **SFRs:** Control and status registers at higher addresses

Mnemonic

“RBBS: Registers Bits Buffer Special”

Question 3(a OR) [3 marks]

List SFRs with their addresses.

Solution

SFR	Address	Function
P0	80H	Port 0
SP	81H	Stack Pointer
DPL	82H	Data Pointer Low
DPH	83H	Data Pointer High


Question 3(c OR) [7 marks]

Explain block diagram of 8051 microcontroller.

Solution

Component	Function
CPU	8-bit processor with ALU
Memory	4K ROM, 128 bytes RAM
I/O Ports	Four 8-bit ports (P0-P3)
Timers	Two 16-bit timers/counters
Serial Port	Full-duplex UART
Interrupts	Five interrupt sources
Special Function Registers	Control registers

Diagram:

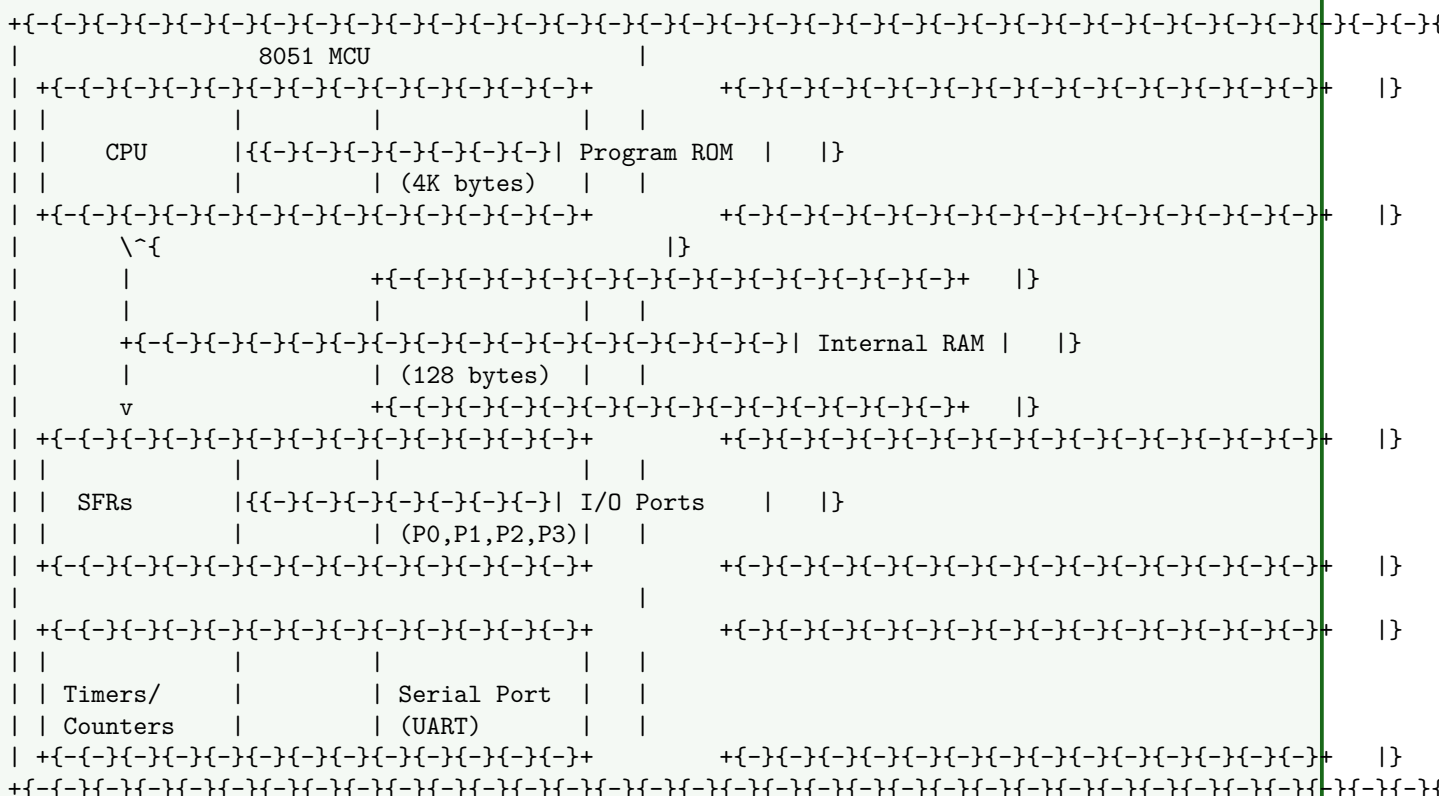

- **Harvard Architecture:** Separate program and data memory
- **CISC Design:** Rich instruction set (over 100 instructions)
- **In-built Peripherals:** No need for external components
- **Single-chip Solution:** Complete system on one chip

Mnemonic

“CAPITALS: CPU Architecture Ports I/O Timer ALU LS-Interface Serial”

Question 4(a) [3 marks]

Write an 8051 Assembly Language Program to add two bytes of data and store result in R4 register.

Solution

```
MOV A, \#25H    ; Load first value (25H) into accumulator
MOV R3, \#18H   ; Load second value (18H) into R3
ADD A, R3       ; Add R3 to accumulator
```

```
MOV R4, A ; Store result in R4 register
```

Key Steps:

- Load first operand into Accumulator
- Load second operand into register R3
- Perform addition using ADD instruction
- Store result from Accumulator to R4

Mnemonic

“LLAS: Load-Load-Add-Store”

Question 4(b) [4 marks]

Write an 8051 Assembly Language Program to OR the contents of Port-1 and Port-2 then put the result in external RAM location 0200H.

Solution

```
MOV A, P1 ; Load contents of Port{-1 into accumulator}
ORL A, P2 ; OR Port{-2 contents with accumulator}
MOV DPTR, \#0200H ; Load DPTR with external RAM address
MOVX @DPTR, A ; Store result in external RAM location 0200H
```

Key Steps:

- Read Port-1 into Accumulator
- Perform OR operation with Port-2
- Set up Data Pointer (DPTR) for external RAM
- Write result to external memory

Mnemonic

“PORT: Port-OR-Register-Transfer”

Question 4(c) [7 marks]

List Addressing Modes of 8051 Microcontroller and explain them with at least one example.

Solution

Addressing Mode	Example	Description
Immediate	MOV A, #25H	Data is in instruction
Register	MOV A, R0	Data is in register
Direct	MOV A, 30H	Data is at RAM address
Indirect	MOV A, @R0	R0/R1 contains address
Indexed	MOVC A, @A+DPTR	Access program memory
Bit	SETB P1.3	Access individual bits
Relative	SJMP LABEL	Jumps with 8-bit offset

Examples:

- **Immediate:** MOV A, #55H (Load A with 55H)
- **Register:** ADD A, R3 (Add R3 to A)
- **Direct:** MOV 40H, A (Store A at address 40H)
- **Indirect:** MOV @R0, #5 (Store 5 at address in R0)
- **Indexed:** MOVC A, @A+DPTR (Read code memory)
- **Bit:** CLR C (Clear carry flag)
- **Relative:** JZ LOOP (Jump if A is zero)

Mnemonic

“I’M DIRBI: Immediate Register Direct Bit Indexed”

Question 4(a OR) [3 marks]

Explain following instructions: (i) DJNZ (ii) POP (iii) CJNE.

Solution

Instruction	Syntax	Operation
DJNZ	DJNZ Rn, rel	Decrement register, Jump if Not Zero
POP	POP direct	Pop data from stack to direct address
CJNE	CJNE A, #data, rel	Compare and Jump if Not Equal

Examples and Explanation:

- **DJNZ R7, LOOP:** Decrements R7 and jumps to LOOP if $R7 \neq 0$
 - Used for loop counters and delays
- **POP 30H:** Copies data from stack to address 30H
 - Increments SP after data retrieval
- **CJNE A, #25H, NOTEQUAL:** Compares A with 25H, jumps if not equal
 - Also sets Carry flag if $A < \text{data}$

Mnemonic

“DPC: Decrement-Pop-Compare”

Question 4(b OR) [4 marks]

For 8051 Microcontroller with a crystal frequency of 12 MHz, generate a delay of 4ms.

Solution

```
; Crystal frequency = 12 MHz
; Machine cycle = 1 s
; Required delay = 4 ms = 4000 machine cycles

      MOV  R7, \#16      ; Outer loop counter (16 x 250 = 4000)
DELAY1: MOV  R6, \#250    ; Inner loop counter
DELAY2: NOP              ; 1 machine cycle
        NOP              ; 1 machine cycle
        DJNZ R6, DELAY2  ; 2 machine cycles (250 x 4 = 1000 cycles)
        DJNZ R7, DELAY1  ; 16 x 250 = 4000 cycles total
        RET              ; Return from subroutine
```

Calculation:

- Each inner loop: $4 \text{ cycles} \times 250 \text{ iterations} = 1000$
- Outer loop: $16 \text{ iterations} \times 1000 \text{ cycles} = 16,000 \text{ cycles}$
- At 12MHz, 1 machine cycle = 1 s
- Total delay = 4ms (4000 cycles)

Mnemonic

“LNDD: Load-NOP-Decrement-Decrement”

Question 4(c OR) [7 marks]

Explain any seven Logical instructions with example for 8051 Microcontroller.

Solution

Instruction	Example	Operation
ANL	ANL A, #3FH	Logical AND
ORL	ORL P1, #80H	Logical OR
XRL	XRL A, R0	Logical XOR
CLR	CLR A	Clear (set to 0)
CPL	CPL P1.0	Complement (invert)
RL	RL A	Rotate left
RR	RR A	Rotate right

Examples with Explanation:

1. **ANL A, #0FH**: Masks high nibble ($A = A \text{ AND } 0FH$)
 - Before:
A = 95H, After:
A = 05H
2. **ORL 20H, A**: Sets bits in memory ($20H = 20H \text{ OR } A$)
 - Before: 20H = 55H,
A = 0AH, After: 20H = 5FH
3. **XRL A, #55H**: Toggles specific bits ($A = A \text{ XOR } 55H$)
 - Before:
A = AAH, After:
A = FFH
4. **CLR C**: Clears carry flag ($C = 0$)
 - Used before subtraction operations
5. **CPL A**: Inverts all bits ($A = \text{NOT } A$)
 - Before:
A = 55H, After:
A = AAH
6. **RL A**: Rotates accumulator left one bit
 - Before:
A = 85H (10000101), After:
A = 0BH (00001011)
7. **RR A**: Rotates accumulator right one bit
 - Before:
A = 85H (10000101), After:
A = C2H (11000010)

Mnemonic

“A-OX-CCR: AND OR XOR Clear Complement Rotate”

Question 5(a) [3 marks]

List Applications of microcontroller in various fields.

Solution

Field	Applications
Industrial	Motor control, automation, PLCs
Medical	Patient monitoring, diagnostic equipment
Consumer	Washing machines, microwaves, toys
Automotive	Engine control, ABS, airbag systems
Communication	Mobile phones, modems, routers
Security	Access control, alarm systems

Mnemonic

“I-MACS: Industrial-Medical-Automotive-Consumer-Security”

Question 5(b) [4 marks]

Interface Push button Switch and LED with 8051 microcontroller.

Solution

Circuit Diagram:

```
Vcc
|
R (10K)
|
P1.0{--}+{--}{--}{--}{--}{--}{--} Push Button {--}{--}{--}{--}{--}{--} GND}

Vcc
|
R (330Ω)
|
P1.7{--}{--}{--}+{--}{--}{--}{--}{--}{--}||{--}{--}{--}{--}{--}{--} LED {--}{--}{--}{--}{--}{--} GND}
```

Program:

```
AGAIN: JB    P1.0, LED\_OFF ; If P1.0=1 (not pressed), LED off
        SETB P1.7          ; If P1.0=0 (pressed), LED on
        SJMP AGAIN         ; Repeat
LED\_OFF: CLR P1.7          ; Turn LED off
        SJMP AGAIN         ; Repeat
```

Component	Connection	Purpose
Push Button	P1.0 (input)	User input, active-low
Pull-up Resistor	10K to Vcc	Prevents floating input
LED	P1.7 (output)	Visual indicator
Current-limiting Resistor	330Ω	Protects LED

Mnemonic

“PLIC: Push-LED-Input-Control”


Question 5(c) [7 marks]

Interface LCD with microcontroller and write a program to display “HELLO”.

Solution

Circuit Diagram:

```
8051                                16x2 LCD
+{--}{--}{--}{--}{--}{--}{--}+    +{--}{--}{--}{--}{--}{--}{--}{--}{--}+
|      |      |      |
| P2.0 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D0      |}
| P2.1 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D1      |}
| P2.2 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D2      |}
| P2.3 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D3      |}
| P2.4 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D4      |}
| P2.5 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D5      |}
| P2.6 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D6      |}
| P2.7 |{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}{--}|D7      |}
```

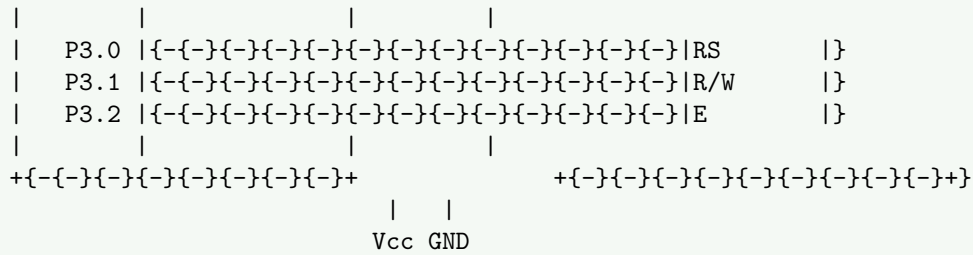

Program:

```

ORG 0000H                ; Start address

; Initialize LCD
MOV A, \#38H              ; 8{-bit, 2 lines, 5x7 dots}
ACALL COMMAND             ; Send command
MOV A, \#0EH              ; Display ON, cursor ON
ACALL COMMAND             ; Send command
MOV A, \#01H              ; Clear display
ACALL COMMAND             ; Send command
MOV A, \#06H              ; Increment cursor
ACALL COMMAND             ; Send command
MOV A, \#80H              ; First line, first position
ACALL COMMAND             ; Send command

; Display "HELLO"
MOV A, \#{H               ; Load H}
ACALL DISPLAY             ; Display it
MOV A, \#{E               ; Load E}
ACALL DISPLAY             ; Display it
MOV A, \#{L               ; Load L}
ACALL DISPLAY             ; Display it
MOV A, \#{L               ; Load L}
ACALL DISPLAY             ; Display it
MOV A, \#{O               ; Load O}
ACALL DISPLAY             ; Display it

SJMP $                   ; Stay here

; Command subroutine
COMMAND:
MOV P2, A                ; Put command on data bus
CLR P3.0                 ; RS=0 for command
CLR P3.1                 ; R/W=0 for write
SETB P3.2                ; E=1
ACALL DELAY              ; Wait
CLR P3.2                 ; E=0
RET                      ; Return

; Display subroutine
DISPLAY:
MOV P2, A                ; Put data on data bus
SETB P3.0                ; RS=1 for data
CLR P3.1                 ; R/W=0 for write
SETB P3.2                ; E=1
ACALL DELAY              ; Wait
CLR P3.2                 ; E=0
RET                      ; Return

; Delay subroutine
DELAY:
MOV R7, \#50             ; Load counter

```


Key Points:


- LM35 produces analog voltage proportional to temperature
- ADC0804 converts analog voltage to digital value
- 8051 controls ADC and reads temperature data
- Resolution: $10\text{mV}/2^8 = 0.2\text{mV}$ resolution with 8-bit ADC

Mnemonic

“TAC: Temperature-Analog-Convert”

Question 5(b OR) [4 marks]

Interface Stepper motor with 8051 microcontroller.

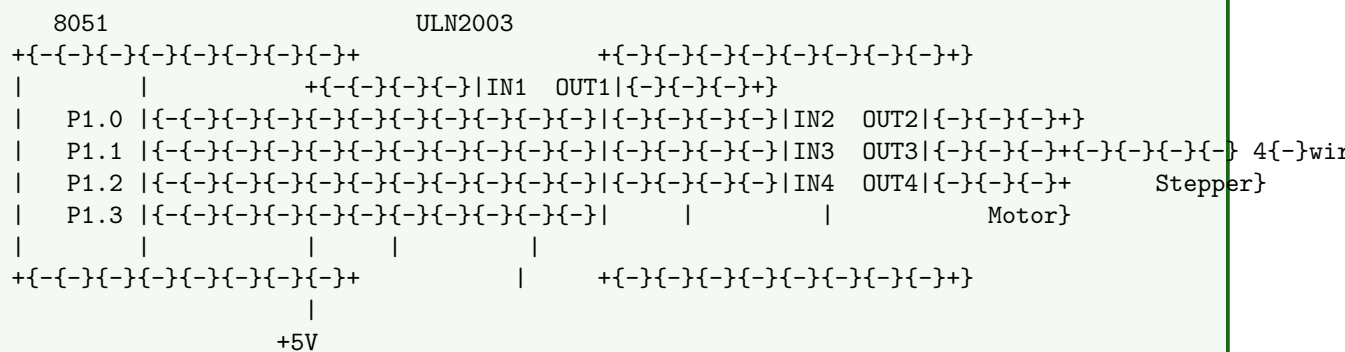Solution**Circuit Diagram:****Program:**

```

ORG 0000H

; Stepper Motor Sequence for Clockwise Rotation
SEQ: DB 00001000B ; Step 1
      DB 00001100B ; Step 2
      DB 00000100B ; Step 3
      DB 00000110B ; Step 4
      DB 00000010B ; Step 5
      DB 00000011B ; Step 6
      DB 00000001B ; Step 7
      DB 00001001B ; Step 8

MAIN: MOV R0, \#00H ; Initialize sequence pointer

STEP: MOV A, R0      ; Get current sequence number
      ANL A, \#07H   ; Keep within 0-7 range (8 steps)
      MOV DPTR, \#SEQ ; Point to sequence table
      MOVC A, @A+DPTR ; Get sequence pattern
      MOV P1, A      ; Output to stepper motor

      ACALL DELAY    ; Wait between steps

      INC R0          ; Next sequence
      SJMP STEP      ; Repeat

DELAY: MOV R6, \#250 ; Delay loop
LOOP:  MOV R7, \#250
LOOP2: DJNZ R7, LOOP2
      DJNZ R6, LOOP
      RET

```

END

Component	Purpose
ULN2003	Driver IC with Darlington arrays
Port pins	P1.0-P1.3 for 4 motor phases
Power supply	Separate supply for motor

Key Points:

- Stepper motor requires specific sequence of pulses for rotation
- ULN2003 provides current amplification for motor coils
- 8-step sequence provides smoother rotation
- Delay between steps controls rotation speed

Mnemonic


“PDCS: Port-Driver-Current-Sequence”

Question 5(c OR) [7 marks]

Interface ADC0804 with 8051 microcontroller.

Solution

Circuit Diagram:

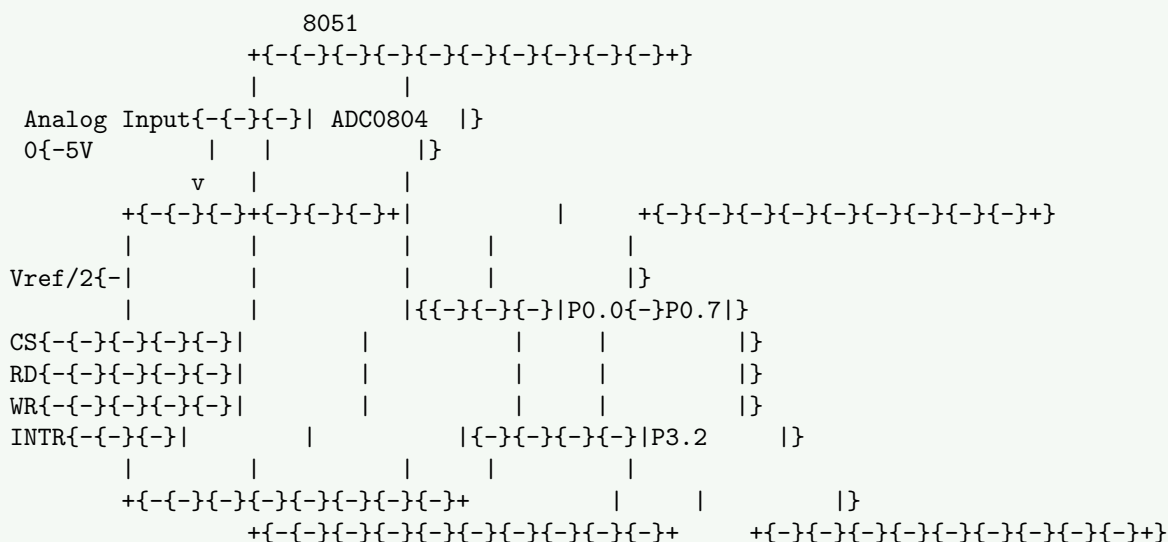

Program:

```
ORG 0000H
```

```
START:  CLR P1.0      ; CS = 0 (Chip Select active)
        CLR P1.1      ; RD = 0
        CLR P1.2      ; WR = 0
        SETB P1.2     ; WR = 1 (Start conversion)

WAIT:   JB P1.3, WAIT ; Wait for conversion (INTR = 0)

        CLR P1.1      ; RD = 0 (Read data)
        MOV A, PO      ; Read converted data into A
        MOV 30H, A     ; Store result in RAM

        SETB P1.0     ; CS = 1 (Chip deselect)
```

PROCESS:

```
; Process the data (e.g., display, compare, etc.)  
; ...
```

```
ACALL DELAY    ; Wait before next conversion  
SJMP START     ; Repeat
```

```
DELAY: MOV R7, \#200 ; Delay routine
```

```
DLOOP: DJNZ R7, DLOOP  
RET
```

END

Connection	8051 Pin	ADC0804 Pin
Data Bus	P0.0-P0.7	D0-D7
CS	P1.0	CS
RD	P1.1	RD
WR	P1.2	WR
INTR	P1.3	INTR

ADC0804 Features:

- 8-bit resolution (256 steps)
- 0-5V input range
- Single-channel operation
- ~100 s conversion time
- Interface protocol:
 1. Activate CS, pulse WR to start conversion
 2. Wait for INTR to go low (conversion complete)
 3. Activate RD to read data
 4. Deactivate CS when done

Mnemonic

“CRIW: Control-Read-Interrupt-Write”